July 1979 $2.50

73 Magazine for Radio Amateurs

Antennas!

30 **A Visit to Antenna Specialists**
—Wayne tours the test range. **W2NSD/1**

34 **Secrets of Guyed Towers**
—put 'em up and keep 'em there. **WB3BQO**

40 **Death-Defying PL Mod for the KDK 2015**
—not for the squeamish. **W8GQL**

44 **Feed-Horn Mounting Made Easy**
—solution to a pesky problem. **WB8DQT**

48 **Antenna Tuning Joy Revisited**
—remember the Tektronix 190B?. **W9CGI**

52 **Modern Solid-State Equipment Design: A Better Way**
—sorry, tube fans. **W4RNL**

58 **Shortened Antennas for 75 and 80**
—designs which fit your QTH. **W4AEO**

66 **Build This Simple 220 Yagi**
—3 elements, 6 dB. **N8AJA**

68 **Beware of the Dreaded Phantom Ground**
—exorcise those antenna gremlins
. . . . . **WA2SUT/NNN0ZVB**

70 **A Close Encounter With Voyager I**
—the W6VIO story. **K6PGX**

72 **GIANT Wire Antennas**
—impress the neighbors. **WD8CBJ**

78 **Microcomputer RTTY . . . a Software TU**
—use your 8080 and very little else. . . . **N1AW**

84 **Baudot Hard Copy For Your SWTPC**
—noisy, but cheap. **K4HBG**

92 **The 9-Element Duoband DX Attention-Getter**
—when you call, they listen. **K4FK, N4OG**

96 **Here's a "Twist"**
—an OSCAR antenna with a difference. . . . **K4TWJ**

98 **A Fortified 2m Whip**
—won't bend in the breeze. **W9AMM**

100 **Ageless Wonder: the Collinear Beam**
—sure beats a dipole. **W1FK**

102 **Three Baluns for a Buck**
—go find yourself a junked TV. **W6SJQ**

104 **So You Want to Raise a Tower**
—do it safely, do it right. **WA7DPX**

118 **The Revolutionary Organic Antenna**
—product of NASA research. . . . . **Gaddie**

126 **DDRR Dipole for VHF**
—experiment!. **W6VX**

132 **Tennamatic: An Auto-Tuning Mobile Antenna System**
—works all of 40 and 75. . . . . **W6TWW**

140 **Add Solid-State Braking to the T²X**
—a worthwhile improvement. **WB2DTY**

144 **Compact Beams for 20 or 15**
—build these when your quad bites the dust. **W8HXR**

150 **"Weeping Willow" Vertical for 40**
—go out on a limb and build one. **WA6OYS**

154 **Marine-Band Activity**
—a complete guide. **WA2KBZ**

Never Say Die—4, Letters—10, Looking West—12, OSCAR Orbits—14, RTTY Loop—14, Contests—19, Microcomputer Interfacing—20, New Products—22, DX—26, Corrections—77, Ham Help—77, 164, 180, Dealer Directory—88, Social Events—130, Propagation—209

the praise is pouring in

*Shown with accessory touch tone pad

Top view

We have never enjoyed such an overwhelming response to a new product. Letters of praise for Tempo's S-1 are coming in daily. Words such as great, fabulous, and fantastic are common. In a few short months the S-1 has taken the Amateur world by storm. In addition to its unique features and its versatility, it has now proven itself to be an extremely rugged and dependable unit...qualities unmatched at any price, but unheard of at the S-1's low price.

This amazing pocket sized radio represents a major breakthrough in 2-meter communications. Other units that are larger, heavier and are similarly priced can offer only 6 channels. The S-1's price includes the battery pack, charger, and a telescoping antenna. But, far more important is its *proven* performance record as a fully synthesized 800 channel hand held transceiver.

The optional touch tone pad adds greatly to its convenience and the addition of a Tempo solid solid state amplifier adds tremendously to its power.

The proven TEMPO S-1 does it all... portable...mobile ...base station and gives you 800 channels in one of the smallest hand helds

SPECIFICATIONS

Frequency Coverage:	144 to 148 MHz
Channel Spacing:	Receive every 5 kHz, transmit Simplex or ±600 kHz
Power Requirements:	9.6 VDC
Current Drain:	17 ma-standby 500 ma-transmit
Batteries:	8 cell ni-cad pack included
Antenna Impedance:	50 ohms
Dimensions:	40 mm x 62 mm x 165 mm (1.6" x 2.5" x 6.5")
RF Output:	Better than 1.5 watts
Sensitivity:	Better than .5 microvolts

SUPPLIED ACCESSORIES
Telescoping whip antenna, ni-cad battery pack, charger.

OPTIONAL ACCESSORIES
Touch tone pad: $55 • Tone burst generator: $29.95 • CTCSS sub-audible tone control: $29.95 • Rubber flex antenna: $8 • Leather holster: $16 • Cigarette lighter plug mobile charging unit: $6 • Matching 30 watt output 13.8 VDC power amplifier (S30): $89 • Matching 80 watt output power amplifier (S80): $169

Price... $349.00 With touch tone pad... $399.00

The Tempo line also features a fine line of extremely compact UHF and VHF pocket receivers. They're low priced, dependable, and available with CTCSS and 2-tone decoders. The Tempo FMT-2 & FMT-42 (UHF) provides excellent mobile communications and features a remote control head for hide-away mounting.

The Tempo FMH-42 (UHF) and the *NEW* FMH-12 and FMH-15 (VHF) micro hand held transceivers provide 6 channel capability, dependability plus many worthwhile features at a low price. FCC type accepted models also available.

Please call or write for complete information. Also available from Tempo dealers throughout the U.S. and abroad.

TEMPO VHF & UHF SOLID STATE POWER AMPLIFIERS

Boost your signal. . . give it the range and clarity of a high powered base station. VHF (135 to 175 MHz)

Drive Power	Output	Model No.	Price
2W	130W	130A02	$209
10W	130W	130A10	$189
30W	130W	130A30	$199
2W	80W	80A02	$169
10W	80W	80A10	$149
30W	80W	80A30	$159
2W	50W	50A02	$129
2W	30W	30A02	$ 89

UHF (400 to 512 MHz) models, lower power and FCC type accepted models also available.

NEW TOLL FREE ORDER NUMBER: (800) 421-6631
For all states except California.
Calif. residents please call collect on our regular numbers.

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

HENRY RADIO 51 YEARS OF SERVICE

Henry Radio

Prices subject to change without notice

NEW, IMPROVED
Wilson's MONO-BANDERS

The Model M-520A offers the discriminating DXer an unexcelled beam antenna that really punches through the QRM . . . ask anyone who owns one! Features 5 full sized elements on a 2" O.D. x 34 ft. boom. Low SWR across the entire 20 meter band. The M-520A is shipped UPS in two cartons.

M-520A
5 ELEMENT MONOBANDER

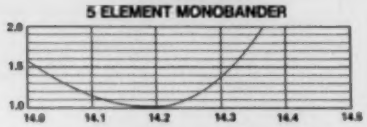

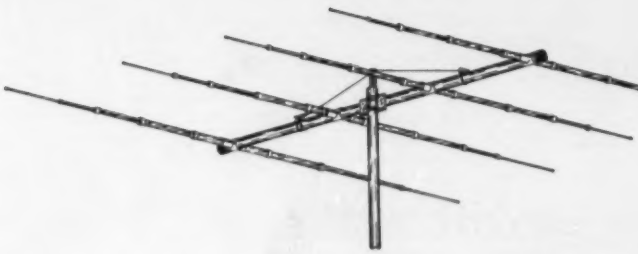

The magic 20 meter beam: M-420A . . . 4 elements on a 26 ft. boom. Super front-to-back and side rejection. The M-420A ships UPS in two cartons.

M-420A
4 ELEMENT MONOBANDER

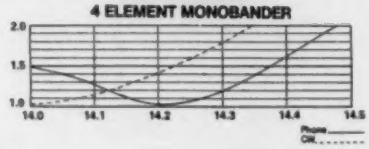

The M-155A is the top of the line 15 meter monobander. This is the one for the serious DXer. Top performance that will make you heard on 15! 5 elements wide spaced on a 25' 7" boom.

M-155A
5 ELEMENT MONOBANDER

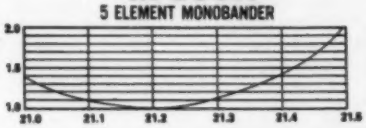

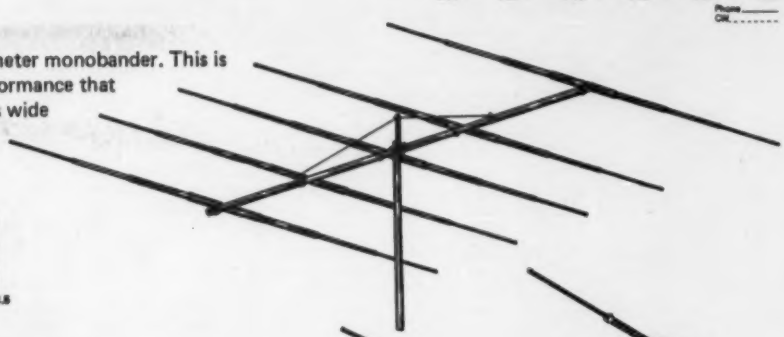

The M-105A — our latest 10 meter design uses W - I - D - E spacing. Well researched design provides the ultimate in a 10 meter antenna. 5 elements on a 23' 5" boom.

With the 10 meter band making a strong comeback, choose our model to fulfill your needs. Five wide spaced elements will provide a top performing antenna.

M-105A
5 ELEMENT MONOBANDER

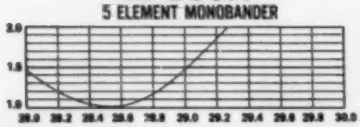

SPECIFICATIONS	MODEL M-520A	MODEL M-420A	MODEL M-155A	MODEL M-105A
Band MHz	14	14	21	28
Maximum Power Input	Legal Limit	Legal Limit	Legal Limit	Legal Limit
Gain (dB)	11.5	10	13.0	13.0
VSWR (at Resonance)	1.1:1	1.1:1	1.1:1	1.1:1
Impedance	52 ohms	50 ohms	50 ohms	52 ohms
Front-to-Back Ratio (dB)	25	25	25	20
Boom (O.D. x Length)	2" x 34'6"	2" x 26'	2" x 25'7"	2" x 23'5"
No. Elements	5	4	5	5
Longest Element	30'6"	26'6"	25'3"	18'2"
Turning Radius	25'	22'6"	17'9"	22'6"
Mast Diameter	2" O.D.	2" O.D.	2" O.D.	2" O.D.
Boom Diameter	2" O.D.	2" O.D.	2" O.D.	2" O.D.
Surface Area (Sq. Ft.)	8.0	7.0	4.25	2.0
Wind Load	237 lbs.	196 lbs.	108 lbs.	75 lbs.
Assembled Weight (Approx.)	70 lbs.	50 lbs.	40 lbs.	35 lbs.
Shipping Weight (Approx.)	75 lbs.	55 lbs.	45 lbs.	40 lbs.
Matching Method	Beta	Beta	Beta	Beta

Prices and specifications subject to change without notice.

Consumer Products Division

Wilson Electronics Incorporated

A Subsidiary of REGENCY ELECTRONICS, INC

W2

4288 So. Polaris • P. O. Box 19000 • Las Vegas, Nevada 89119
Phone (702) 739-1931 • Telex 684-522

Reader Service—see page 211

Staff

EDITOR/PUBLISHER
Wayne Green W2NSD/1

EXECUTIVE VICE PRESIDENT
Sherry Smythe

ASSISTANT PUBLISHER
Jeffrey D. DeTray WB8BTH/1

ADMINISTRATIVE ASSISTANT
Dotty Gibson

MANAGING EDITOR
John C. Burnett

ASSISTANT MANAGING EDITOR
Susan G. Philbrick

NEWS EDITOR
Gene Smarte WB8TOV/1

EDITORIAL ASSISTANTS
Elisabeth Blackmore
Cynthia Smith
Richard Phenix

BOOK PUBLICATIONS
Jim Perry

PRODUCTION MANAGER
Lynn Panciera-Fraser

ART DEPARTMENT
Judith Dalby
Bob Drew
James H. Gray II
Bruce Hedin
Chip Jackson
Dion Owens
Noel R. Self WB1ARP
Robin M. Sloan
John W. White

PRINTING
Gary Steinbach

PHOTOGRAPHY
Bill Heydolph
Tedd Cluff

TYPESETTING
Barbara J. Latti
Sara Bedell
David Dawe
Holly J. Walsh

BOOKKEEPER
Knud E. M. Keller KV4GG/1

CIRCULATION
Pauline Johnstone

DATA ENTRY
Cathy DeSilva
Margaret Sheldon

DIRECTOR OF MARKETING AND CIRCULATION
Robert R. LaPointe

ASSISTANT CIRCULATION MANAGER
Mary Beth Stanek

BULK SALES MANAGER
Judy Waterman

SHIPPING
Ethan Perry, Mgr.
Bill Barry

RECEPTIONIST
Beth Smith

ASSOCIATES
Robert Baker WB2GFE
E. H. Barnett WB8IIX
Schley Cox WB9LHO
Tom DiBlase WB8KZD
Terry Fox WB4JFI
W. Sanger Green
Dave Ingram K4TWJ
Larry Kahaner WB2NEL
Joe Kasser G3ZCZ
Bill Pasternak WA6ITF
John Schultz W4FA
Walter Scott K8DIZ
Peter Stark K2OAW
Chuck Stuart N5KC
Bill Turner WA8ABI

COMPUTER PROGRAMMING
Richard J. Dykema

CUSTOMER SERVICE
Florence Goldman

ADVERTISING
Aline Coutu, Mgr.
Bill York
Nancy Ciampa
Marcia Stone
Gaye Halberg
Lori Mugford
Rita Rivard

W2NSD/1
NEVER SAY DIE
editorial by Wayne Green

DAYTON

Despite the rapid growth of the Atlanta Hamfestival, Dayton pulls 'em in in greater numbers every time. It's gotten so big that it is difficult to see everyone there. No, it's impossible. Whether they have 15,000 or 20,000 in attendance is irrelevant—it's too much to handle.

I had not really intended to get to Dayton this time, feeling that I would do better to spend the four days involved working on Instant Software and a new publishing project. But I began to waver just a bit when they called up and wanted to know where they could reach Jean Shepherd K2ORS in order to get him to entertain at the banquet. Then they asked if I would be available to speak on the microcomputer forum . . . and I gave in.

Shep was outstanding, as usual. I think they had well over 1,500 at the banquet, and he had them in stitches. The banquet was nice . . . grilled hockey pucks, I think. I wasn't sure. The potato was good, which is more than I can say for a lot of restaurants . . . and the company was fine. Most of the entertainment was a bore . . . some local group singing and dancing . . . unfortunately none of them were singers or dancers. That went on incredibly long. The MC was excellent . . . he introduced the two hundred or so people at the head table in a minute and a half, making some very entertaining comments as he went along.

The Dayton crew has been at it for years and they are certainly professional about it. There are few glitches in the Hamvention.

The crowds seemed to be down a bit this year—no one knows why. I heard rumors that they clocked in 14,000, compared to 19,000 last year. The aisles were easier to traverse. Other later reports put attendance at 17,000. Big deal . . . that's numbers. I talked with exhibitors, and sales were the best ever, no matter how many were there. Some dealers went home with over $50,000 in sales for the three days.

Despite long-term delivery delays promised by Drake, I understand that dealers were really loaded up with Drake gear for the show . . . which brought prices down to perhaps $5 or $10 over cost on the big gear. While this is hard on the dealers, it is a bonanza for the rest of us. All HTs were selling well, too. I don't think a single dealer went home with an HT in his truck. The showing of the first prototype of the new Yaesu programmable HT helped convince dealers that long-term stocks of the more traditional HTs would not be prudent. It's getting time to liquidate HT crystal stocks.

Swan showed their new line of transceivers and wowed everyone. Their microprocessor-controlled units will be in short supply for a long time. The Japanese are going to have to work a little harder to keep their large share of the US market.

But long after the new ham gear and the acres upon acres of flea market fade into fuzzy memory, the Jean Shepherd entertainment at the banquet will live on in memory. Long after the old rig we bought off a flea market truck that chilly Saturday has been auctioned off at a local hamfest, we'll remember Shep and his problems with the Texas kilowatt on 7182 kHz back in the '30s. "Doesn't that sonofagun ever sleep?"

ARMA

The most recent meeting of the Amateur Radio Manufacturer's Association came the night before the Dayton Hamvention and was sparsely attended, considering that almost 250 firms run ads in any one month in the ham magazines.

A representative from the Electronic Industries Association was there to try to convince the ham industry that they might do better to join the EIA rather than fritter around with ARMA. It was noted that only one ham manufacturer is presently a member of EIA, and that one admitted discovering the membership with some surprise, a sort of bonus for their CB affiliation.

I don't think I helped that project as much as I might have when I reminded everyone that we had heard this same story ten years ago when Bob Waters lured the ham industry away from a ham manufacturer's association and into the EIA. The ham industry was in the same division as the CB industry, and thus when it came to any conflicts between the two (and there were beauts, like 220 MHz), money talked and the ham industry seemed to get a deaf ear.

The costs of joining the EIA are not insignificant. It would cost *73* about $2,000 per year to belong, with few (if any) benefits which I could pin down. And then, if any special projects for lobbying came up, the cost of them would be on top of the two thou. Someday, I'd like to have a general idea of how much Hy-Gain and Johnson put into the pot to get more CB channels on eleven meters and the 220 MHz band for CB. Both of those projects were bummers, incidentally. The eleven meter expansion project resulted in the serious wounding of CB and cost the industry billions. It sank Hy-Gain.

It was noted that ARMA had not been able to decide on anything and follow it through with success. The effort to stave off FCC actions on linear amplifiers was an abject failure. I feel that this total defeat was primarily due to the lack of support of ARMA by some of the larger firms in the ham industry, the back-stabbing (to put it politely) by the ARRL, and the lack of strong leadership in ARMA to put together a program with which to fight the

TS-120S... *A big little rig.*

It's a compact, up to 200 watts PEP input, all solid-state HF transceiver with such standard features as built-in digital readout, IF shift, new PLL technology ...and requires no tuning!

Exciting and perfect for car or ham shack use! But, there's more to say about the TS-120S! This unique all solid-state HF, SSB/CW transceiver produces a hefty signal and also offers a lot of other great features in a very attractive, compact package.

FEATURES:

- All solid-state with wideband RF amplifier stages. No final dipping or loading, no transmit drive peaking, and no receive preselector tuning! *Just dial your frequency and operate!*
- Five bands, plus WWV. Transmits and receives on 80/75, 40, 20, 15, and all of 10 meters...and receives WWV on 15 MHz.
- 200 watts PEP (160 watts DC) input on 80-15 meters, 160 watts PEP (140 watts DC) input on 10 meters. LSB, USB, and CW.
- Digital frequency display (standard). 100-Hz resolution. Six digits. Special green fluorescent tubes eliminate viewing fatigue. Analog subdial, too, for backup display.
- IF shift (passband tuning), to remove adjacent-frequency interference and sideband splatter.
- Advanced PLL circuit, which eliminates need for heterodyne crystal element for each band. PLL lock frequency, CAL marker signal, and counter clock circuit use single reference frequency crystal. Simplifies circuitry, improves overall stability. Also improves transmit and receive spurious characteristics.
- Attractive, compact design. Measures only 3½" high X 9¼" wide X 13½" long, and weighs only 4.9 kg (11.7 lbs.). A perfect size for convenient mobile operation and rugged enough for either mobile or portable use. Also has all the desired features for optimum ham-shack operation at home.
- Noise blanker. You'll wonder where the ignition noise went.

See the big little TS-120S rig and matching accessories (VFO-120 remote VFO, SP-120 external speaker, PS-30 AC power supply, MB-100 mobile mounting bracket, AT-120 antenna tuner and YK-88C CW Filter) at your nearest Authorized Kenwood Dealer!

STILL AVAILABLE... KENWOOD TS-520S

KENWOOD

...pacesetter in amateur radio

TRIO-KENWOOD COMMUNICATIONS INC.
1111 WEST WALNUT/COMPTON, CA 90220

INFO.

Manuscripts

Contributions in the form of manuscripts with drawings and/or photographs are welcome and will be considered for possible publication. We can assume no responsibility for loss or damage to any material. Please enclose a stamped, self-addressed envelope with each submission. Payment for the use of any unsolicited material will be made upon acceptance. All contributions should be directed to the *73* editorial offices. "How to Write for 73" guidelines are available upon request.

Editorial Offices:

Pine Street
Peterborough NH 03458
Phone: 603-924-3873, 924-3874

Advertising Offices:

Elm Street
Peterborough NH 03458
Phone: 603-924-7138, 924-7139

Circulation Offices:

Phone: 603-924-7209

Subscription Rates

In the United States and Possessions:

One Year (12 issues) $18.00
Two Years (24 issues) $30.00
Three Years (36 issues) $45.00
Lifetime subscription $240.00

Elsewhere:

Canadian subscriptions—add $2.00 per year unless paid with U.S. currency.

All other foreign—one year only—$26.00 payable in U.S. currency through a U.S. bank (surface mail).

To subscribe, renew or change an address:

Write to *73 Magazine*, Subscription Department, PO Box 931, Farmingdale NY 11737. For renewals and changes of address, include the address label from your most recent issue of 73. For gift subscriptions, include your name and address as well as those of gift recipients. Postmaster: Send change of address information to *73 Magazine*, PO Box 931, Farmingdale NY 11737.

Subscription problem or question:

Write to *73 Magazine*, Subscription Department, PO Box 931, Farmingdale NY 11737. Please include an address label.

73 Magazine (ISSN 0098-9010) is published monthly by 73, Inc., Peterborough NH 03458. Second class postage is paid at Peterborough NH 03458 and at additional mailing offices. Copyright (c) 1979 by 73, Inc. All rights reserved. No part of this publication may be reprinted or otherwise reproduced without written permission from the publisher. Microfilm Edition—University Microfilm, Ann Arbor MI 48106.

FCC and win.

One of the more serious problems facing any industry association is the seeming preference for the death of amateur radio over accommodation between the US manufacturers and importers of Japanese (called "foreign") equipment. I can understand the emotions involved, particularly when you consider that somewhere around 70% of the ham gear being sold is being imported from Japan. I've heard repeated claims that the Japanese are selling this ham gear at a loss here in order to destroy the US manufacturers. I'd sure like to see some proof of this contention.

On the surface of it, the high sales of Japanese equipment seems to be the result of a lot of advertising, excellent design, good marketing, and factors such as this. The Japanese have some unfair advantages, I'll admit, in that they have about 400,000 hams in Japan as a market that is virtually closed to our manufacturers. With about double the market for ham gear, they can afford to spend more on design and run larger production runs . . . which means lower costs.

Then there is the matter of Japanese productivity vs. that of the US. A recent article in *Fortune* pointed out that the US has been down toward the bottom of the list in worker productivity improvements. The Japanese have been building new and more automated plants, while our unions and government have been making it almost impossible for us to do the same, thus forcing dealers to sell imported equipment which has more features and costs less.

There have been some strong moves to turn this around. Swan has stopped importing their equipment and is now making everything here in the US. Their new line of transceivers is going to have a strong effect on the market, for they are taking advantage of microcomputer technology. But other US manufacturers have been complacent, telling dealers that they are so busy with other things that ham gear will be six months or more back-ordered. And one major firm which has been making a big deal out of hams buying American has some very clearly indentifiable Japanese parts in its new rig.

Some of the US problems undoubtedly could be cured if we could get the government out of the act. I talked with one manufacturer recently who had had his plant closed down by OSHA because they found a fire escape support column which was painted. It seems that they could not inspect the column for any possible cracks . . . so everyone had to be sent home until the paint could be removed from the fire escape column.

OSHA seems to be the cause of the recent semiconductor plant shutdown which caused incredible consternation in the entire electronics industry. The early estimates are that much over $10 billion was lost as a result of this unnecessary action. Some 20¢ chips were being bid up to $5.00 and more by contractors frantic to finish contracts on time or by manufacturers being pressured by customers for delivery.

I doubt if they are having nearly as much government harassment in Japan . . . and this means that they can be more competitive with us. If you read much about Japan, you know that workers take their jobs very seriously and are dedicated to their employers. The excesses of many industrialists of a hundred years ago spawned a strong union movement in the US, and some of the ramifications of that have not been helpful in making us competitive with other countries. The strong union positions in England have been a powerful factor in keeping that country from being seriously competitive with much of the world.

In the microcomputer field, no other country has been able to provide any serious competition for the US. You can bet that the Japanese microcomputer makers have been over here, sizing up the market, but they haven't been able to do much about it. Between our technological advances and the dollar/yen situation, US firms are getting into better positions to give the Japanese a run for their money. Where we are not being held back by union restrictions on modernization and excessive government regulation, we can raise hell with imports.

Well, getting back to ARMA, the suggestion was made that instead of trying to represent the industry, getting involved with battles with the FCC, or trying to help our WARC position, it be made more of a social club . . . perhaps with an industry friendship dinner during the more important hamfests and conventions. If the group is afraid to tackle anything more meaningful than that, then let's have dinner meetings and eat. That's better than protracted meetings hassling over bylaws, dues, and elections, which are just an enormous waste of time and of little interest.

There is one point of history that I would like to clarify since it seems to already be in the process of being rewritten. It was mentioned at the ARMA meeting that the opinion about trying to do something to help the amateur radio position at WARC was about evenly split. I might remind ARMA that the motion to tackle this project was made by Tom Gentry of Icom—it was carried with one and only one negative vote.

I recognize that the eventual scuttling of the project, which I attribute to *Ham Radio* magazine, calls for a distribution of

Continued on page 164

CB TO 10

Many readers have written or called to ask about obtaining back issues which contain articles in our "CB to 10" series. For everyone's information, the issues which have thus far featured "CB to 10" articles are listed below.

1977—May—Part I—"Bandplan and Crystal Information"
1977—Jul—Part II—"Conversion Data"
Part III—"Converting the TRC-47"
Part IV—"Johnson 123A Mod"
Part V—"Converting the Hy-Gain 670B"
1977—Dec—Part VI—"Antenna Suggestions"
Part VII—"Convert a TRC-11"
1978—Feb—Part VIII—"The Publicom I"
1978—Jul—"How About SSB CB Conversions?"
1978—Aug—Part IX—"A Pair of Radio Shack Rigs"
1978—Sep—Part X—"Realistic's Mini 23"
Part XI—"Hy-Gain's PLL Rigs"
1978—Oct—Part XII—"Convert a Kraco PLL Rig"
1978—Nov—Part XIII—"The Lafayette Telsat SSB-75"
Part XIV—"A Realistic PLL Rig"
Part XV—"A Realistic HT"
1979—Jan—Part XVI—"A CW Conversion"
Part XVII—"SBE and Pace Rigs"
1979—May—Part XVIII—"Several PLL Rigs"
1979—Jun—Part XIX—"Lafayette SSB Rigs"

These issues may be purchased at $8.50 for 5 of your choice (order #STO500), $14 for 10 of your choice (# ST1000), or $25 for 25 of your choice (#ST2501). Include $1 for postage and handling, and send your order to 73 Radio Bookshop, Peterborough NH 03458.

All New! REAL·STATE·OF·THE·ART

DIGITAL INSTRUMENTATION FROM OPTOELECTRONICS, INC.

TWO NEW AC-DC- BATTERY PORTABLE COUNTERS

OPTO-8000.1A **10Hz to 600MHz Frequency Counter**

- Precision TCXO time base 0.1PPM Stability 17-40°C • Super Sensitivity with preamps in both HI-Z & 50 Ohm inputs <10 mV to 150 MHz <50 mV @ 600 MHz
- Auto Decimal Point • Aluminum Case • Socketed IC's • Three position attenuator: X1, X10, X100 (avoids false counting)

#OPTO-8000.1A Factory Assembled - **2 Year Guarantee** $329.95
#OPTO-8000.1AK Kit Form - **1 Year Parts Guarantee** $279.95
#NI-CAD-80 NI-CAD Battery Pack (installs in case) ..... $ 19.95

OPTO-7000 **10 Hz to 600 MHz Miniature Counter**

- XTAL (TCXO) Time Base ±.08PPM/°C Standard • Aluminum Case • HI-Z & 50 Ohm Inputs
- 1 Sec. & 1/10 Sec. Gate times • Auto Dec. Pt. • Built-in Prescaler and Preamps Standard

#OPTO-7000 Factory Assembled - **1 Year Guarantee** $139.95
#OPTO-7000K Kit Form ..... $99.95 #AC-70 AC Power Pak ..... $ 4.95
#NI-CAD-70 NI-CAD Battery Pack and Charger Circuitry ..... $ 19.95
#TCXO-70 Optional Precision TCXO Time Base 0.1PPM, 17-40°C ..... $ 79.95

CM-1000 **Digital Capacitance Meter**

- Featured Sept. 1978 Radio Electronics Magazine • Measures from 1 pf to 9999 uf • 4 Ranges
- .6" Digits • Aluminum Case • Accuracy of .1 % less one digit

#CM-1000 Factory Assembled ..... $179.95 #P-1000 Probe $8.95
#CM-1000K Kit Form ..... $129.95 #P-1000K Probe Kit $7.95

T-100 **Precision Thermometer**

For Use with Digital Voltmeter • Output: 10 mv per Degree • Switchable Fahrenheit/Celsius
• Resolution to .01° with 4½ Digit Meter • Requires two 9V Batteries - not included

#T-100 Factory Assembled & Calibrated $59.95 #T-100K Kit Form $34.95

#D-450, Antenna, Rubber Duck, RF Pickup, 450 MHz $14.95
#D-146 Antenna, Rubber Duck, 146 MHz $14.95
#RA-BNC Right-Angle BNC Adapter for Above Antennas ..... $ 4.95

PROBES

#P-100 50 Ohm, 1X Direct Connection RF Probe $7.95
#P-101 Lo-Pass, Attenuates RF at audio frequencies $7.95
#P-102 HI-Z, 2X High impedance, general purpose $7.95

TERMS: Orders to U.S. and Canada add 5% to maximum of $10.00 per order for shipping, handling and insurance. To all other countries, add 10% of total order. Florida residents add 4% state tax. C.O.D. Fee: $1.00. Personal checks must clear before merchandise is shipped.

Factory Direct - Phone Orders

(305) 771-2050 • 771-2051

OPTOELECTRONICS, INC.

5821 N.E. 14th Avenue, Fort Lauderdale, Florida 33334

Swan's Success Story:

100MX Power House

The Field-Proven Rig the Whole World's Talking About.

235 Watt PEP and CW on **ALL** Bands

Price? You won't believe it! Just ask your dealer.

All solid state quality American construction, with epoxy glass boards to withstand the rugged mobile environment.

Look to Swan for Quality Accessories . . . and Service

SWAN ELECTRONICS

A member of the Gulton Corporation family of companies

306 Airport Road
Oceanside, CA 92054
714-757-7525

A Knob with a new twist "VRS™"

Swan Astro 150 Exclusive Microprocessor Control w/memory gives you over 100,000 fully synthesized frequencies, and more!

- VRS — Variable Rate Scanning, a dramatic new technique for unprecedented tuning ease and accuracy
- POWER — 235 watts PEP and CW on all bands for that DX punch
- Advanced microcomputer technology developed and manufactured in the U.S.A.
- Price? See your authorized SWAN dealer for a pleasant surprise!

Dual Meter
Reads PEP output in watts and receive "S" units.

Full Break-in CW
(or semi, switch selected)

Wide Frequency Coverage
10M — 28.0-30.0 MHz
15M — 20.8-23.0 MHz
20M — 13.8-16.0 MHz
40M — 6.0-8.3 MHz
80M — 3.0-4.5 MHz
160M — 1.8-2.4 MHz*
*in lieu of 10M band on Model Astro 151

Mike Tuning
For accurate 100 Hz steps or fixed rate scan

THE MOST ADVANCED HF SSB TRANSCEIVER AVAILABLE.
FULLY SOLID-STATE **SWAN ASTRO 150**

SWAN ELECTRONICS
A member of the Cubic Corporation family of companies

305 Airport Road / Oceanside, CA 92054 / 714-757-7525

LETTERS

MEMORIES

I was reading my March issue of *73* and noticed your story of the trip we took to Europe in October, 1963. I always felt that the idea of the Institute of Amateur Radio was a very good one and that hams getting to know hams through group tours to other countries was an excellent way of promoting amateur radio.

I am a holder of a lifetime subscription to *73* (yes, I was one of the lucky ones who subscribed in Miami back in '61 or '62), and I have followed you through your editorials. Many times I started to write and tell you how much Anna and I enjoyed the trip, but somehow I never got around to it.

Do you remember your miniature greyhound jumping off the bed and breaking its leg? Or Annora Todd yelling that she wanted to get off at "Arts and Meters" underground station in Paris? Wasn't the cannelloni good at the restaurant in Rome where we went with you one evening and ate in the open-air section? Do you remember when one of the single guys had to double up in the room with the gal in the red coat and her husband? I can't remember her name, but in a crowd we would all say, "Follow the gal in the red coat."

Well, I've finally gotten around to telling you (after all these years) how good I think your idea was and how great the trip was. I have gone many places since then, but never had one-tenth the fun we all did on that momentous trip to Europe by *73* hams. If that trip could ever be duplicated and it leaked out how much fun it was and how interesting it was to meet hams from other countries, you would have to form a full-time travel agency.

I have recently retired from practicing dentistry, and Anna and I moved here to the mountains of western North Carolina from Miami, Florida. Good luck, Wayne, and keep up the good work.

Lamon L. Whiddon K4MHY
Boone NC

It was January, 1961, and you were Life Subscriber #1. I remember it well! The Italian greyhound was named Petite Chienne because that's what everyone called her when we got to Paris. The Rome restaurant was the Tres Scalini and it is still there and superb. I often look at the slides and relive that fantastic trip.—Wayne.

Somehow I was propelled to open the March copy of *73* and I read Never Say Die.

My husband has been dead a year and I had not opened any of his ham magazines until today. As one of the XYLs on that 1963 trip to Europe, I want to thank you for renewing all those wonderful memories.

It would be wonderful to be in contact with the travel group again.

Annora Todd
222 W. Hawthorne St.
Aurora MO 65605

SCHOLARSHIPS

High-school graduates who plan to enter college this fall and who are licensed amateurs may be eligible for one of the $250 scholarships offered by the Atlanta Radio Club. If you qualify, write to the ARC Scholarship Fund, PO Box 77171, Atlanta GA 30357.

Philip J. Latta W4GTS
Marietta GA

ABSURDITY

I feel that the idea of each ITU country having one vote each at WARC is absurd.

Although some people have expressed discontent at the very idea of one country having more say than another, citing it undemocratic, I see it as just the opposite. I see it undemocratic when a handful of radio users have the same vote as millions. This is totally unreasonable for the millions of radio users, since the more operators there are, the more air space is required.

The only truly fair way on which to base votes is on radio population. Because it is not going to change, I feel the US should drop out of the ITU. Many countries play the ITU game during conferences and then disregard the decisions made afterwards, anyway.

William D. Matteo WB2IVI
Toms River NJ

WPIX

From time to time, you mention your television career. With this in mind, I thought you might be interested in the accompanying picture which shows a young (1948) Wayne Green, hair and all, behind a WPIX RCA-TK 10 camera.

I believe the man at the piano is Sigmund Spaeth, who had a program called "The Tune Detective."

I am sure your loss to TV was a gain for amateurs.

Otis Freeman
WPIX, Inc.
New York City NY

Thanks, Otis! Sure, I remember Dr. Spaeth and his program . . . and little things like the night I did the Woody Woodpecker call for him on camera. I remember the Gloria Swanson show, too, with Zasu Pitts and a lot of other old-time stars. Those were fantastic times. The hair? Heck, my father has more hair than I do . . . so did his father, right up until he died . . . but then they didn't have the aggravation of my first wife.—Wayne.

SURPLUS

I just read an article in one of the back issues of *73*. The issue, Feb., '78, had an article by James C. Chapel W9HDA, entitled "Surplus Adventures—pound foolish!" He didn't feel he could trust a company to ship a signal generator to him from a government surplus outlet. Well, this definitely points out a need of hams.

I want to become a ham but suffer from a pecuniary deficiency. Since I work at the Ogden depot, which is a major electronics surplus outlet in Utah, I think I can benefit all those out there who wish to purchase this equipment and who do not wish to suffer expensewise in the process! In short, I offer, for a reasonable fee, to ship what they wish from Ogden to wherever they may desire.

My background consists of thirteen years in electronics, the last 6 months of which have been as a quality control inspector in the same field. I could, most likely, even inspect the item they wish to bid on, given enough lead time. Not only will all the hams out there benefit, but maybe I'll finally be able to join the fraternity.

If I should thrive at this, I shall definitely make it a business and we'll all benefit because then I'll be able to afford to advertise in your superb magazine. Until then, I shall have to rely on your largess to print this in your next Letters column. If anyone out there is interested, please have them include an SASE.

Thomas W. Newbery
610 North Liberty St.
Ogden UT 84404

HOT CHIHUAHUA

I am returning to the frontiers of Texas again, this time backpacking in the arid wilderness mountains of the Chihuahuan Desert. Please publish the particulars of the expedition so that more experimental NBVM stations may participate. One of the following mountain ranges will be selected for a base camp above the desert floor where temperatures will be more tolerable while operating: Chisos, Davis, Glass, Guadalupe, Christmas, Solitario, or Caballo Muerta.

We will carry in all water, radios, a solar array, food, and shelter. We will be operating Sunday, July 1, through Saturday, July 7, with a two-Watt output transceiver in NBVM, SSB, and CW modes on all HF bands. In addition, we will carry a Tempo S1 2-meter FM hand-held (1.5 Watts). There are a few VHF

Continued on page 176

CB TO 10 METER

10 METER CONVERSION KITS FOR CB RADIOS AM and SSB

- Kits for over 300 Models of CB Radios
- Low Cost from $10.00
  Easy to Install with All Instructions
  Tune-Up Procedure Alignment
- KITS FOR MOST POPULAR UNITS
  Over 5,000 Satisfied Customers
- Write or Call Today for FREE list of kits. If we don't stock it—we'll make a kit for you.

AMERICAN CRYSTAL SUPPLY COMPANY
PO Box 638
W Yarmouth, MA 02673
(617) 771-4634
A58

FOR BEST PRICE AND FAST DELIVERY
CALL
1-800-325-3636
TOLL FREE
HAM RADIO CENTER
8840-42 Olive Blvd P.O. Box 28271 St. Louis, MO 63132
H2

CONNECTOR ASSORTMENT
$25.00 Postpaid **$23.50** each lots of three
Includes: 5 - PL259, 5 - SO239, 5 - UG175, 5 - UG176, 2 - PL258, 1 - DM, 1 - M358, 2 - M359, 1 - UG255, 1 - UG273, 2 - PL259PO, 1 - 1021-20, 1 - Lightning Arrestor.
Master Charge & Visa accepted / Send for Free Catalog
COAKIT C21
P.O. Box 101-A Dumont, N. J. 07628
Circle C21 on Reader Service Card

. . . at last . . .
your shack organized!
A beautiful piece of furniture — your XYL will love it!
$149.95 S-F RADIO DESK
Deluxe - Ready to Assemble
Designed with **angled** rear shelf for your viewing comfort and ease of operation.
FINISHES: Walnut or Teak Stain.
Also available in Unfinished Birch, **$134.95**
Additional Information on Request.
Checks, Money Orders, BankAmericard and Master Charge Accepted.
F.O.B. Culver City. (In Calif. Add 6% Sales Tax.) S33
S-F AMATEUR RADIO SERVICES
4384 KEYSTONE AVENUE • CULVER CITY, CALIF. 90230 — PHONE (213) 837-4870

BI-DIRECTIONAL CASSETTE RECORDERS
★SPECIAL BARGAIN SALE★

Every now and then we run into something unusual in our shopping for equipment. In this case it was a particularly good buy on Sonex cassette recorders. We needed a bunch of recorders for code tape duplication . . . but in order to buy at a low price we had to take about 50 more than we needed. *You benefit.* These cassette recorders record and play both directions without stopping. You might expect to pay from $250 up for a recorder like this . . . we'll pass them along at our cost . . . after all, we're not in the recorder business. While they last, get these recorders for $75 each. One to a customer, please . . . don't be greedy. You can call up the Radio Bookshop and place your order with a charge card: 603-924-3873.

73 MAGAZINE, PETERBOROUGH, NEW HAMPSHIRE 03458

THE SMART CHOICE IN
MC REPEATER CONTROL
Now with three exciting new features:

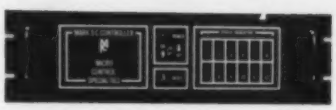

- **Long Distance Calling**
- **Autodialing**
- **Remotely selectable timeout limits**

IMAGINE A CONTROLLER —
SO VERSATILE It provides four different classes of output functions in addition to autopatch and reverse autopatch.
SO RESPONSIVE It sends thirteen Morse codded messages to keep you fully informed. Messages like BZ if you try to access a busy autopatch line.
SO ADVANCED It uses microprocessor technology and non-falsing digital tone decoding.
SO PERSONALIZED that many features are custom programmed to accommodate your unique needs.
SO EASY It can be installed in minutes with only five essential connections.

NOW imagine automatic dialing of emergency telephone numbers, long distance autopatch calling under control op supervision, plus remotely commandable timeout limits to match various operating conditions and you've just imagined the MARK 3C.
The MARK 3C is a complete control system with all audio and logic circuitry, status display, and power supply in one handsome cabinet. Its third generation design can replace racks of hardwired equipment while giving vastly expanded capability.
Get the field-proven power that only a MARK 3C can give at $995. (100% factory assembled and tested)

M69
Call or Write for specifications
MICRO CONTROL SPECIALITIES (617) 372-3442
23 Elm Park, Groveland, Ma. 01834

Reader Service—see page 211

Looking West

Bill Pasternak WA6ITF
24854-C Newhall Ave.
Newhall CA 91321

Mike Davis WD6FFV of Torrance, California, is a real live 13-year-old hero. On the evening of April 24th, Mike's parents gave him permission to stay up late in order to indulge in a bit of his favorite pastime: operating his station and hunting DX. Everyone else in the house was asleep as Mike searched the band looking for the western Caroline Islands. At about 1:00 am on the morning of April 25th, Mike happened across a QSO between someone on a fishing boat off the coast of Jamaica and someone in New Zealand. Conditions between the craft (later identified as the fishing vessel *Carmen*) and ZL-land were poor at best, and the information exchanged showed that an emergency existed. When those aboard the *Carmen*, identified as the boat's owner Leonard Hutchinson and crew members David Dalquist and Sergio Perez, again sent out a "Mayday" call, Mike responded, obtained their latitude and longitude, and phoned this information to the Long Beach Coast Guard station, which in turn relayed same to Miami. The situation was this: The *Carmen* was some 60 miles off the coast of Jamaica. It had been severely battered by high winds and rough seas and was taking on water. Those aboard knew that the craft would sink; they needed immediate rescue. Mike spent the next 45 minutes relaying information between the Coast Guard and the stricken *Carmen* until the signal from the vessel disappeared due to changes in propagation. It was at that time that a W5 in New Mexico acquired the *Carmen*'s signal and continued the relay between the Miami Coast Guard and the *Carmen*.

As a result of Mike's quick thinking, the Coast Guard dispatched a rescue plane which dropped a pump, rescue raft, and marine Coast Guard radio. Later, the cutter *Sherman* took the stricken 75' *Carmen* in tow and brought it back to Montego Bay, Jamaica. A spokesman for the Coast Guard credited the success of the rescue to Mike's quick thinking and positive action. Because he maintained his cool, three men who might have drowned are alive today. They have a 13-year-old amateur radio operator in Torrance, California, to thank for this.

THE "HAIL-TO-THE-QUEEN" DEPARTMENT

Nate Brightman K6OSC is another amateur we can all take pride in. He is a ham who had a dream and persevered for twelve years to see it come true. Thanks to Nate, amateur radio is now operational in full view of the general public on a day-to-day basis aboard one of southern California's most renowned tourist attractions: the *Queen Mary* ocean liner now permanently docked in Long Beach harbor.

Nate is a member of the Associated Radio Amateurs of Long Beach, California. Twelve years ago, when the *Queen Mary* made her last sea voyage from England to her final home in Long Beach, Nate and his club thought that it would be fitting to have an operational amateur station on the trip. Nate spearheaded the drive and succeeded. It was at that time that the idea of a permanent station came to him. Having an idea and making it come true are not always one and the same. In this case it took years. During its transition from an ocean liner to a tourist attraction and hotel, the original wireless room had been dismantled. Nate's idea was to restore this room to as close to its original state as possible and then add a permanent amateur station.

On April 22, 1979, Nate's dream came true. On that evening, Sharon and I attended a special invitational press preview of what had been accomplished by Nate and the Associated Radio Amateurs of Long Beach. On the top deck of the illustrious *Queen*, the wireless room had indeed been restored. Amid the relics of times gone by was nestled neatly, in a special panel arrangement, some of today's most sophisticated amateur equipment on indefinite loan from such well-known firms as Yaesu, Trio-Kenwood, Swan, DenTron, and others. What about antennas? Neatly built into one of the *Queen's* stacks and rising above it stands a triband beam and a two-meter Ringo from Cushcraft. The array is rotated by an Alliance rotor. Shortly, two dipoles (one for 75/80 and another for 40 meters) will give the ship's station 80- through 2-meter capability (six meters excluded).

Something very apropos happened the evening that the station opened. After the initial ceremony was concluded, it was time to place the station on the air. One of those present was famed DXer Don Wallace W6AM. When his turn came, Don contacted a station in New Zealand. As the QSO progressed, it was learned that the ZL had been one of the wireless operators who served on the *Queen Mary* during World War II. I remember the ZL saying, "Don, if you are where I think you are, then I preceded you some 30 years ago and had my feet in the same spot that yours are now." All of us gathered around the TS-820's speaker beamed with delight. If the QSO had been planned—and it was not—nothing could have been

Continued on page 170

A very happy Nate Brightman K6OSC (center) chats with Roy Neal K6DUE (left) and WA6ITF during a break in the filming of "The World of Amateur Radio" aboard the Queen Mary. *(Photo by KH6IAF)*

OMNI HAS IT *ALL*. All the advantages and capabilities, all the new conveniences and new levels of performance you need, whatever your HF operating specialty. All built-in, ready to use.

***ALL* SOLID-STATE.** All the advantages of total solid-state from the pioneer of HF solid-state technology. Reliable, cool, stable — from receiver front-end to transmitter final.

***ALL* HF BANDS.** From 160 through 10 meters (and all the crystals) plus convertible 10 MHz and "AUX" band positions for possible future needs.

***ALL* BROADBAND.** Band changing without tuneup — without danger to the final amp.

***ALL* READOUTS.** Choose OMNI-A for analog dial (1 kHz markings) or OMNI-D for six 0.43" LED digits (100 Hz readability.)

***ALL* VOX AND PTT FACILITIES** built-in; 3 VOX controls plus PTT control at front and rear jacks for external PTT switch.

***ALL* SQUELCH NEEDS** for tuning and monitoring are built-in.

***ALL* FILTERS INCLUDED:** 4-position CW/SSB filter (150 Hz bandwidth with 3 selectable skirt contours) plus 8-pole Crystal filter (2.4 kHz bandwidth, 1.8 shape factor.)

***ALL* MODE SWITCH** puts all filters to work in any mode.

***ALL* BREAK-IN:** Instant or delayed receiver muting to fit any band condition or mobile operation.

***ALL*-VERSATILE OFFSET TUNING;** dual ranges, ±5 kHz range for off-frequency DX or ±0.5 kHz range for fine tuning.

***ALL*-SENSITIVE RECEIVER;** from 2 μV on 160 m to 0.3 μV on 10 m (10 dB S+N/N) for ideal balance between dynamic range and sensitivity.

***ALL* OVERLOADS HANDLED;** dynamic range typically exceeds 90 dB and PIN diode switched 18 dB attenuator also included for extra overload protection.

***ALL* LINEAR/ANTENNA BANDSWITCHING FROM FRONT PANEL;** auxiliary bandswitch terminals on back panel for external relays or circuits are controlled simultaneously by the OMNI bandswitch.

***ALL* INTERFACE JACKS FOR PHONE PATCH;** access to speaker and microphone signals.

***ALL*-LEVEL ADJUSTABLE ALC;** set output from low power to full, retain low distortion at desired drive to power amp.

***ALL* SIDETONE ADJUSTMENTS;** pitch and volume.

***ALL*-POWERFUL, *ALL*-WARRANTED FINAL AMPLIFIER.** 200 watts input to final. Proven design with full warranty for first year and pro-rata warranty for additional 5 years.

***ALL* 100% DUTY CYCLE.** For RTTY, SSTV or sustained hard usage.

***ALL*-MODE POWER:** basic 12 VDC for easy mobile use, external supplies for 117/220 VAC operation.

***ALL* FRONT PANEL MICROPHONE AND PHONE JACKS.** Convenient.

PLUS *ALL* THE OTHER HANDY BUILT-INS: "Timed" 25 kHz crystal calibrator in OMNI-A with automatic 5-10 sec."on" time for easy 2-hand dial skirt adjustment . . . Zero-Beat switch for placing your signal exactly on CW listening frequencies . . . SWR bridge switches "S" meter to read SWR each time you transmit for continuous antenna monitoring . . . Separate receive antenna capability . . . Dual speakers for greater sound at lower distortion . . . Plug-in circuit boards for fast, easy field service.

***ALL*-FUNCTIONAL STYLING.** "Clamshell" aluminum case clad in textured black vinyl with complementary nonreflective warm dark metal front panel and extruded aluminum bezel and bail. Convenient controls. Complete shielding. And easier-to-use size: 5¾"h x 14¼"w x 14"d.

AND *ALL* THE OPTIONS: Model 645 Keyer, Model 243 Remote VFO, Model 248 Noise Blanker, Model 252MO AC Power Supply.

Model 545 OMNI-A $899 **Model 546 OMNI-D $1069**

Experience the *all*-encompassing HF world of OMNI. See your TEN-TEC dealer or write for *all* the details.

arma

TEN-TEC, INC.
SEVIERVILLE, TENNESSEE 37862
EXPORT: 5715 LINCOLN AVE., CHICAGO, ILL. 60646

TEN-TEC's "OMNI" FILLS *ALL* YOUR HF NEEDS

OSCAR Orbits

Courtesy of AMSAT

The listed data tells you the time and place that OSCAR 7 and OSCAR 8 cross the equator in an ascending orbit for the first time each day. To calculate successive OSCAR 7 orbits, make a list of the first orbit number and the next twelve orbits for that day. List the time of the first orbit. Each successive orbit is 115 minutes later (two hours less five minutes). The chart gives the longitude of the day's first ascending (northbound) equatorial crossing. Add 29° for each succeeding orbit. When OSCAR is ascending on the other side of the world from you, it will descend over you. To find the equatorial descending longitude, subtract 166° from the ascending longitude. To find the time OSCAR 7 passes the North Pole, add 29 minutes to the time it passes the equator. You should be able to hear OSCAR 7 when it is within 45 degrees of you. The easiest way to determine if OSCAR is above the horizon (and thus within range) at your location is to take a globe and draw a circle with a radius of 2450 miles (4000 kilometers) from your QTH. If OSCAR passes above that circle, you should be able to hear it. If it passes right overhead, you should hear it for about 24 minutes total. OSCAR 7 will pass an imaginary line drawn from San Francisco to Norfolk about 12 minutes after passing the equator. Add about a minute for each 200 miles that you live north of this line. If OSCAR passes 15° east or west of you, add another minute; at 30°, three minutes; at 45°, ten minutes. Mode A: 145.85-.95 MHz uplink, 29.4-29.5 MHz downlink, beacon at 29.502 MHz. Mode B: 432.125-.175 MHz uplink, 145.975-.925 MHz downlink, beacon at 145.972 MHz.

OSCAR 8 calculations are similar to those for OSCAR 7, with some important exceptions. Instead of making 13 orbits each day, OSCAR 8 makes 14 orbits during each 24-hour period. The orbital period of OSCAR 8 is therefore somewhat shorter: 103 minutes.

To calculate successive OSCAR 8 orbits, make a list of the first orbit number (from the OSCAR 8 chart) and the next thirteen orbits for that day. List the time of the first orbit. Each successive orbit is then 103 minutes later. The chart gives the longitude of the day's first ascending equatorial crossing. Add 26° for each succeeding orbit. To find the time OSCAR 8 passes the North Pole, add 26 minutes to the time it crosses the equator. OSCAR 8 will cross the imaginary San Francisco-to-Norfolk line about 11 minutes after crossing the equator. Mode A: 145.85-.95 MHz uplink, 29.4-29.50 MHz downlink, beacon at 29.40 MHz. Mode J: 145.90-146.00 MHz uplink, 435.20-435.10 MHz downlink, beacon on 435.090 MHz.

OSCAR 7 Orbital Information				OSCAR 8 Orbital Information			
Orbit	Date (July)	Time (GMT)	Longitude of Eq. Crossing °W	Orbit	Date (July)	Time (GMT)	Longitude of Eq. Crossing °W
21151	1	0021:39	58.3	6728Jbn	1	0045:35	56.3
21164qrp	2	0115:58	82.9	6742Abn	2	0050:46	57.6
21178	3	0015:16	67.8	6756Abn	3	0055:56	58.9
21189X	4	0109:33	81.3	6770X	4	0101:06	60.2
21201	5	0008:53	66.2	6784Abn	5	0106:17	61.5
21214	6	0103:10	79.8	6798Abn	6	0111:27	62.9
21226	7	0002:31	64.6	6812Jbn	7	0116:37	64.2
21239	8	0056:48	78.2	6826Jbn	8	0121:48	65.5
21252qrp	9	0151:04	91.8	6840Abn	9	0126:58	66.8
21264	10	0050:25	76.7	6854Abn	10	0132:08	68.1
21277X	11	0144:42	90.3	6868X	11	0137:18	69.4
21289	12	0044:02	75.1	6882Abn	12	0142:29	70.7
21302	13	0138:19	88.7	6895Abn	13	0004:25	46.2
21314	14	0037:39	73.6	6909Jbn	14	0009:35	47.5
21327	15	0131:56	87.1	6923Jbn	15	0014:46	48.8
21339qrp	16	0031:16	72.0	6937Abn	16	0019:56	50.1
21352	17	0125:33	85.6	6951Abn	17	0025:06	51.4
21364X	18	0024:54	70.4	6965X	18	0030:16	52.7
21377	19	0119:11	84.0	6979Abn	19	0035:26	54.1
21389	20	0018:31	68.9	6993Abn	20	0040:36	55.4
21402	21	0112:48	82.5	7007Jbn	21	0045:46	56.7
21414	22	0012:08	67.3	7021Jbn	22	0050:56	58.0
21427qrp	23	0106:25	80.9	7035Abn	23	0056:07	59.3
21439	24	0005:45	65.8	7049Abn	24	0101:17	60.6
21452X	25	0100:02	79.4	7063X	25	0106:27	61.9
21465	26	0154:19	92.9	7077Abn	26	0111:37	63.2
21477	27	0053:40	77.8	7091Abn	27	0116:47	64.5
21490	28	0147:56	91.4	7105Jbn	28	0121:57	65.8
21502	29	0047:17	76.2	7119Jbn	29	0127:07	67.1
21515qrp	30	0141:34	89.8	7133Abn	30	0132:17	68.4
21527	31	0040:54	74.7	7147Abn	31	0137:27	69.8

RTTY Loop

Marc I. Leavey, M.D. WA3AJR
4006 Winlee Road
Randallstown MD 21133

Oh, heavy sigh and deja vu, didn't we have a computer program in last July's RTTY Loop? Of course we did, but, as promised last month, this is the other half: the transmitting program for the 6800. Let's plunge right into the program, shown in Program 1. If you have the flowcharts from last month handy, use them along side.

The first 96 memory locations ($20 to $7F) are reserved for the table used to convert ASCII to Baudot. The ASCII value is used as an index to retrieve the data, representing the Baudot representation of that ASCII code. The encoding used represents the Baudot case as the Most Significant Bit (MSB), "1" for Letters and "0" for Figures, and the next five bits the character itself. Thus, ASCII "R", which has a value of $52, is found at memory location $72 [$20 (start of table) + $52 (R value) = $72]. The data at that location is $A8, which, in binary, is 10101000. This interprets to 1 - 01010 - 00, or LTRS - Baudot code 01010 (R). The last two bits are not used in this scheme. Note that, for example, a "4", which is ASCII $34 and found at location $54 in the table, would be represented by $28. This is binary 0 - 01010 - 00. That is, FIGS - Baudot code 01010 (R), since "4" is the uppercase Baudot "R".

Continued on page 166

Program 1.

```
0010                    NAM     RTTYXMIT
0020                    OPT     O,NOG

0040                *
0050                * RTTY TRANSMIT PROGRAM
0060                * VER 0.6 - 06 MAY 79
0070                * MARC I. LEAVEY, M.D.
0080                *

0100                * EXTERNAL REFERENCES
0110                *
0120    801C    PIADA   EQU     $801C
0130    801D    PIACA   EQU     $801D
0140    E07E    PDATA   EQU     $E07E
0150    E1AC    INEEE   EQU     $E1AC
0160    A048    PGCTR   EQU     $A048
0170                *
0180 0020               ORG     $20
0190 0020 FE    TABLE   FCB     $FE             LETTERS
0200 0021 00            FCB     0,0,0
0210 0024 00            FCB     0,0,0
0220 0027 50            FCB     $50             BELL
0230 0028 00            FCB     0,0
0240 002A A0            FCB     $A0             LINE FEED
0250 002B 00            FCB     0,0
0260 002D FF            FCB     $FF             CARRIAGE
0270 002E 00                    FCB     0,0,0   RETURN
0280 0031 00                    FCB     0,0,0
0290 0034 00                    FCB     0,0,0
0300 0037 00                    FCB     0,0,0
0310 003A 00                    FCB     0,0,0
0320 003D 00                    FCB     0,0,0
0330 0040 90            FCB     $90             SPACE
0340 0041 58            FCB     $58             !
0350 0042 44            FCB     $44             "
0360 0043 FF            FCB     $FF             #
0370 0044 48            FCB     $48             $
0380 0045 FF            FCB     $FF             %
0390 0046 2C            FCB     $2C             &
0400 0047 68            FCB     $68             '
0410 0048 78            FCB     $78             (
0420 0049 24            FCB     $24             )
0430 004A FF            FCB     $FF             *
0440 004B FF            FCB     $FF             +
0450 004C 18            FCB     $18             ,
0460 004D 60            FCB     $60             -
0470 004E 1C            FCB     $1C             .
0480 004F 5C            FCB     $5C             /
0490 0050 34            FCB     $34             0
0500 0051 74            FCB     $74             1
0510 0052 64            FCB     $64             2
0520 0053 40            FCB     $40             3
0530 0054 28            FCB     $28             4
0540 0055 04            FCB     $04             5
0550 0056 54            FCB     $54             6
0560 0057 70            FCB     $70             7
0570 0058 30            FCB     $30             8
0580 0059 0C            FCB     $0C             9
0590 005A 38            FCB     $38             :
0600 005B 3C            FCB     $3C             ;
0610 005C FF            FCB     $FF             <
0620 005D FF            FCB     $FF             =
0630 005E FF            FCB     $FF             >
0640 005F 4C            FCB     $4C             ?
0650 0060 FF            FCB     $FF             @
0660 0061 E0            FCB     $E0             A
0670 0062 CC            FCB     $CC             B
0680 0063 B8            FCB     $B8             C
0690 0064 C8            FCB     $C8             D
0700 0065 C0            FCB     $C0             E
0710 0066 D8            FCB     $D8             F
0720 0067 AC            FCB     $AC             G
0730 0068 94            FCB     $94             H
0740 0069 E0            FCB     $E0             I
0750 006A E8            FCB     $E8             J
0760 006B F8            FCB     $F8             K
0770 006C A4            FCB     $A4             L
0780 006D 9C            FCB     $9C             M
0790 006E 98            FCB     $98             N
0800 006F 8C            FCB     $8C             O
0810 0070 B4            FCB     $B4             P
0820 0071 F4            FCB     $F4             Q
0830 0072 A8            FCB     $A8             R
0840 0073 D0            FCB     $D0             S
0850 0074 84            FCB     $84             T
0860 0075 F0            FCB     $F0             U
0870 0076 BC            FCB     $BC             V
0880 0077 E4            FCB     $E4             W
0890 0078 DC            FCB     $DC             X
0900 0079 D4            FCB     $D4             Y
0910 007A C4            FCB     $C4             Z
0920 007B FF            FCB     $FF             [
0930 007C FF            FCB     $FF             \
0940 007D FF            FCB     $FF             ]
0950 007E FF            FCB     $FF             ↑
0960 007F FF            FCB     $FF             ←
0970 0080 23    SPTABL  FCB     $23,$98,$A8     #=NR
0980 0083 25            FCB     $25,$B4,$B8     %=PC
0990 0086 2A            FCB     $2A,$E0,$D0     *=AS
1000 0089 2B            FCB     $2B,$B4,$A4     +=PL
1010 008C 3C            FCB     $3C,$A4,$B4     <=LT
1020 008F 3D            FCB     $3D,$C0,$74     ==EQ
1030 0092 3E            FCB     $3E,$AC,$B4     >=GT
1040 0095 40            FCB     $40,$E0,$B4     @=AT
1050 0098 5B            FCB     $5B,$78,$78     [=((
```

Continued on page 166

WHEN OUR CUSTOMERS TALK...WE LISTEN.

We've Been Taking Notes.

Combining your ideas with some of our own, we've come up with what has to be the most advanced and convenient terminal available. These are some of the conveniences you can now enjoy by putting the DS3100 ASR in your RTTY and CW station.

ASR Operation (Compose your transmission *WHILE* receiving)

- 150-line Receiver Buffer
- 50-line Transmit Buffer
- Split Screen to Show Buffers
- Internal Real-Time Clock
- 10 Programmable Messages
- Automatic Answer-Back (WRU)
- Morse, Baudot, or ASCII Operation
- RTTY and CW Identification
- Full 128-Character ASCII
- 110-9600 baud ASCII
- 60-130 WPM Baudot
- 1-175 WPM Morse

Write or call for the DS3100 ASR specifications and see how *YOU* have helped design the new standard in amateur radio terminals.

HAL COMMUNICATIONS CORP.
Box 365
Urbana, Illinois 61801
217-367-7373

For our European Customers Contact
Richter & Co., Hannover
I.E.C. Interelco, Bissone

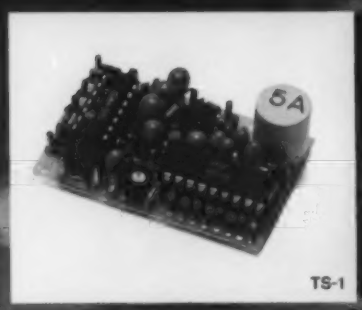

TS-1

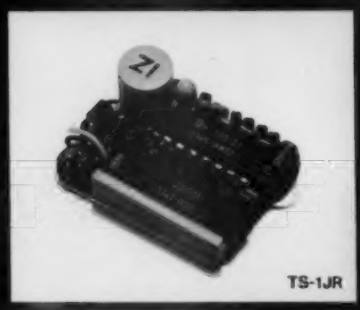

TS-1JR

PE-2

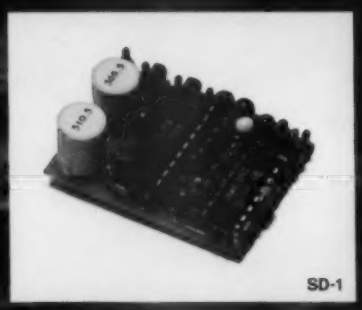
SD-1

THE DAWNING

The age of tone control has come to Amateur Radio. What better way to utilize our ever diminishing resource of frequency spectrum? Sub-audible tone control allows several repeaters to share the same channel with minimal geographic separation. It allows protection from intermod and interference for repeaters, remote base stations, and autopatches. It even allows silent monitoring of our crowded simplex channels.

We make the most reliable and complete line of tone products available. All are totally immune to RF, use plug-in, field replaceable, frequency determining elements for low cost and the most accurate and stable frequency control possible. Our impeccable 1 day delivery is unmatched in the industry and you are protected by a full 1 year warranty when our products are returned to the factory for repair. Isn't it time for you to get into the New Age of tone control?

ME-3

TE-8

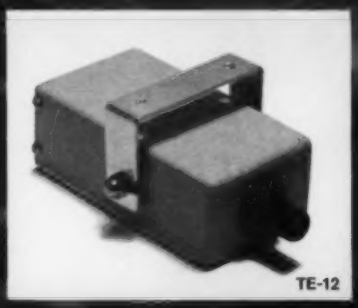
TE-12

ST-1

OF A NEW AGE.

TS-1 Sub-Audible Encoder-Decoder • Microminiature in size, 1.25" x 2.0" x .65" • Encodes and decodes simultaneously • **$59.95** complete with K-1 element.

TS-1JR Sub-Audible Encoder-Decoder • Microminiature version of the TS-1 measuring just 1.0" x 1.25" x .65", for hand-held units • **$79.95** complete with K-1 element.

ME-3 Sub-Audible Encoder • Microminiature in size, measures .45" x 1.1" x .6" • Instant start-up • **$29.95** complete with K-1 element.

TE-8 Eight-Tone Sub-Audible Encoder • Measures 2.6" x 2.0" x .7" • Frequency selection made by either a pull to ground or to supply • **$69.95** with 8 K-1 elements.

PE-2 Two-Tone Sequential Encoder for paging • Two call unit • Measures 1.25" x 2.0" x .65" • **$49.95** with 2 K-2 elements.

SD-1 Two-Tone Sequential Decoder • Frequency range is 268.5 - 2109.4 Hz • Measures 1.2" x 1.67" x .65" • Momentary output for horn relay, latched output for call light and receiver muting built-in • **$59.95** with 2 K-2 elements.

TE-12 Twelve-Tone Sub-Audible or Burst-Tone Encoder • Frequency range is 67.0 - 263.0 Hz sub-audible or 1650 - 4200 Hz burst-tone • Measures 4.25" x 2.5" x 1.5" • **$79.95** with 12 K-1 elements.

ST-1 Burst-Tone Encoder • Measures .95" x .5" x .5" plus K-1 measurements • Frequency range is 1650 - 4200 Hz • **$29.95** with K-1 element.

mastercharge
VISA

COMMUNICATIONS SPECIALISTS
426 West Taft Avenue, Orange, CA 92667
(800) 854-0547. California residents use: (714) 998-3021

FOR BEST PRICE AND FAST DELIVERY

CALL

1-800-325-3636

TOLL FREE

HAM RADIO CENTER

8400-02 Olive Blvd. P.O. Box 28271 St. Louis, MO 63132

H2

HAMTRONICS, INC.

WHERE THE HAM IS KING — FOR OVER 30 YEARS

H8

Let Us Fill Your Specific Needs From

OUR $2,000,000.00 AMATEUR GEAR INVENTORY

ALL THE FAMOUS NAMES—TRANSCEIVERS—AMPLIFIERS—ANTENNAS—TOWERS

Give us a try before you buy • Call Jim Titus

a Division of TREVOSE ELECTRONICS, INC/ 4033 Brownsville Road, Trevose, PA 19047

FREE UPS SHIPPING ON PREPAID ORDERS

VISA

215-357-1400

13-510 MIDLAND OWNERS 13-513 SCANNER KITS

CLEGG FM-28 OWNERS: SCANNER KITS

Does everything the TR-7400A scanner does only you select the MHz segment you want. The scan rate is 200 kHz/sec.
Kit $39.95. Preassembled and tested $59.95
(Add $1.50 for postage and handling)

TR7400A "KENWOOD" OWNERS: SCANNER KIT

- Installs completely inside rig. No obtrusive external connections.
- Scans the complete band or only the portion you select on the MHz switch of your rig (e.g., 144-148 or 146-148 MHz).
- Scan frequency is displayed on digital readout.
- Two miniature toggle switches supplied with kit (scanner: on-off, scan-lock may be mounted externally or on the top or bottom cover of the rig.
- In the scanner off mode the TR-7400A behaves normally. In the scanner ON mode the scanner locks up on an occupied frequency, pauses for a preset time (3-30 seconds) and then resumes scanning. This means you can eavesdrop all over the band without lifting a finger. When you hear something interesting you flip the switch to the lock mode and the rig is ready to transmit.
- Scans at the rate of 50 kHz per second.
- Complete with detailed instructions (even for the beginner).

INTRODUCTORY OFFER
Kit: $39.95; preassembled and tested: $59.95
Add $1.50 for postage and handling

FT-227 "MEMORIZER" OWNERS: SCANNER KIT

- Selectable sweep width (up to full band).
- Scans *only* the portion of band you select.
- Scans at the rate of 200 kHz per second.
- Switch modification on mike allows you to scan past, or lock on, any occupied frequency.
- Complete kit with detailed instructions.
- Installs *inside* rig; no obtrusive external connections.
- Rig can easily be returned to original condition whenever desired.
- Scans to preset limits and reverses.
- Automatic bypass of locked frequency in 3½ seconds unless you press lock-on switch.

Kit: $34.95, preassembled and tested $54.00
Add $1.50 for postage and handling

IC22S SCANNER KITS

Also available
Kit $34.95; $54.00 Assembled add $1.50 postage and handling

DEALER INQUIRIES INVITED

VISA

AED ELECTRONICS A60

750 LUCERNE RD., SUITE 120
MONTREAL, QUEBEC, CANADA H3R 2H6
TEL. 514-737-7293

NOW from BETTS

Hypersil power transformer
Pri has 4 115 for 230 or 440;
Sec 803 @ 735 ma.—Use 2 xfmrs bridged for 1500 VDC
Price pre-paid USA **$39.95**

Jennings vacuum variables
UCS-500 @ 7.5KV **$165.**
UCSXF-1000 @ 10KV **$255.**
UCSXF-1200 @ 10KV **$275.**

Filter choke, swinging
3-15 hy @ .6-.06 amp res 112
1KV ins. 5x6x7 29 lbs.
Ship pre-paid USA **$39.95**

Oil filter capacitor
10 mfd @ 2KV 3x4x5 5 lbs
Ship pre-paid USA **$15.95**

Send check with orders

J. S. BETTS COMPANY B49

P.O. Box 426 Fairburn, GA 30213
Phone (404)-964-3764

NEW ELECTRONIC PARTS

Brand name, first line components. Stocked in depth. 24 hour delivery. Low prices and money back guarantee on all products we carry.
STAMP BRINGS CATALOG

SPECIALS

KEYBOARD ENCLOSURES

SIX SIZES

	W	D	H	PRICE
14"	8.3"	3"		$15.20
17"	8.3"	3"		18.35
20"	8.3"	3"		19.25
14"	11.3"	3"		16.50
17"	11.3"	3"		18.80
20"	11.3"	3"		20.75

Blue base, specify white or black top.

MAGNA-LITE JR
ONLY $5.79

- Printed Microcircuit reading
- Electronics — Design, Production & Inspection
- Industrial — Engineers, Technicians, Draftsmen
- Laboratory & Research

RTTY
UT4 SPEED CVTR BOARD KIT $109.95
BOARD ALONE $18.95
AUTO CW ID KIT $37.90

VISA

SHIPPING INCLUDED IN PRICE

Daytapro Electronics, Inc.

Formerly NuData Electronics — D35

3029 N. WILSHIRE LN., ARLINGTON HTS., ILL. 60004
PHONE 312-870 0555

FAST SCAN 420-450 MHz
an ATV FIRST • • • from APTRON
our NEW-
Model 1570B

ATV REPEATER

a COMMERCIAL QUALITY system providing for COLOR operation with AURAL SUBCARRIER sound plus many more features.....
a complete, single package unit ready to put on the air... also complete antenna available...
Call us at 1-812-336-4775, or write us for details and pricing.

APTRON LABORATORIES A6
PO Box 323 Bloomington IN 47401

Reader Service—see page 211

Contests

Robert Baker WB2GFE
15 Windsor Dr.
Atco NJ 08004

COLOMBIAN INDEPENDENCE DAY CONTEST
Starts: 0001 GMT
Saturday, July 14
Ends: 2359 GMT
Sunday, July 15

The purpose of this contest is to commemorate the Colombian 169th independence anniversary and to promote and increase DX activity of HK radio amateurs. Entry classifications include: single operator/single band, single operator/multiband, multi-operator/multiband/one rig. Use all amateur bands 80 through 10 meters on phone, SSB, or CW. Only one contact per band with the same station will be permitted. No crossband or crossmode contacts. Club stations can only take part as multi-operator/multiband/single transmitter. A minimum of 50 QSOs must be shown in logs when applying for any award.

EXCHANGE:

RS(T) and QSO number from 001.

SCORING:

Each QSO with an HK station scores 5 points, each station in another continent counts 3 points, a station in a DX country counts 2 points, and stations in the same country count 1 point. The multiplier is the total number of different countries worked on each band. The total score will be the sum of QSO points on each band multiplied by the sum of different countries worked on each band.

ENTRIES AND AWARDS:

Logs must show all times in GMT; keep separate logs for each band and enter the country only the first time it is contacted. Each entry must be accompanied by a summary sheet listing all scoring info. The logs not summarized according to the abovementioned instructions will be used only as check logs. Awards include a silver plate for the world winner, certificates for continental winners, and winners in each classification. Violation of the regulations of amateur radio in the country of the contestant or the rules of the contest, taking credit for incorrect QSOs or multipliers, or duplicate contacts in excess of 2% of the total made will be deemed sufficient cause for disqualification. The LCRA Contest Awards Committee decisions shall be final. All logs must be mailed to: LCRA—Concurso Independencia, c/o Contest Committee Manager, Apartado Postal 584, Bogota, Colombia, SA. All entries must be postmarked no later than September 30.

CW COUNTY HUNTERS CONTEST
Starts: 0000 GMT July 28
Ends: 0200 GMT July 30

The CW County Hunters Net invites all amateurs to participate in the 1979 contest. All mobile and portable operation in less active counties is welcome and encouraged. General call is "CQ CH." Stations may be worked once on each band and again if the station has changed counties. Portable or mobile stations changing counties during the contest may repeat contacts for QSO points. Stations on county lines give and receive only one number per QSO, but each county is valid for a multiplier. Suggested frequencies are 3575, 7055, 21070, and 28070. It is requested that only portable or mobile category stations call CQ or QRZ on 40 meters below 7055 and on 20 meters below 14070 with all stations spreading out above those frequencies.

EXCHANGE:

QSO number, category (portable = P, mobile = M), RST, state/province/country, and US county.

SCORING:

QSOs with fixed stations are 1 point; portable or mobile stations are 3 points. Multiply the number of QSO points times the number of US counties worked. Mobiles and portables calculate their score on the basis of total contacts within a state.

AWARDS:

Certificates will be awarded in three categories: Fixed—highest fixed or fixed portable station in each state, province, and country with 1,000 or more points; Portable—highest station in each state operating portable from a county which is not his normal point of operation with 1,000 or more points; Mobile—highest mobile in each state operating from 3 or more counties with a minimum of 10 QSOs per county.

Trophies will be awarded to the highest single-operator station in the US in categories P and M. The awards committee will issue additional awards where deemed appropriate.

ENTRIES:

Logs must show category, date/time in GMT, station worked, exchanges, band, QSO points, location, and claimed score. All entries with 100 or more QSOs must include a checksheet of counties worked or be disqualified from receiving awards. Enclose a large SASE if results are desired. Logs must be postmarked by September 1 and sent to: CW County Hunters Net, c/o Jeffrey P. Bechner W9MSE, 673 Bruce Street, Fond du Lac WI 54935.

RHODE ISLAND QSO PARTY
Contest Periods: 1700 GMT Saturday, July 28 to 0500 GMT Sunday, July 29
1300 GMT Sunday, July 29 to 0100 GMT Monday, July 30

This contest is sponsored by the East Bay Amateur Wireless Association. RI stations work other RI stations and the rest of the world. Others work RI only. The same station may be worked once per band and mode. No repeater contacts are allowed.

EXCHANGE:

RS(T), QTH = RI county or state, province, or country for others.

SCORING:

RI stations score 2 points per QSO; RI Novice and Tech stations score 5 points per QSO. Others score 2 points per RI QSO and 5 points per QSO with RI Novices or Technicians. RI Novices and Technicians sign with /N or /T to designate license class. RI stations multiply total QSO points by the number of RI counties, states, provinces, and DX countries worked. Others multiply total QSO points by the number of RI counties worked (5 max.). All stations score 10 points for QSO with multi-op station operated by club members, N1RI.

FREQUENCIES:

CW—1810, 3550, 3710, 7050, 14050, 21050, 21110, 28050, 28110.

Continued on page 168

Calendar

June 30-July 1*	**Seven-Land QSO Party**
July 4	**ARRL Straight Key Night**
July 14-15	**ARRL IARU Radiosport Competition**
	Colombian Independence Day Contest
July 28-30	**CW County Hunters Contest**
	Rhode Island QSO Party
	New Jersey QSO Party
Aug 4	**DAFG 10 Meter Contest**
Aug 4-5	**ARRL UHF Contest**
Aug 25-26	**All Asian DX Contest—CW**
Sept 8*	**DAFG Short Contest—VHF**
Sept 8-9	**ARRL VHF QSO Party**
Sept 9*	**DAFG Short Contest—SW**
Sept 14-15	**Kentucky QSO Party**
Sept 15-16	**Scandinavian Activity—CW**
Sept 15-17	**Washington State QSO Party**
Sept 22-23	**Scandinavian Activity—Phone**
Sept 29-30	**Delta QSO Party**
Oct 13-14	**ARRL CD Party—CW**
Oct 20-21	**ARRL CD Party—Phone**
Nov 3-4	**ARRL Sweepstakes—CW**
Nov 10-11	**CQ-WE Contest**
Nov 11	**OK DX Contest**
Nov 17-18	**ARRL Sweepstakes—Phone**
Nov 24*	**DAFG Short Contest—SW**
Nov 25*	**DAFG Short Contest—VHF**
Dec 1-2	**ARRL 160 Meter Contest**
Dec 1-3	**North Carolina QSO Party**
Dec 8-9	**ARRL 10 Meter Contest**

*** = described in last issue**

Results

RESULTS OF THE COLOMBIAN INDEPENDENCE DAY CONTEST 1978

AWARDS

World Winner of the Contest—UK2GKW

Continental Winners of the Contest:
North America K5UR
South America HK4DF
Africa
Asia 9K2FX
Oceania
Europe UK2GKW

Multi-Operator/Multiband/One Rig Highest Scoring Station —UK2GKW

Single Operator/Single Band—9K2FX

Single Operator/Multiband—HK4DF

Microcomputer Interfacing

Christopher A. Titus
David G. Larsen
Peter R. Rony
Jonathan A. Titus

SAMPLE-AND-HOLD DEVICES

Sample-and-hold (S/H) devices or sample-and-hold amplifiers (SHA) are analog circuit elements that are the analog equivalent of the digital latch. They are used when we wish to sample an analog signal and then hold it steady at a particular point so that a voltage of interest may be measured or used elsewhere in a system. The operation of an ideal sample-and-hold device is shown in Fig. 1. In this example, the S/H output follows, or *tracks*, the input during the sample period and then holds the latest analog voltage when it switches to the hold mode. In the figure, the input and output voltage lines are offset slightly for clarity.

Sample-and-hold devices are widely used in conjunction with digital-to-analog and analog-to-digital converters. For example, they may be used to:

- Hold an analog signal steady so that an A/D conversion may be performed;
- Simultaneously sample many analog inputs for later measurement (requires one S/H device per analog input);
- Deglitch a D/A converter's output to eliminate output voltage spikes or settling transients; and
- Distribute one D/A converter's output to several points, where analog voltages must be constantly maintained.

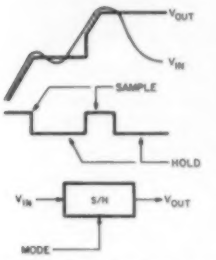

Fig. 1. Inputs and output for an ideal sample-and-hold device. Both the sample and hold modes of operation are shown.

The second and fourth uses listed above are becoming less important than they were two or three years ago. It is probably less expensive now to dedicate an A/D converter to each input to be measured and to have one D/A converter per output, depending upon the specific application.

The most common use of sample-and-hold devices is to sample and hold an analog signal at a particular point while it is measured with an A/D converter. A sample-and-hold device is particularly useful in situations in which a DAC and a comparator are being used in conjunction with microcomputer software to create an A/D converter.[1] When a sample-and-hold device is used prior to the input of the unknown signal to the comparator (or an A/D converter module if one is used), the digitization may proceed to give an accurate representation of the unknown voltage. For example, in Fig. 2 we provide a block diagram for a typical sample-and-hold computer interface that permits you to measure the peak voltage from an instrument. We have assumed here that the instrument provides a positive clock pulse, called PEAK, when the peak maximum is reached. The SAMPLE pulse from the computer allows the S/H module to sample the unknown signal from the instrument. When the peak is reached, the PEAK signal clocks a logic 0 into the output of the flip-flop, forcing the S/H device into the hold mode. Fig. 3 shows the timing diagram that would be generated by the interface circuit shown in Fig. 2. Again, the S/H output and the instrument output have been offset for clarity. Now, either a slow ramp A/D converter or a fast successive approximation A/D converter can be used to provide the correct value for the peak voltage since the S/H device will maintain the voltage until it can be digitized.

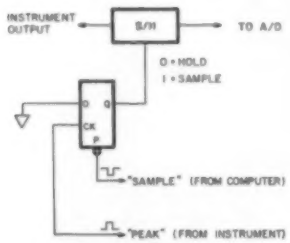

Fig. 2. Block diagram for a typical sample-and-hold microcomputer interface circuit. The instrument supplies the PEAK input pulse to the flip-flop. The SAMPLE pulse from the computer presets the flip-flop to logic 1.

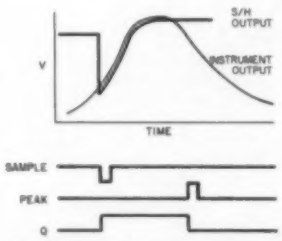

Fig. 3. Typical timing diagram for the interface circuit shown in Fig. 2.

acquisition time	The time required to go from the hold state to the tracking state, in which the output remains within a 0.01% range of the input. This may also be called the settling time when the S/H device is already in the sample mode. The acquisition time is generally a few microseconds. See Fig. 4.
aperture time	The time period required by the device to go from the sample mode into the hold mode once the hold command has been received. The aperture time is generally a few nanoseconds. See Fig. 5.
droop rate, decay rate	The rate of discharge of the sample-and-hold capacitor. The rate is a function of switch leakage current and the current required by other circuit elements connected to the capacitor. It is expressed as millivolts per second. See Fig. 6.
gain error, linearity	The variation of the observed output from the expected output over the entire sample-and-hold device's output voltage range. It is usually expressed as a percentage, say 0.01%. See Fig. 6.
offset	The difference between the input and the output voltages of the device when the input is ground. It is usually expressed as millivolts. The offset may be adjusted to zero using external components, but it will generally change with time and temperature. See Fig. 4.
slew rate	The maximum rate of change for the output, expressed as volts per second. It is a limitation imposed by the charging rate of the capacitors and the actual slew rates of the operational amplifiers present in the S/H circuit. See Fig. 4.

Table 1. Some important concepts associated with sample-and-hold devices.

Sample-and-hold devices are not ideal, and there are some terms that will help you better understand their limitations and uses. These are listed in Table 1, which is keyed to Figs. 4, 5, and 6. As can be observed, there are important limitations to the capabilities of S/H devices. Those devices that have short acquisition times use small capacitors and thus the voltage droop rate will be large. The use of larger capacitors means that the acquisition time will be longer, but the voltage droop will be less. When high acquisition speeds and long hold times are required in an application, two S/H modules may be used. The first quickly acquires the analog signal at the point of interest and the second acquires and holds the output from the first device. The second S/H device takes longer to acquire the voltage presented by the first device, but since a larger capacitor is used, its droop rate will be much lower. For further details, the reader is referred to reference 2.

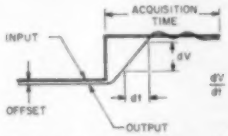

Fig. 4. Representation of the acquisition time, offset, and slew rate. (Courtesy of Analog Devices, Inc.[3] All rights reserved.)

There are a number of commercially available sample-and-hold devices which eliminate the need for you to construct your own. The following modules are representative of those available:

Analog Devices, Inc., Norwood, Massachusetts 02062—SHA-5, general purpose, $47; SHA-1A, general purpose, $150.

Burr-Brown, Tucson, Arizona 85734—SHC80KP, low cost, $34; SHM60, high speed, $104.

Datel, Inc., Canton, Massachusetts 02021—SHM-LM2,

Continued on page 77

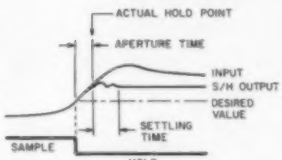

Fig. 5. Representation of the aperture time and the settling time. (Courtesy of Analog Devices, Inc.[3] All rights reserved.)

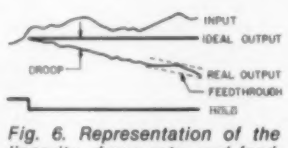

Fig. 6. Representation of the linearity, droop rate, and feedthrough. (Courtesy of Analog Devices, Inc.[3] All rights reserved.)

NEW FROM *DSI!*

50 Hz — 500 MHz 8 DIGITS
1 Meg INPUT — 1 Hz RESOLUTION — 1 PPM TCXO

- AC—DC Operation
- BNC Inputs 1 Meg Direct 50 Ohms Prescaled
- 8 Large .4" LED Readouts
- Auto Decimal Point & Zero Blanking
- 1 Year Limited Warranty Parts & Labor
- 100% Factory Assembled in U.S.A.

$149.95

MODEL 500 HH
50 Hz — 500 MHz
Without Battery Capability

SAVE $5.00
With Battery Capability
MODEL 500 HH . . $169.95
MODEL 100 HH . . $119.95

MODEL 100 HH
50 Hz — 100 MHz
$99.95
Without Battery Capability

The 100 HH and 500 HH hand held frequency counters represent a significant new advancement, utilizing the latest LSI design . . . and because it's a DSI innovation, you know it obsoletes any competitive makes, both in price and performance. No longer do you have to sacrifice accuracy, ultra small readouts and poor resolution to get a calculator size instrument. Both the 100 HH and 500 HH have eight .4 inch LED digits — 1 Hz resolution — direct in only 1 sec. or 10 Hz in .1 sec. — 1 PPM TCXO time base. These counters are perfect for all applications be it mobile, hilltop, marine or bench work. CALL TODAY TOLL FREE: (800—854-2049) Cal. Res. CALL (800—542-6253) TO ORDER OR RECEIVE MORE INFORMATION ON DSI'S FULL PRODUCT LINE OF FREQUENCY COUNTERS RANGING FROM 10 Hz TO 1.3 GHz.

FREQUENCY COUNTER CONSUMER DATA COMPARISON CHART

MANUFACTURER	MODEL	SUG'STD. LIST PRICE	FREQUENCY RANGE	TYPE OF TIME BASE	ACCURACY OVER TEMPERATURE		SENSITIVITY			DIGITS		PRE-SCALE INPUT RESOLUTION	
					17° - 40°C	0° - 40°C	100 Hz - 25 MHz	20 MHz - 250 MHz	250 MHz - 450 MHz	No.	SIZE IN INCHES	.1 SEC	1 SEC
DSI INSTRUMENTS	100 HH	$ 99.95	50Hz-100MHz	TCXO	1 PPM	2 PPM	25 MV	NA	NA	8	.4	100 Hz	10 Hz
DSI INSTRUMENTS	500 HH	$149.95	50Hz-550MHz	TCXO	1 PPM	2 PPM	25 MV	20 MV	30 MV	8	.4	100 Hz	10 Hz
CSC‡	MAX-550	$149.95	1kHz-550MHz	Non-Compensated	3 PPM @ 25°C	8 PPM	500 MV*	250 MV	250 MV	6	.1	NA	1 kHz
OPTOELECTRONICS	OPT-7000	$139.95	10Hz-600MHz	TCXO	1.8 PPM	3.2 PPM	NS	NS	NS	7	.4	1 kHz	100 Hz

* 1 KHz - 50 MHz ‡ Continental Specialties Corp.

The specifications and prices included in the above chart are as published in manufacturer's literature and advertisements appearing in early 1979. DSI INSTRUMENTS only assumes responsibility for their own specifications.

100 HH . . . $ 99.95 W/Battery Pack . . . $119.95
500 HH . . . $149.95 W/Battery Pack . . . $169.95

Prices and/or specifications subject to change without notice or obligation.

These prices include factory installed rechargeable NiCad battery packs.

DSI INSTRUMENTS, INC.
7924 Ronson Road, Dept. G
San Diego, California 92111

T-500 Ant. . . . . $ 7.95
AC-9 Battery Eliminator . . . . . $ 7.95

TERMS: MC - VISA - AE - Check - M.O. - COD in U.S. Funds. Please add 10% to a maximum of $10.00 for shipping, handling and insurance. Orders outside of USA & Canada, please add $20.00 addition to cover air shipment. California residents add 6% Sales Tax.

New Products

KANTRONICS' AMATEUR UPGRADE™

Kantronics' "Amateur Upgrade" is an educational board game that familiarizes players with FCC rules governing amateur radio and elementary radio concepts. The game comes complete with playing surface, playing pieces (coil, grommet, etc.), a die, a deck of exam cards, and corresponding answer sheets.

"Amateur Upgrade" is packaged in a colorful light blue box; it measures 1.5" high by 8.25" wide by 15.5" long. Game pieces and exam cards fit in a pocket adjacent to the support tray. The game surface is 15.4 inches square and is printed in five colors corresponding to beginner, Novice, General, Advanced, and Extra class.

Players roll the die to determine the number of spaces to move. Some spaces players land on have a consequence, such as "taught a Novice class—move again," or "exceeded 1000 Watts—answer question; if wrong, go to start," or "illegal third party traffic—lose one turn."

When a player lands on an exam space, he must take an exam card from the card pile corresponding to the license level he is trying to upgrade to. After three cards have been collected by one player, he must "take the exam." All three questions must be answered correctly to pass the exam. Answers can be checked against the answer sheets. If the exam is passed, the player moves up (upgrades) to the adjacent exam space on the next license level. If the exam is failed, the player remains on the same level and must collect another three exam cards.

The first person to progress through all levels to obtain the Extra-class license wins!

Novice, General, Advanced, and Extra-class questions are included. For a less advanced game, the Novice cards can be used exclusively for all license levels.

Kantronics, Inc., 1202 E. 23rd St., Lawrence KS 66044; phone (913)-842-7745. Reader Service number K13.

NEW COMMUNICATIONS RECEIVER FROM NATIONAL RADIO

National Radio now offers the latest version of its Model HRO-600 high precision/performance solid-state general-coverage communications receiver, conceived for applications requiring wide frequency coverage, high stability, sensitivity, and selectivity. The frequency stability of this professional receiver, over the temperature range of 0° to 50° C., will drift less than one part in one million, and, under normal operating conditions, it can be expected to drift less than one part in one hundred million. The receiver's fine-tune mode, using the Model 602 plug-in module, permits tuning to a fraction of 1 Hz without any loss of stability.

The HRO-600 was originally designed and built to the exacting requirements of the International Maritime Standards. With its versatile plug-in modules and accessories, the Model HRO-600 becomes a custom receiver designed to meet users' specific needs at the lowest cost. The manufacturer states, "The HRO-600 is unmatched in performance and versatility in its price range."

The receiver's excellent rf selectivity from 16 kHz to 30 MHz is achieved by a built-in tunable preselector. Depending upon the plug-in module selected, the receiver will operate at any frequency between 10 kHz and 30 MHz in any of the following reception modes: AM, CW, SSB, FSK, and FAX.

The basic applications of the HRO-600 include: commercial communication, ship-to-ship, ship-to-shore, ground-to-air, frequency/time measuring, process control, laboratory instrumentation, military, paramilitary, international monitoring, limnology, etc.

The HRO-600 meets applicable military standards as to shock and vibration, has an operating temperature range from 20° to +55° C., measures 5¼" high x 17" wide x 15½" deep, and is provisioned for self-supporting rack mounting. The approximate weight is 40 lbs., available from stock, FOB factory.

For additional information, write or call Robert Reeves, Sales Manager, *National Radio Company, Inc., 89 Washington St., Melrose MA 02176; phone (617)-662-7700.* Reader Service number N23.

The Astro 150 from Swan.

SWAN'S ASTRO 150 TRANSCEIVER

Swan Electronics Corporation has announced its newest entry into the amateur radio market with the introduction of the Astro 150 transceiver, featuring microprocessor control and memory.

The new solid-sate transceiver, with its microprocessor control, provides more than 100,000 digital-controlled frequencies and variable rate scanning (VRS). VRS is a dramatic new method of tuning which provides ease and accuracy and works in conjunction with hand-held microphone scanning. With microphone "up" and "down" pushbuttons, the Astro 150 can be tuned in accurate 100-Hz steps or at a fixed rate scan. VRS is a supplement to the Astro 150's conventional tuning knobs.

The compact new radio also has additional features which include 235 Watts input power, full and semi break-in CW, narrowband CW filter, expanded frequency coverage, and microprocessor-controlled frequency memory.

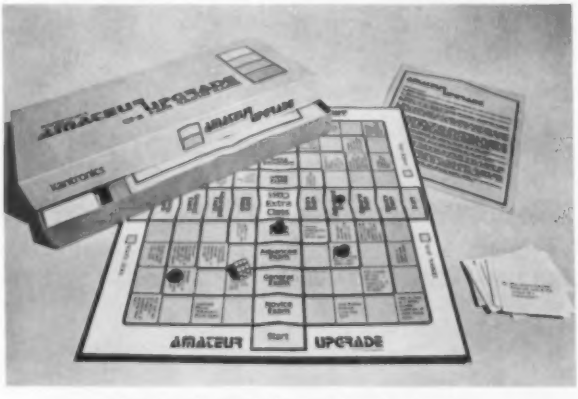

"Amateur Upgrade" game from Kantronics.

National Radio's latest version of the HRO-600.

The Astro 150 will be sold through Swan's worldwide network of dealers. For further information, contact Gary Pierce at *Swan Electronics Corporation, 305 Airport Road, Oceanside CA 92054; phone (714)-757-7525.* Reader Service number S44.

METZ COMMUNICATION'S AMATEUR ANTENNAS

Metz Communication Corporation has broad experience in producing mobile-type antennas. However, until recently, the company has concentrated its sales efforts in the commercial land mobile and marine radio markets. Now Metz has entered the amateur marketplace with mobile antennas for the 10-meter, 2-meter, and 70-cm bands. I installed and operated the 2-meter version, the Mobile 2, in preparation for this review.

The commercial heritage of the Metz amateur antennas is readily apparent. Instead of the usual plastic tube to protect the base loading coil from the weather, the Metz coil is housed inside a machined stainless steel cylinder. This cylinder, in turn, is filled with epoxy to completely encapsulate the coil . . . no more worries about a leaky base coil.

The tapered stainless steel whip is held in place by a metal ferrule that is (would you believe?) gold-plated to prevent corrosion. Overall, the construction of the Metz Mobile 2 is so rugged that it will probably still be going strong when you and I are long gone.

The Mobile 2 is designed to operate as a half-wavelength antenna on the 2-meter band. This design makes the antenna a bit shorter than the more familiar 5/8-wavelength 2-meter antennas. I consider the reduced length a plus; in my case, it made the difference between being able to mount the antenna on the car roof (the best location) and being relegated to the trunk lip (for fear of bashing the whip against the garage door).

In operation, the Mobile 2 is a breeze. When cut for lowest swr in the center of the 2-meter band, it's possible to operate from 144-148 MHz with an swr of 2.5:1 or better. Of course, if you work primarily in one end of the band or another, you can optimize the performance for that portion of the spectrum.

I found the Metz to be equal to or better than my 5/8-wave antenna in every respect. Additionally, the completely weatherproof design of the Mobile 2 means that leaking and condensation around the coil are never going to be a problem; you get full performance even in the worst weather. The Mobile 2 is rated at 200 Watts for those who need the extra punch of a linear amplifier. Several mounting styles are available in addition to the excellent magnetic mount I used.

For those who demand quality construction in everything they own, the Metz antennas are going to be tough to beat. *Metz Communication Corporation, Corner Routes 11 and 11C, Laconia NH 03246.* Reader Service number M100.

Jeff DeTray WB8BTH/1
Assistant Publisher

A NEW CONSUMMATE DIGITAL VOLKSMETER

Non-Linear Systems' new Model LM-353 3½-digit digital Volksmeter was designed to include numerous advanced state-of-the-art features. The LM-353 is packaged in a small 1.9-inch-high by 2.7-inch-wide by 4-inch-deep attractive plastic case. It weighs only 9.2 ounces.

Basic functions include ac and dc volts, Ohms, and ac and dc milliamperes. Full-scale ranges are 1, 10, 100, and 1000 volts, 1, 10, 100, 1000, and 10,000 kilohms, and 1, 10, 100, and 1000 milliamperes.

In addition, a low-Ohms capability is present which provides for in-circuit test of resistive components. It is particularly useful for in-circuit test of resistors shunted by semiconductor devices because the low compliance voltage provided does not turn on the semiconductor.

The low-Ohms function adds other capabilities to the meter. It can be used to increase the sensitivity of the voltage ranges by a factor of 10. It provides a 0.1-kilohm resistance range having 100 milliohm resolution. In addition, the milliamperes function is enhanced in two ways. First, a .1-milliampere range is available. Second, the voltage drop across the internal current shunt is reduced by a factor of 10. Measurements from 100 nanoamperes to 100 milliamperes can be made in this mode.

The LM-353 utilizes an LCD display. Replaceable AAA-size batteries allow up to 100 hours of operation. Standard features include auto polarity, decimal location, input overload protection, and automatic zeroing.

Options include a tilt-stand case for bench use and a panel-mount flange case for installation into equipment. A 45-kV high-voltage probe and leather carrying case are also available.

The complete NLS digital Volksmeter line is sold through a worldwide network of leading electronic distributors. The Model LM-353 will be available from distributors in July. *Non-Linear Systems, Inc., PO Box N, Del Mar CA 92014; phone (714)-755-1134.* Reader Service number N22.

Model LM-353 digital Volksmeter from Non-Linear Systems.

NEW 300-WATT DRY RF LOAD RESISTOR

The new Bird model 8173 TERMALINE® dry high-power coaxial load is designed for 50-Ohm rf-line and system termination during design, test, and alignment. At 300 Watts continuous duty, it complements the present Bird Dry Loads group ranging from 2 Watts through 600 Watts. The group, with its rugged construction and air dielectric (no liquid coolants), now includes 2-, 5-, and 10-Watt loads with fixed input connectors, and 25-, 50-, 100-, 150-, 300-, and 500/600-Watt loads with Quick-Change connectors.

The use of Bird QC Quick-Change connectors offers unsurpassed flexibility; a choice of any common rf connector either at the time of order or in the field eliminates adapters and degradation of performance.

Available from *Bird Electronic Corporation, 30303 Au-*

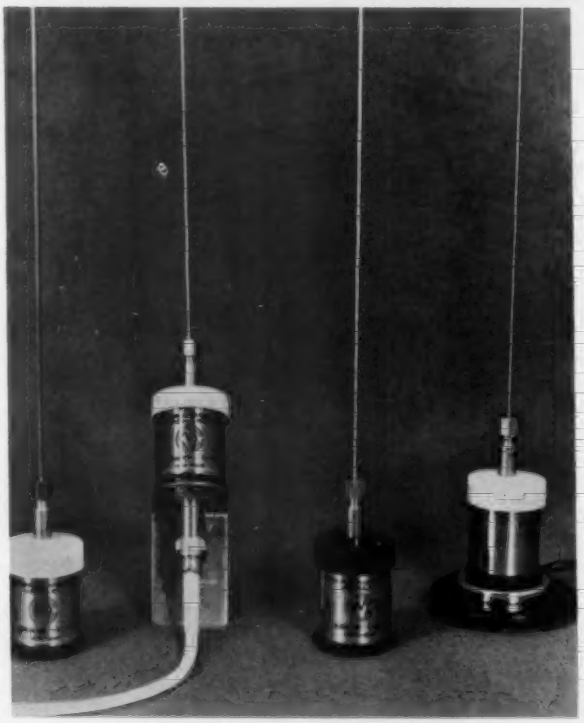

Amateur mobile antennas from Metz.

Model 8173 Termaline from Bird.

rora Road, Cleveland (Solon) OH 44139. Reader Service number B10.

CDE INTRODUCES TWO NEW ANTENNA ROTOR SYTEMS

Two new models of high-performance antenna rotor systems, the Ham IV™ and the CD-45, have been introduced by Cornell-Dubilier Electric Corporation, Newark NJ.

The new Ham IV is designed for large communication antenna arrays up to 15.0 sq. ft. wind load area when tower-mounted. Highlights of the Ham IV include power braking, machined steel drive gears, dual transformer circuitry, and other design features that make it "the engineered choice" for serious communicators.

The new CD-45 accommodates antenna arrays up to 8.5 sq. ft. wind load area when mounted in a tower and features a professionally-styled control unit, illuminated metered readout, all-steel drive components, automatic disk braking, and more.

Both the Ham IV and the CD-45 operate at safe low-voltage control levels with reliable snap-action rotational controls for accurate, trouble-free operation.

For more information, write Leonard Sabal, *Cornell-Dubilier Electric Corporation, subsidiary of Federal Pacific Electric Corporation, 150 Avenue L, Newark NJ 07101; phone (201)-589-7500.* Reader Service number C143.

New antenna rotor systems from CDE.

ANTECK MT-1 MOBILE ANTENNA

Improved conditions on the HF DX bands has stirred increased interest in mobile operation on those frequencies by many amateurs. In mobile operation, the antenna is even more important than it is in fixed installations. For one thing, if you've got an inefficient antenna at home, you can always help to make up for its shortcomings by running more power. However, while there are a handful of mobile kilowatts around, most amateurs have to be satisfied with the output from their transceiver, usually in the 100-Watt range.

So, for effective mobile operation, an efficient antenna is of prime importance. It should also be easy to install and tune, weatherproof, and allow band changes without having to change coils. The new Anteck MT-1 certainly meets those requirements and, when properly installed and tuned, should provide a high degree of performance on the HF bands.

The frequency coverage of the MT-1 is 3.5 to 30 MHz, making it perfect for use on MARS and other non-amateur frequencies (in addition to the 10 through 80 meter amateur bands). Its power handling capability is 750 Watts PEP. The MT-1 consists of three main assemblies: mast or base section, loading coil, and whip. The overall length of the mast section and loading coil is 60 inches and the diameter is approximately 1 inch. The total antenna length is 116 inches at 3.5 MHz and 92½ inches at 30 MHz. The antenna is center-loaded on all frequencies except 29 to 30 MHz, where it works as a quarter-wave vertical.

Properly mounted and tuned, the MT-1 will display the vswr/bandwidth shown in Table 1.

The loading coil is tuned from the base of the antenna, using a non-inductive plastic rod which is attached to the base of the whip assembly and extends down into the bottom mast section. The antenna comes with a handy chart that correlates the numbers on the antenna's tuning scale to frequency. To set the antenna for a particular frequency, loosen the knurled nut in the slot in the base section four turns and push the tuning rod to the middle of the base tube so that the tuning rod will move freely without binding. Then set the top of the nylon collar to the position called for on the tuning chart for the frequency in use and retighten the knurled nut. That's all there is to tuning the Anteck MT-1.

The MT-1 mobile antenna is manufactured entirely in the United States using only the best-quality military-standard materials and components. Its three-piece modular construction (base section, loading coil, whip assembly) makes for ease of repair or replacement if damaged. There is a 90-day warranty. Factory service is available.

The net price for the MT-1 mobile antenna is $119.95. *Anteck, Inc., 239 Cedar Street, Box 543, Jerome ID 83338; (208)-324-3400.* Reader Service number A80.

Morgan W. Godwin W4WFL
Brattleboro VT

Band	*Vswr*	*Bandwidth*
80 meters	*Less than 1.2 to 1*	*25 kHz**
40 meters	*Less than 1.2 to 1*	*50 kHz**
20 meters	*Less than 1.2 to 1*	*300 kHz**
15 meters	*Less than 1.5 to 1*	*150 kHz**
10 meters	*Less than 1.2 to 1*	*500 kHz**

*Table 1. *From resonant frequency.*

MICRONTA 12-VDC 8-AMP POWER SUPPLY

Now available from Radio Shack is a new power supply that converts standard 120 V ac house current to 12 V dc at up to 8 Amps output for powering high-power auto sound equipment, mobile CB transceivers, and amateur radio equipment at home.

The Micronta 12-volt 8-Amp power supply includes a heavy-duty transformer and 35-Amp bridge rectifier for handling high current demand devices. Filtered output reduces "hum," and ripple is less than 2 volts peak-to-peak with a full 8-Amp load, according to Radio Shack.

A built-in manually resettable circuit breaker protects the supply and your equipment from damage. An LED indicates power on.

Manufactured in Radio Shack's own USA factory, the power supply is housed in a metal cabinet with rubber feet. Size—3-3/4" x 8" x 5-5/8".

The Micronta 12-volt 8-Amp power supply is available exclusively from participating

Continued on page 174

IC-701, Your Synthesized Passport

Enter the exciting world of HF DX with ICOM's outstanding, fully synthesized **IC-701**. Globe-spanning QSO's are as easy as hook-up and tune-in. Complete installation requires only a good 50 Ohm antenna and an AC power plug-in. Your **IC-701** comes with everything else you need for beginning DX transmissions, including the matching **IC-701PS** external speaker and power supply, the fine **SM-2** base microphone, and even two built-in VFO's.

Turn on the power, and the world's at your single fingertip. The **IC-701** lets you scan all the Amateur HF bands from 160M to 10M (plus some MARS coverage above and below some of the Ham bands) with one finger. No more fooling around with two or more tuning knobs, and no complicated retuning when you QSY.

When talking on your **IC-701**, you get a 200 watt PEP input signal whose punch is significantly increased by the high quality built-in RF speech processor. This makes your 200 watts sound like so much more that we recommend you leave the speech processor on all the time.

For adding on frequency memory and remote frequency control, the **IC-701**'s synthesizer is completely compatable with ICOM's **RM2** remote computer controller: and with ICOM's optional **EX1** extention, you can operate with the **RM2** and a linear amplifier at the same time.

Nothing else matches the value and ease of the **IC-701**. Plunge into the excitement of HF DX now, and get the whole HF world with ICOM's **IC-701** LSI system.

IC-701: DXterity

HF/VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT

DISTRIBUTED BY:

ICOM

ICOM WEST, INC.
Suite 3
13256 Northrup Way
Bellevue, Wash. 98005
(206) 747-9020

ICOM EAST, INC.
Suite 307
3331 Towerwood Drive
Dallas, Texas 75234
(214) 620-2780

ICOM CANADA
7087 Victoria Drive
Vancouver B.C. V5P 3Y9
Canada
(604) 321-1833

All ICOM radios significantly exceed FCC regulations limiting spurious emissions.

DX

Chuck Stuart N5KC
5115 Menefee Drive
Dallas TX 75227

NOVICE CORNER

This month we want to pass along a little QSL advice that is aimed not only at the newcomer but to a lot of the old-timers as well.

If you work a station, such as a DXpedition, several times on different modes at different times, please do not place a card for each contact in an envelope addressed to the QSL manager and include only one SASE.

Because there are often several logbooks involved and several different people or groups handling the QSLing chores, you will stand a much better chance of getting a fast return if you include a separate SASE for each QSL card. If the extra expense is too much to bear, then you really don't need the extra cards.

While we are on QSLing, we will remind you again to always use GMT/UTC time on your card including the date, be sure that your call appears plainly on the report side of your QSL, and to always include a self-addressed, stamped envelope when sending a card to a QSL manager. When sending a card overseas, either direct or to a foreign QSL manager, include a self-addressed envelope along with a dollar bill, foreign mint stamps, or sufficient IRCs to prepay the return postage.

CARIBE DX ASSOCIATION'S PLANS

The Caribe DX Association's Alex Kasevich W1CDC is presently in the process of engineering a large DXpedition to some rare place on the globe. All interested persons who feel they meet the requirements listed should apply for an interview. The time window for this adventure is August, 1980; exact dates will be made available when government legalities and logistics permit.

They have a large seaplane with a pilot and a co-pilot at their disposal. A large manufacturer of amateur equipment has endorsed their intentions by the loan of some top-of-the-line ham gear.

All persons who apply must hold a current amateur radio license, General class or higher; they must also have a doctor's endorsement indicating that they have no physical restrictions that could be affected by extreme heat, sun, humidity, sea/air sickness, possible physical exhaustion, and insect bites. All members shall be proficient CW/SSB contest-style operators and must have a secondary ability to contribute to the expedition in the following categories: 2 persons with some paramedic training; 1 doctor; 2 cooks; 1 navigator; 1 antenna specialist; 1 electronics (solid-state) technician; 1 mechanic, gasoline generator maintenance.

All members of the expedition must be able to swim and have some climbing ability.

These requirements have been made not to discourage anyone from taking part, but to ensure the safety of all members and make the DXpedition a success. It must also be clearly understood with all members that there is always the possibility of hidden dangers in pulling off a trip of this magnitude. I'm sure all of you will have various questions about this subject, and they will be answered in the best interest of all parties concerned.

Please send your reply with your remarks, phone number, and best time to contact you to: The Caribe DX Association, c/o Alex M. Kasevich W1CDC, PO Box 93, East Glastonbury CT 06025.

HEARD ON THE BAND

That 4W2AA being heard from time to time appears to be I2YO who travels to Yemen on a regular although infrequent basis. QSL to I2MVS.

GJ2LU is the official QSL manager for any Isle of Jersey stations.

PY1RO is the first DX station ever to make WAS on 160 meters.

A recent article in the Russian *Radio* magazine notes a decision by the USSR State Commission on Radio Frequencies to allow amateur activity between 1850 kHz and 1950 kHz. Although no date was given, it seems definite that you should be hearing the Russians on 160 meters any day.

Anyone wanting to learn more about the action on 160 meters should drop a note to W1BB along with an SASE and request a copy of Stu's very informative bulletin.

The African swing by N6VR and WA6VNR netted some 3000 contacts from C5ABX/C5ABZ and 2200 from /6W8. They had a 5T5 permit, but time and funds ran out before they got to Mauritania. QSL to 48 South Chestnut Street, Ventura CA 93001.

Slim has been pulling overtime lately what with the good band conditions and cheap airline rates. If you worked any of the following, then know that you have met Slim himself: 6B1B, J1A, 7O1AA, 9N1AB, BY1USA, CR9CB, XZ2BC, KL8AA, and, of course, VR0M from Malden Island. Being the bashful sort, Slim generally prefers CW, but on occasion he can be found on the phone bands. If you hear the generator whine, you know it's Slim.

SV9JI on Crete has a weekly schedule with W2TDQ on Tuesdays at 2100Z on 14288 kHz.

Lloyd and Iris Colvin, of YASME DX fame, report that with the end of their recent West Indies swing, they have held 104 different callsigns, visited 135 countries, and have made over 500,000 QSOs. They have a QSL file of over 250,000 alphabetized cards, probably the largest collection in the world. *Guinness Book of World Records* is missing out.

A station has been worked on fifteen signing HV2VO and giving his name as Brother Edmund. Said to QSL via I0GPY. This could be the Vatican Observatory station we mentioned a few months back.

Those EJ prefixes heard over the May 18/20 weekend were special calls issued for operation by several GI stations from Inishmurray Island. QSL to GI4FUM.

VR6HI was number 100 on 160 meters for PY1RO.

VP8SU from South Georgia can usually be found with WA2JUQ in a list-type operation every Tuesday/Wednesday/Friday on 14240 kHz around 0100Z. QSL to G3RCA.

After much waiting, the necessary documentation was forwarded to ARRL Headquarters and they are now accepting HZ1BS/8Z4 cards for DXCC credit.

For some time now, rumors have been thick concerning an upcoming Franz Joseph Land effort by some of the UA/UK types. Along this line, UA1OE advised W4ORT that there would be something coming this July. UK1ZAA advised KH6GI that UK1PAA was the only station on FJL and it was crystal controlled on 14030 kHz. Listen for Franz Joseph Land to be activated . . . someday . . . maybe.

9N1BMK was true blue. QSL to his home call JA8BMK.

YU2DX returned home from the Sudan where he was doing some educational work in the electronic field. A radio club has been organized in Khartoum and the club call is 6T1YP. Both 6T1YP and 6U1DX can be QSLed to YU2DX. Other new calls being heard out of the Sudan lately are ST2FF and ST2MM.

U0CR was Leo UA3CR, part of a seven-man skiing team headed for the North Pole. U0CR counts for the RAEM award.

That linear shipped to Father Dave CE0AE should be in use now and the signal should be much improved. CE0AE can often be found on the various DX nets such as the Family Hour on 14225 kHz at 1500Z or the Afrikaner Net, 21358 kHz from 1830Z. Overseas commercial interference has forced the Afrikaner Net to move up from its normal 21355-kHz spot.

4U1UN has moved its location to the 48th floor of the Secretariat at UN Headquarters in NYC. They still have only dipoles and a vertical, but they are working on permission to install a beam.

3B8DA has been inactive most of this year trying to clean up the backlog of some 20,000 cards received as the result of some of his recent operations.

The VR6HI operation from Pitcairn Island by ZL1AMO and ZL1ADI produced an almost unbelievable QSO total of better than 33,000 contacts spread out over six bands. The fewest contacts came on 160 meters with 170, and the most, 10,885, were made on 10 meters. During this same period, VR6BJ and VR6DX from the *Yankee Trader* made 753 and 1100 QSOs respectively. 193 of VR6BJ's contacts were on RTTY. These three operations should have dropped VR6 well down on the needed list.

New officers for the Mile-Hi DX Club are Roger Preece WB0RTZ—President, Bob Pierce WB0OGJ—VP, and Joe Hart WB0HAD—Secretary/Treasurer.

SV1JG expects to be on Rhodes in the Dodecanese group this summer signing SV1JG/SV5. Under the new call allocation scheme there in Greece, SV5 is Dodencanese and SV9 is Crete. This was done no doubt to aid the deserving DXer in his never-ending search for a new one.

Several VE types are working on the necessary permission to activate Sable Island during July or August. They have authorization from the DOC but were awaiting other required documents before firming up the details.

As this column is being written, the YV0AA DXpedition is going hot and heavy giving out a new one to deserving DXers all over the world. While we realize the DX bands are crowded these days, it seems a little ridiculous to spread the calling stations out over a forty kHz section of the band. Listening from 14200 kHz to 14240 kHz makes that section of the band useless for any normal DX activity and certainly does little to

enhance our image among the sizable segment of our fellow amateurs who somehow fail to see the need to bring the normal day-to-day activities of amateur radio such as skeds, ents, SSTV, etc., to a screeching halt while we deserving ones strive to exchange signal reports with a temporary station located on an uninhabited island covered solid with birds and their natural residue. How anyone could fail to understand this and start complaining about *those DXers* is certainly beyond us. Transmitting below the American phone band and listening up is the only way for many DX stations to be able to make any contacts with USA stations, but it seems that listening over, at most, a fifteen or twenty kHz portion of the band should be sufficient. How do you feel about this practice?

Still nothing heard from China but a few phonies. A usually reliable source from Europe reports that one of the eastern Eurpean countries will be sending a team of radio technicians to help the Chinese develop knowledge in that area. Some among this team will be amateurs ready to demonstrate the finer points of amateur radio should the opportunity arise. The source seems rather definite that something will be heard this fall.

There are serious discussions going on between some of the biggest of the big-gun-type DXers concerning a concentrated effort this summer to wipe Mt. Athos (SY) from the face of the most needed lists. More information will come as plans gel.

If you think some exciting times can't be experienced in amateur radio, then you obviously were not in on the recent 1S1DX operation from Spratly. The initial landing was planned for Amboyna Cay. When the Spratly crew got close, they could see that there were people on the island and they cautiously came inside the reef to a point some 300 yards offshore. Through binoculars it was easy to detect military personnel in black uniforms grouped around what appeared to be weapons. One of the military types began signaling with semaphore signals, but unfortunately no one in the crew understood the signals. As the crew moved in closer, the message became somewhat clearer as four warning shots were fired across their bow. Feeling at this point they were not wanted and seeing that they could easily be blown out of the water with little effort, the little group again headed out to sea.

After this initial problem, the group returned to Brunei, regrouped, and decided to make another run, but this time to Pearson Reef, located some eighty miles northeast of Amboyna Cay and hopefully less inhabited since it had an elevation of only three feet above high tide. The approach to Pearson Reef showed how when it rains, it pours. Not only was the small reef occupied, but there were buildings and small craft around. Fortunately, the group had selected a third alternate, which they now headed for. It was from this spot, Barque Canada Reef, a sand bar some 150 feet in length, that the much-delayed, constantly-in-danger 1S1DX operation finally took place.

Most of the sixty hours stay on Barque Canada Reef was spent operating, often with more than one station on the air. Ten, fifteen, and twenty netted some 13,300 contacts with about half coming on fifteen. Phone seemed to result in a higher QSO/hour rate, so the concentration on this mode resulted in a 77%/23% phone/CW spilt. Forty percent of the contacts were with Japan, thirty-five percent were with stateside, fifteen percent were with Europe, and the remainder were scattered around the world.

QSL to Harry Mead, Box 85, Round Corners, 2158 Australia. Expenses were excessive due to the problems and any financial aid can go to K2TJ or via the Northern California DX Foundation.

The recent volcanic activity on St. Vincent Island in the West Indies found VP2SQ providing emergency communications for the local authorities. He is reported as having phone-patched Prime Minister Cato to other islands when there was a need for quick communications. It is this type use of amateur radio that we have been trying to demonstrate to the Third-World nations preceding WARC 79.

Rubin WA6AHF and his XYL Ferne have had to curtail their YASME QSLing efforts on the recommendation of their doctor. Although giving up the YASME effort, they will continue to handle cards for those stations they are QSL managers for.

Some EP stations are again being heard on a sometime basis, although the situation is far from being settled in Iran.

That 9N1YU being worked a few months back is reported by HS1ABD to be a true-blue type used by a Yugoslav mountaineering group in the Mt. Everest area.

S2BTF continues to show from Bangladesh on the weekends working a list-type operation. Look for him on 14226 kHz Saturdays from 1300Z and Sundays from 1200Z. QSL Peter via Box 108 in Dacca.

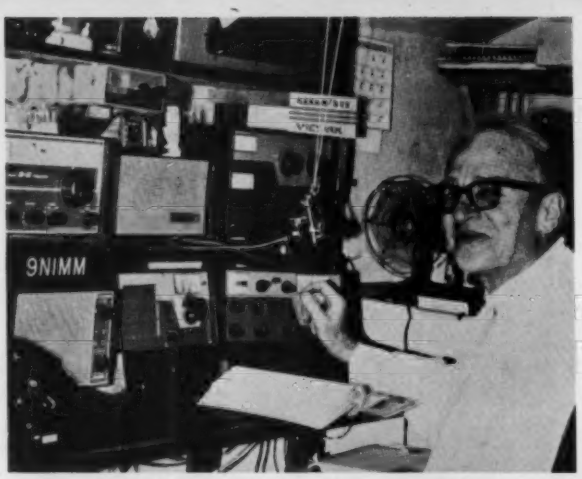

Father Marshall D. Moran, S.J., Kathmandu, Nepal, better known around the world as 9N1MM. Father Moran has been a regular fixture on the DX bands since 1961.

9N1MM has been keeping a fairly regular schedule around 14243 kHz after 0100Z. QSL to Ed Blaszczyk N7EB, 12802 Sun Valley Drive, Sun City AZ 85351. Ed has been handling Father Moran's QSL duties since 9N1MM first came on the air in 1961. Ed, who has also held the calls W3KVQ, W2KV, and KX6EB, asks that we remind those needing a 9N1MM QSL to please enclose an SASE. It makes the job much easier.

As we have often mentioned, it's usually easier and cheaper to just enclose a dollar bill (green stamp) with your QSL when a direct airmail reply is required than to go through the hassle of buying IRCs or foreign mint stamps. We also mentioned that there were situations when it was best not to enclose money with a QSL going overseas. A letter from Mansur AP2MQ brings up a case in point. Incoming mail is often checked by the Pakistani postal authorities, and since the importation of foreign currency is illegal in Pakistan, this often leads to embarrassing circumstances for the amateur to whom such mail is addressed. It is always best to follow the QSL instructions given by the DX station. In the future, do not send green stamps to Pakistan.

There is a report that the number of complaints to the FCC concerning the Russian "woodpecker" have risen sharply. It is sometimes a bit frustrating to report such interference and realize that the person on the other end has never heard of the "woodpecker." Check last month's column for the telephone number of your closest FCC monitoring station. Keep them advised of the "woodpecker's" activity and someday the "woodpecker" will vanish. Some claim that if we had reacted immediately two years ago, he would now be only a bad memory.

A couple of months back we mentioned the possibility of a Swedish group operating from Albania. The expected callsign was mentioned as being ZA5T. Late word on this operation has been zilch, but if anything new develops, we will certainly pass it along.

Those new Pacific area prefixes still seem to be causing trouble. It was sure easier to remember when KM6 was Midway, KW6 was Wake, etc. To help you learn the new designations, we will list them again:

KH1	Baker, Canton, and Howland
KH2	Guam
KH3	Johnston
KH4	Midway
KH5	Kingman if K suffix, Palmyra if not
KH6	Hawaii
KH7	Kure
KH8	American Samoa
KH9	Wake
KH0	Northern Marianas

UK0YAH is being worked around 14050 kHz after 1800Z. We mention this as a reminder that Soviet Siberian stations whose suffix begins with a Y are located in Tana Tuva in rare Zone 23.

The Brussels Millennium Award is available to anyone working ten of the OS prefixes on at least two bands. Send log data and three IRCs to Brussels Millennium Award, PB 1000, B-1040, Brussels, Belgium.

Continued on page 172

Introducing –
the new
SCR 4000
the Super Deluxe
450 MHz
FM Repeater!
FEATURES:
*30 Watts Output
2 Low Noise JFET Rcvr. RF Amp Stages w/6 Poles of front end filtering for excellent sensitivity & "out of band" rejection
*Double-Balanced Rcvr. Mixer for super dynamic range, (i.e., very low IMs, spurious responses, etc.)
*8 Pole 21.4 MHz IF Crystal Filter for excellent adjacent channel & image rejection
*Front Panel Receiver Discriminator & Deviation Meter functions!
*Built-in Ultra High Stability Transmitter Crystal Oscillator/Oven Unit—for the ultimate in frequency stability over wide temp. ranges.
*Plus—all of the many other well-known features found in the SCR1000 VHF Repeater
SPECTRUM COMMUNICATIONS
SCR 4000
UHF FM REPEATER
Shown in optional cabinet
180 Day Warranty!

180 Day Warranty!

Spec Comm is proud to announce the brand new SCR4000 UHF FM Repeater! There has been great customer demand for a repeater such as this for many months, and our engineers have put in hundreds of man-hours to develop a unit which incorporates all of the features requested by our customers over the last 2½ years.

The SCR4000 includes completely new transmitter and receiver boards, which were designed from the ground up specifically for this new repeater. The rest of the unit is basically the same as our tried and proven SCR1000 VHF Repeater *which has an excellent reputation for performance and reliability throughout the world!*

Of course, as with other Spec Comm products, only the latest state-of-the-art designs and the very finest quality components and workmanship are used throughout. Also, you'll be happy to hear one of the most amazing things about the SCR4000—*its price! About ½ that of repeaters sold by "the big two names" in 2 way radio . . .* And their older design units don't even offer many of the excellent convenient features which are *standard* on the SCR4000!

The SCR4000 is sold factory direct only, or through authorized Foreign Sales Reps. Since there has been a tremendous demand for the SCR4000, *we suggest that you get your order in as soon as possible!*

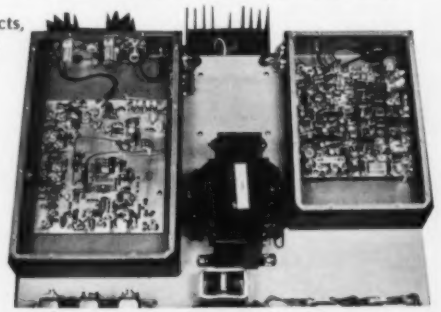

Transmitter **SCR 4000** Receiver

SCR 4000 Specifications

RF Output: 30 Watts typ. Infinite VSWR proof
Sensitivity: 0.35 uV/12 dB SINAD typ.
Selectivity: −6dB @ ±6.5 kHz; −100 dB @ ±30 kHz.

FEATURES

- **Full Metering** of critical levels. (Voltages, currents, Rel. RF out, RX Sig. strength, etc.)
- **Front Panel** Controls for timers & AF levels.
- **Lighted push-buttons** for control/tet functions & status indicators.
- **State-of-the-Art CMOS**—control logic & timers—No Relay problems!
- **Built-in AC Supply** w/instant btry. switchover for emergency pwr. (+ Trickle Chgr.)
- **Supplied with ± .0005% International Precision Xtals & local mic.**
- **Built-in CW IDer**—Low current draw, 250 bit PROM Memory! Adjustable speed, pitch, time, etc.
- **Jacks Provided** for Remote Control, Auto-Patch, DC out, AF in/out, COR Switch, etc.
- **True FM**—for Rpt. Audio so good, "It sounds like direct!"!

OPTIONS

- **Full Autopatch**, with or without reverse patch, and **"Landline"** or **Radio Remote Control of the Repeater.** (0/1 Inhibit Available).
- **Radio and/or Landline TouchTone Remote Control** of such repeater functions as Patch Inhibit/Reset; Switch ID Tracks; Repeater ON/OFF; PL ON/OFF.
- **"PL"-CTCSS**
- Up to **4 different IDs;** Automatic switching to **"Emergency Power ID"** when on battery pwr.
- **"Kerchunker Killer"**—5 sec. Rptr. Xmtr. turn on timer.
- **Timeout—Timer Reset Tone Annunciator**

Along with a complete line of Repeater System Accessories . . . such as: The Finest Duplexers, Cavities, Cabinets from 7" to 7', Antennas, "Hardline," Cables, etc.

new ID1000 Automatic Base Station CW Identifier

For Commercial & Amateur Applications

- **Automatically IDs your Station** (Base or Repeater) per FCC requirements every 5-30 min. (adjustable).
- **Meets all FCC requirements** for Parts 89, 91, 93, 95, 97 & other applications.
- **Convenient Front Panel Controls** for AC Power; Trigger Mode; (Automatic/COR, Continuous, or Disable); Manual ID; Local Monitor Spkr. Volume.
- **Front Panel Status Indicator Lights** for AC Power; ID in progress; DC Power operation.
- **Built-in AC Power Supply**
- **12VDC Battery Input** w/auto-switchover to "Emergency Power."
- Optional **"Emergency Power ID."**
- **Adjustable CW Tone Pitch, Speed & Level.**
- Provision for up to **4 different ID channels!**
- **Plug-in IC Memory Chip!**
- **Two Inhibit Inputs.**
- **Std. 19" Rack Mount.**

new COMMERCIAL MOBILE & BASE TRANSCEIVERS

Spec Comm "Professional Communications" line

- 136-174 MHz & 220-240 MHz (450 soon)
- 6 channels
- 0.35 uV Rcvr.
- 6 or 8 Pole Crystal Fltr.
- Beautiful Audio—RX & TX
- Very Reasonable Price!

- *Very attractive woodgrain housing*

SC 250 25 wt. Mobile unit

- *"Super Rugged" Housing*

SC 300 25-30 wt. Base station

SPECTRUM COMMUNICATIONS

S8

Write or call for Data Sheets, prices, etc. • Export orders—Contact our International Dept.

1055 W. Germantown Pk., Dept. S7 • Norristown PA 19104 • (215) 631-1710

A Visit to Antenna Specialists

—Wayne tours the test range

Wayne Green W2NSD/1
Editor/Publisher

The science of measuring antenna performance as part of the design process has come a long way in the last twenty years. A recent visit to the Antenna Specialists test site in northeastern Ohio brought back memories of my past visits to other such sites . . . and the enormous changes in test equipment and procedures which have come about.

Let me tell you about my visit to Antenna Specialists' test site.

Sherry and I were met at the Cleveland airport by Al Dolgosh K8EUR, who led us out to the test site, over an hour's drive away. There we met Dick Leach WA3HSE/WB8ZAA, Tom Baker K8MMM, and Rick Davis K8DOC, the test site team. The lab was set up in a trailer with a reference dipole nearby. The test antennas were set up on a platform a couple hundred feet away.

This is the trailer with the laboratory equipment for running the antenna field strength tests. The tower to the left is for a ham station in the house to the rear of the trailer. It's nice to have a ham living right there to watch out for the test lab equipment.

Was it only a little over twenty years ago that I visited a top manufacturer of ham antennas and watched them run tests on a long two-meter beam, measuring the signal strength every few degrees and writing down the figures? Today, this is all automatic. Today, they can run tests in a few minutes that used to take days, thus making it possible to design much more effective antennas. When you can make a small change in the antenna design and measure the results of that change quickly, it is relatively simple to explore many more variables for optimum performance.

With modern equipment at a test site, it is possible to measure the vertical and horizontal radiation characteristics of an antenna as well as the frequency response—all in a few minutes.

This is a small tower right beside the mobile lab. It is designed for mounting the transmitting antenna for the tests. Notice that this antenna can be raised and lowered to get the optimum vertical pattern of radiation.

You're looking at an enormous investment in test equipment. This gear is made just for labs of this nature and allows the automatic testing of the antennas, complete with the graphing system on the right.

Here Tom is showing the reference antenna which he set up by the receiving platform. This is a simple reference dipole.

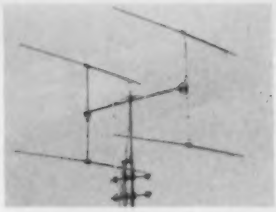

The tests this day were going to be run on the Antenna Specialists 44-element beam.

This is the mechanism which is used to hold up the antenna to be tested and to turn it in time with the graph in the lab. The tilting gears allow the antenna to be brought down for mounting or changes. The whole mechanism is on the track and can be moved toward or away from the lab.

That's Tom on the left in back, Al on the right in back, Rick on the left in front, and Dick on the right in front.

The test platform is being rotated so that the other two 11-element yagi antennas can be mounted on the boom. The rotating is all done remotely from the trailer.

Al Dolgosh K8EUR, who organized everything for us.

Rick Davis K8DOC, who is lucky enough to live at this extremely low-noise test site, complete with his ham rig and a good beam.

Tom Baker K8MMM.

Dick, Al, and Tom get the beam onto the boom and tightened in place for the tests.

Here's the beam all set up and raring to go, about 300 feet from the source site.

Dick runs the antenna array through a complete rotation, watching the pen on the chart as it traces the pattern of the beam.

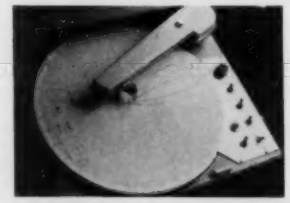

Here you see the finished pattern of the array. How about all that gain! And you surely can null out the interference with that incredible front-to-back ratio.

Over to the right of the test platform I found these tracks. They are for rotating cars to measure the radiation patterns of mobile antennas mounted on different parts of different cars. They drive the

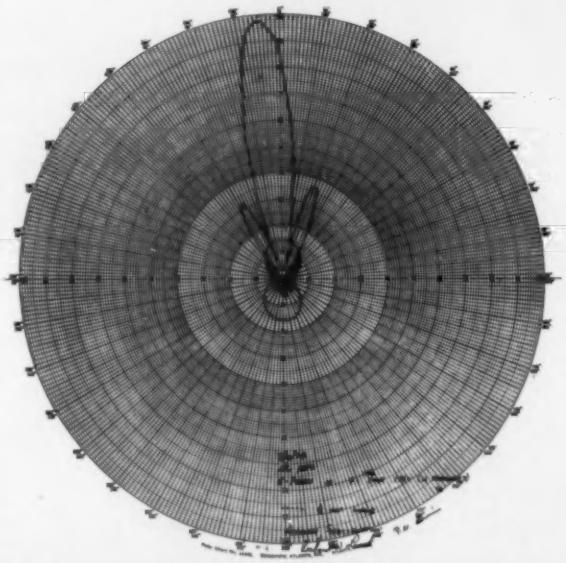

This is the pattern drawn by the chart recorder for the 44-element array on 146 MHz with the comparison from a reference dipole (dotted line).

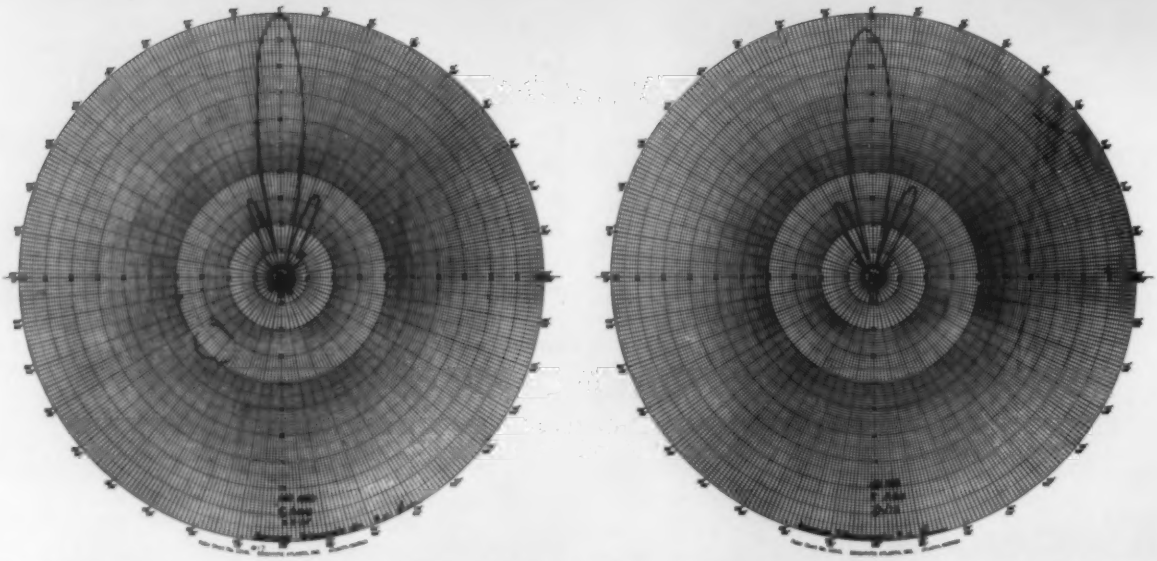

This is the same array, but measured at 148 MHz. Not a lot of difference—certainly none that you would ever notice in use.

One more run was made with the array on 144 MHz to make sure that it was capable of working over the entire 2m band. It takes a lot of careful design to make a high-gain array such as this work over a four-megahertz bandwidth with as little loss as this one shows.

car with the test antenna onto the tracks and then rotate the whole works to get the pattern. It's quite a complete test site facility.

After the test, Al had the 44-element array boxed up and shipped to the 73 lab. It took longer than we figured to get it airborne, due to some serious delays in getting a promised tower. The antenna puts out one whale of a signal, as you can see from the pattern on the graph. ■

ROBOT'S MODEL 400 CONVERTER MAKES SSTV OPERATING EASY!

Contacts are established by voice communications.

SSTV is voice alternated with video operation.

Your SSTV system applies the SSTV audio signal to the transmitter microphone jack in place of the voice signal from your microphone.

Operation requires no more than the ability to focus a camera and adjust a TV set.

Any home TV set can be used for a display monitor without modification. The Model 400 connects to your TV set's antenna terminals by means of the RF adaptor kit.

In fact, SSTV is so easy, it's the first ham radio activity that permits the whole family to be involved.

TUFTS ELECTRONICS
209 Mystic Avenue
Medford, Mass. 02155
1-617-395-8280 (Mass. residents)
1-800-225-4428

R9

ROBOT

SSTV EQUIPMENT

Model 400 Scan Converter $795
Slow-to-fast and fast-to-slow converter; all solid state. Shipping weight: 15 lbs.

RCA TC1000 CCTV Camera $280
500 line resolution; 10,000: 1 ALC; ext. adj: Beam, Target Focus, vidicon position; Weight: 3 lbs., 10 oz. Comes with 16mm lens. 2¾" H x 4½" W x 9½" D. Shipping weight: 7 lbs.

RF Modulator Kit . . . . . $ 25
P.C. board, assembled and tested, for converting video to RF for input to TV receiver antenna terminals (Channel 2 or 3), with tuning tool. Requires +5V d.c. power supply.

20 ft. coax video cable with BNC connectors . . . . . $ 15

UHF Plus to BNC jack adaptor $2.00

Reader Service—see page 211

10% DISCOUNT ON ALL LUNAR PRODUCTS

DURING LUNAR'S 2ND ANNIVERSARY SALE!

(July 1 through July 31 at all participating dealers).

LUNAR'S 28-432 LOW NOISE FIGURE RECEIVING PREAMPLIFIERS

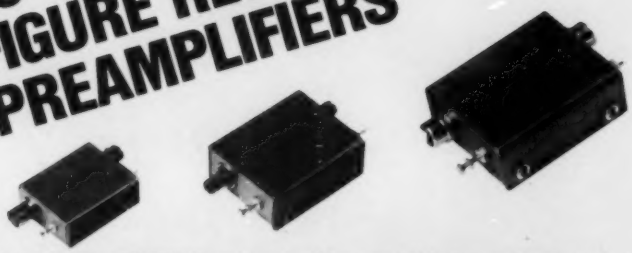

These ultra-performance "ANGLELINEAR" receiving preamplifiers are suitable to the most demanding needs where low noise figure is important. Amateur Radio, Commercial, NASA & Military users have lauded their superior performance. Uses include all types of weak signal work such as EME, Tropo & Ionospheric Scatter, Satellite Communications, Radio Astronomy, Meteor Scatter, etc.

Construction of highest quality; small physical size, gold alodined conductive chem film encloses for maximum shielding. RFI filtering of DC line yields -50 dB at 30 MHz and >-70 dB, 1-10 GHz attenuation. PC Boards are double sided plated holes to ensure maximum performance. All amplifiers are aligned on automatic noise figure measuring equipment, with traceability to standard Hot-Cold noise test system.

MODEL	NOISE FIGURE	GAIN	3 dB BW	1 dB COMP.	1c @ 12VDC	PRICE
PA 28	1.1 dB	15 dB	1.3 MHz	+1 dBm	10 mA	$35.95
PAI 28	1.5 dB	14 dB	1.3 MHz	+1 dBm	10 mA	$49.95
PA 50	1.3 dB	12 dB	2.5 MHz	+1 dBm	10 mA	$35.95
PAI 50	1.6 dB	11 dB	2.5 MHz	+1 dBm	10 mA	$49.95
PA 144	1.5 dB	11 dB	2.5 MHz	+1 dBm	10 mA	$35.95
PAI 144	1.9 dB	10 dB	2.5 MHz	+1 dBm	10 mA	$49.95
PA 220	2.0 dB	11 dB	6 MHz	+1 dBm	10 mA	$35.95
PAI 220	2.5 dB	10 dB	6 MHz	+1 dBm	10 mA	$49.95
PA 432-2	1.6 dB	14 dB	150 MHz	-20 dBm	6 mA	$41.95
PAF 432-2	3.0 dB	13 dB	50 MHz	-20 dBm	6 mA	$49.95
PAE 432-5	1.0 dB	16 dB	180 MHz	-20 dBm	4 mA	$64.95

KEN PRO KR 500 ROTATOR

Designed for 180 rotation Brake holds up to 2000 kg/cm (1750 lbs./inch) torque.

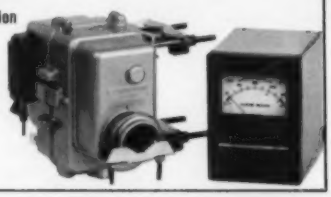

10% OFF

LUNAR'S PORTABLE ANTENNA TOWER

- Manufactured in our San Diego plant.
- Ideal for ground or roof mounts.
- One man can assemble and erect.
- Extremely rugged.
- Lightweight.
- Modular and portable.
- High stability with proper guying.
- High quality aluminum alloy construction.

AIGA ROTORS

ART 3000

Handles up to 10 sq. ft. antennas and to 500 lbs., balanced weight. 8 conductor cable.

ART 8000

Handles extra heavy duty asmuth rotator for the most demanding installations. 10 conductor cable. The King Kong of rotors. Loads in excess of 1 ton.

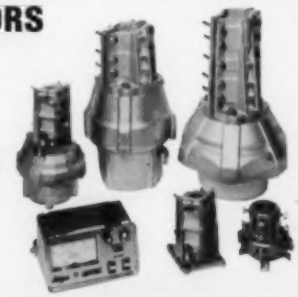

M&M RF DISTRIBUTORS

M78

P.O. Box 82183, San Diego, CA 92138

2785 Kurtz Street, Suite 4, San Diego, CA 92110

CALL (714) 299-9741

Secrets of Guyed Towers

—put 'em up and keep 'em there

Trade real estate for security.

Peter Carr WB3BQO
329 Little Avenue
Ridgway PA 15853

There is an old saying among hams that "if it stays up, it's too small." Who among us can truthfully say that on those long winter days we haven't spent a moment or two thinking how great it would be to have a five-element, 40-meter beam in the backyard, fed with 2 kW, and a hundred feet above ground? Dreams? Well, maybe. But it's sure that whatever your idea of the "ultimate" antenna array, it's got to be held up by something.

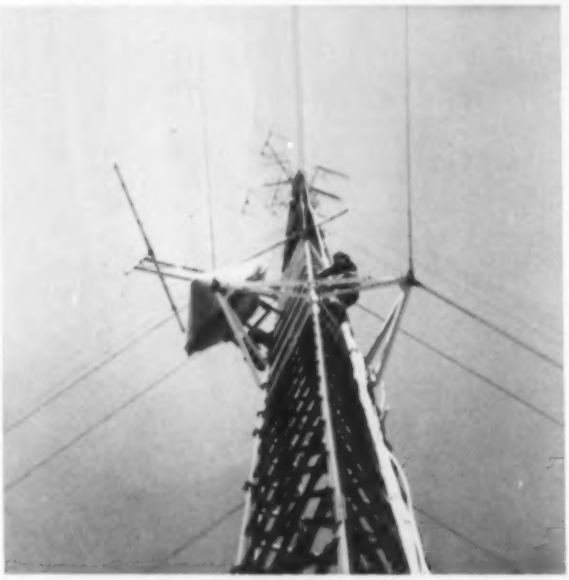

This is a commercial CATV tower. The dish at the left is a microwave receiving antenna. Mounted below it is a "star mount" anti-torque guy wire/frame system. The tower height is 500 feet.

Since the best antenna farm starts with the support equipment, let's look at the best antenna support: the guyed tower. A tower is like a chain, in that it is only as strong as the weakest link. Self-supporting towers are linked to Mother Earth at one point—the base. Guyed towers, on the other hand, have four support points over which to spread the load—three anchors and the tower base. The penalty for this added strength is the larger chunk of real estate required to accommodate the guy-anchor supports.

In planning to erect a tower, there are some decisions and compromises to be made. One must be realistic about what will adorn the top of the tower and the worst case of wind loading that can be anticipated. The antenna load must be added to the wind loading to determine the total load environment in which the tower will be operating. Most antenna manufacturers publish load figures as part of their advertising, or will furnish data on request. The same goes for tower makers, and they also have data about

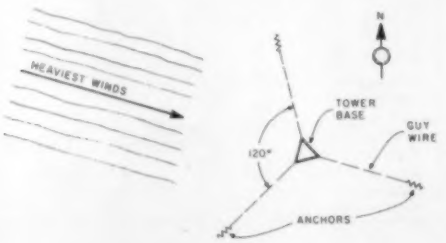

Fig. 1.

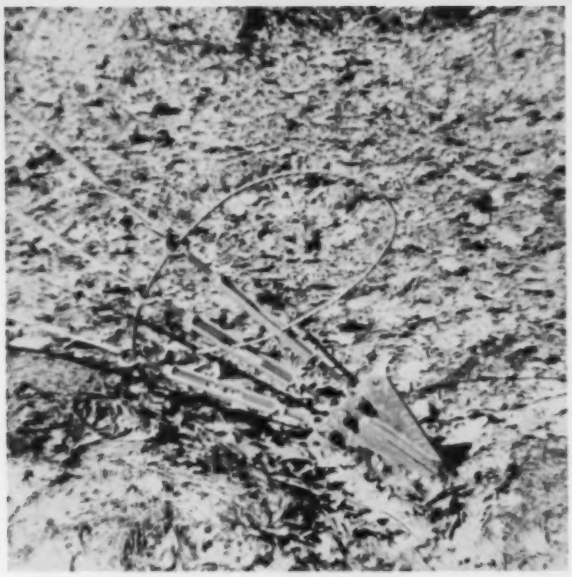

Here is a commercial tower anchor and "eyeplate." Note the length of guy wire laced through the turnbuckles to prevent loosening.

The bottom two guys shown here are attached to the anchor plate and to the "star mount" just below the microwave dish.

wind and ice conditions throughout the country to help in figuring the operating load.

As a rule of thumb, anchors should be placed out from the tower base a distance of between one-half and two-thirds the tower height. For a hundred-foot tower, this means the distance from base to each anchor will be from fifty to seventy-five feet. Since this distance determines the angle of the guys at the tower, it represents a compromise between the ideal one-foot-up for one-foot-out, or guy angle of forty five degrees, and some even sharper guy angle which conserves real estate. These considerations outline the practical limits of tower height.

Other factors which limit tower height are: surrounding objects like houses and trees, sloping terrain, local building codes, and neighbors. Each should be taken into careful consideration since towers are no less expensive to take down than to put up.

Since the load of a tower is in two parts, it is best to look at each in choosing a brand and model of tower. The side load is the force which is supported by the anchors and guy lines. The vertical load is supported by the tower and base alone. Most towers are triangularly shaped, and the wider the spread between the vertical legs and the larger in diameter they are, the greater the vertical load they will hold. Knowing the antenna loading figures and the weather conditions for your area, it is possible to have a tower manufacturer recommend the proper size tower for your needs.

Two last considerations should be figured into the choice of heights. How far will the rig be from the antenna, and what will the cable loss be, compared to the benefit of added height? In addition, who will service the array? It seems that the number of volunteer climbers varies inversely with the height of the work!

Planning the actual construction is the next step in the process. Survey the land for the locations of the base and anchors. Let's say you come up with a layout similar to the one in Fig. 1.

In this "helicopter" view of the project, we see that the anchors are laid out 120 degrees apart and that two of them are upwind of the tower base. This spreads the worst of the wind loading between two anchors.

The type of soil will determine what type of anchor should be used. There are screw-type units which don't need a hole but are screwed into the undisturbed earth. These are okay for smaller systems with light loading and with firm to slightly-rocky soil. The other type is the bell anchor which requires that a hole be dug. The bell-shaped bottom of this type of anchor is attached to a long rod which sticks out of the ground after the anchor is placed in the hole. When the bell is struck with a heavy bar, the anchor will spread out and dig into the sides of the hole. The hole is then backfilled using small rocks and well-tamped dirt. These bell anchors hold a larger load since they are bigger at the bottom and deeper in the ground than the screw type.

The tower base also is chosen after considering the type of soil at the construction site. Since the base has to support only the vertical load, it doesn't have to be very deep. It should be down far enough, however, so that frost will not cause it to shift position. Manufacturers' recommendations should be followed here so that a firm footing is assured.

Finally, make a list of the required tools and gear for the actual job. Try to obtain the services of someone who has done similar work before, and rely on his experience. If no hams are around to fill the bill, try the local power or telephone company. Their construction crews routinely handle projects similar to this, and probably will know where you can obtain the ropes, guy/jacks, strain dynomometers, and climbing equip-

Guy wires and preformed wrap-on grips are shown at the tower end. Note that the bolt acts as an axle for the grip. The height is 375 feet.

A Dill tower in CATV service is pictured here. The tower is 100 feet tall, in 10 foot sections weighing about 60 pounds each. The sections are 11 inches on a side.

ment you will need.

Before getting into the actual nuts and bolts of hanging up the tower, it's good to discuss various aspects of safety on the job. Advance planning on paper of each step in the process will allow each member of the crew to familiarize himself with the sequences involved. Line up enough people to do the job, and don't forget that at least one should be experienced. All climbing tools and small hand tools should be in first-class shape. Hardhats are a must for the ground crew, and no one should be closer than twenty feet to the tower base for any reason other than to attach gear to the ropes going up the tower. The auxiliary leg, which sometimes is used to hold the weight of a tower section as it is placed on already erected sections, should be inspected carefully. The combined weight of the leg and section can do considerable damage and injury if they fall.

The Dill tower base rests on a large flat rock two feet down and buried in small rocks and well-tamped dirt.

When everything needed is on hand, the anchors are dug in, and the necessary personnel have been lined up, it is time to pick a day to complete the job. Weather is the main consideration here since to be safe the entire job should be completed in one day. The Flight Service Center at the local airport is an excellent source of weather information, and their forecasts of wind conditions are especially good.

On the morning of the big day, begin by bolting the first three sections of tower together on the ground. Attach to the top of the assembly three guy wires which have been cut to roughly the correct length. Set the bottom of the assembly next to the tower base (which is in the ground) and lay out the guy wires down the length of the three-section assembly, over the base, and straight out beyond. With one man holding down on the bottom to make it dig into the ground, and three more pulling at the guy wires, have the remaining people lift the top of the tower and raise it over their heads. As they walk toward the base raising the tower above them, the guy wire attendants will steady the tower side-to-side while at the same time helping to pull the tower vertical.

When this move is completed, the tower should be standing on the ground next to the base, stabilized by the guy wires. Next, lift the tower onto the base and install the three bottom bolts. Attach the guy wires to their respective anchors, and, using a spirit level, a plumb bob, or other sighting line, snug up the guys until the tower is exactly vertical. This operation is important since when later sections are installed, the tower will be put into a bind if it is not

The anchor rod holds three guys using preformed grips. The rod is six feet long and is buried nearly five feet down.

This is a partly installed preformed grip. No tools are needed, and it may be removed for re-tensioning of the guys and easily reapplied.

exactly vertical.

The climbing people are now sent aloft, and the auxiliary leg (or stiff-leg), pulleys, and hand ropes are made ready to raise the next tower section. Since it is very hard for a person to get good lifting leverage while leaning back in a line belt, the ground crew should raise each section while the climbing crew steadies it and guides its placement atop the last section erected.

Remember that during this operation those on the ground should not stand near the tower base, or in an area where dropped tools or parts might fall.

Continue adding tower sections and guy wire sets until the tower is complete. Since the last section normally is built to accept an antenna rotator and mast, these items are more easily installed before that section is raised.

Having aligned the tower each time that a set of wires was installed, the complete unit should be pretty close to vertical. By sighting upward along each leg of the tower, any bends will be seen easily and can be removed by adjusting tension on the appropriate guy wire.

Now that the tower is straight, the next step is to equalize the tension on each set of guy wires. A device called a strain dynomometer is used to read tension on a cable. If this is not available, the only recourse is to pull each guy wire slightly out of line and feel the tension by hand. Sighting up each guy wire from anchor toward the tower and judging the sag is another method, but it is not as reliable due to the varying lengths of the lines. The aim is that each guy wire should carry the same strain as every other.

The tower is now complete and ready to accept antennas and downleads. Even though it is ground-mounted and is attached to guy wires and anchors which also are at earth ground potential, it still is wise to electrically ground the tower. Most commercial installations use a six-foot ground rod at each tower leg, driven as close to the base as possible. This is sufficient to protect the tower, although lightning protection at the shack end of the downleads still should be used. In the event that lights are required, or any source of commercial power is used at the tower, the ground system should be tied into the neutral of the electric line.

When very large arrays are rotated on a tower, the torque will cause twisting of the structure. While this does not affect the life of the tower, it does affect the aiming accuracy of VHF directional arrays during windy conditions. The cure is to install another guy system by bolting to the tower a length of pipe or angle iron about six feet long, as per Fig. 2.

Guy wires and grip are attached to a tower leg.

Since this guy system carries only the twisting load applied to the tower, it need not be as heavily constructed as the main system. Screw-type anchors and number ten steel fence wire are more than adequate, along with TV-type U-bolts connecting the pipe to the tower legs. With this arrangement mounted about three-fourths of the way up the tower, it should remove most of the twisting action and considerably reduce the whiplash effect on the antenna elements.

There you have it. Guyed towers offer the most stable platform for large arrays and greater heights under the most extreme weather conditions. They also offer confidence in the knowledge that those expensive antennas are mounted up where they operate best and are supported by a system which will offer safe and reliable operating for years to come. ■

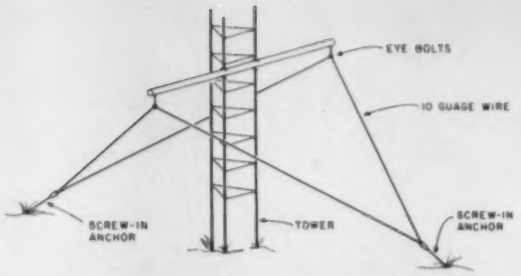

Fig. 2.

There's a new, eighth OSCAR satellite in orbit, and the AMSAT team helped put it there!

Your help is needed for future satellites. Join AMSAT and support the new, advanced Phase III series of OSCARs, engineered to provide communications over transcontinental distances for hours at a time.

Send $10 membership dues to AMSAT, P.O. Box 27, Washington, D.C. 20044. Life membership is available for a tax-deductible donation of $100 or more, payable in quarterly installments if you wish.

Phase III satellite solar cells may be sponsored for $10 each, and we'll send you a certificate specifying the cells you are sponsoring.

For a tax-deductible contribution of $1,000 or more, we'll even inscribe your name on a plaque to be placed in orbit aboard the Phase III spacecraft for posterity, and we'll send you a replica honoring your contribution.

Dues and contributions may be charged to VISA or Master Charge. Phone us at (202) 488-8649.

Radio Amateur Satellite Corporation
P.O. BOX 27, WASHINGTON, D.C. 20044
AMSAT
AMSAT MEMBER

Hustler:
The First Family
of mobile amateur two meter antennas!

Maximum range, improved gain and better SWR at resonance put you ahead on the highway with Hustler. Our mobile two meter antennas are known for quality. And long service life, too. Featuring the finest stainless steel and chrome plated components.

It's quality and performance like this that make Hustler the mobile amateur two meter antenna you should be riding with!

Most models available in 1-1/4 meters.

HUSTLER INC H36
3275 North B. Ave. • Kissimmee, Florida 32741

Clearly the choice of those who know quality.

HUSTLER DEALERS

Calumet Electronic Supply
3772 Arthur St.
Gary IN 46408
219-887-4961

Communications Services
Main St.
Philadelphia MS 39350
601-656-5345

Gismo Communications
2305 Cherry Rd.
Rock Hill SC 29730
803-366-7157

HI, Inc.
Post Box 864
Council Bluffs IA 51501
712-323-0142

Honolulu Electronics
819 Keeaumoku St.
Honolulu HI 96814
808-949-5564

Kryder Electronics
5520 North Seventh Ave.
Phoenix AZ 85013
602-249-3739

Reader Service—see page 211

10% DISCOUNT ON ALL LUNAR PRODUCTS

DURING LUNAR'S 2ND ANNIVERSARY SALE!

(July 1 through July 31 at all participating dealers).

LUNAR'S MODULAR ERECTABLE TOWERS

- Manufactured in our San Diego plant.
- Ideal for ground or roof mounts.
- One man can assemble and erect.
- Lightweight.
- Extremely rugged.
- Modular and portable.
- High stability with proper guying.
- High quality aluminum alloy construction.

These unique antenna towers can be installed on the ground or roof. Since they're easily transported and site erected, they're a natural for field and portable operations.

Constructed of sturdy aluminum alloy, they're sturdy enough to handle large size HF beams and EME arrays as well. Also available with optional stainless steel hardware for harsh environments.

Base and one tower section are packed in a 6'x3½"x3½" carton. Each additional tower section is packed in a 6'x3½"x3½" carton. Rotor mounting plate and base flanges are in a separate box. Can easily be car topped to any location. Guy rings included. Guy wire and hardware not included.

10% OFF

LUNAR'S RECEIVING PRE-AMPS.

Suitable to the most demanding needs where low noise figure is important. Uses include all types of weak signal work such as EME, Tropo & Ionospheric Scatter, Satellite Communications, Radio Astronomy, Meteor Scatter, etc. Highest quality construction and components.

LUNAR'S LINEARIZED POWER AMPS

10% OFF

- Covers entire Amateur Band w/o Tuning
- Built-in Receive Preamplifier
- Automatic variable TR switching
- Exceeds FCC R&O 20777 Requirements of –60 dB
- Preamp & Power Amp Independently Controllable
- Preamp nom 10 dB gain, 2 dB Overall NF
- Functionally Designed Package includes mounting lip

BOB'S AMATEUR RADIO CENTER

318 N. Main St. Salisbury, N.C. 28144 Hours: M-Sat 9am-7pm, Wed. to 9pm. ✓B53

Call For Quotes Toll-Free VISA master charge N.C. residents call 1-704-636-7959

1•800•438•2006

Announcing our new Second Location near Miami Airport
7322 N.W. 46th St., Miami, Florida

✓ Reader Service—see page 211

William A. Bleher W8GQL
18678 Negaunee
Detroit MI 48240

Death-Defying PL Mod for the KDK 2015

— not for the squeamish

No more clipping.

Author's Note: Since this article was written, KDK has improved their "fix" by adding additional RC filters between the NOR gate and the base of the output transistor.

This article is not for the timid soul. It takes considerable courage to take a brand new rig and cut the circuit foil and drill holes in the PC boards. This statement is not intended to scare you off, but to forewarn you. The results, however, are well worth the effort.

A prerequisite for outlining any solution is to first define the problem. The basic complaint with the original KDK PL is that it may or may not activate a given repeater, and when it does, there are complaints of the PL being audible and clipping with modulation.

Investigation of the existing PL circuit reveals a CMOS 2-input NOR gate chip (MC14001) connected as a square-wave oscillator as shown in Fig. 1. They couldn't have planned it worse. The fast rise and fall time of the square wave produces many harmonics of the 100-Hz fundamental at 200, 300, etc., accounting for the audible complaint.

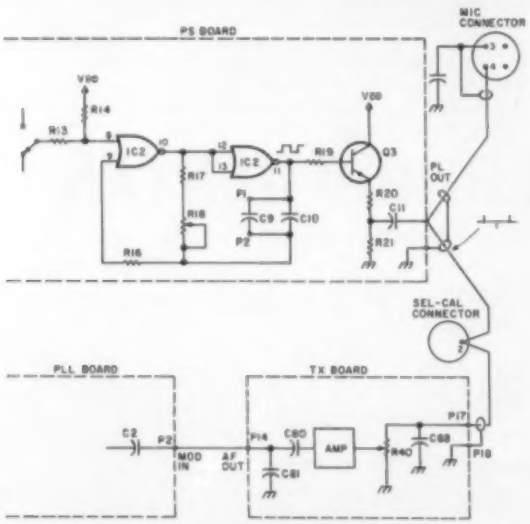

Fig. 1. Existing KDK PL circuit.

To make matters worse, the square wave is differentiated by the .01-uF coupling capacitor to the speech amplifier, producing narrow pulses from each edge of the square wave (pulse modulation, yet). This has to be a terrible shock to the preamp and is probably the reason why the repeater does not recognize the PL. Attempts to activate the repeater by increasing the PL level further aggravate the audible problem.

The official "fix" available as a modification kit from the US distributor of the KDK units leaves much to be desired, since it simply adds a 0.1-uF shunt capacitor from the base of Q3 to ground to drastically slow up the rise and fall times, making it a triangular wave.

The ultimate solution, of course, is to change the PL signal to a sine wave. This is where the timid souls can leave to purchase their ME-3. The hardy and courageous individuals, however, should stay while we discuss how to linearize the existing CMOS digital gate for analog operation to generate a sine wave.

Any digital logic-inverting element (NAND or NOR gate or inverter) produces a high-level output with a low-level input and vice versa. The input switching threshold for a CMOS logic element is approximately 45% of the supply voltage (9 volts in the KDK). When the input signal passes through the threshold (4 volts), the output switches. It is at this switching level that the gate is operating in the linear region. A feedback resistor connected from output back to input, as shown in Fig. 2, linearizes the gate since a high output fed back to the input would tend to drive the output low, which when fed back to the input tends to drive the output high, which . . . etc. The gate finally compromises itself with both input and output floating at the 4-volt switching threshold level.

This circuit configuration lends itself very well for a Wein bridge sine-wave oscillator (sometimes

called a twin-T) by simply dividing the feedback resistor into two parts and adding the other necessary RC constants as shown in Fig. 3. The basic frequency of oscillation is given as $F = 1/(2\pi RC)$, but this is not exact and may vary considerably. A word of caution here: The capacitors must be a good quality ceramic or mica with good temperature stability, and the resistors must be 100 part-per-million temperature-coefficient units. One such circuit constructed with miniature plastic capacitors changed frequency by 50% when sprayed with Quick Freeze circuit cooler.

The final circuit design and KDK modifications are shown in Fig. 4. Note that the second gate is no longer used. The IC pad of pin 11 on the circuit board is still utilized, however, so the legs of the chip (pins 11, 12, and 13) were cut and a jumper added to connect circuit board pad 10 to 11 to complete the path to the output transistor. The legend for the various circuit modifications appears below the schematic. The 0.15-uF capacitor across the 287-Ohm resistor and 1k pot was required to eliminate a secondary high-frequency oscillation. The value of this capacitor, although not critical, will have some effect on frequency.

The major problem encountered was getting the PS board out far enough to work on it. There are a few wires from the PS board which are routed under the PLL board. This problem is solved by removing the four PLL mounting screws and tilting the board forward towards the front panel. A piece of masking tape will hold this board in the upright position.

The second problem is caused by the choke mounted on the rear plate and the ground wire from the power input connector. These leads are very short and make it impossible to move the PS board. It may be possible to unsolder the choke leads; however, I chose to unmount the choke, leaving it attached to the board. This is accomplished by gently removing the rear identification plate by lifting with a small screwdriver (sticky back) to expose the choke-mounting screws. The ground wire can easily be unsoldered at the power input connector.

The transceiver is then positioned on its side and the PS board separated as far as possible from the chassis with all other wires still connected. Not an ideal work situation, but tolerable.

The following is a complete step-by-step procedure for making the modification. Refer to the PS board layout diagram on page 12 of the KDK manual to locate the various points referenced.

1. Unsolder the two shielded audio cables from the PS board, cut them to a length sufficient for splicing, and cover the splices with shrink tubing. This disconnects the PL output and completes the microphone cable routing to the SEL-CAL connector and speech amplifier.

2. Cut the legs of pins 11, 12, and 13 on IC2.

3. Solder a jumper across pads 10 and 11 on rear of board.

4. Cut circuit foil between P1 and junction of R19 and C10.

5. Cut circuit foil between P2 and R18 potentiometer.

6. Replace R16 470k resistor with a 16.9k resistor.

7. Replace R17 33k resistor with a 14.3k resistor.

8. Replace R18 50k pot with a 5k pot.

9. Replace C9 .033-uF capacitor with a .15-uF capacitor.

10. Replace C10 .068-uF capacitor with a .15-uF capacitor.

11. Replace C11 .01-uF capacitor with a .22-uF capacitor.

12. Replace the combination of R20 4.7k and R21 470-Ohm resistors with a single 5k miniature potentiometer (about the size of a transistor). Mount this pot with one end in the R21 ground pad, the other end in the R20 pad which connects to the emitter of Q3, and the rotor in either of the two pads at the junction of R20, R21, and C11.

13. Drill a hole through the ground plane at the edge of the PC board in line with R16 and next to the nicad battery. Mount the .33-uF capacitor from the junction of R18 pot and R16 resistor to the ground-plane hole.

14. Position the 1k pot next to the nicad battery such that the rotor and one end are over the ground plane and the other end is over the open area (no ground plane). Mark the points, drill the holes, and mount the pot. Make sure the speaker clears the pot when the bottom cover is mounted.

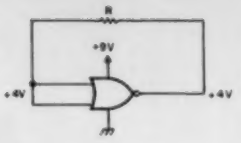

Fig. 2.

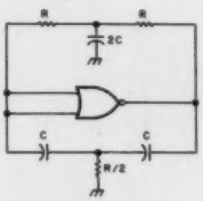

Fig. 3.

15. Drill two more holes in the open area for mounting the 287-Ohm resistor next to the 1k pot. Mount the resistor in the holes and bend one lead over and solder it to the open pot lead.

16. Drill another hole in the open area next to the 287-Ohm resistor hole and also another hole through the ground plane for mounting the .15-uF bypass capacitor across the 187-Ohm 1k pot combination.

17. Connect a wire from

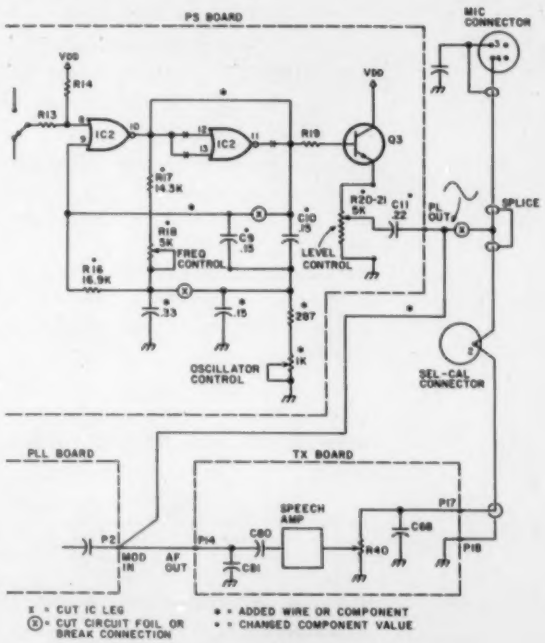

Fig. 4. Modified KDK PL circuit.

the junction of the .15-uF bypass and the 287-Ohm resistor to P2.

18. Connect a jumper wire from P1 to the pin 9 end of R16.

19. Connect a wire from "PL OUT" (open end of C11) to P2 "MOD IN" on the PLL board (terminal with green wire).

Adjustment is best accomplished with a scope and counter; however, it may be possible to "ballpark" the frequency adjustment by comparing it to a strong signal with PL on the repeater input with an auxiliary receiver. The 1k oscillation control should be adjusted for the maximum resistance possible that will sustain oscillation without distortion of the sine wave. A rough setting of the level control can be made by measuring the audio voltage level with a voltmeter at the "MOD IN" terminal under normal modulation and adjusting the PL "LEVEL" for 10% of this value. Final tweaking may require on-the-air tests with assistance from another operator.

This modification has been in use for several months with excellent results. Temperature stability is very good (±0.2 Hz) when sprayed with Quick Freeze circuit cooler (−50° F.) and heated with a heat gun. Both temperatures were well beyond my operating thresholds. Final results—no more clipping or complaints of audible PL with 100% solid QSOs.

Next project—slowing down the scanning rate so more than two words can be heard when continuously scanning the memory channels for familiar voices or calls. Maybe we can start a KDK "mod squad." ■

KLM MAKES 40 EASY!

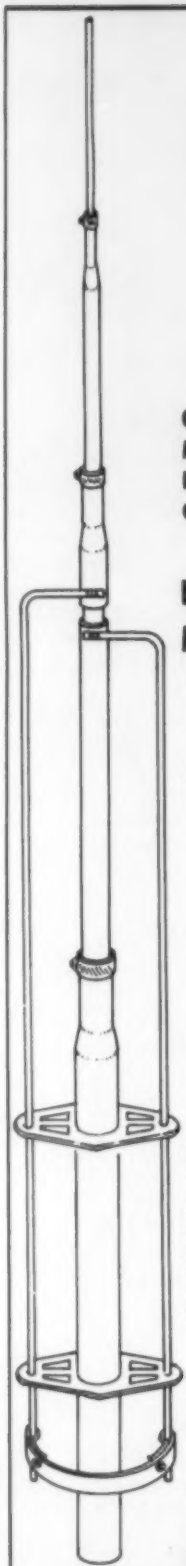

½ element condensed

GOT A HOLE IN YOUR COVERAGE? MISSING THE CONSISTENTLY GOOD LOCAL COMMUNICATIONS AND DX CAPABILITIES OF 40 METERS?

KLM's 7.2-1 Dipole Module is the Answer!

- **LIGHTWEIGHT** — *for easy one man installation on your boom or mast (horizontal or vertical)*
- **ROTATABLE** — *right along with your other antennas*
- **BROADBANDED** — *VSWR 2:1 and better across the whole amateur band — or OPTIMIZE, 6.95 to 10 MHz*
- **VERSATILE** — *divide for 2 el. vertical or add modules later and upgrade to 2 or 3 el. beam!*
- **COMPACT** — *KLM's unique linear loading system reduces size to a practical and efficient 46 ft.*

You get the same quality materials as KLM's world famous HF "Big Stickers"; virtually indestructable Lexan insulator, stainless steel electrical hardware, seamless 6063-T832 alloy elements. Assembly is simple and speedy. No special tools or skills are needed.

Why wait any longer? **40 METERS IS EASY WITH KLM'S 7.2-1 DIPOLE MODULE. IT'S AVAILABLE NOW. SEE YOUR LOCAL KLM DEALER . . . . . .**

KLM ALSO BUILDS THE FULL SIZE 7.2-4 ELEMENT "BIG STICKER" AND A VARIETY OF MONOBANDERS, LOGS, DIPOLES, VERTICALS, AND OTHER ANTENNAS FOR HF, VHF, OSCAR, AND UHF. POWER AMPS, PREAMPS, AND CONVERTERS, TOO. WRITE FOR A COMPLETE CATALOG.

KLM — HELPING YOU MAKE THE MOST OF AMATEUR RADIO ✓K4

17025 LAUREL ROAD, MORGAN HILL, CALIFORNIA 95037

CUSTOM TRANSFORMERS

HEAVY DUTY REPLACEMENT TRANSFORMERS

ALPHA A77D Power	$135	HEATH DX-100 Modl	$ 95
BTI LK-2000 Plate	$135	HEATH HX-10 Power	$ 95
COLLINS 30S-1 Power	$215	HEATH SB-220 Plate	$125
COLLINS KWS-1 Plate	$135	HENRY 2K Plate	$150
COLLINS 516F-2 Power	$ 95	HENRY 2K-2 Power	$155
DENTRON 160-10L Power	$125	HENRY 2K-4 Power	$165
DRAKE L4B Plate	$165	HENRY 3K-A Plate	$165
GONSET GSB-100 Power	$ 95	HENRY 3K-A DC Choke	$ 85
GONSET GSB-201 Power	$135	EJ] T-BOLT Plate	$125
H-CRAFTERS HT-32 Power	$ 95	EJ] 500 Modulation	$ 95
H-CRAFTERS HT-37 Power	$ 95	EJ] 500 DC Choke	$ 75
HEATH DX-100 LV Power	$ 95	NATL NCL-2000 Plate	$125

OFF-THE-SHELF SPECIALS

PLATE XFMR:	2400 VAC @ 1.5A ICAS 220/240 PRI-41LB	$150
PLATE XFMR:	3000 VAC @ 1.5A CCS 230 PRI-60LB	$195
PLATE XFMR:	3000 VAC @ 0.7A ICAS 115/230 PRI-27LB	$115
PLATE XFMR:	3500 VAC @ 1.0A ICAS 115/230 PRI-41LB	$150
PLATE XFMR:	4000/4600 VAC @ 1.5A ICAS 230 PRI-60LB	$195
PLATE XFMR:	6000 VCT @ 0.8A CCS 115/230 PRI-41LB	$150
FILMT XFMR:	5.0 VCT @ 30A 117 PRI-9.5LB	$ 30
FILMT XFMR:	7.5 VCT @ 21A 117 PRI-9.5LB	$ 30
FILMT XFMR:	7.5 VCT @ 55A 115/230 PRI-14.6LB	$ 65
FILMT XFMR:	7.5 VCT @ 75A 115/230 PRI-20.2LB	$ 95
FIL CHOKE:	30 AMP Bifilar Wound on ½"x7" rod	$ 9
DC CHOKE:	8.0 Henries @ 1.5 AMP DC 41LB	$150
SWG CHOKE:	5-30 Henries @ 1.0 AMP DC 23LB	$100

ALL TRANSFORMERS & CHOKES GUARANTEED FOR 24 MONTHS

Many others also available. Write for free list or quote on any custom transformer, choke, or saturable reactor.

✓D8

Peter W. Dahl Co.

4007 Fort Blvd. • El Paso, Texas 79930

Telephone (915) 566-5365 or (915) 751-4856

✓ Reader Service—see page 211

10% DISCOUNT ON ALL LUNAR PRODUCTS

DURING LUNAR'S 2ND ANNIVERSARY SALE!

(July 1 through July 31 at all participating dealers).

LUNAR'S MODULAR ERECTABLE TOWERS

- Manufactured in our San Diego plant.
- Ideal for ground or roof mounts.
- One man can assemble and erect.
- Lightweight.
- Extremely rugged.
- Modular and portable.
- High stability with proper guying.
- High quality aluminum alloy construction.

These unique antenna towers can be installed on the ground or roof. Since they're easily transported and site erected, they're a natural for field and portable operations.

Constructed of sturdy aluminum alloy, they're sturdy enough to handle large size HF beams and EME arrays as well. Also available with optional stainless steel hardware for harsh environments.

Base and one tower section are packed in a 6'x3½"x3½" carton. Each additional tower section is packed in a 6'x3½"x3½" carton. Rotor mounting plate and base flanges are in a separate box. Can easily be car topped to any location. Guy rings included. Guy wire and hardware not included.

10% OFF

LUNAR'S RECEIVING PRE-AMPS.

Suitable to the most demanding needs where low noise figure is important. Uses include all types of weak signal work such as EME, Tropo & Ionospheric Scatter, Satellite Communications, Radio Astronomy, Meteor Scatter, etc. Highest quality construction and components.

LUNAR'S LINEARIZED POWER AMPS

10% OFF

- Covers entire Amateur Band w/o Tuning
- Built-in Receive Preamplifier
- Automatic variable TR switching
- Exceeds FCC R&O 20777 Requirements of -60 dB
- Preamp & Power Amp Independently Controllable
- Preamp nom 10 dB gain, 2 dB Overall NF
- Functionally Designed Package includes mounting lip

BRODIE ELECTRONICS CO.

B42

VISA TEL. (405) 794-0406 master charge

2537 Edgewood Dr., Moore, Oklahoma 73160

Reader Service—see page 211

Feed-Horn Mounting Made Easy

—solution to a pesky problem

More on microwaves.

Dr. Ralph E. Taggart WB8DQT
602 S. Jefferson
Mason MI 48854

Until you know a little bit about the subject, the antenna portion of a microwave project seems quite simple. The most difficult aspect is building or finding a dish—or so it seems! No matter how you acquire the dish, however, you will discover that your problems have just begun.

Photo A. This is a feed-horn assembly for use at the 1.7-GHz satellite frequency.

Next you must find a suitable feed, and if this search leads you into the literature, you will discover that that subject can be quite complex indeed.

In the final analysis, one of the simplest and most effective feeds in the low-frequency end of the microwave region is the horn feed. Rectangular horn feeds are superior, in the sense that the illumination pattern can be controlled with some precision. Their main drawback is that they are mechanically unwieldy.

Despite their reduced illumination efficiency, cylindrical feed horns are quite popular in that they can be constructed of metal pipe, tubing, or cans. A number of articles have appeared in the amateur literature describing the construction of horn-feed systems. They are quite non-critical in use—particularly in receiving applications.

Horn Mounting

Once you have obtained a dish and constructed a horn, you inevitably encounter the real problem—how to get the darn thing mounted! I have been working on antennas in the low microwave region (S-band) for the past two years now, in conjunction with a series of projects involving the GOES weather satellites. These satellites transmit pictures on a frequency of 1691 MHz, and thus I was forced to deal with the feed-horn mounting problem. The answer to it has proved to be quite simple and effective and should be applicable to similar situations involving operations on 1296, 2304, and 3300 MHz.

The key point in any mounting scheme is to avoid obscuring the open end of the horn with metal in any form. Any metal will serve to shield out a certain portion of the received rf, all of which will be focused into the mouth of the horn in a well-designed system. The two most common mounting schemes are shown in Fig. 1. One of

these is excellent but largely impractical, while the second is very inelegant and somewhat inefficient.

The first involves the use of either three or four spider-arm assemblies running from the horn to the periphery of the dish. The arms do not impede the rf front reflected from the dish surface into the horn, and they can be made even of metal for, although they do intercept the wave front as it arrives at the dish, their area is quite small compared to the area of a typical dish; the gain reduction is not measurable.

This does, however, highlight why obstructions to the horn are so critical. *All* the rf energy reflected by the dish surface must pass into the relatively small opening represented by the mouth of the horn. Any metal obstruction here can cancel out a good percentage of the gain!

The primary disadvantage of the spider-arm system is the difficulty in fabricating it. One must have considerable mechanical ingenuity to devise fastenings to secure the arms to the horn and to the edge of the dish. The arms must be of equal length, provide rigid support, and must hold the horn at the proper focal length for the dish in use while also permitting rotation of the horn to match polarization with the transmitted signal. Since the precise position of a particular feed horn relative to a particular dish at a given frequency can be determined only approximately at first, one is in for a considerable period of tinkering to get everything right.

The second approach is to use a support rod at the center of the dish—usually fabricated of plumbing tubing and fittings—with an offset to accommodate the horn radius, as shown in Fig. 1(b). The horn is clamped to the tubing using large hose clamps or some other system. It is an easy system to adjust, since the horn can be moved up or down the tube for focusing prior to being clamped in place. The major disadvantage is that the tube does absorb rf coming in from the dish surface. Also, the system looks terrible!

Figs. 2 and 3 show a much better system. The horn is mounted to a square of unclad G-10 board material (no copper) using four small metal brackets outside of the horn. The G-10 square is just slightly larger than the outside diameter of the horn, and the horn brackets attach within the corner areas that extend beyond the edge of the horn.

Other materials may be used for the mounting square if they pass a simple test. Simply hold a sheet of the material across the mouth of the horn and observe the indicated signal strength on the receiver. If there is no noticeable drop in the signal level, you are getting minimal attenuation and the material may be used. Most plastics appear to work fine, but be sure to check them out anyway, as the composition of a few plastics or their additives can sometimes show unexpected rf absorption at some frequencies in the microwave region.

The mounting square is attached to a mast of PVC plumbing tubing (don't use metal!) that holds the horn at the proper focal point. The mast is mounted to the center of the dish by sliding it over a stub of metal pipe secured to the center of the dish with a pair of pipe-mounting flanges. The PVC mast is slit where it slides over the pipe, and the entire mast assembly can be moved both up and down the pipe to optimize focus and rotated to match polarization. Once the proper orientation is achieved, the mast is locked into place with one or more hose clamps.

Fig. 1. Two common methods used to mount cylindrical feed horns. (A) shows the use of spider-arm support rods—an efficient system, but difficult to construct; and (B) shows the use of a support pipe, offset to accept the horn. This system is easy to construct but is unsightly and somewhat inefficient.

If the mast is quite long or the feed horn is heavy, the assembly can be guyed with dacron lines run from the corners of the G-10 mounting plate to screw-eye and turnbuckle assemblies attached to the rim of the dish.

Construction

The diagrams in Figs. 2 and 3 provide most of the information required, but a few points are worth discussing. First, the mounting plate *must* be attached to the PVC mast using nylon mounting brackets and hardware. If you use metal here, you will eliminate most of the advantages of this particular mounting scheme. The brackets and hardware can be obtained from hobby shops that carry supplies for radio-controlled airplanes.

The PVC tubing is cut about four inches shorter than the focal length of the dish. This permits the focal point to fall about 2 inches (5 cm) into the horn while

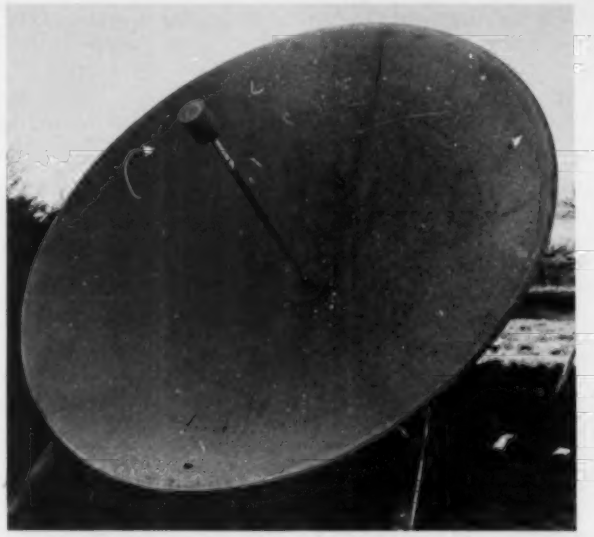

Photo B. Pictured here is a 10-foot (1.3 m) dish, complete with horn feed, used for GOES satellite reception. With a small dish in the 4- to 6-foot range, and depending on its weight, the horn may not require guying. With a larger dish of the sort shown here, the long mast does need dacron guys.

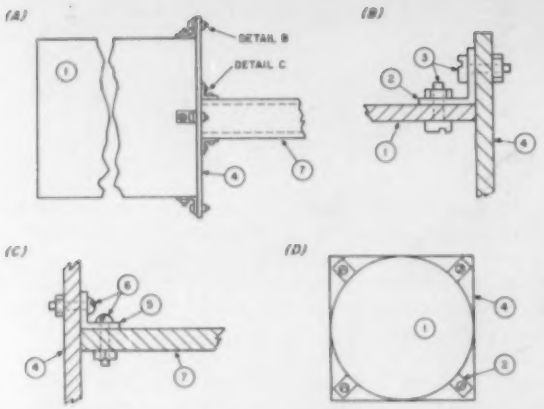

Fig. 2. (1): feed horn; (2): metal mounting brackets; (3): 6-32 pan-head hardware; (4): G-10 fiberglass mounting plate; (5): nylon mounting brackets; (6): 4-40 nylon hardware; (7): PVC pipe mast. (A) General view of the relationship of the cylindrical feed horn, mounting plate, and PVC mast. (B) Detail showing the attachment of the horn to the plate using metal brackets and 6-32 hardware. Use pan-head screws with the heads inside the horn to minimize metal protrusions into the cavity. (C) Detail of the attachment of the mounting plate to the PVC mast using nylon brackets and hardware. (D) End view of the horn, looking toward the dish, showing the relationship of the metal mounting brackets to the corners of the square G-10 mounting plate.

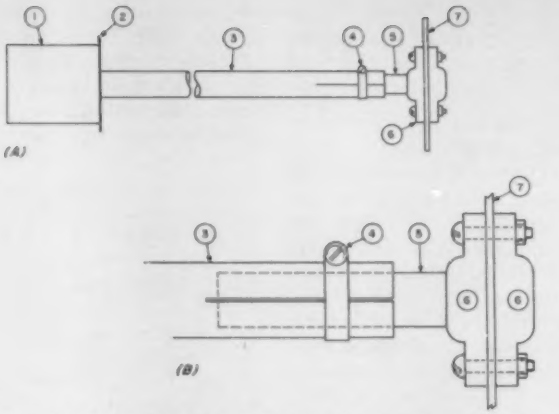

Fig. 3. (1): horn; (2): G-10 plate; (3): PVC pipe mast; (4): hose clamp; (5): steel pipe stub; (6): pipe mounting flanges; (7): dish surface. (A) The general relationship of the horn mounting-plate, PVC mast, pipe stub, and the pipe flanges used to secure the mast to the center of the dish. (B) Detail showing the attachment of the mast to the dish surface. Two pipe flanges, one on either side of the dish center, are used to provide rigidity. A pipe stub, which may be up to 1/3 of the dish focal length, is used to provide support to the mast. PVC and steel pipe sizes should be chosen so that the steel pipe is a slide-fit in the PVC pipe. The PVC mast is slit at the dish end and tightened down with one or more hose clamps.

still permitting about the same distance for downward movement of the assembly if required for focusing. The following assembly sequence should be followed:

(1) Mount the nylon mounting brackets to the end of the PVC mast. Doing this first lets you get pliers or fingers down inside the mast to tighten the hardware!

(2) The mounted brackets then can be used as a guide for marking the G-10 plate which can be drilled then and mounted to the end of the mast—again, use nylon hardware!

(3) The brackets (aluminum, brass, or other metal is OK) then may be mounted to the horn and the horn attached to the plate. In mounting the horn brackets, be sure to use pan-head screws with the heads inside the horn and the nuts outside. This minimizes metal protrusions into the horn which could distort the wavefronts in the waveguide horn assembly.

(4) The entire assembly is placed over the pipe stub, its position optimized, and then everything is tightened up with hose clamps.

If guying is required, it can be installed now. In the case of an antenna used for support of a satellite ground station, the guying system can perform a fine-tuning function in the alignment department. Large dishes (8-10 feet or larger) are quite critical in orientation, and it often is possible first to horse the dish into the best possible orientation, and then to use the guy adjustments to shift the horn position laterally as required to peak the signal level. If large displacements of the horn are required (more than an inch or so), it means that the dish was not aligned properly. The horn should be centered (guy lines of precisely equal length) and the alignment of the dish altered to bring up the signal. You then can fine-tune the alignment with the guy cables.

Since the pipe attached to the dish can provide some rigidity to the PVC mast, it is useful to know how long the pipe can be without absorbing significant rf. This is dependent upon dish focal length. Generally, if the pipe is about one-third of the focal length, it will not affect the signal level. This is because the horn obscures the center of the dish and the converging wavefront from other areas of the dish will not intersect the pipe as it would if the pipe were much longer.

If desired, you can run a bead of silicone seal around the edge of the horn where it attaches to the G-10 plate, to provide some weather-sealing. This is usually most important with antennas used for point-to-point ground service, as the horn is not likely to pick up water or snow when pointed up in the air at a satellite! In the latter case, it is not even necessary that the plate cover the entire opening to the horn. I have built several feed assemblies where the plate was simply a wide strip across the opening of the horn. In making an inspection of one GOES satellite installation, however, I discovered a nice wasps' nest in the feed horn! I suppose that if a bird decided to use the horn for its spring nesting ritual, it might result in some puzzling signal-level anomalies! It probably is best to seal up the horn—if only to exclude the local wildlife!

This mounting scheme has been used in a number of GOES satellite ground station installations, with antennas ranging from 3 to 10 feet in diameter, with excellent results in all cases. Cylindrical feed horns are certainly simple to construct, and they provide fine results. I think you will find that this mounting system will make them just as easy to use! ■

10% DISCOUNT ON ALL LUNAR PRODUCTS

DURING LUNAR'S 2ND ANNIVERSARY **SALE!**

(July 1 through July 31 at all participating dealers).

LUNAR'S LINEARIZED AMPS

WITH BUILT-IN RECEIVE PRE-AMPS

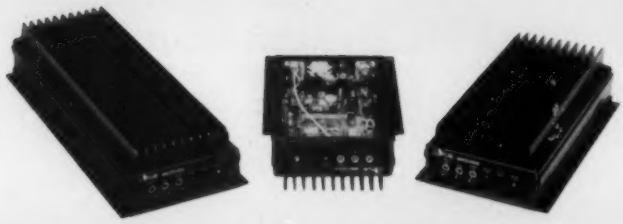

INTRODUCING OUR NEW AMPS MODELS 2M10-150P AND 2M3-150P

- 3 watts in, 150 watts output (3-150P).
- 10 watts in, 150 watts output (2M10-150P).
- Linearized amp for SSB use.
- Preamp 10 dB gain, 2 dB noise figure.
- Other specs similar to existing amps.

BI-LINEAR VHF MODELS

- Low Power Input Yields nom 10 dB gain
- Covers entire Amateur Band w/o Tuning
- Built-in Receive Preamplifier
- Automatic variable delay PR switching
- Exceeds FCC R&O 20777 Requirements of -60 dB
- Preamp & Power Amp Independently Controllable
- Preamp nom 10 dB gain 2 dB Overall NF
- Functionally Designed Package, including mounting lip
- Models available for the 50, 144 and 220 MHz bands
- Type accepted models also available. Models for 432 MHz due in near future.

10% OFF

LUNAR'S RECEIVING PRE-AMPS.

Suitable to the most demanding needs where low noise figure is important. Uses include all types of weak signal work such as EME, Tropo & Ionospheric Scatter, Satellite Communications, Radio Astronomy, Meteor Scatter, etc. Highest quality construction and components.

10% OFF

LUNAR'S PORTABLE ANTENNA TOWER

- Manufactured in our San Diego plant.
- Ideal for ground or roof mounts.
- One man can assemble and erect.
- Extremely rugged.
- Lightweight.
- Modular and portable.
- High stability with proper guying.
- High quality aluminum alloy construction

Power Supplies

- 13.8 VDC output (115 VAC input)
- Continuous Current ratings
- Hammertone Metal case
- 5 year Limited Warranty

MODELS: 6 AMP to 30 AMP
PRICES: $ 49.95 to $ 124.95

½" Hardline

- 50Ω cable with jacket
- Solid copper center conductor
- 500' or 1000' rolls . . . $.45 / ft.

RG-213/U MIL TYPE (MIL-C-17)50Ω coax. 100' Multiples . . . $.23 / ft.
400' roll (via UPS) . . . $.21 / ft.

SASE for info. - Add shipping to check or money order - COD accepted
WA8OGS — Joe K8FO — Roger WB4CTP — Steve

J R S ELECTRONICS

P.O. BOX 1893 CINCINNATI, OHIO 45201

Antenna Tuning Joy Revisited

—remember the Tektronix 190B?

Amplifying K5QY.

Dave Brown W9CGI
RR 5, Box 39
Noblesville IN 46060

In the May, 1978, issue of *73 Magazine* there was an excellent article by Dick Sander K5QY entitled "Make Antenna Tuning A Joy." The article described the modification of a Tektronix 190B constant-amplitude sine wave generator. It is my intention in this follow-up article to add to Dick's comments and ideas and give a few basic details that he left out on the generator itself.

I can testify to the long-term worth of his unit, because I did the same modification 2 years ago. It has proven to be worth at least a hundred times the time spent on it. When I say I did the same modification, like any ham, I have to add an important word—almost. It is additional information and some of the ways I did things as a VHF ham that I believe will be of additional value to readers.

To keep this as short and to the point as possible, I'll first cover the additional specifications you may find of interest. We both started off with the 190B. This unit will run on 105 to 125, or 210 to 250 V ac, with a very slight wiring change similar to Heathkit® equipment (change jumpers, etc.). Further, it runs fine on 50 to 400 Hz. The latter part may not seem important, but I have found that I can use part of an old 6 meter AM mobile power pack unit that was designed to put out around 250 V dc. If you take out or disconnect the dc portion (mine was shot and burned up, anyway), you get, from the ac portion, about 230 V ac and 360 Hz, in my case. The 190B requires about 100 W on 120 V ac, 60 Hz, but the power pack only warms to the touch after about 30 minutes of use. Just a thought for those of you who really must be portable and dc only.

The gear is quite compact and portable compared to some of the older tube-type bench or rack-mounted equipment. It measures only 9-3/4" wide, 13½" high, and 11" deep. Its all-aluminum alloy construction gives it a total weight of only 24 pounds, so it is no surplus boat anchor.

The frequency indication specification for the dial readout is quite good at 2%. This is nice, even if you use the generator only as a generator, but invaluable if you modify it, as Dick and I did, into an antenna bridge.

The output amplitude is continuously variable over a 40-mV-to-10-V peak-to-peak range. Looking into a 50-Ohm load, you have 5 volts peak (times .707 for rms volts). Square that result over a 50-Ohm load, and indeed you have an output of about 250 mW.

This brings out the only point I question in Dick's article. I am a QRP power nut and a VHF/UHF ham. I often have worked another ham 63 miles away with only 16.5 mW on 6 meter CW. That's no great feat, but it all started by accident and has continued using the same setup: my transmitter coupled to a light bulb dummy load in the basement! All I am driving at is, while this may be the handiest device you have ever built for antenna work, remember: You are radiating! Use the minimum on-air time you need for antenna pruning and try to pick non-peak hours in your locale—especially on VHF.

The original ouput meter read the output peak-to-peak volts at that funny-looking connector your unit will come with and is accurate only to ± 10% of full scale. This is really no problem in the modified version, as the absolute value of forward power (voltage) is not important as long as it will drive the swr meter to full scale in the forward mode. Dick mentions changing to a plain voltmeter with a different scale from the original and using a chart supplied by him in the article to calculate vswr. I went one better, I think, and it is by total accident that we were working toward the same general ends at nearly the same time. I found the meter for the Heath VHF wattmeter (HW-2102) to be a great replacement in the $15 range, as it has a direct reading scale for swr. You can ignore the power out-

put scales! I used the bridge basically out of the Heath wattmeter, but have constructed Dick's, too, and either seems to be fine for my VHF work. If you are HF inclined, stay with Dick's resistive version. The Heath meter has a white-on-black scale that is both very attractive and easy to read out in the bright sunlight.

If you contemplate operating at the stock upper limit of 50 MHz, for 6 meter work, by all means use an N-type (50-Ohm) panel-mount female connector to replace the weird little output connector on the front panel of the 190B. Dick used a UHF-type connector here, which is fine at HF frequencies. Unfortunately, due to the huge demand created by the CB market, some UHF connectors are showing up that are UHF in style and name only. Some are OK at CB frequencies and useless at 50 MHz and up. Some would be junk at dc! Why have your worst swr "lump" built right into your test equipment? The extra cost for the N connector is worth it.

If you are *un*fortunate enough to get the attenuator that plugs into that same weird little connector on the panel, do *not* get any ideas about using it for any kind of accurate readings on antennas or any other load with reactance. As you do the band-wandering trick to prune an antenna, as Dick describes, the output impedance of the attenuator wanders all over, and right on the specification sheet it states the following information: Output amplitude is constant ±5% from 30 to 50 MHz, *if* the load capacitance does not exceed 10 pF on the 10-V range. This can be a fixed C, or the antenna reactance! In the 1-V-to-.5-V range, it improves by allowing 50 pF for the same ±5%. Further, it is stated that all changes will be related to, and dependent on, the load capacitance, the length of cables (more on that later), the voltage range in use, and the frequency.

These facts are primarily for those of you who may want to use the generator as a generator with the attenuator. Dick comes right off the generator at the strange little plug you replace with the N fitting, and so did I. Speaking of the attenuator, and to further induce you to go buy a 190B, consider the following.

It's an old flea-market sales trick, but the truth is that you don't want the attenuator unless you intend to outboard the bridge in a box, and swap back and forth between it and the attenuator as the attenuator replacement accessory. So, why let someone run the price up on you by saying he is offering more, or something the unit won't work without? On the other hand, if he doesn't have an attenuator to sell with it, you may succeed in driving down the price by screaming that you must have one!

Fair? It all depends which side of the flea-market table you are standing on at the time, and I have spent 18 years on one side or the other. "*Caveat emptor*," no doubt, has a seller's corollary, too, and rightly so. The only good deal is where both parties feel they have a bargain—so bargain away!

Before we get away from the specifications on the stock 190B, there is one more thing you should know. If you are working with wideband or multiband antennas (log periodics, discones, trap dipoles or verticals, etc.), you should know that there is *no* specification made for the harmonic content of the 190B! I heard of a case where it was typically less than 5%, but that was a new unit in perfect shape.

If you are going to use your unit seriously, then it would pay to at least spot check it at your points of interest. Even a simple check on a shortwave/allband-type receiver will give you a good idea of where the unit is at. For instance, set the generator up on 7 MHz into a 50-Ohm resistor, with enough leads to radiate a little, and drive the generator up to where the S-meter reads S6 to S9 depending on the linearity of your particular receiver's agc system. Tuning the receiver to 14, 21, 28 MHz, etc., should produce readings in the range of S1 or at least as low as the meter reads, with the receiver input terminals shorted by a 50-Ohm resistor (or proper load to match receiver input impedance).

As for the unit you are looking for, I assume you are not rich enough to see Tektronix for a new one (and I doubt if they still even build it), and the used gear catalog prices are still quite high and are aimed at the small business user. This leaves the hamfests/flea markets. I mention this because the unit is easy to open up so you can look at the condition inside. You can plan on cleaning up a little dust, but beware of anything that resembles saltwater corrosion (white, chalky, lumpy), extreme rust, or missing, bent, or battered shields or covers. You want a piece of test equipment, not junk.

I got a real bargain on mine—fully working and intact, for $20, from a man who knew not what he had!

I sprayed over the slightly-scratched case with a forest green by Rust-oleum, which is great for equipment you want never to rust or corrode. Besides, this is a nice match for the Heath meter, which has a black face and green plastic bezel, and it contrasted nicely with the brushed-aluminum panel.

My next modification will obviously be to get higher frequency operation out of this wonder of wonders. Even if I get a sudden interest in the low bands and get my Advanced license, I don't really need the .35- to .75- and .75- to 1.7-MHz bands. The 21- to 50-MHz band on my unit does make it usable on 6 meters, but a bit of coil adjustment may be required on some you might purchase. If you have to juggle, my suggestion is to move the whole band up by 1 MHz and recheck the tracking. Use the allband receiver again to align the tracking by adjusting C on the high end and L on the low end until the dial tracking is as close as possible.

That wraps up my way of attacking the 190B and achieving the joy Dick mentioned in his title. I got my first exposure to this instrument at work and know it is a good one. I kick myself for not seeing the full LC impedance bridge Dick goes on to mention, but you can bet I am working on trying it soon. If anyone has any ideas on putting the higher bands into this gear (at least 2 meters), please write it up or contact me.

I promised to cover more on the capacitance effects, cables, etc., and I left it for last because it really does not pertain only to the 190B. Dick touched briefly on using the modified generator to check old coaxial cable. A lot of bridge, swr, and loading problems can be eliminated or minimized by using the same general techniques. By using a *new* piece of RG-8 foam, commercial grade and quality (not the CB-grade junk), and cutting it to ½ wavelength or even 1 wave-

State of the art
TECHNICAL EXCELLENCE
in RTTY

the FSK-1000 Demodulator

If you demand the finest, no compromise technology, you need the FSK-1000 demodulator. Can't be outcopied because its design, computer grade parts, and modern technology offer landline copy over radio circuits.

Stops QRM with selectable 55 or 100 Hz. filters and two tone limiterless operation

Decision level correction improves selective fading

Uses either 170 volt, 60 Ma. or RS-232 loops

Video operation available. Interfaces microcomputers. We can install your Xitex SCT-100 board inside, too

Continuously adjustable shift from 100 to 1000 Hz.

Write for details. Visa and Master Charge accepted.

Being introduced now at
$397.00
FOB Columbus, Ohio

$449.00 August 1, 1979

IRL
700 Taylor Road
Columbus, Ohio 43230
(614) 864-2464

127

length at the desired and most-used frequency (allow for the velocity factor of the cable), you can make a simple swr transformer. As you know, voltage and current repeat themselves in the cable at ½-wave intervals, and, therefore, so does the swr reading. By first cutting the coax close to the calculated length, but slightly long, and shorting out the far end from the generator, you can determine the exact resonance of the coax just like an antenna. When you have it properly trimmed for the frequency chosen and connectors are on it, hook it up to a good 50-Ohm load like a Heath "Cantenna." Your resonant point should remain the same (matched resistive load) and the swr should be 1:1. If the coax is good and cut to the correct length and the load is really 50-Ohms resistive, any remaining swr is the combined result of bridge unbalance, coax connectors, and coax reflections (bumps or imperfect cable); all, in total, should be very small. Note it on the generator panel for future reference if you can't eliminate it. If the unit won't get 1:1 with a perfect load, it will never get it with the antenna under test. A digital swr meter readout would make the unit perfect, and I am working on that very thing right now.

I can only repeat Dick's closing statement that the 190B in modified form is the "... most practical and economical antenna tuning aid I've used in my antenna experimentation . .," and I hope my article will help make Dick's article and a great piece of gear more useful to all of you who try it. Drop me a note and an SASE if you have any problems with what I've written here. ■

Peoria Superfest 1979

NOW 2 BIG DAYS

SEPT. 15TH AND 16TH. 1979

21st Annual Hamfest
EXPOSITION GARDENS
W. NORTHMOOR RD.
PEORIA, ILL.

Giant free indoor and outdoor **FLEA MARKET**
Camping on the Grounds
Programs for the ladies and kids
Super Smorgasbord Saturday Night

PRIZES INCLUDE:
TR 7 Station
520 S (Sat.)
210 X
13510

ADVANCE TICKETS
$2.00

DOOR TICKETS
$3.00

COMMERCIAL EXIBITORS WRITE OR CALL
FOR INFO ON FREE COMMERCIAL TABLE SPACE

FOR TICKETS AND INFO WRITE:
PEORIA HAMFEST
5808 N. Andover Ct.
Peoria, Ill. 61614
(309) 692-8763

Reader Service—see page 211

10% DISCOUNT ON ALL LUNAR PRODUCTS

DURING LUNAR'S 2ND ANNIVERSARY SALE!

(July 1 through July 31 at all participating dealers).

LUNAR'S 28-432 LOW NOISE FIGURE RECEIVING PREAMPLIFIERS

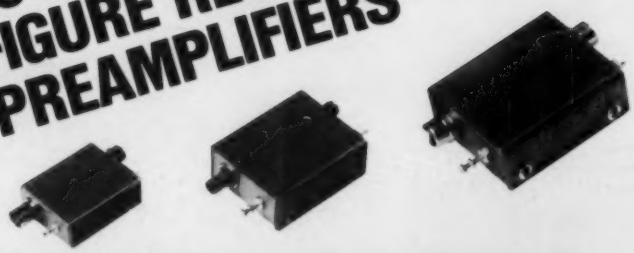

These ultra-performance "ANGLELINEAR" receiving preamplifiers are suitable to the most demanding needs where low noise figure is important. Amateur Radio, Commercial, NASA & Military users have lauded their superior performance. Uses include all types of weak signal work such as EME, Tropo & Ionospheric Scatter, Satellite Communications, Radio Astronomy, Meteor Scatter, etc.

Construction of highest quality: small physical size, gold alodined conductive chem film encloses for maximum shielding. RFI filtering of DC line yields –50 dB at 30 MHz and >–70 dB, 1-10 GHz attenuation. PC Boards are double sided plated holes to ensure maximum performance. All amplifiers are aligned on automatic noise figure measuring equipment, with traceability to standard Hot-Cold noise test system.

MODEL	NOISE FIGURE	GAIN	3 dB BW	1 dB COMP.	Ic @ 12VDC	PRICE
PA 28	1.1 dB	15 dB	1.3 MHz	+1 dBm	10 mA	$35.95
PAI 28	1.5 dB	14 dB	1.3 MHz	+1 dBm	10 mA	$49.95
PA 50	1.3 dB	12 dB	2.5 MHz	+1 dBm	10 mA	$35.95
PAI 50	1.6 dB	11 dB	2.5 MHz	+1 dBm	10 mA	$49.95
PA 144	1.5 dB	11 dB	2.5 MHz	+1 dBm	10 mA	$35.95
PAI 144	1.9 dB	10 dB	2.5 MHz	+1 dBm	10 mA	$49.95
PA 220	2.0 dB	11 dB	6 MHz	+1 dBm	10 mA	$35.95
PAI 220	2.5 dB	10 dB	6 MHz	+1 dBm	10 mA	$49.95
PA 432-2	1.6 dB	14 dB	150 MHz	–20 dBm	6 mA	$41.95
PAF 432-2	3.0 dB	13 dB	50 MHz	–20 dBm	6 mA	$49.95
PAE 432- 5	1.0 dB	16 dB	180 MHz	–20 dBm	4 mA	$64.95

10% OFF

LUNAR'S PORTABLE ANTENNA TOWER

- Manufactured in our San Diego plant.
- Ideal for ground or roof mounts.
- One man can assemble and erect.
- Extremely rugged.
- Lightweight.
- Modular and portable.
- High stability with proper guying.
- High quality aluminum alloy construction.

LUNAR'S LINEARIZED POWER AMPS

10% OFF

- Covers entire Amateur Band w/o Tuning
- Built-in Receive Preamplifier
- Automatic variable TR switching
- Exceeds FCC R&O 20777 Requirements of –60 dB
- Preamp & Power Amp Independently Controllable
- Preamp nom 10 dB gain, 2 dB Overall NF
- Functionally Designed Package includes mounting lip

CALL FOR FAST QUOTE! SPECIAL ORDERS WELCOME

MADISON

ELECTRONICS SUPPLY, INC.

M35

1508-G McKINNEY • HOUSTON, TEXAS 77002

713 / 658-0268

MASTER CHARGE — VISA

Reader Service—see page 211

Modern Solid-State Equipment Design: A Better Way

—sorry, tube fans

L. B. Cebik W4RNL
5105 Holston Hills Road
Knoxville TN 37914

Most books and articles on solid-state design for rf stress the parallels between transistor/FET circuitry and tube circuitry. These parallels are accurate enough as far as they go, but they also are misleading. To the average reader, they imply that equipment design using transistors or FETs should parallel tube equipment. In many ways, especially for the amateur, this inference is wrong and accounts often for why we never get some piece of equipment to work.

In this article, I want to compare old-style tube techniques with some tried and proven principles for transistors. These principles are not for the engineer or the commercial manufacturer; they are for the home builder. They call for some changes in the way we think about building up a fairly complex piece of rf equipment. In this review of the similarities and differences between vacuum tubes and transistors, all of the ideas I give will be commonplace. But when set next to each other, they suggest new ways of doing things for the ham constructor.

Changing an old way of thinking is probably the hardest thing for any of us to do, but if you think through these ideas, and then take a look at some of the projects that have appealed to you (transmitters, vfos, receivers, and the like), you will be in a position to make the change. No longer need you believe that you can never get a bunch of transistors to do what the original author got them to do. By some simple redesign work, you can have confidence that you can do it, too—and maybe do it better.

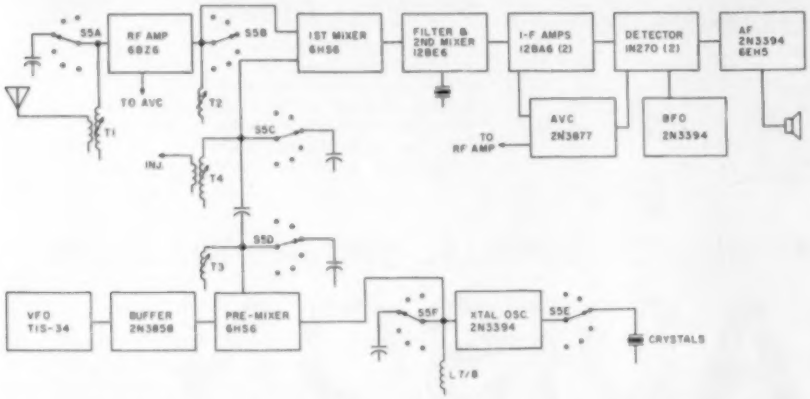

Fig. 1. Simplified block diagram of a tube-type receiver, adapted from the R-4B and drawn to show the methods of switching rf-tuned circuits for each stage prior to the mixer, i-f, and af stages. Note that a 6-pole, 6-position switch is required to accomplish band changes. Although the method of mixing frequencies to reach the i-f differs among manufacturers, the relationship of band changing to the various stages is common to almost all of them. In this late model tube-type receiver, some solid-state devices have been introduced. Tuned circuits have not been terminated because of complexities in the full schematic of this Drake receiver.

Designing with Vacuum Tubes

The design of rf equipment using vacuum tubes has changed little in the past forty years. Perhaps the major change—outside of improved tube construction and improved individual circuits—has been the introduction into amateur gear of the heterodyne vfo system of frequency control. The 5- to 5.5-MHz vfo heterodyned to the ham band of choice has eliminated most of the prob-

lems inherent in the bandswitching vfo or the vfo multiplied to frequency. The instability of vfos required to cover a ten-to-one frequency spread, as well as instabilities introduced by switching tuned circuits, held back single sideband and serious communication on VHF frequencies for many years. Likewise, when we used frequency multipliers, we also multiplied any flaws in the vfo.

Other than this, equipment design has changed little. To illustrate this fact, let us look at Fig. 1, a simplified diagram of a straightforward receiver. In the diagram, I have shown most of the switching circuits, but omitted other circuit details. In both amateur gear and commercially-made gear, this basic system design has been standard. With vacuum tubes, there are good reasons for this standardization.

Notice that most of the switching involves the replacement of one frequency-determining circuit for another. To switch bands requires the exchange of several tuned circuits, as well as a change of crystals. Here are some of the basic reasons for working out the system design in this way:

1. The system permits the least number of tubes, which is desirable because, (a) tubes are large—they take up space; and (b) tubes are heat generators, and this system minimizes heat.

2. Tubes, being high-impedance devices (high especially when compared to the frequency-determining circuits associated with them), usually require little attention to perfect matching, and are, therefore, reliable for a given biasing arrangement over a large frequency spread.

3. Tubes are large compared with tuned circuits and switches (especially at low power levels), thus making it more economical of space and cost to switch tuned circuits.

4. Tubes are inherently expensive; for receivers, five tubes can cost five times as much as one five-position switch section.

5. Tubes, as they come into the hands of either the commercial manufacturer or the building amateur, are reliably similar, varying well within a 20 percent range in characteristics within types.

6. Most modern tubes have input and output capacitances which are small enough to present no design problems in the 3- to 30-MHz range (unlike the old '24 and '27, so popular around 1930).

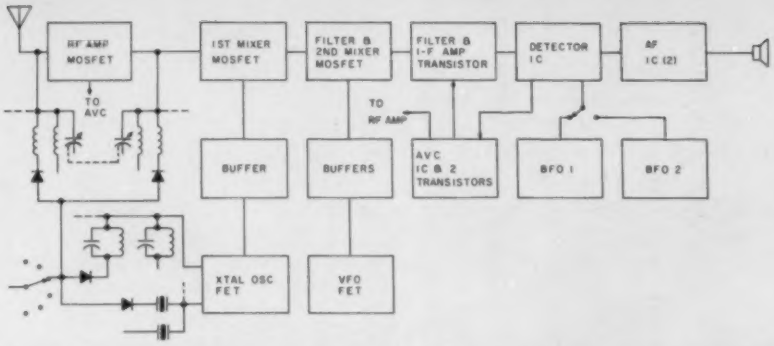

Fig. 2. Simplified block diagram of a recent commercially-manufactured solid-state ham-band receiver. Note the similarities to Figs. 1 and 3: All use single devices in the critical rf circuits and switch-tuned circuits. Problems of lead length and switch expense are solved in this design by the use of a diode switching system. The switch handles dc, and all rf remains on the printed circuit board. This, plus the use of a high-impedance device, the MOSFET, minimizes some problems of multiband operation, but not all. Compare this to Fig. 4 in which the rf circuits are optimized for one band. This diagram, with modifications for simplicity, is based on the Heath HR-1680. Both the HR-1680 and the Drake R-4B of Fig. 1 are fine receivers in their respective price classes, but their design philosophies may not be best for the ham builder.

Fig. 2 shows a simplified diagram of a relatively recent piece of ham gear. The diagram has been drawn to bring out the similarities between tube and transistorized gear commercially available. Note that the switching arrangement is not materially different from that of Fig. 1. Single solid-state devices are used at each stage, and the frequency-determining circuits are switched with the traditional bandswitching arrangement.

Fig. 3 shows a simplified diagram of a piece of equipment taken from a recent ham publication. Notice that it, too, uses the very same system of switching and design.

Unless one is an engineer or has access to select components, circuit design of this order is difficult to replicate. Among the reasons for the difficulties we face in making a complex circuit work just as some article claims are these:

1. Transistors may vary greatly in characteristics from a design center. This problem is aggravated by the fact that hams generally have access to culls, hobbyist-grade devices, or surplus, any of which may vary by an even greater extent. For this reason, the amateur designer must do his own selection from among the batches of 20-cent transistors he has on hand, and he must be willing to rework bias and drive circuits to make the device work as it did in the original. To expect a complex group of transistors to perform reliably over a wide frequency range under these conditions often strains the imagination and the experimenter's patience.

2. Other materials of the system of circuits may not be available, and the amateur designer substitutes what he has on hand. He may use surplus or junk box coil forms or toroids of dubious ferrite or iron content. What this may do to circuit Q is anyone's guess. Capacitor quality is another overlooked problem, one aggravated by the uncertain history of the short lead parts in the junk box.

3. Those who attempt to reproduce equipment shown in articles and books often lack the test equipment necessary to perform the right measurements so as to find out what in a circuit may not be working correctly. Among our common building practices are these: tapping coils just as specified in the article, rather than determining the actual impedance to be matched; assuming that the bias circuitry of a transistor provides the correct parameters, rather than measuring actual currents drawn; and assuming that proper

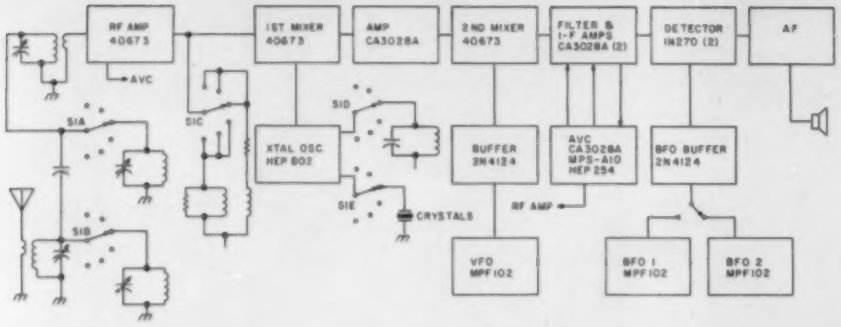

Fig. 3. Amateur receiver (simplified block diagram), adapted from the 1974 Handbook. *This particular unit was originally built in two pieces: a basic receiver from the CA3028A amp through the af board, and a converter section for all the HF bands. Note the attempt to use high-impedance devices—MOSFETs and JFETs—to minimize problems with switching-tuned circuits. Even so, a long five-section ceramic switch is required. Among the positive design features of this receiver are the provision of avc voltage to the first rf stage, upward conversion to minimize birdies, and switched bfos. Front end compromises would have been further minimized through the use of separate converters for each band.*

drive levels are present from stage to stage, rather than measuring rf voltage.

Add up all these conditions and practices, plus perhaps a dozen others peculiar to certain kinds of builders, and it is little wonder that the amateur who tries to build a receiver designed like one in Figs. 2 and 3 has little luck making it work.

Now, it is not reasonable to believe that every ham builder will spend the money it takes to obtain select components or to set up complete test facilities. Nor should we expect that in the near future, circuit reliability will increase to make every wide-range rf system easily repeated. Does this doom the amateur builder to failure? No, not if we change some parts of our design philosophy.

Some Useful Things to Remember about Transistors

Transistors and FETs resemble tubes in these two main ways: First, they may be operated Class A, AB, B, or C (plus some other ways to which experimenters have given new class names); second, any element may serve as the common element, so that we have corresponding common cathode/emitter/source amplifiers, common grid/base/gate amplifiers, and common plate/collector/drain (cathode/emitter/source follower) amplifiers. Knowing this much is important in determining the details of individual circuits. However, transistors also have significant differences from tubes, differences which are very important in the development of a design philosophy for complex pieces of equipment. As we did with vacuum tubes, let us set them out together:

1. Transistors and FETs are very small and take up little space on a chassis or circuit board. About fifty of them might fill the space taken up by one miniature tube and its socket. *Principle: Unless we are interested in the greatest degree of microminiaturization, it really does not matter how many transistors we use, so long as each is used well.*

2. Transistors and FETs create little heat at low powers, i.e., under a Watt. *Principle: No matter how many low power stages we use, heat will probably not be a factor in either the stable operation of a circuit or in the lifetime of the circuit.*

3. While MOSFETs are very high input impedance devices, transistors especially, and to some extent JFETs, will have lower impedances which require attention to matching. There are, of course, many more wide-range circuits for FETs than for transistors, which require little attention to matching. *Principle: For transistors, at least, matching to the individual device is still best.*

4. Transistors, especially in the hobbyist class available to most ham building, will vary in characteristics and require attention to operating levels. *Principle: Bias levels for transistors may need to be fiddled with, and may not work consistently across wide frequency excursions.*

5. Transistors and most FETs are cheap; to buy them five for a dollar is not uncommon, and even specified types like the popular 40673 or MPF 102 cost under a dollar. *Principle: The number of transistors and FETs in low power stages is not likely to make a ham project too costly to build.*

7. Compared to other components, such as switches, coils, and capacitors, transistors and FETs are small and inexpensive, and their associated biasing resistors may cost a nickel or less apiece. *Principle: It is better to substitute small, inexpensive components for big expensive ones wherever circuit reliability can be maintained or improved.*

From these points of comparison and their associated principles, you can see a design philosophy beginning to emerge. Since it is often (though not always) necessary to tweak a circuit up for an individual frequency band, and since the necessary components are cheap (and for other reasons which will become obvious in a few more paragraphs), it is better for the ham to build rf systems of circuits for one band at a time, and then to switch them in and out as needed, rather than to use the tried and true (for tubes but not necessarily for transistors) method of switching frequency-determining components. Not only can this method assure better circuit reliability, but it can also simplify the process of building, provide operational equipment before the entire unit is functional, and save money for the builder.

Some Examples

Let us look at a couple of examples of this design philosophy and see how they work out in practice. First, go back to the receivers of Figs. 1, 2, and 3. Fig. 4 shows how the receiver can be designed using the principles above.

The revised receiver employs converters for each band except 80 meters. This is a scheme used extensively and, with the exception of separate converters, goes as far back as the Drake 2 series of tube-type receivers. The i-f frequency is a matter of choice in accord with the design objectives, and can be a function of up or down conversion. The

main design features to note are these:

1. No device operates at more than one frequency or band, thus allowing for optimization of all parameters. Among these are gain, bandwidth, oscillator-output level, stability, and avc action. For each converter, bias values, coupling capacitors, LC values, and the avc voltage-divider network can be juggled either to provide equal gain for all bands or to emphasize or de-emphasize some bands. (Maximum gain for 80 and 40 meters usually means more noise than signal.) The remainder of the circuit is standard, in the sense that almost all receivers operate i-f and detector stages at one frequency.

2. Note the switching system. Converters which are not in use are not powered, thus eliminating some potential birdies. Switching, however, requires only a three-pole switch, one each for antenna input, converter output, and Vcc. Moreover, by using shielded signal leads (and shielding the power lead is not a bad idea) and minimal inter-section shielding of the switch, the entire switching network can be made very compact. In some receivers using similar schemes, I have seen retained the classic long switch, running from front to rear on the chassis. It is quite unnecessary.

3. The avc system employs resistor-divider sections to limit or expand voltage excursions so that the avc action is controlled for each band. Many receivers of this design omit avc to the converters, relying upon the basic receiver sections to do the job. Given the gain of the converter sections, overloading can become a problem. Tailoring the avc action to each converter solves the problem. Avc voltage can be switched or not, depending on circuit design; it should be switched out unless the converter, when not in use, shows an open circuit to the avc voltage. Otherwise, it will load the avc system. A compact fourth pole on the bandswitch solves this potential problem.

4. Unlike many handbook designs, there is no need to make each converter identical. Single-ended rf stages operate well on all HF frequencies with MOSFET devices, but experimentation with a pair of grounded grid amplifiers in cascade, or with cascode circuits, is worthwhile. Moreover, one can try push-pull circuits, since the usual mechanical problems of band changing with balanced LC circuits are not present. I am often amazed at the lack of experimental ingenuity which appears in rf designs in the ham journals, despite the large number of possible circuits available for use, and the variety of devices which just might make one or more of them a good performer.

5. The main limitation on this design philosophy is that it does not produce the most compact equipment possible. For subminiature gear, perhaps another method of design should be used, but for home station use, miniaturization is not the ideal situation. The two main physical considerations should be experimental flexibility and accessi-

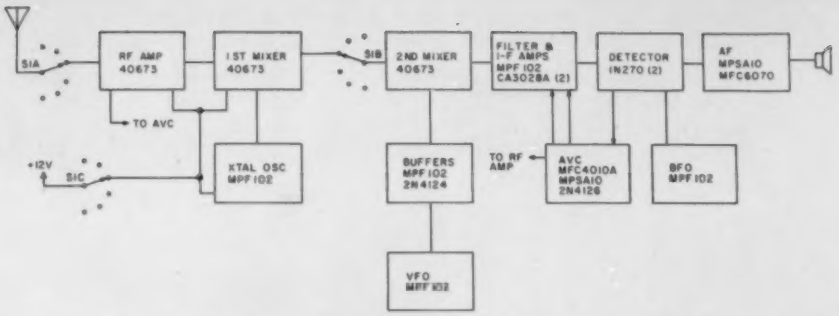

Fig. 4. Block diagram of a receiver most closely meeting the design principles enumerated in the article. In general, this is part of WA1JZC's receiver in the 1978 Handbook, *with some alterations. Unlike the original, avc is shown for the rf amplifier. My personal choice calls for different circuitry, but this design is readily available for study by the prospective home builder. Note the simplified switching of rf circuitry. The originator in fact optimized converter design for each band using JFETs in a grounded-gate circuit (except on 80, where he omits the rf amplifier) and a 2N4124 crystal oscillator. His commentary is worth repeating: "Separate converters were incorporated to eliminate the need for complicated bandswitching, and also to permit optimization of circuit values for each band of interest. The system used in this receiver calls for switching of only dc and 50-Ohm circuitry. Low-impedance switching eliminates problems caused by long switch leads. Switching at high impedance points, which is the usual technique in multiband receivers, can impair the quality of the tuned circuits and makes isolation of critical circuits more difficult." (See pp. 280-281.) Although some of these problems can be overcome by the diode-switching techniques of Fig. 2, optimizing performance and being able to assure full frequency range repeatability with home construction techniques require adoption of something similar to the design philosophy of this receiver.*

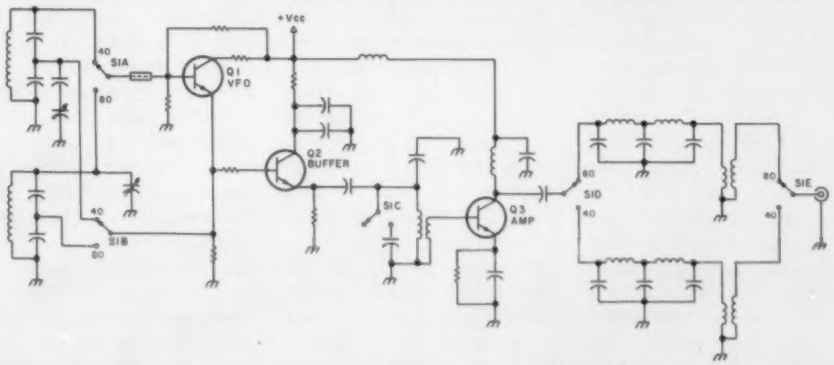

Fig. 5. Simplified schematic diagram of a vfo capable of driving tube-type transmitters. Note that LC combinations are switched by S1A and S1B, while the input to Q3 is tuned by switching a capacitor across a fixed coil with S1C. From the ARRL Handbook.

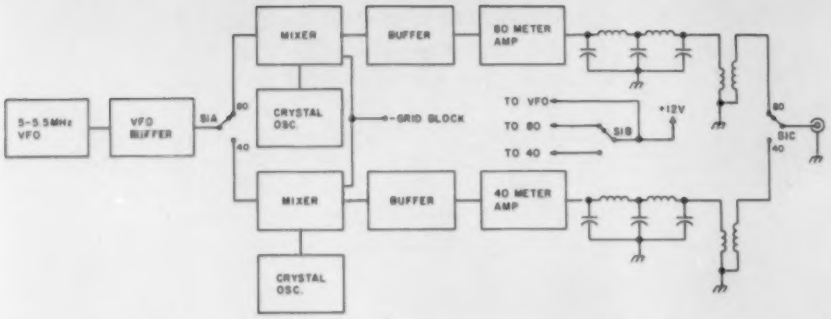

Fig. 6. Block diagram of mixing vfo for tube-type transmitters. Individual circuits are similar to those of Fig. 5. Buffers are untuned. Mixers are FETs with about −4 volts grid/gate block. Note especially the simplification of switching, which allows a single wafer to be used rather than the 8" switch used in the original of Fig. 5. Notice also that either mixer-amplifier section may be removed for adjustment or experimentation without disabling the vfo completely. Total cost of the "extra" mixer-oscillator-buffer-amplifier devices was under $2.00.

bility, and operating ease. The mechanical size of easily read digital- or mechanical-readout systems is still the main factor limiting miniaturization. Within the size limits of most convenient readouts for main station use, there is plenty of room for the boards for each converter. In fact, many of the imported transceivers, when mobile use is not intended by the operator, appear to be excessively compact both for operating ease and for maintenance convenience. Heat is a constant worry with them.

The amateur designer, therefore, might well take a page from the notebooks of home computer designs. Within whatever case one uses, develop a main frame with plug-in units at every stage, along with space for future, more complex circuits. With careful attention to routing rf paths, you can use plug-in circuit boards or plug-in perfboards. Shielding between most boards is a must. The advantage of this system is that replacement circuits can be developed independently and tried in the receiver, without losing the receiver from service for long and without mechanical alteration to the basic unit. This not only ensures an operative receiver at all times, but also eliminates future mechanical costs for new versions. Your equipment will be as up to date as your latest experiments, however old the case may get.

These advantages accrue not just to receiver design, but also to transmitter stages as well. Fig. 5 shows an 80/40 meter vfo that appeared in the *ARRL Handbook* for several years. Notice that the tuned circuits in the vfo are switched. Note, too, that the input circuit to the power amplifier is changed from 40 to 80 meters by the addition of a capacitor. Neither of these schemes is optimal, and their correction is hinted at by the design itself. The output filters are switched in their entirety. Why not the entire power train?

Fig. 6 shows a simplified diagram of the revised system built for a ten-Watt standby rig using tubes. The 5- to 5.5-MHz oscillator runs all the time. Separate mixer, buffer, and amplifier stages give 80 and 40 meter output. They are built on separate boards and require only a three-pole switch, one each for vfo input, amplifier output, and power. If one desires separate output jacks for each band, one pole of the bandswitch can be eliminated. Tuned circuit and bias values have been optimized for each band. Since the transmitter with which the vfo is used supplies not only the twelve volts, but also blocked grid-keying voltage, the mixers are keyed. Because of the transmitter design, more output was required on 80 than 40, a problem easily solved using this scheme. If I ever use the vfo with another rig, equalizing the vfo output will be no problem either. Despite the fact that the vfo uses an old ARC-5 tuning capacitor, the entire unit fits in a 4 x 5 x 6 case. Obviously, little is lost to compactness by the use of the design principles enumerated here.

The purpose of this article is not to get you to build what I have built. Instead, it is designed to encourage you to build what you want, by showing that there are some basic principles which take the scariness out of complex rf equipment that appears in the ham journals. The basic idea to get rid of is that you have to make a tricky device like a transistor operate all the way from 80 or 160 up to ten meters. Doing your work one band at a time and building your equipment one section at a time not only makes building for the amateur nonengineer possible, but also makes it fun. What you learn from trying new bias values and schemes, or from trying different LC values, will soon give you confidence that you can make almost anything work.

building, and that is to give you my personal prejudices about what test equipment the ham builder ought to have. A VTVM with regular and rf probes is essential—preferably one that has a range of about a volt and a half for reading partial volts. My trusty Heathkit has stood me in good stead for many years. A grid-dip meter for testing LC circuits or for a signal source is also very useful. A VOM for current readings is needed, but it need not be an expensive model. Beyond that, the rest is up to you. Oscilloscopes, frequency counters, impedance bridges, and the like are all useful, but with them I notice that I do not have to clean off my fingerprints nearly as often as I do with other pieces of test gear. Finally, station operating meters for swr, power output, and dummy loads are useful only for some projects. An all-wave HF receiver, however inexpensive and inexact in dial reading, can help a great deal, especially in testing things like heterodyne oscillators. For me, however, the big three are the VTVM (and rf probe), the gdo, and the VOM.

The principles I have given can be expressed in many ways. I welcome additions to the list, and new ideas to improve my own techniques. Hopefully, the ones given here are enough to encourage you to make the move from building station accessories to building your entire station. Then you can use that commercial rig as your standby. ■

10% DISCOUNT ON ALL LUNAR PRODUCTS

DURING LUNAR'S 2ND ANNIVERSARY **SALE!**

(July 1 through July 31 at all participating dealers).

LUNAR'S LINEARIZED AMPS

WITH BUILT-IN RECEIVE PRE-AMPS

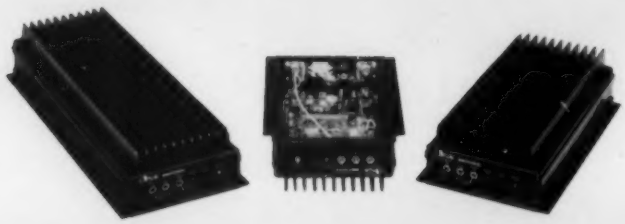

INTRODUCING OUR NEW AMPS MODELS 2M10-150P AND 2M3-150P

- 3 watts in, 150 watts output (3-150P).
- 10 watts in, 150 watts output (2M10-150P).
- Linearized amp for SSB use.
- Preamp 10 dB gain, 2 dB noise figure.
- Other specs similar to existing amps.

BI-LINEAR VHF MODELS

- Low Power Input Yields nom 10 dB gain
- Covers entire Amateur Band w/o Tuning
- Built-in Receive Preamplifier
- Automatic variable delay PR switching
- Exceeds FCC R&O 20777 Requirements of –60 dB
- Preamp & Power Amp independently Controllable
- Preamp nom 10 dB gain 2 dB Overall NF
- Functionally Designed Package, including mounting lip
- Models available for the 50, 144 and 220 MHz bands
- Type accepted models also available. Models for 432 MHz due in near future.

10% OFF

LUNAR'S RECEIVING PRE-AMPS.

Suitable to the most demanding needs where low noise figure is important. Uses include all types of weak signal work such as EME, Tropo & Ionospheric Scatter, Satellite Communications, Radio Astronomy, Meteor Scatter, etc. Highest quality construction and components.

10% OFF

LUNAR'S PORTABLE ANTENNA TOWER

- Manufactured in our San Diego plant.
- Ideal for ground or roof mounts.
- One man can assemble and erect.
- Extremely rugged.
- Lightweight.
- Modular and portable.
- High stability with proper guying.
- High quality aluminum alloy construction

UPS SHIPPING PREPAID (EXCEPT TOWERS)

SERVING THE SOUTHEASTERN STATES

✔M101 **MAURY'S VHF-UHF**

M. W. "Maury" McMahan (K4GMJ)

253 Providence Square

Greenville, South Carolina 29615

Phone: (803) 288-4671

Daily & Saturdays Until 10:00 P. M.

Specializing in VHF-UHF 50-144-220-432-1296 MHz Amateur Equipment

G. E. Smith W4AEO
1816 Brevard Place
Camden SC 29020

Shortened Antennas for 75 and 80

— designs which fit your QTH

Slopers exposed.

During 1975 and 1976, I tested various 75 meter antennas with several ZLs and VKs. This band is generally open from there to the United States during the early mornings (local US time) around 1000 to 1200Z. I have been trying to determine if there is any particular 75m antenna best suited for this 7- to 8-multihop 8000-mile-plus path. There are usually a number of US hams working the ZLs and VKs on SSB between 3775 and 3850 kHz. The ZLs are permitted to work this portion of the band. As the VKs' highest frequency end is 3700, they generally transmit SSB between 3680 to 3695; therefore, split operation must be used with them.

75m antennas tested here during 1975-76 were: several dipoles at various heights (40 to 70 feet); three delta loops; a two-λ horizontal quad at 70 feet; two ½-λs in phase, collinear at 70 ft. (broadside to NZ); several ¼- and ½-λ verticals; a 3-element yagi at 60 feet; and three horizontal monoband dipole log periodics (DLP), one 3-element, one 4-element, and one 5-element, all at 60 feet.

At times, I have had as many as 3 or 4 75m antennas up at the same time for making direct comparisons between the various types. During the tests, the best reports from the ZLs and VKs have been with the log periodics and the yagi. As all of my antennas are supported by pine trees, the maximum height above ground for the horizontal antennas is limited to 60 to 70 ft., or approximately only ¼ λ above ground at 3.8 MHz. These are, of course, fixed-wire beams.

At times, the yagi or the log periodic would be reported as much as 10 dB better than some of the other types being tested. The yagi and the LPs were all beamed west or SW.

The log periodics and

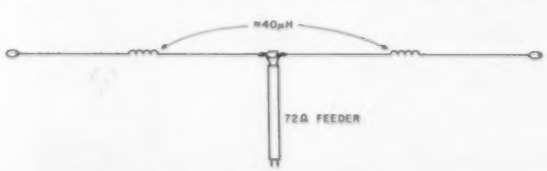

Fig. 1(a). Coil-loaded shortened ½-λ dipole.

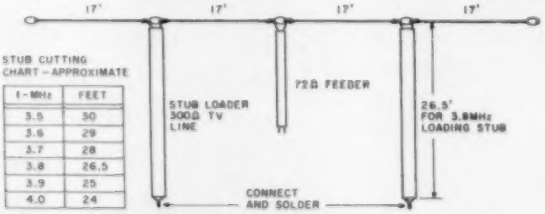

f - MHz	FEET
3.5	30
3.6	29
3.7	28
3.8	26.5
3.9	25
4.0	24

Fig. 1(b). Stub-loaded shortened ½-λ dipole.

the yagi, although producing the best reports from "Down Under," are quite large, requiring a width of approximately 150 feet and a boom length of at least 100 feet. The general design of the 5-element monoband log periodic is given in reference 1, Fig. 6, reference 2, Fig. 2, and reference 3, Fig. 4. The dimensions for the frequency range 3.8-4.0 MHz are given by reference 2, Table 1. This LP was supported at about 60 feet by 8 pines.

As an antenna of this size is generally impractical for the average ham on a city lot, during 1977 I tested 75m antennas requiring less space but still giving some gain and more directivity than the usual 75 or 80m dipole or inverted vee when limited to a height of only sixty to seventy feet. These are described in the following.

Shortened Dipole Slopers

During the tests with the ZLs and VKs, it was noted that W2GO, one of the more consistent early morning DXers, uses a single shortened (66-foot) dipole as a sloper to the west with very good reports.

Shortened dipoles using off-center loading coils were well covered by Jerry Hall K1PLP (*QST*, Sept., 1975, page 28). By use of two 40-μH loading coils, the 75m dipole was shortened to 66 feet. This is the type used by W2GO for his shortened 75m centerfed ½-λ sloper, which requires only a single 60- to 70-foot pole, tower, or tree support. It is sufficiently compact to be used on a small lot. This was the type which I selected as being the most simple and compact antenna requiring minimum space.

As I did not have a pair of loading coils as specified in the *QST* article and did not wish to take time to wind them, I used instead two lengths of 300-Ω TV line as loading stubs for the shortened dipole. See Fig. 1(b). As a start, I used 30-foot stubs which resonated the shortened 68-foot dipole at approximately 3.5 MHz. Resonance can be determined by a GDO or by running an swr.

Next, the stubs were each pruned about 6 inches and the resonance was again checked, and then another 6 inches were removed and the frequency checked. This procedure was continued until the dipole resonated at 3.8 MHz. A total of 3.5 feet had been removed from each stub, making them each 26.5 feet in length. These loaded the dipole to the desired center frequency, 3.8 MHz. An swr was then run to determine the usable bandwidth of the shortened stub-loaded dipole, illustrated in Table 1. It will be noted that the bandwidth is quite narrow but usable ±100 kHz covering the DX portion of the 80m phone band.

This shortened or loaded dipole was then suspended as a sloper (Fig. 2) from the top of a 70-foot tree and sloped SW for tests with the ZLs. Although the overall length of the sloper was only 68 feet, it worked surprisingly well, considering its simplicity and ease of construction. It was fed with 72-Ω twinlead connected via a 1:1 balun to a buried coax to the shack.

For a dipole-type sloper to be effective for DX, or rather to have a fairly low angle of radiation, it should form an angle of at least 60° to ground. 70° to 80° would probably be better. It, no doubt, acts as a ½-λ vertical or semivertical. Being centerfed, the necessity of an elaborate ground radial system as required with a ¼-, ½-, or basefed vertical is probably not as important. None was used during

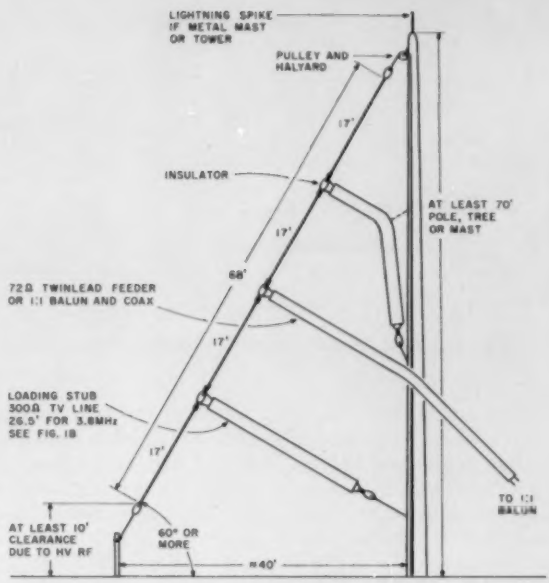

Fig. 2. Shortened ½-λ dipole sloper, stub-loaded.

these tests. If the slope angle is less than 60°, say 45°, it will probably have more horizontal polarization and higher angle radiation and would become more like a low horizontal dipole with the major radiation lobe at 90° or straight up. In this configuration, it would no doubt show an improvement with nearby stations up to a few hundred miles, but DX operation would suffer.

A second sloper using an old Hy-Gain 40/75 trap dipole (overall length about 110 feet) also was tried, suspended from a 100-foot tree and aimed SW. This sloper seemed slightly better than the original 68-foot stub-loaded sloper. This was no doubt due to greater overall radiating length, more effective height, and an angle of about 70°. It had the advantage of also being usable on 40, though no extensive tests have been made with it on this band.

Phased Slopers—Endfire Array

As above slopers gave fair results considering their simplicity and ease of construction, it was decided to try a 3-element phased sloper (all elements driven) in a log periodic, endfire sloper array configuration. This was constructed by using a nylon line catenary stretched between two high pines separated by about 200 feet and oriented to give a beam at about 225°. The higher, rear tree was about 75 feet in height and the forward tree was about 60 feet high.

As the use of stub-loaders was not desirable due to complications in suspending the stubs so that they would come off at about 90° with respect to the sloper elements, it was decided to use end loading instead of stubs. This was accomplished by folding about 25% of each element end to the rear and securing them to the top and bottom catenaries, as illustrated in Fig. 3(a).

As it was desired to operate this beam centered on 3800 kHz, it was adjusted so that the longest rear element, #1, resonated at 3.7 MHz, #2 at 3.8 MHz, and the short forward element, #3, at 3.9 MHz. The easiest

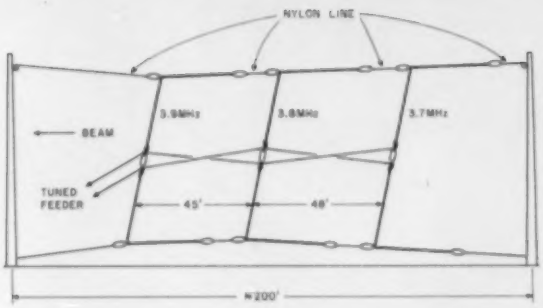

Fig. 3(a). Log periodic phased sloper, end-loaded.

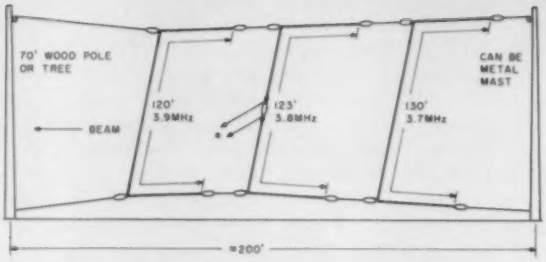

Fig. 3(b). Yagi phased sloper, end-loaded.

way to adjust this is to cut each element slightly longer than its required frequency. Then put temporary jumpers across the center insulators (feedpoints). Secure the ends of each element (folded back portion) to the catenaries and then raise the array to its normal suspended height. At this point, the 2-wire center feeder is not used.

Next, check resonance of each of the three elements separately by holding the GDO near the horizontal section at the bottom of the catenary, and pruning the ends as necessary to the three frequencies, 3.7, 3.8, and 3.9 MHz, as mentioned above. This must be done with the array suspended at its final location due to variations of resonance depending on the height of the three elements above ground. These three frequencies were selected so that the completed antenna would be centered on approximately 3800 kHz, and also to allow the array to operate as a log periodic.

Once the three elements are tuned, the array can be lowered, the jumpers across the three center insulators removed, and the 2-wire open feeder or phasing line connected as shown in Fig. 3(a). Note the transposition required for the array to perform as a log periodic or an endfire array. Each element must be out of phase with its neighbor, as required of any log periodic. The construction of the feedline is presented by the articles in references 1, 2, 3, 4, and 6, covering log periodic wire beam construction, and will not be repeated here.

A large array of this type for 75, even though using only 3 elements, must be assembled and tuned on site for its particular surroundings and height above ground. Table 2 is overall swr covering 3.5 to 4.0 MHz, after adding the center feeder to the array. It then centered on about 3.7. However, as the swr at 3.8 was only 1.25:1, no further changes were made since the beam was usable between 3.6 to 3.9 MHz.

Although this phased-sloper log periodic was only tested for about one week, it appeared to have gain and directivity as hoped. During one of the tests on 3808 kHz, Bob Tanner ZL2BT advised that it was about the same as the 3-element horizontal yagi at 60 feet which I was using at the same time.

The main advantage of the above phased sloper is that only two trees or masts are required, as compared to 6 or 8 necessary to support the 3-element yagi or an equivalent 3- to 5-element DLP. Further, the phased array, being primarily vertically polarized, should have a lower angle of radiation. Since the radiating elements are semivertical dipoles (centerfed), a ground screen or counterpoise was not used during the tests. Although the length requires about 200 feet of mast spacing, its width is less than 1 foot, compared with the 150-foot width of a 75m dipole log periodic or yagi.

For those who prefer yagis, the same 3-element sloper could, no doubt, be arranged as a 3-element yagi by deleting the open wire center feeder, deleting the center insulators from elements #1 and #3, and feeding the center of #2 element directly with 72-Ω twinlead or, better still, with an open tuned line. See Fig. 3(b).

The array would then become a yagi with #2 the driven element, #1 a parasitic reflector, and #3 a parasitic director. The yagi sloper array would, no doubt, have a more narrow bandwidth (possibly no more than ±50 kHz) than the bandwidth of the log periodic configuration. I have not tested the sloper array as a yagi, but, on previous tests comparing a 3-element horizontal monoband DLP with an equivalent 3-element yagi, a greater bandwidth was given by the log periodic.

Test Results

Shortened loaded slopers—

From the tests made with ZLs and VKs on these 75m antennas, and also from comparing notes with the previous tests with ZL1BKD during 1975-76, it appeared that the single shortened loaded-dipole sloper was equal to the larger delta loops, 2-λ horizontal quad, verticals, etc., which were tested then versus the large 75m yagi and/or log periodic (horizontal dipole-type) beams. The latter did average out about 10 dB better than the more simple antennas, including the slopers.

Considering the simplicity and ease of building the loaded sloper, and the fact that only one support is required as against 6 to 8 to support my large beams, it is believed the loaded sloper is the least expensive 75m DX antenna and about the only one suited for a city lot except, possibly, a single ¼- or ½-λ vertical, which can be quite expensive if a 60- or 120-foot tower or mast is used and the required 60 feet or more of ground radial system buried. The latter may also be a problem on a city lot.

During the tests, the large beams would show as much as 15-dB increase over some of the more simple antennas, but these differences would vary from day to day. The 10-dB gain over the more simple antennas was more the average.

Comparing the simple sloper with the delta loops, the type with apex topside requires only one high support but needs about 120 feet of space for the lower horizontal section. The type with the horizontal section up and apex down requires two supports spaced at about 120 feet.

Comparing it with the

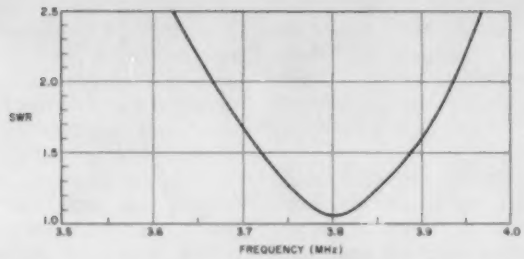

Table 1. Shortened dipole sloper.

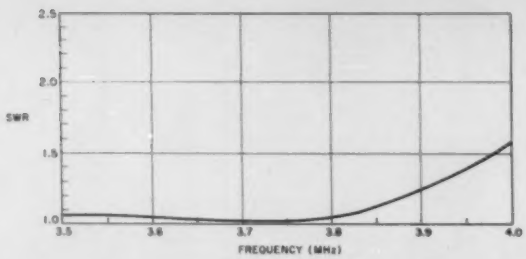

Table 2. Log periodic as in Fig. 3(a).

horizontal 2-λ quad, the latter requires four supports arranged in a square with about 130-foot separation, hardly suited for a city lot. The delta loops and quads also require more wire. 75m phased verticals are also impractical in a small space.

Therefore, the simple loaded-dipole sloper is recommended as a good all-around and inexpensive DX antenna if one does not have an open space of about 150 x 150 feet for a large beam to provide gain. Further, the latter, requiring 6 to 8 supports, also requires considerably more wire, insulators, etc., and a great deal more effort and labor!

For anyone not interested in 75m DX, a shortened or loaded sloper used as a high-angle radiator, either as a sloper at about 45° or as a low dipole at about ¼ λ or at approximately 60 feet above ground, will be a good average short-haul antenna for several hundred miles.

One suggestion would be to have two anchor posts for the bottom end, one to provide a slope angle of at least 60° for low-angle DX, and the other to give about a 45° slope for general short-haul communication.

The 3-element phased sloper—

Although this is a more elaborate beam, having gain, it is not generally suited for a city lot, since two masts with a 200-foot separation are required. It does have an advantage in that very little width is required, but it does require considerably more wire, insulators, and labor to assemble. It did appear to be about neck and neck with the yagi (also being used at the same time) from the ZL and VK reports. It may have been just a bit noisier on reception due to being more nearly vertically polarized. However, I did not have time to determine this for sure. It did make a good showing "down under" when compared directly with the yagi being used then.

A 3-element wide-spaced horizontal log periodic beamed west was set up later, which Bob Tanner ZL2BT advised was the best antenna tested here over the past 3 years.

I might add that, when comparing the various 75m antennas during this period, if the ZL or VK reported a 1 or 2 S-unit or 5- to 10-dB increase or difference between two antennas, the same difference on reception of their signal would generally be noted, as would be expected.

On this multihop 75m path, there is generally less QSB than on the higher bands. When there is fading, it is usually slow, unlike rapid QSB on 20.

For the information of those who do not work 75m DX, the VK and ZL signals generally have a slow buildup about 15 minutes before sunup, when they peak. They remain peaked for 15 to 30 minutes, and then start a decline for 30 minutes to 1 hour after sunup, local time.

As yet, I have not determined if the sunrise peak is due to "gray line" propagation or possibly due to a change in ionization of the F-layer, causing less attenuation at this end or possibly in the last hop (received at this end), thus giving the 5- to 10-dB signal increase which is generally noted at sunup.

It is doubtful that "gray line" affects the US-NZ path since they are in total darkness approaching midnight (sunup here in the east). "Gray line" might affect the W-VK path since sunup here is about sundown in certain parts of Australia.

To get more firsthand information on this, I am now (as of this writing) in the process of putting up two beverage receiving antennas, one N-S and one E-W. These are 2-wire reversible-direction beverages, each 520 feet in length, for use on 160, 80, and 40. Some very excellent data, suggestions, and material have been made available to me by Paul W6PYK for this test, for which I am very grateful. I had previously tested several simple single-wire beverages, resistor-terminated, to improve S/N.

The beverage project was started here originally to try to improve reception which is extremely poor, especially on 75, at this QTH. This is due to very poor ground conductivity, extremely high noise level (both QRN and man-made) on 75, and the fact that it is surrounded by high pine trees (60 to 90 feet) except to the NE and E. They extend for several miles to the SW and W.

For this reason, there is little open space for verticals, since trees higher than a ¼-λ vertical would surround it. There would be some trees separated from them by less than 50 feet, very thick in the direction of the ZLs and VKs. The two single-wire slopers which were tested were suspended from trees in open areas, although there were trees within about 100 feet to the W and SW.

For those who may become interested in 75m DX, there are some very good suggestions on propagation, "gray line," 75m antennas, receivers, a list of 75m DXers, beverage antennas, etc., presented in John Devoldere ON4UN's ham book *80 Meter DXing*, published in 1977. He includes a very complete list of 86 previously-published articles in the various ham publications covering these subjects.

Other Suggested Sloper Designs

In addition to the shortened loaded sloper and the 3-element phased sloper described above, the following are several suggested slopers and phased slopers. I have not actually tried these, but they are described briefly for anyone wishing to experiment or

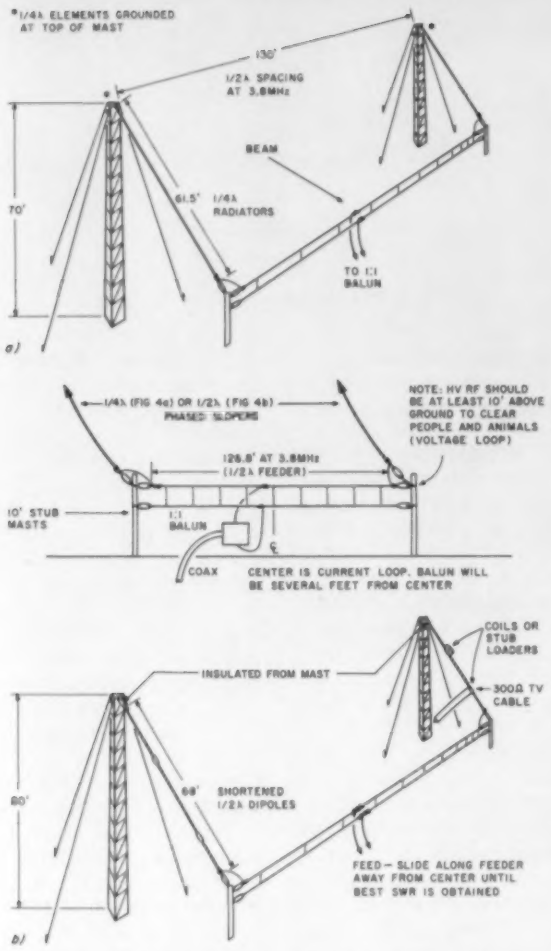
*1/4λ ELEMENTS GROUNDED AT TOP OF MAST
130'
1/2λ SPACING AT 3.8MHz
BEAM
70'
61.5' 1/4λ RADIATORS
TO 1:1 BALUN
a)
1/4λ (FIG 4a) OR 1/2λ (FIG 4b) PHASED SLOPERS
NOTE: HV RF SHOULD BE AT LEAST 10' ABOVE GROUND TO CLEAR PEOPLE AND ANIMALS (VOLTAGE LOOP)
126.8' AT 3.8MHz (1/2λ FEEDER)
10' STUB MASTS
1:1 BALUN
COAX
CENTER IS CURRENT LOOP. BALUN WILL BE SEVERAL FEET FROM CENTER
COILS OR STUB LOADERS
INSULATED FROM MAST
300Ω TV CABLE
80'
68' SHORTENED 1/2λ DIPOLES
FEED— SLIDE ALONG FEEDER AWAY FROM CENTER UNTIL BEST SWR IS OBTAINED
b)

Fig. 4.(a) ¼-λ phased slopers. (b) ½-λ shortened phased slopers.

who is interested in antenna design.

Multidirectional slopers—

If there is sufficient open area around a single high mast or tree, 3 or 4 of the shortened 75m dipole slopers could be used for several directions as per K1THQ's 40m four-direction sloper described in the *ARRL Antenna Book* (Figs. 8-12, page 200, 13th edition). According to his measurements, the forward gain was about 4 dB and front-to-back up to 20 dB. Note that the coax to the relay box must be just over 3/8 λ. At 3.8 MHz, this length would be approximately 63.4 feet of RG-8/U or RG-58/U (VF = 66%), or 74.9 feet of RG-8/AU or RG-58/AU (VF = 78%).

I have not tried this 4-directional sloper, but it sounds interesting for anyone having the room and needing a lobe in more than one direction. If a mast at least 130 feet in height is available, full ½-λ sloping dipoles could be used without loading and would no doubt be more effective. The dimensions would then be about double those given for K1THQ's 40m switchable sloper.

¼-λ slopers—

Not having a tower, I have been unable to test a ¼-λ inverted sloper fed by coax at the top of the tower (with the coax sheath grounded to the tower near the feedpoint). I have worked several on 75 who have reported good results with this type of inverted sloper.

Theoretically, this should be a good antenna, since the current loop of the ¼-λ sloper is topside and generally in the clear. The tower provides a ground plane or acts as a reflector, which should give some directivity. However, this type appears to be tricky (and they either work or they don't). No doubt the ¼ wavelength and the angle between the sloper and the tower are critical, probably affecting the impedance at the top feedpoint, which is probably low. Possibly a matching network between the coax and the feedpoint would help, or possibly the top of the ¼-λ element could be grounded directly to the towers and the lower end voltage fed at the bottom with a tuner or a ¼-λ tuned line used to voltage or end feed, similar to the old Zepp. Using voltage feed at the bottom also saves the length of coax from bottom to top of tower.

I have one friend, YV5DLT, who put up two of these ¼-λ inverter slopers (topfed), one for 75 and one for 40. He said the 75 worked with no problem, whereas the 40m refused to work. I have noted that about 25% of those using the ¼-λ sloper have gotten them to work; the rest had problems or became discouraged if they did not work right away.

Possibly those using these successfully can give some suggestions. Also, the estimated angle of radiation, H-plane pattern, etc., would be interesting.

Dual ¼-λ phased slopers—

Possibly, using two of these side by side, in phase, spaced ½ λ broadside to the desired direction, might be of interest, as per Fig. 4(a). The two ¼-λ elements spaced ½ λ would be grounded topside, as mentioned above. The two bottom ends (voltage loop) would be voltage-fed with a ½-λ open phasing line feeding the ends, so the two ¼-λ radiators will be in phase. The ½-λ phasing line is current-fed, slightly off center directly with the coax or with a 1:1 balun. For 3.8-MHz operation, the two ¼-λ slopers would be approximately 61.5 feet and the 2-wire open phasing feedline approximately 126.8 feet long. This beam requires two 70-foot towers spaced about 130 feet apart and oriented broadside to the desired direction. A few wire reflectors between the towers might improve the lobe in the desired direction.

This array would be similar to the broadside or side-by-side phased slopers described below, except ¼-λ slopers would be used in place of the ½-λ shortened dipoles. See Fig. 4(b).

½-λ phased-sloper or vertical-dipole arrays—

If a mast at least 130 feet high is available, it could be used to support a full ½-λ phased sloper or vertical dipole endfire array. The elements would then be a full ½ λ (no endloading required), thus being more efficient and having greater effective height.

Another advantage of greater height would be the possibility of having the three elements near or exactly vertical, so the array would then become a 3-element vertical (dipole) log periodic or 3-element vertical yagi (whichever configuration is preferred) as was described above under "Phased Slopers—Endfire Array."

With the shortened dipole sloper or multielement sloper arrays, the loaded elements probably reduce efficiency about

10% DISCOUNT ON ALL LUNAR PRODUCTS

DURING LUNAR'S 2ND ANNIVERSARY **SALE!**

(July 1 through July 31 at all participating dealers).

LUNAR'S LINEARIZED AMPS

WITH BUILT-IN RECEIVE PRE-AMPS

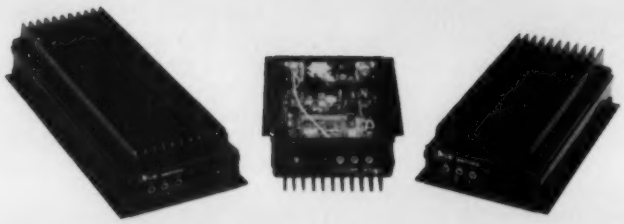

INTRODUCING OUR NEW AMPS MODELS 2M10-150P AND 2M3-150P

- 3 watts in, 150 watts output (3-150P).
- 10 watts in, 150 watts output (2M10-150P).
- Linearized amp for SSB use.
- Preamp 10 dB gain, 2 dB noise figure.
- Other specs similar to existing amps.

BI-LINEAR VHF MODELS

- Low Power Input Yields nom 10 dB gain
- Covers entire Amateur Band w/o Tuning
- Built-in Receive Preamplifier
- Automatic variable delay PR switching
- Exceeds FCC R&O 20777 Requirements of -60 dB
- Preamp & Power Amp Independently Controllable
- Preamp nom 10 dB gain 2 dB Overall NF
- Functionally Designed Package, including mounting lip
- Models available for the 50, 144 and 220 MHz bands
- Type accepted models also available. Models for 432 MHz due in near future.

10% OFF

LUNAR'S RECEIVING PRE-AMPS.

Suitable to the most demanding needs where low noise figure is important. Uses include all types of weak signal work such as EME, Tropo & Ionospheric Scatter, Satellite Communications, Radio Astronomy, Meteor Scatter, etc. Highest quality construction and components.

10% OFF

LUNAR'S PORTABLE ANTENNA TOWER

- Manufactured in our San Diego plant.
- Ideal for ground or roof mounts.
- One man can assemble and erect.
- Extremely rugged.
- Lightweight.
- Modular and portable.
- High stability with proper guying.
- High quality aluminum alloy construction

New Jersey's fastest growing Ham Store.
Stocking most major brands ✓R36

RADIOS UNLIMITED

1760 Easton Ave. (Rte. 527)
P.O. Box 347
Somerset, N.J. 08873

201-469-4599

VISA

master charge

50%, as the shortened radiating portion is only approximately ¼ λ. Their ¼-λ radiating portion should be about the same as the vertical radiating portion of a Bruce array.

The end-loaded sloper array might be considered as a 3-element endfire array, as opposed to a 3-element Bruce array which is a bidirectional, broadside one using ¼-λ radiating elements in phase spaced ¼ λ. The 3-element endfire array would be unidirectional and should give greater gain. The Bruce would, however, probably have a greater null to the sides (180°).

If a single high mast is available, it could also be used as the center support for 3 or 4 separate phased endfire arrays, thus providing 3 or 4 separate beam headings or separate selectable lobes at 120° for 3 arrays or 90° for 4, for beaming N, E, S, or W.

Granger, Trylon, and Hy-Gain manufacture commercial or military fixed-wire monopole and vertical dipole log periodic wire beam arrays of these types for frequency ranges 2.5-32, 3.0-32, 4.0-32, and 6.0-32 MHz. These are recommended for long-haul HF circuits. See the Hy-Gain commercial catalog E, 1969.

Incidentally, if any hams are interested, these commercial wire beams are generally in the $20,000 to $50,000 class. However, this does include an 100- to 240-foot steel tower. A 3- to 5-element vertical (monoband) dipole log periodic for 75m can generally be ham-built for $100.00 or less for wire, insulators, etc., less tower and coax.

Broadside or side-by-side shortened slopers—

Another suggested phased sloper could be the use of two shortened 78-foot ½-λ (loaded) sloper dipoles suspended from two 70-foot masts spaced ½ λ (approximately 130 feet at 3.8 MHz). See Fig. 4(b). The two slopers would be operated in phase with 130 feet of separation. A ½-λ tuned feeder/phasing line would be required for feeding and phasing the two slopers, similar to the dual ¼-λ phased slopers described above in Fig. 4(a).

Better still, if the two phased slopers could be a full ½ λ (requiring two 130-foot masts), they should give about maximum gain to broadside for an array of this type. I believe I have heard of some ham using this type of beam.

There are, no doubt, many phased-sloper-array combinations which can be designed. I again wish to point out that I have only built and tested the loaded sloper of Fig. 2 and the 3-element (end-loaded) phased sloper of Fig. 3(a).

I would appreciate hearing from anyone who is using or has tried any phased-sloper arrays or has any suggestions along this line. ■

References

1. *73 Magazine*, Aug., 1973, "Single Band Log-Periodic Antennas," part I, G. E. Smith W4AEO.
2. *73 Magazine*, Sept., 1973, op. cit., part II.
3. *73 Magazine*, March, 1975, "Yes, I've Built *Sixteen* Log Periodic Antennas!", G. E. Smith W4AEO.
4. *Ham Radio*, Sept., 1972; May, 1973; Aug., 1973; Sept., 1973; May, 1974; Oct., 1974; May, 1975, G. E. Smith W4AEO.
5. *Communications News*, June, 1974, "Designing Log-Periodic Beam Antennas by the Graphic Method," G. E. Smith W4AEO.
6. *QST*, Apr., 1977, "Quad Log-Periodic Fixed-Beam Antennas," G. E. Smith W4AEO.

ALL-MODE VHF amplifiers

FOR BASE STATION & REPEATER USE

MODEL: V350

☆ Built-in 115/230 VAC Supply
☆ AM-FM-CW-SSB-RTTY
☆ 60dB Harmonics
☆ 60dB Spurious
☆ Heavy Duty Design

All Solid-State!

MODEL: V180

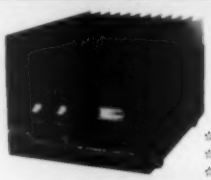

☆ Illuminated Panel Meter
☆ Automatic T/R Switching
☆ VSWR Protected
☆ +13V/3A Accessory Socket
☆ U.S. Manufactured

MODEL	FREQUENCY	INPUT	OUTPUT	SIZE WxDxH	WEIGHT	FAN KIT REQUIRED	PRICE
**V76	50-52MHz	8-15W	100-120W	216x330x178mm	11.7 kg (26 lbs)	No	$339.00
**V360	50-52MHz	5-10W	400-450W	432x330x178mm	23.4 kg (52 lbs)	Yes	$895.00
V70	144-148MHz	10-15W	75-90W	216x330x178mm	11.7 kg (26 lbs)	No	$315.00
V71	144-148MHz	1-3W	75-90W	216x330x178mm	11.7 kg (26 lbs)	No	$349.00
V180	144-148MHz	5-15W	170-200W	216x330x178mm	13.5 kg (30 lbs)	CW & FM	$539.00
V350	144-148MHz	10-20W	350-400W	432x330x178mm	23.4 kg (52 lbs)	Yes	$895.00
V130B	220-225MHz	10-15W	70-85W	216x330x178mm	11.7 kg (26 lbs)	No	$329.00
V135B	220-225MHz	25-35W	140-160W	216x330x178mm	11.7 kg (26 lbs)	CW & FM	$469.00
F110	Fan Kit, 115VAC			135x135x50mm	1 kg (2.2 lbs)	–	$ 33.00
F220	Fan Kit, 230VAC			135x135x50mm	1 kg (2.2 lbs)	–	$ 33.00
*F135	Fan Kit, 115VAC			381x140x89mm	3.2 kg (7 lbs)	–	$ 59.00
*F235	Fan Kit, 230VAC			381x140x89mm	3.2 kg (7 lbs)	–	$ 59.00
RM-1	19 Inch Rack Adaptor			483x3x178mm	1 kg (2.2 lbs)	–	$ 25.00
*RM-2	19 Inch Rack Adaptor			197x32x28mm	.5 kg (1.1 lbs)	–	$ 12.00

*Used with the V360 & V350 Amplifiers / **For Export Only / **Other Frequencies Available on Request**

Dealer Inquiries Invited

rf POWER LABS

RF POWER LABS, INC. ✓R27

master charge VISA

11013-118th Place N.E. • Kirkland, Washington 98033 Telephone: (206) 822-1251 • TELEX No. 32-1042

NEW FT-7B 100 W MOBILE/BASE HF TRANSCEIVER

Enough power to drive those linears! The FT-7B is the high powered version of the popular 20 watt FT-7 that so many hams are running mobile in cars, boats, and planes around the world. Use the FT-7B as a top quality base station. New improvements include an audio peak filter (like our FT-901DM) to give you super CW selectivity, drive control, four 10M positions, full 80-10M coverage, 28.5-29.0 MHz crystal supplied (other crystals available as options), optional YC-7B Plug-in Remote Digital Readout, optional FP-12 Speaker/Power Supply Console.

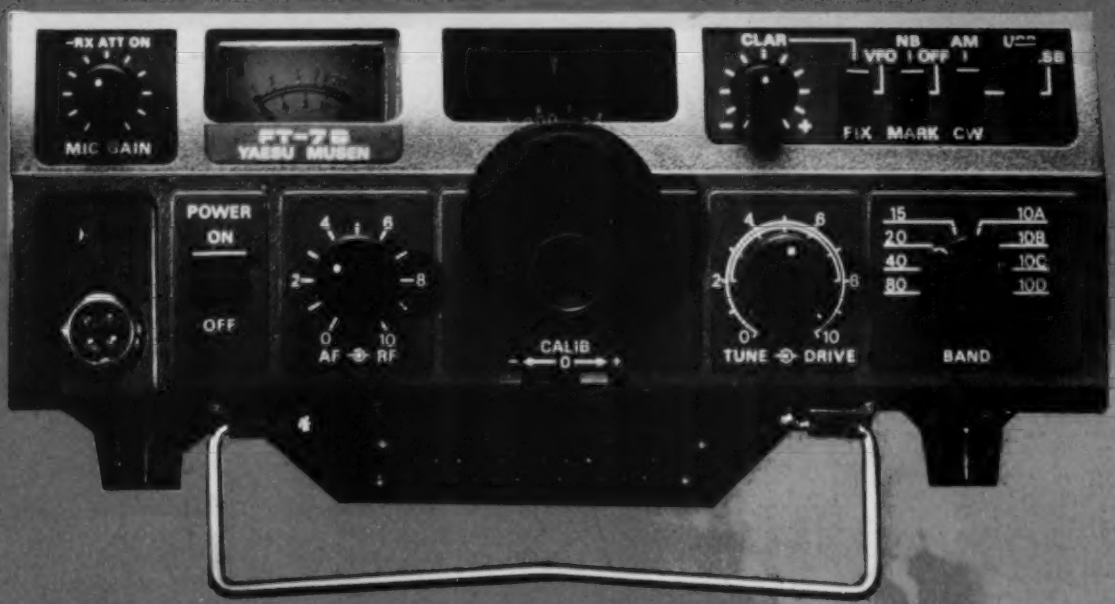

RECEIVER

Sensitivity: 0.5uV for S/N 20 dB
Image rejection: Better than 50 dB
IF rejection: Better than 50 dB
Selectivity: -6 dB: 2.4 KHz, -60 dB; 4.0 KHz
Cross-modulation: Better than 60 dB immunity at 20 KHz off a 20 dB input signal typical
Audio output: 3 watts @ 10% THD

TRANSMITTER

Emission: LSB, USB (A3j), CW (A1), AM (A3)
Input power: A1, A3j; 100 watts DC
Carrier suppression: Better than 50 dB below rated output
Unwanted sideband suppression: Better than 50 dB @ 1000 Hz
Spurious emission: Better than -40 dB
Distortion products: Better than -31 dB

arma

Price And Specifications Subject To Change Without Notice Or Obligation

YAESU
The radio.

579X

YAESU ELECTRONICS CORP., 15954 Downey Ave., Paramount, CA 90723 ● (213) 633-4007
YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246

Frederick James Bartolomei N8AJA
19442 Rockport Drive
Roseville MI 48066

Build This Simple 220 Yagi

—3 elements, 6 dB

The $5 AJA special.

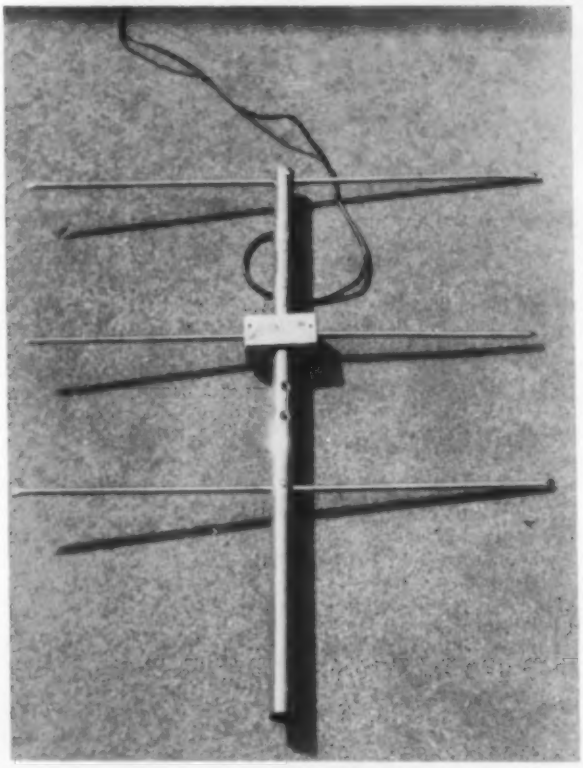

The completed 220-MHz beam.

If you're looking for an expensive, double-figure-dB gain HF antenna, try another article, because this construction project won't help you at all—especially if you want an HF skyhook. However, if the idea of a $5.00, 3-element yagi with about 6 dB of gain for 220 MHz suits you, then read on.

When the June, 1978, issue of *220 Notes* (volume 1, number 4) arrived at my doorstep, I was new to 220 MHz; in fact, the ink on my Tech ticket was still moist! So the blurb titled "Your Own Little 220 Beam" on page one captured my immediate interest. Although *220 Notes* included a marvelous sketch of the antenna (which they adapted from C. N. Zornes W9TAL), the newsletter contained no instructions for assembly. Fig. 1 is redrawn from *220 Notes* and shows antenna dimensions.

To build W9TAL's beam, I purchased a GEC-52 conical TV antenna, made by RMS Electronics, 50 Austin Place, Bronx NY 10462, for five bucks from a local radio-electronics store. I chose this model because of the cheap price, but any television antenna will do. Another route is to buy a boom and 1/8" or 3/8" aluminum rods separately.

Step 1: After taking the TV antenna from the shipping carton, remove the elements (secured to plastic hubs with pop rivets) by drilling out the rivets with a bit slightly larger than the head. Now you have several aluminum elements of various lengths and a boom.

Step 2: Measure the length of your boom. It must be at least 30 inches. The mast-cum-boom supplied with the GEC-52 is 31½ inches long. If your boom exceeds three feet, I recommend shortening it

to 30 inches. A hacksaw or saber saw will do the job. Now mark a ¼-inch point in from either end; mark another ¼-inch point on the other side, i.e., directly behind it. You will be drilling through these points, so make sure they line up! Make similar marks 19½ inches in front of the first two. Measure the diameter of your elements, add 1/16 of an inch, and drill holes in each of the four marks. The drill bit will not slip if you first punch holes in the boom with a large nail.

Step 3: Make marks midway between the holes you drilled for the reflector element. These are perpendicular to and ¼ diameter away from the original holes. Stove bolts will drop through these points to secure the reflector. Repeat this procedure for the director. Once the spots are marked, drive a large nail through them and wiggle it around to ream out the aperture.

Step 4: Time to cut your elements. Measure and cut one element 27-1/8 inches long—this is the reflector. Measure and cut another 24-1/8 inches long—this is the director. Measure and cut two elements each 12 inches long—these are the driven elements.

Step 5: Crimp the open ends of the reflector and director and one open end of each driven element with pliers to prevent water from entering and rusting them. If the crimped ends are rough, a file or sandpaper will smooth them off. Locate the midpoint of each element (13-9/16 inches for the reflector; 12-1/16 inches for the director) and punch a hole, using the nail from Step 3, to allow a bolt to pass through it.

Step 6: Take a 4-inch piece of 2" x 4" and bore a hole in it as shown in Fig. 2, to accommodate the boom. Use a smaller bore (or large bit) to drill holes in the sides of the 2" x 4". These holes should be ¾ of an inch to 1 inch deep and under no circumstance should they intersect with the boom bore.

Set a driven element in each of the two side holes (make sure it is snug against the back) and screw a 1½-inch wood screw into the top of the 2" x 4" about ½" from the edge. The screw will secure the element and will later serve as a conductor between the coax and element. Slide the 2" x 4" on the boom so that the elements' centers are 10½ inches from the middle of the reflectors' holes.

Step 7: You're in the home stretch . . . final assembly begins here. Place the reflector (remember that's the longer element) in the large holes near the rear of the boom. Align the holes in the boom and reflector so that they match. Set a flat washer over the topside hole and drop in a bolt. Tighten the bolt with a lock washer and nut on the underbelly. Repeat this for the director.

Strip 1½ inches of the coax's outer covering off the end. Twist the shielding braid into a "wire" and remove the plastic insulator from around the center conductor. The total distance between the split in the coax to the end of each driven element is 12½ inches. Measure the length from one screw in the 2" x 4" to the tip of the corresponding driven element. Subtract this size from 12½ inches and wrap all but the difference of the twisted coaxial braid around the head of the wood screw. Drive the screw as deeply as possible into the 2" x 4". Repeat this part of Step 7 for the remaining screw and the cable's center conductor.

I wrapped silver duct tape around the 2" x 4" to isolate it from the nasty Michigan winters and to increase the beam's life.

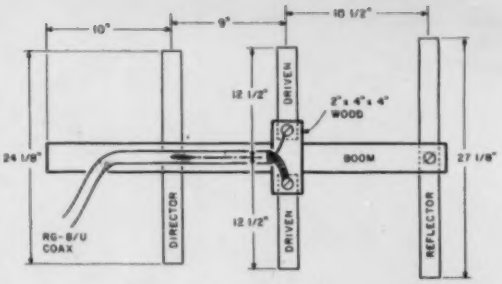

Fig. 1. Antenna and dimensions. Adapted from: 220 Notes, volume 1, number 4, June, 1978, page 1.

Bathtub caulking is another solution.

Results

In preliminary tests the yagi performed admirably. My first simplex contact was with Tom WB8GVC in Detroit (a distance of about fifteen miles), and the antenna was only ten feet above ground level. When I taped the beam on a twenty-foot makeshift mast (and had my father and Tom WD8OTN take turns playing rotor), I raised the WR8AOK repeater in Livonia, Michigan. WR8AOK sits forty-five miles from my home QTH—not bad for a ten-Watt Midland 13-509 rig and a twenty-five-foot run of RG-58/U. In the low power position (one Watt), I full-quieted the WR8AEF machine in Mt. Clemens, Michigan, a six-mile haul. All in all, I've been impressed with the results of W9TAL's design.

For maximum results, mount the beam as high up as possible—or, at least above surrounding trees—away from other metallic objects, and use RG-8/U coaxial cable to minimize transmission line loss.

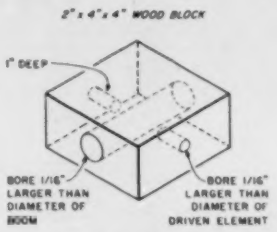

Fig. 2. Sketch of wood block holding driven elements.

I purposely neglected VHF/UHF antenna theory in this article. If you're curious about why it works, then consult one of these fine books: *VHF Antenna Handbook* from *73 Magazine* for $4.95 or *The Radio Amateur's VHF Manual* from the ARRL for $4.00. I felt the underlying theory was too much to tackle here and many hams, like myself, are more concerned with putting out a good signal. Any comments, questions, or objections you have on this fine, 6-dB, 220-MHz antenna at the minimal cost of five bucks will be answered, provided, of course, that you enclose an SASE.

As for me, I'm heading back to the radio . . . "QRZ rare DX from N8AJA in Roseville, Michigan." ■

Parts List

TV antenna (GEC-52) *or* 6½' of 1/8" or 3/8" aluminum rods and 30" boom
4" piece of 2" x 4" wood
saber saw or hacksaw with blade
2 wood screws (1" long)
2 stove bolts (1½" long) and lock and flat washers
wood bore and drill bits
electric drill
RG-8/U coax with 1 PL-259
rosin core solder and soldering iron

Alexander MacLean WA2SUT/NNN0ZVB
18 Indian Spring Trail
Denville NJ 07834

Beware of the Dreaded Phantom Ground

— exorcise those antenna gremlins

Avoiding the non-radiant antenna.

The article by John Cranston WB2DYU/2 in the March, '78, issue of *73* ("I Need A Contact!") brought back many unpleasant memories of past station operation and more than too many of how it works now. I, too, have a long history of inventing the non-radiant antenna. However, a few of the rules of thumb (or burned fingers, if you will) arrived at may be of help to other hams starting out.

If you don't read too much theory, it is harder to build an antenna that will not work than to build one that works.

From the description of what Cranston has, there seem to be a few old friends. One of my favorites is the phantom ground. All the books say that you should ground the equipment, particularly the transmitter, to avoid all sorts of troubles. Usually this leads to all sorts of troubles just like the ones you wanted to avoid, like TVI and rf burns when you touched the rig.

So what happened? Well, the ground was always shown in a picture-book station. There was all that beautiful gear, all hooked up together with a heavy copper braid ground bus to a conveniently located ground. It is the "conveniently located" that kills you. When they say ground, they mean ground, as in nice wet earth. To work, the direct earth connection must be quite close to your equipment and connected with a solid hunk of metal.

Many hams have some heavy copper water pipe that goes right through the basement shack and into the ground. Now that is a reasonable ground. If you don't have that, you don't have a ground. The further away from that you are, the less ground you have.

If your shack is on the first floor, or more probably the second floor or attic, you don't have any ground at all. What you do have is a hunk of far too thin wire draped all through the house to a water pipe and maybe a long run of that to the ground. For rf purposes, you aren't even connected to the ground. What your transmitter sees is what looks like another hunk of antenna. That, added to your nominal antenna, results in almost as good a radiator as your store-bought dummy load.

I have tried a number of different configurations of this basic circuit and can recommend it for tune-up purposes. It also is very impressive to show visitors how you can light a small neon bulb with your nose when you key the rig.

Let's get back to practical for a bit. There is no such thing as a long ground unless you can run something the diameter of a sewer pipe from the rig to the ground. I don't think that will work well, either.

So, forget the ground. Build an antenna that will work without the ground. This is not as hard as it sounds. Without the false ground to give trouble, many antennas will do the job without trouble.

Most rigs are coax-fed these days, so the basics will be for that type of output. The coax-fed antennas, dipole, beam, quad, etc., will work fine without the earth ground. Here you may want a balun or other matching device to go from unbalanced line to balanced, but it should not be critical.

If you can do it, the attic shack is the ideal location for the roof-mounted antenna. A simple mast with a small beam or quad will do nicely. From there it will be a short coax run to the rig.

So far, so good. What about that dipole you wanted to have? It doesn't matter that the rig is in the attic, but it usually happens that when you have met the condition that your rig is nowhere near a good ground, it probably is situated where you can't have a good antenna. Somehow the landscape has been carefully arranged so that there is no possibility of stringing a dipole, inverted V, or

anything resembling the antennas shown in the book.

Now what? This is where the all-time easy antenna comes into its own—the classic random-length antenna. What this is is a long piece of wire. You make it as long and as high as you can. Nominally, you want it more than ¼ wavelength long. It would be nice if it was in a straight line, but it is quite accommodating to being bent into odd shapes. It would like to be free and clear of other objects, particularly metal ones.

With a little thought, it is almost impossible to not be able to meet the requirements of this antenna, but there are a few little hitches.

It runs from your transmitter to where it ends. That means there will be radiation in the shack; however, this should not be what is usually thought of as rf in the shack, i.e., burned fingers when you touch the rig. It just has to be hooked up right. Most rigs have a 50-Ohm output. The random is high impedance. You have to use an antenna tuner. This can be as simple as a coax jack, a variable capacitor (with insulated shaft), a coil and a few clip leads, or a fancy store-bought tuner. A short run of coax from the rig to the tuner and the antenna goes from there to the great outdoors. It works quite well.

It's hard to miss, but you're not home free yet. The books still say to ground everything together. This is how you get all that rf in the shack, plus assorted rf burns and minor jolts.

You still will have your phantom ground problem. It wasn't until I got rid of both the ground and connecting the various chassis together that my setup got tamed.

Don't connect anything to anything else that you don't have to. They fight with each other. This will leave you with only one problem.

There may be potential differences between the various chassis. If you are holding onto one and reach for another, you may get bitten. This is not pleasant, so learn not to do that any more. Don't grab two pieces of gear when both are live (or plugged in). This is a small price to pay for a reliable attic system. It may not happen that your particular gear does that. Some of mine does and some doesn't.

Of course, you are going to ground your antenna when not in use . . . or are you? You will have the same problem trying to ground your antenna to a phantom ground as your transmitter had working with it.

Antenna grounding is supposed to serve two purposes. It is fondly believed that it will protect your rig from a direct lightning hit.

Lots of luck. Even with the usual textbook ham ground setup, that is asking a lot. A direct lightning hit will go to ground, but it is probably going to take everything along the path with it. I don't know if the usual antenna, lead-in, and grounding setup is going to stay put for that, not to mention any gear connected to it. The best you usually hope for, and the usual case, is protection against the static charge buildup from a nearby electrical storm. While this is not usually big enough to turn your antenna into abstract artwork, it is often big enough to put a walloping charge into the front end of any rig that's there.

Here the solution is simple. It is not so much a direct earth ground you need as a chassis ground connection. Any of the antenna switching arrangements can usually be hooked up to short the antenna lead directly to the ground of the coax connector (chassis ground).

I haven't seen it mentioned in years, but there was a time when many schematics made a distinction between chassis ground and earth ground. There are different schematic symbols for each. The familiar ground symbol, Fig. 1(a), is the one for chassis ground. Fig. 1(b) is the symbol for earth ground.

If your shack location is such that you can't get a good earth ground for antenna grounding, the chassis ground will still work a lot better than leaving your rig there to get hit.

It also doesn't cost much to run a ground wire to your shack and try it for rf purposes. Then if you have trouble with operating, remove it when you use your rig and reconnect it just for electrical safety when you are not operating.

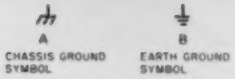

Fig. 1. Schematic ground symbols.

The key is to go by the book as far as you can and only make such modifications as you have to for your particular circumstances. Then do as much as you can to restore non-operating safety.

I hope these two particular techniques, the use of a tuned random-length antenna and the avoidance of a phantom ground, will help solve a few problems for those who are just beginning or not able to use a more conventional configuration.

It drove me nuts for quite some time until I got the hang of it. It's not the best, but it will be reliable when properly applied. ■

Code Made Easy.

To really master code, get Pickering Code Master instruction tapes. They're easy to use, easy to learn; complete and reliable. But don't just take our word for it, ask any ham. Or order a set and see for yourself.

CM-1 Novice. A complete course with 5, 7 and 9 WPM code group practice.

CM-1½ General. No instruction, just practice. ½ hr. at 11 WPM, 1 hr. at 14 WPM and ½ hr. at 17 WPM. Tape includes coded groups and straight text.

CM-2 Extra Class. Mostly straight text, some groups. 1 hr. at 20 WPM, ½ hr. at 25 and 30 WPM.
All courses are two hours long and come with key sheets for checking problem areas.

To order, send your check, money order, Master Charge or Visa number (along with card expiration date) to Codemaster. Specify number and quantity of tapes desired. Tapes are $7.95 each, two for $14, and three for $19. Also specify 7" reel or cassette. We'll send your tapes post paid by fourth class mail. First class, Canada and Mexico orders, add $1 per reel, 50¢ per cassette. To order by phone, call (401) 683-0575.
R.I. residents, add 6% sales tax.

Pickering Codemaster Co., P.O. Box 396 D, Portsmouth, R.I. 02871

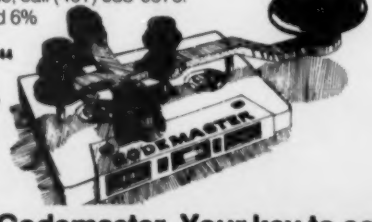

Pickering Codemaster. Your key to code.

A Close Encounter With Voyager I

—the W6VIO story

Voyager II is next.

Dr. Norman L. Chalfin K6PGX
JPL Amateur Radio Club
4800 Oak Grove Dr.
Pasadena CA 91103

Jet Propulsion Laboratory Amateur Radio Club members gave up lunch periods, many after-work hours, and weekends during the period from March 1-11, 1979, to operate their club station W6VIO in celebration of the close approach of the *Voyager I* space probe to the planet Jupiter and its four Galilean satellites, Io, Europa, Ganymede, and Callisto.

Dick Piety K6SVP at the SSTV position. The image on the screen is of Callisto, one of Jupiter's moons.

Dick Piety K6SVP organized and managed the operation. He was assisted by Jim Lumsden WA6MYJ. Jim mounted a Herculean effort in getting the newly refurbished trailer which constitutes the W6VIO shack ready for the event. Equipment, stored in many locations during the refurbishing, had to be returned to the shack and reinstalled in the beautifully arranged shelves and decks.

The 1540 contacts made in the various bands on which the operation was mounted include:

10m	phone	281
(includes a number of SSTV contacts)		
10m	CW	21
15m	phone	123
15m	CW	164
20m	phone	362
(includes many SSTV contacts)		
20m	CW	157
40m	CW	10
75m	phone	1

One of the SSTV monitor views of the W6VIO ID during the Voyager I commemorative.

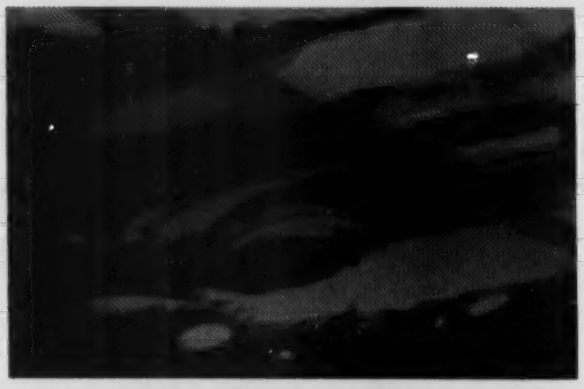

A slow-scan image of the great red spot on Jupiter.

2m	FM	348
(includes check-ins to various JPL/Goldstone* nets run during the commemorative)		
220 MHz	FM	72
OSCAR		1

There were 79 contacts outside the United States.

Interesting sidelights arose during the commemorative. Dick says he "doesn't believe" the contact on 2 meters who gave a K7 call and said he was speaking from Seattle. (Seattle to Pasadena on 2m?) Merv MacMedan N6NO began a CW contact with a Spanish amateur who wouldn't let him go on to others. Merv explained to him in Spanish about the *Voyager* commemorative. The Spanish amateur wanted to "rag-chew." Jim made a contact on SSTV with a Wichita Falls, Texas, amateur who said he was recording the pictures for his high school class of fourteen-year-olds. Dave Ingram K4TWJ telegraphed that he was recording the Jupiter images and sending them to the local press as fast as he received them. A Denver amateur contacted the Denver *Post*. They called K6SVP on the phone to interview him about the operation. A contact with F6KCP by W6VIO led to five or six other French amateurs joining the activity.

The promised QSL card, including Jupiter pictures made by *Voyager I*'s cameras, was a magnet to pull in the contacts. All who contacted W6VIO during the March 1-11, 1979, period will receive QSLs if they send an SASE to W6VIO or QSL through their bureaus. The card also identifies the major discoveries about Jupiter and its moons made by the *Voyager I* spacecraft in its close encounter of the most spectacular kind. Those who remember the *Viking* commemorative card from N6V, operated by the JPL club during the landings on Mars, can appreciate the beauty of these very special QSLs.

From July 6-15, 1979, there will be a second Jupiter fly-by commemorative for the *Voyager II* Mission. It will have a somewhat different card. If you missed out on *Voyager I*, try for *Voyager II*.

The individual members of the JPL ARC (in addition to myself) who took part in the *Voyager I* commemorative are: Dick Piety K6SVP (chairman of the commemorative operation), John Repar WA6LWD, Stan Sander N6MP, Ron Zenone W6TUZ, Warren Apel K6GPK, Merv MacMedan N6NO, Jim Longthorne WA6KPW (off-lab member), Bob Gosline AE6S, Rich Soikkele WD6ERI (an Arcadia, California, high school student, 16 years old, who is communications associate on the Sunfire I project), George Morris W6ABW, Jim Lumsden WA6MYJ (facilities chairman for W6VIO), Mike Griffin N6WU (president of the JPL ARC), and Glenn Berry K6GHJ (who organized the reconstruction of the trailer). ■

*The JPL Amateur Radio Club (operating on 220 with WR6APS at La Canada CA) and its affiliated Goldstone Club (operating on 220 with WR6AZN from Table Mountain, near Wrightwood CA), are linked together for a general amateur radio news net on each Tuesday at 8:00 pm PST and for an AMSAT/OSCAR news net on each Wednesday at 8:00 pm PST. The combined net covers all of southern California.

BELDEN

	Part Number	MHz	dB/ 100 ft.	dB/ 100 m
9888 42¢/ft		50	1.2	3.9
		100	1.8	5.9
		200	2.6	8.5
		300	3.3	10.8
		400	3.8	12.5
8214 26¢/ft.		50	1.2	3.9
		100	1.8	5.9
		200	2.6	8.5
		300	3.3	10.8
		400	3.8	12.5
8237 23¢/ft		100	2.0	6.6
		200	3.0	9.8
		400	4.7	15.4
		900	7.8	25.6
8267 27¢/ft		100	2.0	6.6
		200	3.0	9.8
		400	4.7	15.4
		900	7.8	25.6

8448 17¢/ft — No. of Cond. — 8; AWG (in mm) — 6-22, (7x30), [.76]; 2-18, (16x30), [1.19]

9405 28¢/ft — No. of Cond. — 6; AWG (in mm) — 2-16, (26x30), [1.52]; 6-18, (16x30), [1.17]

MADISON ✔M35
ELECTRONICS SUPPLY, INC.
1508 McKINNEY • HOUSTON, TEXAS 77002
713/658-0268
MASTERCHARGE • VISA

Alan M. Christman WD8CBJ
Box 44
Granville WV 26534

GIANT Wire Antennas

—impress the neighbors

Have you ever found yourself wanting an antenna that was easy to put up, had gain over a dipole, was simple to match, and could work on more than one band? Then read on. This article shows how to design and build wire antennas which are longer than a half wavelength. These antennas may be operated as dipoles or V-beams. By careful choice of leg length, it is possible to build an antenna which will work on several amateur bands, but requires only a single feedline. The input impedance is about 200 Ohms and may easily be matched to 50-Ohm coax with a 4:1 balun.

Background

One advantage of the half-wave dipole is its low feedpoint impedance. The reason for this is shown in the upper drawing of Fig. 1. This drawing shows the standing waves of voltage and current which are present on a resonant antenna. From Ohm's Law, the input impedance is equal to the voltage divided by the current at the feedpoint of the antenna. For a half-wave dipole, the voltage at the feedpoint is low and the current is high, which gives a low value of impedance —typically, 50 to 70 Ohms.

Many hams use half-wave antennas, but it is also possible to make a dipole in which each leg is much longer than a quarter wavelength. Fig. 1 also shows the voltage and current distributions for 1-wavelength and 3/2-wavelength dipoles. Notice that the current in the center of a full-wave antenna is low and the voltage is high, resulting in a very high input impedance on the order of several thousand Ohms. However, the 3/2-wavelength antenna has a voltage minimum at its center, similar to the half-wavelength dipole. The feedpoint impedance is again relatively low—around 100 Ohms or so.

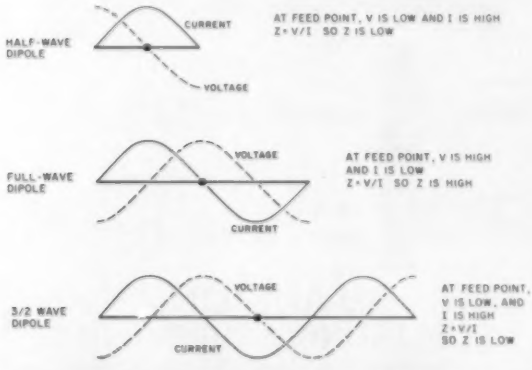
HALF-WAVE DIPOLE
CURRENT
VOLTAGE
AT FEED POINT, V IS LOW AND I IS HIGH
Z = V/I SO Z IS LOW
FULL-WAVE DIPOLE
VOLTAGE
CURRENT
AT FEED POINT, V IS HIGH AND I IS LOW
Z = V/I SO Z IS HIGH
3/2 WAVE DIPOLE
VOLTAGE
CURRENT
AT FEED POINT, V IS LOW, AND I IS HIGH
Z = V/I
SO Z IS LOW

Fig. 1. Antenna impedance is determined by voltage and current at the feedpoint.

At the ends of each dipole drawn in Fig. 1, the current is shown to be at a minimum value and the voltage is maximum. This makes good sense if you think about it. The current flowing at the end of a piece of wire must be zero because it has nowhere to go. On the other hand, the voltage at the end of a wire easily can be quite high. The important point to remember is that to get a low value of input impedance, there must be a voltage minimum at the center of the antenna. In other words, each leg of the antenna must be an odd number of quarter wavelengths. For the half-wave dipole, each leg is ¼ of a wavelength, while for the 3/2-wavelength dipole, each leg is ¾ of a wavelength. Each of these antennas has a voltage minimum at its center, and each also has a low value of input impedance.

Determining the Correct Antenna Length

Table 1 shows the formulas to use in order to calculate the right length for each leg of the antenna at the frequency of interest, once you have chosen how many quarter wavelengths you want each leg to be. Notice that a ¾-wavelength leg is *more* than 3 times as long as a ¼-wavelength leg. This is because the influence of "end effect" diminishes as the number of quarter wavelengths in each leg increases.

The antenna may also be oriented as a V-beam rather than a dipole, if directivity is desired. Table 2 shows the included angle (angle between the two legs of the V) for several different V-beam leg lengths, as well as the approximate gain of each configuration.

For those of you with lots of real estate, Table 3 gives the data required to design and build antennas which are truly giants. The feedpoint impedance of these monsters is in the neighborhood of the 200-Ohm value given for the antennas of Table 1.

Ham Radio Center has a Branch Store on the corner.

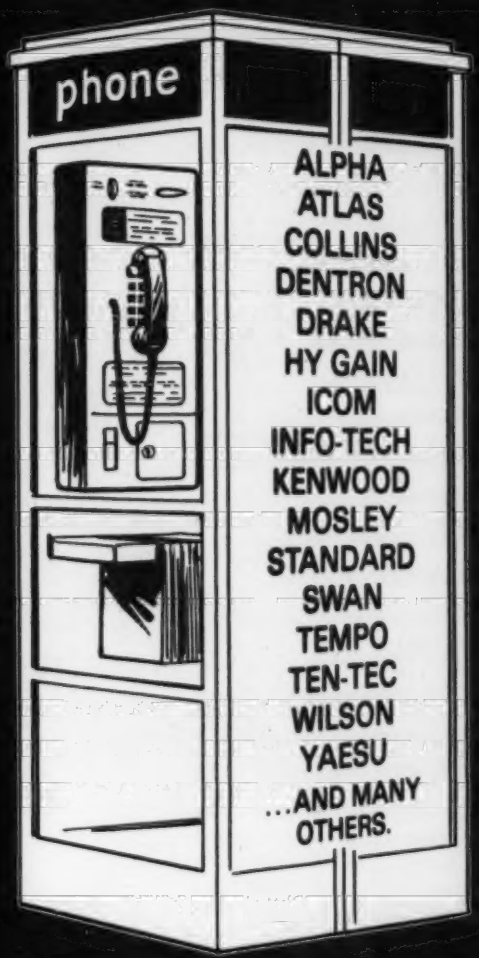

Special!

YEASU FT-227R—2-Meter

RETAIL $385.00

NOW $279.00

Add $3.00 shipping and handling/unit (USA)

CALL TOLL FREE

BEST PRICE

FAST DELIVERY

1-800-325-3636

arma

HAM RADIO CENTER

8340-42 Olive Blvd • P.O. Box 28271 • St. Louis, MO 63132

master charge

VISA

(Cut on dotted line and keep next to your radio equipment)

Leg Length in Wavelengths	Leg Length in Feet (f in MHz)
1/4	234/f
3/4	738/f
5/4	1230/f
7/4	1722/f
9/4	2214/f
11/4	2706/f
13/4	3198/f
15/4	3690/f
17/4	4182/f
19/4	4674/f
21/4	5166/f
23/4	5658/f
25/4	6150/f
27/4	6642/f
29/4	7134/f
31/4	7626/f
33/4	8118/f
35/4	8610/f
37/4	9102/f
39/4	9594/f
41/4	10086/f
43/4	10578/f

Table 1. Determining the correct leg length.

The formulas shown in these tables will give leg lengths which are approximately correct, but these values should be used only as starting points. All antennas should be cut a little bit long to allow for trimming to the exact length which is required. The actual resonant frequency of any antenna is affected by factors such as height above the earth and proximity to other objects.

Multiband Use

Certain leg lengths will resonate on more than one amateur band, which can be very convenient. I used to work in a small coal-mining town deep in the hills and hollows of southern West Virginia. I lived in a mobile home and had 340 feet of RG-8 coax which ran from my ham shack up the hollow to a hilltop behind my trailer. I badly needed an antenna which could cover several bands with a single feedline and which had some gain to make up for the cable losses.

While reading Ed Noll's book, *73 Dipole and Long-Wire Antennas*, I came across the information given here as Table 1. Ed explained that multiband operation was possible, so I got out my calculator and made a list of antenna lengths which would be resonant in the bands I wanted to operate (80 and 20 meters). Then I looked through my list to see if any of the numbers matched. It turned out that a ¾-wavelength leg on 80 meters was the same size as a 11/4-wavelength leg on 20 meters—about 190 feet in length.

This antenna was built from #12 copperweld wire and fed through a W2AU balun with a 4:1 impedance ratio. The swr was below 2:1 across the whole 20 meter band. On 80 meters, the resonant frequency was lower than I had planned (3.7 MHz versus 3.9 MHz), but I still was able to operate my Triton II on 75 meter phone with the swr around 3:1.

Other suitable combinations can be found by plugging desired frequencies of operation into the various equations and making a list of the resulting leg lengths. For example, a leg length of about 440 feet should resonate on both 80 and and 40 meters, while 428 feet looks good for 20 and 15 meters. It has been my experience that the actual leg lengths on 80 meters are somewhat shorter than the formula values, so a leg length of 428 feet may work well on all bands from 80 to 15 meters. A leg length of 362 feet should work on 40 and 20 meters, 330 feet on 10 and 15 meters, and 310 feet on 80 and 15 meters. For really big antennas, a leg length of 710 feet looks good on 40, 20, and 15 meters, 943 feet for 160 and 80 meters, and 673 feet for 160 and 20 meters.

Leg Length in Wavelengths	Included Angle in Degrees	Gain in dB
11/4	60	5.3
13/4	56	5.8
15/4	52	6.3
17/4	48	6.8
19/4	46	7.2
21/4	44	7.6
23/4	42	8.0
25/4	40	8.4
27/4	38	8.8
29/4	37	9.2
31/4	36	9.6
33/4	35	10.0
35/4	34	10.3
37/4	33	10.5
39/4	32	10.7
41/4	31	10.9

Table 2. Gain and included angle for V-beams.

Conclusion

This article has described large centerfed antennas where the length of each leg is an odd number of quarter wavelengths. Multiband use of a single antenna is possible by a judicious choice of leg length, and low-standing wave ratios are achieved by placing a 4:1 balun at the feedpoint. These large antennas show gain over a normal dipole and may be oriented in either straight-line or V-beam configuration. ■

Acknowledgement

Formulas and tables in this article were taken from *73 Dipole and Long-Wire Antennas* by Ed Noll W3FQJ.

Leg Length in Wavelengths	Leg Length in Feet (f in MHz)
45/4	11070/f
47/4	11562/f
49/4	12054/f
51/4	12546/f
53/4	13038/f
55/4	13530/f
57/4	14022/f
59/4	14514/f
61/4	15006/f
63/4	15498/f
65/4	15990/f
67/4	16482/f
69/4	16974/f
71/4	17466/f
73/4	17958/f
75/4	18450/f
77/4	18942/f
79/4	19434/f
81/4	19926/f
83/4	20418/f
85/4	20910/f
87/4	21402/f

Table 3. Leg lengths for very long antennas.

This NEW MFJ Versa Tuner II . . .

has SWR and dual range wattmeter, antenna switch, efficient airwound inductor, built in balun. Up to 300 watts RF output. Matches everything from 1.8 thru 30 MHz: dipoles, inverted vees, random wires, verticals, mobile whips, beams, balanced lines, coax lines.

MFJ LOWER PRICES!

NEW, IMPROVED MFJ-941B HAS . . .
- More inductance for wider matching range
- More flexible antenna switch
- More sensitive meter for SWR measurements down to 5 watts output

NEW LOWER PRICE

$79.95

Transmitter matching capacitor. 208 pf. 1000 volt spacing.

Sets power range, 300 and 30 watts. Pull for SWR.

Meter reads SWR and RF watts in 2 ranges.

Efficient airwound inductor gives more watts out and less losses.

Antenna matching capacitor. 208 pf. 1000 volt spacing.

Only MFJ gives you this MFJ-941B Versa Tuner II with all these features at this price:

A SWR and dual range wattmeter (300 and 30 watts full scale) lets you measure RF power output for simplified tuning.

An antenna switch lets you select 2 coax lines direct or thru tuner, random wire/balanced line, and tuner bypass for dummy load.

A new efficient airwound inductor (12 positions) gives you less losses than a tapped toroid for more watts out.

A 1:4 balun for balanced lines. 1000 volt capacitor spacing. Mounting brackets for mobile installations (not shown).

With the NEW MFJ Versa Tuner II you can run your full transceiver power output — up to 300 watts RF power output — and match your transmitter to **any** feedline from 160 thru 10 Meters whether you have coax cable, balanced line, or random wire.

ANTENNA SWITCH lets you select 2 coax lines direct or thru tuner, wire/balanced line, dummy load.

You can tune out the SWR on your dipole, inverted vee, random wire, vertical, mobile whip, beam, quad, or whatever you have.

You can even operate all bands with just one existing antenna. No need to put up separate antennas for each band.

Increase the usable bandwidth of your mobile whip by tuning out the SWR **from inside your car.** Works great with all solid state rigs (like the Atlas) and with all tube type rigs.

It travels well, too. Its ultra compact size 8x2x6 inches fits easily in a small corner of your suitcase.

This beautiful little tuner is housed in a deluxe eggshell white Ten-Tec enclosure with walnut grain sides.

SO-239 coax connectors are provided for transmitter input and coax fed antennas. Quality five way binding posts are used for the balanced line inputs (2), random wire input (1), and ground (1).

NEW 300 WATT MFJ VERSA TUNER II'S: SELECT FEATURES YOU NEED.

NEW MFJ-945 HAS SWR AND DUAL RANGE WATTMETER. NEW LOWER PRICE

$69.95

Same as MFJ-941B but less 6 position antenna switch.

NEW MFJ-944 HAS 6 POSITION ANTENNA SWITCH ON FRONT PANEL. NEW LOWER PRICE

$69.95

Same as MFJ-941B but less SWR/Wattmeter.

NEW MFJ-943 MATCHES ALMOST ANYTHING FROM 1.8 THRU 30 MHz. NEW LOWER PRICE

$59.95

Same as MFJ-941B, less SWR/Wattmeter, antenna switch, mounting bracket. 7x2x6 in.

ULTRA COMPACT 200 WATT VERSA TUNERS FOR ALL YOUR NEEDS.

MFJ-901 VERSA TUNER MATCHES ANYTHING, 1.8 THRU 30 MHz. NEW LOWER PRICE

$49.95

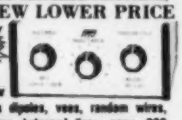

Efficient 12 position air inductor for more watts out. Matches dipoles, vees, random wires, verticals, mobile whips, beams, balanced lines, coax. 200 watts RF, 1:4 balun, 5x2x6 in.

MFJ-900 ECONO TUNER MATCHES COAX LINES/RANDOM WIRES. NEW LOWER PRICE

$39.95

Same as MFJ-901 but less balun for balanced lines. Tunes coax lines and random lines.

MFJ-16010 RANDOM WIRE TUNER FOR LONG WIRES. NEW LOWER PRICE

$29.95

1.8 thru 30 MHz. Up to 200 watts RF output. Matches high and low impedances. 12 position inductor. SO-239 connectors. 2x3x4 inches. Matches 25 to 200 ohms at 1.8 MHz. Does not tune coax lines.

For Orders Call toll-free 800-647-1800

M52 **Order any product from MFJ and try it. If not delighted, return within 30 days for a prompt refund (less shipping).**

Order today. Money back if not delighted. One year unconditional guarantee. Add $2.00 shipping/handling.

For technical information, order/repair status, in Mississippi, outside continental USA, call 601-323-5869.

Order By Mail or Call TOLL FREE 800-647-1800 and Charge It On VISA master charge

MFJ ENTERPRISES, INC. P. O. BOX 494 MISSISSIPPI STATE, MISSISSIPPI 39762

Reader Service—see page 211

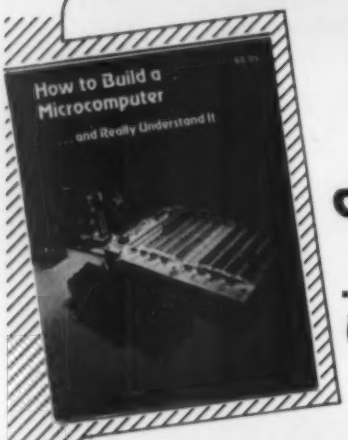

How to Build a Micro-computer

... and Really Understand It

$9.95

- ★ ***Complete circuit board layouts included***
- ★ ***Ready-made boards available***
- ★ ***Uses the popular 6502 chip (same as the KIM, PET, APPLE)***
- ★ ***Uses readily-available parts***
- ★ ***Component kits available***

While considerable information is available on the generalities of how a microcomputer works or how to program a microcomputer, you'll be hard pressed to find information concerning the construction of a single, specific system.

Finally, electronic hobbyists are able to build their own microcomputer system with Sam Creason's book, "How To Build A Microcomputer and Really Understand It." Creason's book is a combination technical manual and programming guide that takes the hobbyist step-by-step through the design construction, testing, and debugging of a complete microcomputing system.

Once your computer has been properly programmed, it can be a powerful tool for use in the amateur radio station. Examples include a CW generator, a digital voltmeter, and a programmable signal generator. This book is must reading for anyone desiring a true understanding of small computer systems.

To order, write 73 Magazine Mail-Order Dept. #S95 Peterborough NH 03458. Include name and address and $10.95 ($9.95 plus $1.00 shipping and handling).

☐ **Please rush my copy of "How To Build A Microcomputer" (BK7325)**

Name _____

Address _____ Apt#____

City_____State_____Zip_____

☐ I enclose $10.95 ($9.95 plus $1.00 shipping and handling)

☐ Bill my credit card

☐ Visa ☐ Master Charge

Credit Card#_____Exp. date_____

Signature _____

73 Magazine Mail-Order Dept. #S95
Peterborough NH 03458

MY COMPETITION KNOWS ME, YOU SHOULD TOO.

COMPLETE KITS: CONSISTING OF EVERY ESSENTIAL PART NEEDED TO MAKE YOUR COUNTER COMPLETE. **HAL-600A** 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 600 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY ±.001%, UTILIZES 10-MHz CRYSTAL 5 PPM.
COMPLETE KIT.....$129

HAL-300A 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 300 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY ±.001%, UTILIZES 10-MHz CRYSTAL 5 PPM.
COMPLETE KIT.....$109

HAL-50A 8-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 50 MHz OR BETTER. AUTOMATIC DECIMAL POINT, ZERO SUPPRESSION UPON DEMAND. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY INPUT, AND ONE ON PANEL FOR USE WITH ANY INTERNALLY MOUNTED HALTRONIX PRE-SCALER FOR WHICH PROVISIONS HAVE ALREADY BEEN MADE. 1.0 SEC AND .1 SEC TIME GATES. ACCURACY ±.001%. UTILIZES 10-MHz CRYSTAL 5 PPM.
COMPLETE KIT.....$109

PRE-SCALER KITS

HAL 300 PRE.....$19.95
(Pre-drilled G10 board and all components)

HAL 300 A/PRE.....$24.95
(Same as above with preamp)

HAL 600 PRE.....$34.95
(Pre-drilled G10 board and all components)

HAL 600 A/PRE.....$39.95
(Same as above but with preamp)

TOUCH TONE DECODER KIT

HIGHLY STABLE DECODER KIT. COMES WITH 2 SIDED, PLATED THRU AND SOLDER FLOWED G-10 PC BOARD, 7-567's, 2-7402, AND ALL ELECTRONIC COMPONENTS. BOARD MEASURES 3½ x 5½ INCHES. HAS 12 LINES OUT. ONLY **$39.95**

DELUXE 12-BUTTON TOUCHTONE ENCODER KIT utilizing the new ICM 7206 chip. Provides both VISUAL AND AUDIO indications! Comes with its own two-tone anodized aluminum cabinet. Measures only 2 3/4 x 3 3/4". Complete with Touch-Tone pad, board, crystal, chip and all necessary components to finish the kit.
PRICED AT.....$29.95

For those who wish to mount the encoder in a hand-held unit, the PC board measures only 9/16" x 1 3/4". This partial kit with PC board, crystal, chip and components.
PRICED AT.....$14.95

ACCUKEYER—MEMORY OPTION KIT THIS ACCUKEYER MEMORY KIT PROVIDES A SIMPLE, LOW COST METHOD OF ADDING MEMORY CAPABILITY TO THE WB4VVF ACCUKEYER. WHILE DESIGNED FOR DIRECT ATTACHMENT TO THE ABOVE ACCUKEYER, IT CAN ALSO BE ATTACHED TO ANY STANDARD ACCUKEYER BOARD WITH LITTLE DIFFICULTY. **$16.95**

ACCUKEYER (KIT) THIS ACCUKEYER IS A REVISED VERSION OF THE VERY POPULAR WB4VVF ACCUKEYER ORIGINALLY DESCRIBED BY JAMES GARRETT, IN QST MAGAZINE AND THE 1975 RADIO AMATEURS HANDBOOK. **$16.95**

ACCUKEYER—MEMORY OPTION KIT—TOGETHER ONLY **$32.00**

6-DIGIT CLOCK • 12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 6 FND 359 READOUTS, 13 TRANSISTORS, 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSH-BUTTON SWITCHES, POWER TRANSFORMER AND INSTRUCTIONS.
DON'T BE FOOLED BY PARTIAL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA.
PRICED AT.....$12.95

CLOCK CASE Available and will fit any one of the above clocks. Regular Price . . . $6.50 **But Only $4.50 when bought with clock**

SIX-DIGIT ALARM CLOCK KIT for home, camper, RV, or field-day use. Operates on 12-volt AC or DC, and has its own 60-Hz time base on the board. Complete with all electronic components and two-piece, pre-drilled PC boards. Board size 4" x 3". Complete with speaker and switches. If operated on DC, there is nothing more to buy.*
PRICED AT.....$16.95
Twelve-volt AC line cord for those who wish to operate the clock from 110-volt AC. **$2.95**

SHIPPING INFORMATION
ORDERS OVER $15.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN $15.00 PLEASE INCLUDE ADDITIONAL $1.00 FOR HANDLING AND MAILING CHARGES. SEND SASE FOR FREE FLYER.

"HAL" HAROLD C. NOWLAND
W8ZXH

HAL-TRONIX H24
P. O. BOX 1101
SOUTHGATE, MICH. 48195
PHONE (313) 285-1782

Reader Service—see page 211

Microcomputer Interfacing

from page 20

low cost IC, $8; SHM-CM, general purpose, ± 12 V, $89.

Hybrid Systems Corporation, Bedford, Massachusetts 01730 —SH703, low cost, $22.

Intersil, Inc., Cupertino, California 95014—IH5110, low cost IC, $9.

National Semiconductor Corporation, Santa Clara, California 95051—LF-398, low cost IC, $5.

Teledyne Philbrick, Dedham, Massachusetts 02026—Model 4853, high speed, $125.

Prices of the above S/H devices are subject to change without notice. However, keep in mind that the general price trend is down, as is true for almost all semiconductor devices.

References

1. Titus, J. A., *Microcomputer Analog-Digital Conversion Devices*, E&L Instruments, Inc., Derby, Connecticut 06418, 1977.
2. *LF-398 Data Sheet*, National Semiconductor Corporation, Santa Clara, California 95051, 1976.
3. Sheingold, D. H., *Analog-Digital Conversion Handbook*, Analog Devices, Inc., Norwood, Massachusetts 02062, 1972.

Corrections

It has been called to our attention that the breadboard shown on page 51 of our June, 1979, issue is indeed Continental Specialties Corporation's Model EXP-300 Experimentor Proto-Board®.

John C. Burnett
Managing Editor

In my article "Build the $80 Wonder" (November, 1978), there was an error in the input amplifier shown in Fig. 6. The corrected portion is shown below.

Howard M. Berlin W3HB
Newark DE

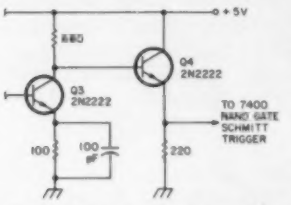

Fig. 6 (partial), "Build the $80 Wonder."

In my article "12 Volts, 5 Amps, 3 Terminals" (April, 1979), there was an error in the schematic—the electrolytic cap should be somewhere in the range of 2500-4000 uF at 30 volts or so, not 500 uF at 1000 volts. My power supply has two 100-uF, 35-volt caps in parallel, but it should be emphasized that this was a commercially-built supply (minus the regulator which is what the article was intended to introduce). The designer of the supply took a shortcut in the cap's value in order to retain the small size of the supply. I am recommending the 2500-4000 uF, 35-volt electrolytics to those who have been writing, if they can get along with the extra space that is required.

Again, the intended purpose of the article was to introduce a very effective way to obtain regulation of a power supply with a minimum of external parts (one!). If anyone was to duplicate the circuit shown, it does work, and will make an effective supply at a small cost as long as the cap's value is changed as noted here. Any "computer-grade" electrolytic with a rating of 30 volts or more—and many are advertised at bargain prices in *73*—should work just fine.

Readers might also be interested in knowing that one supplier of the chip, Tri-Tek, has just dropped their price for the 78H12 to $6.50. Fairchild has also introduced several other new regulator chips that might prove of value.

Gary H. Toncre WA4FYZ
Miami FL

Ham Help

I am looking for a schematic of a device which would allow me to tune in a CW signal and have the received Morse characters translated into Baudot and ASCII. Once translated, the signal could produce a teletype™ copy of the CW being received.

There did exist the Converter Shift Register Group AN/UGA-3A (designed and built in the 1960s) which translated CW to Baudot. This unit used discrete components and weighed some 110 lbs. Its CW speed capability range was 10-110 wpm, machine-sent. Two-level Morse-keyed dc, or Morse-keyed audio signal inputs were accepted and translated to 5-level Baudot, and then to TTY copy.

I would appreciate hearing from anyone who may have an arrangement such as this. Thank you.

C. H. Wiedeman K4KOE
204 Anne Burras
Newport News VA 23606

Would anyone who has had problems with the Sigma XR3000 linear please write to me and state the trouble and where they obtained parts?

Jack W. Greenwood WB7QDN
Box 249
Wolf Point MT 59201

I am looking for any modifications to the Collins R-388, especially in the area of a product detector.

W. Cooledge, Jr. W1IOO
15 Newport Dr.
Westford MA 01886

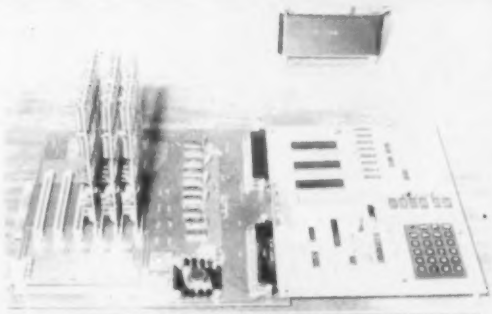

SPECIAL PACKAGE DEAL!!!
KIM-1, power supply, 2 excellent books: "The First Book of KIM" and Programming a Microcomputer: 6502". This is probably the best tutorial package on microcomputers available. Includes listings of over 50 utility and game programs! Special Package: KIM, with 3 manuals power supply, plus both books listed above, EVERYTHING NEEDED TO LEARN AND USE AN ADVANCED MICROCOMPUTER List Price: $238.00, Now save over 10%–$199.00!

call toll free 1-800-633-8727

A COMPUTER FOR HAM RADIO APPLICATIONS

Articles in "73" have featured the KIM-1 in RTTY, OSCAR, and high speed CW applications.

Features include:

-Completely self contained with cassette tape interface, 1K RAM, 2K ROM monitor, 400 pages documentation.
-(K)eyboard (I)uput (M)onitor (KIM) allows entry, debug, and execution of programs using the 23 key keypad and 6 digit LED display, OR use a standard ASCII terminal with KIM's 20 ma. current loop interface. Up to 9600 baud.
-Powerful 6502 microprocessor, now second sourced by 4 manufacturers (plus Commodore/Mos). 13 addressing modes and advanced architecture result in an efficient, fast, and easy to program computer.
-15 programmable I/O lines and 2 programmable interval times allow the KIM to execute complex "real-time" programs with a minimum of programming overhead. Radio teletype, and other "timing sensitive" applications are simple.
-Expand to 64K RAM, etc. via the 22/44 pin expansion bus.
-Expand with a full size or minifloppy disk from HDE (write). The KIM bus is now supported by numerous manufacturers including Rockwell Int'l, Synertek, RNB, HDE the Computerist.
-Well proven design—over 40,000 in the field. KIM-1 with documentation—$169.00. Power supply, 5V and 12V, 8V at 4 amps, 16V at 1 amp —$40.00: KIM-4 motherboard $85.00. HDE 8K RAM $169.00, 3 for $465.00!: HDE proto board $49.50.

Master Charge/Visa: Free shipping on orders prepaid with cashier's check.
PLAINSMAN MICRO SYSTEM: P.O. Box 1712: Auburn, Al. 36830
ALL ITEMS ASSEMBLED/TESTED WARRANTEED FOR AT LEAST 90 DAYS

in Alabama call (205) 745-7735

Microcomputer RTTY . . . a Software TU

—use your 8080 and very little else

Count frequencies, too.

Albert S. Woodhull N1AW
Enfield Road, RFD 2
Pelham MA 01002

Microprocessors are not just super calculators. They are general-purpose electronic circuits waiting only for programs to transform them into specialized devices. In this article I will describe how a computer can be used as a frequency counter, and I will show how the counting program can become the basis of a microprocessor-centered RTTY terminal unit. I am writing this also to show how easy it can be to replace hardware with software. Applications such as the one I will describe require only a fraction of the amount of memory that is needed to do calculations with a high-level language such as BASIC. And, for the experimenter, replacing gadgets with programs has another great advantage. No longer do you need to worry about the condition of your gear if a lengthy equipment modification doesn't work. Rewind your tape cassette and you can have the old version up and running in a few seconds.

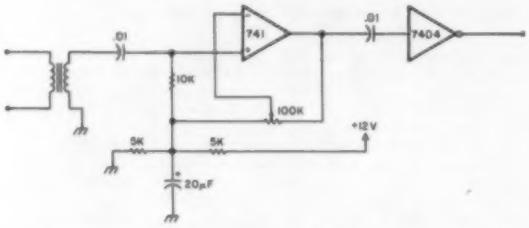

Fig. 1. Input interface. The pot is used to adjust the gain of the 741 amplifier until it drives the 7404 TTL inverter to the point of producing a clean square wave output of the same frequency as the input. 60- or 120-cycle hum is the villain that can make this difficult; the transformer may not always be necessary, but sometimes eliminating the common ground connection gets rid of hum.

Counting Frequencies With a Computer

The computer works with ones and zeros; counting is a very simple task for it. A little bit of external hardware help is needed, however, to get the signal from the outside world into the form the computer requires. Fig. 1 shows an adequate arrangement. An operational amplifier circuit boosts the input signal to a level adequate to drive a TTL inverter. The resulting square wave is applied to one bit of an input port of the computer. On most systems, the other seven bits can just be left floating, but, if you are picky, you can tie them to either ground or +5 volts. On my home-brew computer, I have a number of input and output ports that are implemented as single bits for applications like this. The transformer shown may not be necessary, but may help in keeping 60-cycle interference out of the system.

The easiest way to measure audio frequencies is to time the duration of a half cycle. Fig. 2 shows a flowchart, and Fig. 3 shows an 8080A program to do this. Two registers are used, one to hold the previous input, and one to count up the number of times the program loops between changes in the input. Suppose, at the starting time, the input signal from the inverter is in the 0 phase of the square wave. The unused seven bits will be read as ones, and 11111110 will be stored. Until the input changes to the 1 phase, the program will loop and the counter will count. Eventually, a time will come when the input is read as 11111111. When this happens, the count will be displayed and a new count started. If desired, a bit of programming could be done to calculate the frequency in decimal units from the binary representation of the duration of a half cycle, but, for many purposes, it is adequate to know what pattern on the LED display corresponds to a desired frequency.

For a typical 8080A system with a 500-ns clock, the instruction loop just

discussed will require 14.5 μsec. If you were trying to measure the tones from an AFSK generator, this counter would produce a count of 16 (00010000 in binary) for a 2125-Hz input or a count of 15 (00001111) for a 2295-Hz input. That might be good for some purposes, but it obviously is not very accurate. The way to make a timer more accurate is to time longer intervals. The counting time can be doubled by timing whole cycles of the input instead of half cycles. This also will eliminate inaccuracy due to asymmetry in the square wave input. For the 8080A program illustrated, this can be accomplished by changing the JZ (jump on zero) instruction to JNC (jump on no carry). Following a comparison operation, the zero flag is set when the numbers compared are equal, so in the original version of the program, the loop is broken whenever the input changes from 1 to 0 or from 0 to 1. The carry flag is set when the number in the accumulator register is less than the comparison number. Thus, by using the no-carry condition to stay in the loop, the timer ignores transitions from 0 to 1 and the count accumulates until a transition from 1 to 0 occurs.

A second way to increase accuracy is to put the basic program inside a larger loop that counts down a predetermined number of cycles of the input signal. Figs. 4 and 5 show the flowchart and program for this approach. The inner loop again takes 14.5 μsec, but now the JNC instruction is used to keep the timer going for the entire duration of an audio cycle. The outer loop causes the inner loop to be repeated as many times as the value initially loaded into register D calls for. With this approach, standard AFSK tones in the range of 2000 to 3000 Hz can be measured to the nearest 10 Hz or so. This will suffice for adjusting an AFSK generator or calibrating an oscillator to be used in adjusting a RTTY demodulator. More accuracy yet can be achieved by timing a larger number of cycles and accumulating the count in a 16-bit register pair. Still other software frills could turn the computer into a fancy frequency meter indeed, but that is not my present goal. Instead, I would like to show how the basic timing program can be used to build a radioteletype terminal unit with capabilities not usually found in the simpler analog TU circuits.

The Software Terminal Unit

My home-brew computer decodes audio signals from an audio cassette recorder by means of a simple cycle timer program which is stored in read-only memory. Compared to the problems of decoding over-the-air RTTY signals, it is trivial to decode a tape. A few preliminary experiments showed me that the simple frequency measuring routines could work on clear and strong signals, so I set out to define the additional requirements for RTTY.

Essential features for RTTY are some kind of filtering to minimize the effects of interferences and some kind of tuning indicator. Another feature, not necessary, but very desirable, is a squelch or mark-hold provision to keep the printer from running wild when a useful signal is not present. Finally, an easy way of throwing in a locally-generated line feed or carriage return can sometimes prevent loss of print. Doing all this in software is easy.

The flowchart of Fig. 6 shows how all these provisions are included. Entry and exit from the program are through a control section which allows a local ASCII keyboard to direct operations. Next, a cycle timer section determines the frequency of the incoming audio. Decision routines cause execution to branch, first to display the current state on a tuning indicator, and then to take appropriate action. A "noise counter" disables the printer whenever the signal-to-noise ratio becomes lower than the preprogrammed acceptable limit. A "signal counter" takes over the functions of a post-detection low-pass filter, and the processed data then drives the printer magnet through an output port and very simple interface circuitry.

The details can be seen in the program listing. In my system, a surplus 8-bit parallel-output ASCII keyboard has its data lines connected to one input port and its strobe line connected to another. The control section of the program first examines the strobe signal and skips to the frequency-measurement section if no key is depressed. If a key is pressed, a subroutine in my monitor program is called which converts the ASCII to Baudot and drives the printer. The subroutine checks for control characters and returns immediately when one is encountered. The TU program then checks for ↑B (control B) or ↑E characters, which cause exits to either a RTTY transmit routine or the control level of my monitor program. ↑T, ↑N, or ↑R characters are stored for later reference; they signify Tune (no printing), Normal (low tone is mark), and Reverse (high tone is mark).

The frequency measurement portion of the pro-

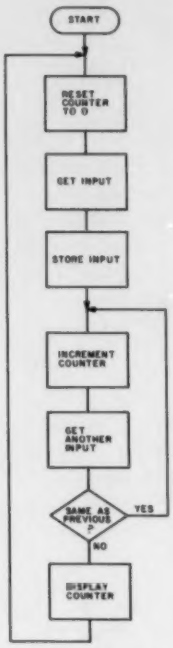

Fig. 2. Flowchart for frequency measurement by cycle timing. Note that this simple version times the duration of a half cycle of input.

```
START   MVI C 00     reset counter
        IN AUDIO     get input
        MOV B,A      store it
LOOP    INR C        increment counter
        IN AUDIO     get new input
        CMP B        compare with first input
        JZ LOOP      if same repeat cycle
        MOV A,C      otherwise display count
        OUT DISPLAY
        JMP START    and do it all again
```

Fig. 3. An 8080 program that times half cycles of audio according to the flowchart of Fig. 2. The DISPLAY output port can be a row of LEDs or 7-segment displays which show the count in octal or hexadecimal. The meaning of the count in real-time units will depend on the clock frequency of the processor.

gram works like the routines described in the first part of this article, with two refinements. It doesn't matter that a simple continuously-cycling routine gives a short count on its first cycle. For RTTY decoding, an accurate count is needed the first time. This problem is solved by an extra loop which causes the computer to wait for the cycle in progress to finish before the following five cycles of audio are timed. The other refinement is a more complicated nesting of the inner and outer loops which keeps the execution time constant regardless of which branch is followed. This is aided by inserting a "nonsense instruction" (MOV B,B) into one branch to compensate for the execution time of the DCR C instruction in the other branch.

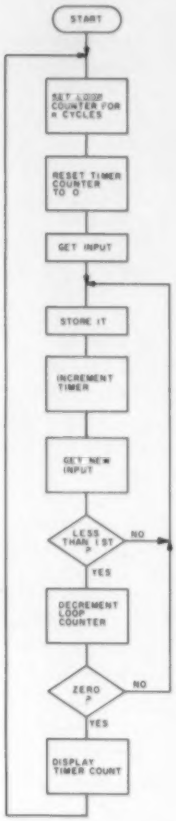

Fig. 4. Flowchart for an accurate frequency-measurement program that times the duration of n whole cycles of the input signal.

All the information needed to accurately tune in a RTTY station and drive the printer is in the output of the frequency measurement section of the program. With analog circuitry, at this point one would use a comparator to decide whether a voltage was above or below a criterion level. Having a count, not a voltage, and having the power of the microprocessor makes possible a six-way decision. Try setting up comparators to do that at the output of a phase-locked loop! I use the various possible outcomes of this six-way decision to light up a row of LEDs on the front panel of my computer. As the receiver is tuned across a signal, the light appears to move from left to right as the audio tone goes from low to high. Fig. 7 illustrates the patterns observed. The effectiveness of the technique is due to the criteria for the comparisons having been chosen in such a way that a clear indication that the signal is not tuned in exactly on center is given before the error is great enough to cause inaccurate printing. With practice, it is also easy to spot shifts which are too wide, or stations transmitting "upside down."

The mark-hold and low-pass filtering techniques I use are also examples of simple software implementation of functions that would be relatively complex with analog circuits. Each of these features uses a counter. The mark-hold is controlled by the noise counter. This register is incremented when a tone too high or too low to be a valid RTTY signal is encountered. Valid signals decrement the same counter. Limits are placed on the maximum and minimum values the noise counter can hold, and, after each frequency measurement, the noise-counter value is compared with an intermediate criterion.

When the criterion is exceeded, operation of the printer is suppressed. With the values given in the listing, printing will proceed when a good signal is decoded one-third of the time. When the signal drops out, the printer is silenced almost immediately, but a fraction of a second of steady mark tone at the beginning of a transmission immediately enables the printer.

The low-pass filter also uses a counter, which I call the signal counter. Mark signals increment this counter and space signals decrement it. The counter is limited to a minimum value of zero and a maximum value of seven. A mark signal is sent to the printer when the value is four or higher; otherwise, a space signal is generated. Thus, at any time, the printer is given a signal corresponding to the majority of the eight previous samples of audio from the receiver. Without some

Constant	Locations In Assembled Listing
CRIT1	044A
CRIT2	044F
CRIT3	0454
CRIT4	0459
CRIT5	045E
KBDSTB	0401
KBD	0408
KBDW	04E1
PRINT	040A 04E8
MONITOR	0429
AUDIO	0430 0433 043A
PRINTER	0479 04CE 04DC
LEDDISP	0468 0480 0487 0499 04A0

Table 1. The above locations will probably have to be changed to make the TU program run on a different machine. The values for CRIT1, CRIT2, CRIT3, CRIT4, and CRIT5 will depend on the clock frequency of the computer being used. The other values listed are port numbers or, in the case of PRINT and MONITOR, routines in the author's ROM monitor.

```
START   MVI D,n      set loop counter
        MVI C,O      reset timer counter
        IN AUDIO     get input
LOOP    MOV B,A      store it
        INR C        increment timer
        IN AUDIO     get new input
        CMP B        compare with first input
        JNC LOOP     if equal to or greater than first repeat cycle
        DCR D        otherwise decrement cycle counter
        JNZ LOOP     and continue timing another cycle
        MOV A,C      when done, retrieve the total count and show it
        OUT DISPLAY
        JMP START    and do it all again
```

Fig. 5. The 8080 program corresponding to the flowchart of Fig. 4. The count indicates the duration of n complete cycles of the audio input signal.

form of filtering of this sort, the information in 80% of the received signal is lost, since the printer itself samples only 20% of each bit.

The last part of the listing isn't really part of the RTTY receiving routine at all. This is a simple loop that enables me to use the ASCII keyboard for transmitting RTTY. It includes a test to recognize a ↑C character as a command to leave the transmit routine and return to the receive routine. It is not a misprint that the keyboard is called by a different port number here than that used in the control section of the program. I decode two different port numbers for my keyboard; the one used here initiates a WAIT state in the 8080A which is terminated by the falling edge of the keyboard strobe signal. This allows me to simplify the coding used for getting keyboard input in cases like this.

It would be cruel to present a program listing of this sort without pointing out the parts of the program that might need to be changed to make it run on another system. Table 1 lists the instructions which are unique to my own computer. For the most part, patching the program will require changing only I/O port assignments and relocating addresses, but it should be noted that a major and crucial difference between my computer and most others is the clock frequency. My junk-box crystal gives me a clock period of 694 ns instead of the usual 500 ns. The various criteria constants will need to be reevaluated to suit the timing of another system. This can be done experimentally by using a calibrated audio oscillator (calibrate it with the timer progam!) and trying different values for each criterion, using the tuning indicator to check results. For example, CRITERION3 should be a value that causes the low space and high mark lights to blink as the audio input is rocked around 2210 Hz.

Interfacing and Operation

A few pieces of hardware external to the computer are needed, of course. At the input, a circuit such as the one already described in Fig. 1 is needed to convert the receiver audio to digital levels. It will help if a bit of audio filtering precedes this. Fig. 8 shows a simple filter which gives good results when followed by the recommended 10k-Ohm load. The .05-uF capacitor should be chosen to give a peak at around 2200 Hz. The last external item

Program listing for RTTY TU.

```
TYPE RTTYTU.PRN
                        ;
                        ;
                        ;
                        ;                       DIGITAL RTTY TERMINAL UNIT
                        ;
                        ;THIS IS A PROGRAM TO DECODE AFSK SIGNALS AND DRIVE A BAUDOT PRINTER
                        ;WRITTEN FOR RIAW'S 8080A SYSTEM WHICH USES A 694 NSEC CLOCK.  OTHER
                        ;SYSTEMS WILL REQUIRE CHANGES OF THE TIMING BYTES.  THE PROGRAM
                        ;IS BASED ON NOMINAL AUDIO FREQUENCIES OF 2125 HZ FOR MARK AND 2295
                        ;HZ FOR SPACE.  FOR THIS 170 HZ SHIFT A MAXIMUM MISTUNE OF +/- 85 HZ IS
                        ;PERMISSIBLE.  FREQUENCIES ABOVE 2380 HZ OR BELOW 2040 HZ ARE ACCORD-
                        ;INGLY REJECTED AS INVALID.  OPERATION OF THE PRINTER IS SUPPRESSED BY
                        ;OUTPUTTING A CONTINUOUS MARK LEVEL TO THE MAGNET DRIVER WHEN AN EXCESS-
                        ;IVE PROPORTION OF INCOMING SIGNALS CORRESPOND TO INVALID TONES.  AN AN
                        ;AID TO TUNING PROVISION IS MADE FOR DISPLAY OF THE APPROXIMATE FREQUENCY
                        ;OF THE INCOMING TONE ON A ROW OF LEDS, SO TUNING BECOMES A MATTER OF
                        ;KEEPING THE CENTER OF THE LED ROW ILLUMINATED.  DIGITAL PROCESSING
                        ;ALSO SIMULATES THE EFFECT OF POST-DETECTION LOW PASS FILTERING OF THE
                        ;DRIVING SIGNAL TO THE PRINTER MAGNET.
                        ;THE FOLLOWING PROGRAM REQUIRES LESS THAN 256 BYTES OF MEMORY TO RUN,
                        ;EXCEPT THAT SOME CALLS ARE MADE TO A PRINTER-DRIVER ROUTINE FOR THE
                        ;PURPOSE OF ECHOING THE KEYBOARD THAT CONTROLS EXECUTION.  THIS IS
                        ;NECESSARY ONLY FOR LOCAL OVERRIDE OF INCOMING SIGNALS SO EXTRA CARR-
                        ;IAGE RETURNS OR LINE FEEDS MAY BE INSERTED.
                        ;   WRITTEN 23 MARCH 1978;COPYRIGHT 1978 ALBERT S. WOODHULL
                        ;

0400                    ORG 1024
0003 =          KBDSTB  EQU 3
0005 =          KBD     EQU 5
0020 =          PRINT   EQU 20H
0000 =          MONITOR EQU 0
0001 =          AUDIO   EQU 1
007E =          CRIT1   EQU 7EH
0040 =          CRIT2   EQU 40H
0043 =          CRIT3   EQU 43H
0046 =          CRIT4   EQU 46H
0048 =          CRIT5   EQU 48H
0060 =          NOISEMAX EQU 60H
0040 =          HOLDCRIT EQU 40H
0011 =          PRINTER EQU 11H
0000 =          LEDDISP EQU 0               ;FRONT PANEL LEDS
0000 =          KBDW    EQU 0
                ;CONTROL ROUTINES TO SAMPLE KEYBOARD
                ;
0400 DB03       RECEIVE IN KBDSTB           ;CHECK KEYBOARD STROBE
0402 E601               ANI 1
0404 CA2904             JZ TIMER            ;SKIP TO TIMER IF KEYBOARD INACTIVE
0407 DB05               IN KBD              ;LOOK AT ASCII KEYBOARD
0409 CD2000             CALL PRINT          ;ECHO THE INPUT BY ROUTINE IN MONITOR
040C FE0E               CPI 0EH             ;WAS IT "N" (CONTROL, N=NORMAL MODE)
040E CA1E04             JZ STOW
0411 FE13               CPI 13H             ;WAS IT "R? (REVERSED MODE)
0413 CA1E04             JZ STOW
0416 FE14               CPI 14H             ;WAS IT "T? (TUNE MODE, NO PRINTING)
0418 CA1E04             JZ STOW
041B C32104             JMP SKIPSTOW
041E 32EE04     STOW    STA FORMAT
0421 FE02       SKIPSTOW CPI 2    ;WAS IT "B? (TRANSMIT MODE)
0423 CA6004             JZ TRANSMIT
0426 FE05               CPI 5               ;WAS IT "E? (EXIT TO MONITOR)
0428 CA0000             JZ MONITOR
                ;
                ;TIMER ROUTINES TO DETERMINE FREQUENCY OF INCOMING AUDIO SIGNAL
                ;
042B 0E00       TIMER   MVI C,0             ;PRELOAD CYCLE COUNTER
042D 1600               MVI D,0             ;ZERO TIMER
042F DB01               IN AUDIO            ;LOOK AT AUDIO INPUT
0431 5F         LOOP1   MOV E,A             ;STOW INPUT IN REGISTER E
0432 DB01               IN AUDIO            ;GET ANOTHER SAMPLE OF AUDIO
0434 BB                 CMP E               ;SEE IF THERE WAS A CHANGE
0435 023104             JNC LOOP1           ;IF NOT KEEP LOOKING
                ;
0438 5F         LOOP2   MOV E,A             ;STOW LATEST INPUT
0439 DB01               IN AUDIO            ; GET A NEW SAMPLE
043B 14                 INR D               ;INCREMENT THE TIMER
043C BB                 CMP E               ;LOOK FOR END OF AUDIO CYCLE
043D DA4404             JC CYCLECNT         ;CARRY FLAG WILL BE SET BY CHANGE FROM 1 TO 0
0440 90                 SUB B,B             ;IF NO CHANGE KILL DONE TIME
0441 C33804             JMP LOOP2           ;THEN LOOK AGAIN
                ;
0444 0D         CYCLECNT DCR C              ;DECREMENT CYCLE COUNTER
0445 C23804             JNZ LOOP2           ;AND KEEP ON TIMING UNTIL 5 CYCLES TIMED
                ;
                ;CRITERION ROUTINES DECIDE WHICH OF SIX POSSIBILITIES THE INCOMING AUDIO
                ;REPRESENTS: TOO HIGH, HIGH SPACE TONE, LOW SPACE TONE, HIGH MARK TONE,
                ;LOW MARK TONE, OR TOO LOW
                ;
0448 7A                 MOV A,D             ;GET COUNT FROM TIMER
0449 FE7E               CPI CRIT1           ;WAS FREQUENCY ABOVE 2380 HZ?
044B DA4504             JC INVHI            ;IF SO IT IS INVALID, TOO HIGH
044E FE40               CPI CRIT2           ;WAS FREQUENCY ABOVE 2330 HZ?
0450 DA9404             JC SPHI             ;HIGH, BUT IN RANGE VALID AS SPACE TONE
0453 FE43               CPI CRIT3           ;WAS IT ABOVE 2210 HZ?
0455 DA9504             JC SPLO             ;LOW SPACE TONE, OK
0458 FE46               CPI CRIT4           ;WAS IT ABOVE 2085 HZ?
045A DA8404             JC MKHI             ;HIGH END OF MARK TONE RANGE
045D FE48               CPI CRIT5           ;WAS IT ABOVE 2040 HZ?
045F DA7504             JC MKLO             ;LOW MARK TONE
                ;
                ;IF NO JUMP TAKEN FROM CRITERION ROUTINES THIS POINT IS REACHED WITH AN
                ;INVALID LOW TONE REPRESENTED BY THE DATA IN THE ACCUMULATOR
                ;
                ;FOLLOWING GIVES VISIBLE DISPLAY OF INVALID TONES AND CHECKS TO SEE IF
                ;PRINTER SHOULD BE DISABLED TO PREVENT GARBAGE PRINTING, THEN DOES SO IF
                ;REQUIRED
                ;
                        MVI A,0CH           ;PREPARE VISIBLE SIGNAL FOR TONE TOO LOW
                        JMP INVDISPLAY
0462 C36704             
0465 3E03       INVHI   MVI A,3H            ;PREPARE VISIBLE SIGNAL FOR TONE TOO HIGH
0467 D300       INVDISPLAY OUT LEDDISP      ;SHOW IT ON FRONT PANEL LEDS
0469 24                 INR H               ;INCREMENT NOISE COUNTER
046A 7C                 MOV A,H
046B FE60               CPI NOISEMAX        ;CHECK AGAINST MAX VALUE PERMITTED
046D DA7204             JC SKIPRESET        ;IF OK SKIP RESET
0470 263F       RESET   MVI H,NOISEMAX-1
0472 FE40       SKIPRESET CPI HOLDCRIT      ;ALSO COMPARE WITH MARKHOLD CRITERION
0474 D40004             JC RECEIVE          ;JUST IGNORE AND START OVER IF BELOW CRITERION
0477 AF                 XRA A               ;OTHERWISE SET ACCUMULATOR TO ZERO
0478 D311               OUT PRINTER         ;AND OUTPUT TO PRINTER DRIVER A LOW LEVEL
047A C30004             JMP RECEIVE         ;THEN START OVER
                ;
                ;WHEN VALID TONES RECEIVED EXECUTION TRANSFERS TO ONE OF THE
                ;FOLLOWING ROUTINES WHICH FIRST DISPLAY TONE RECEIVED THEN INCREMENT OR
                ;DECREMENT THE SIGCOUNTER.  THE SIGCOUNTER IS PREVENTED FROM OVERFLOWING
                ;OR UNDERFLOWING BEFORE THE NEW VALUE IS STORED.
                ;
047D 3E20       MKLO    MVI A,20H           ;DISPLAY LOW MARK SIGNAL
047F D300               OUT LEDDISP         ;ON FRONT PANEL LEDS
0481 C38804             JMP MARKCNT
0484 3E10       MKHI    MVI A,10H           ;DISPLAY HIGH MARK SIGNAL
0486 D300               OUT LEDDISP         ;ON FRONT PANEL LEDS
0488 3A0E04     MARKCNT LDA SIGCNTR         ;GET THE SIGCOUNTER
048B 3C                 INR A               ;INCREMENT IT
048C FE00               CPI 0H              ;BUT KEEP IT BELOW 0
048E C29404             JNZ CNTSTORE        ;PUT IT BACK IF NOT OVERFLOWED
0491 3E07               MVI A,7H            ;OTHERWISE RESET IT
0493 C39404             JMP CNTSTORE        ;THEN PUT IT BACK
0496 3E04       SPHI    MVI A,4H            ;DISPLAY HIGH SPACE SIGNAL
0498 D300               OUT LEDDISP
049A C3A104             JMP SPACECNT
049D 3E08       SPLO    MVI A,8H            ;DISPLAY LOW SPACE SIGNAL
049F D300               OUT LEDDISP
04A1 3A0E04     SPACECNT LDA SIGCNTR        ;GET THE SIGCOUNTER
04A4 3D                 DCR A               ;DECREMENT IT
04A5 F2A904             JP CNTSTORE         ;SKIP NEXT IF VALUE ZERO OR HIGHER
04A8 AF                 XRA A               ;OTHERWISE RESET TO ZERO
04A9 320E04     CNTSTORE STA SIGCNTR        ;PUT THE UPDATED SIGCOUNTER BACK
                ;
                ;THE SIGCOUNTER MUST BE EQUAL TO OR GREATER THAN 4
                ;TO PRINT A MARK, LESS THAN 4 TO PRINT A SPACE.  THIS ACTS AS A LOW PASS
                ;FILTER, PREVENTING SUDDEN CHANGES OF THE DRIVE TO THE PRINTER
                ;
04AC FE04               CPI 04H             ;COMPARE SIGCOUNTER WITH MK/SP CRITERION
04AE DAB504             JC SPACE            ;IF LESS THAN 4 IT IS A SPACE
04B1 AF                 XRA A               ;OTHERWISE IT IS MARK, SET TO OUTPUT
04B2 C3B704             JMP SPACESKIP       ;SO SKIP NEXT
04B5 3E01       SPACE   MVI A,1             ;SET TO OUTPUT SPACE
04B7 47         SPACESKIP MOV B,A           ;PUT SET PRINTDRIVE DATA AGIBE FOR NOW
                ;
                ;BEFORE PRINTING WE CHECK FOR LOW VALUE OF NOISE COUNTER AND NORMAL OR
                ;REVERSED FORMAT
                ;
04B8 25                 DCR H               ;DECREMENT THE NOISE COUNTER
04B9 F2BE04             JP CONT             ;IF ZERO OR ABOVE THEN CONTINUE
04BC 2600               MVI H,0             ;OTHERWISE RESET NOISE COUNTER TO ZERO
04BE 7C         CONT    MOV A,H
04BF FE40               CPI HOLDCRIT        ;COMPARE WITH MARKHOLD CRITERION
04C1 D2CC04             JNC HOLD            ;IF ABOVE CRITERION GO TO HOLD
04C4 3AEE04             LDA FORMAT          ;GET FORMAT INFORMATION
04C7 FE14               CPI 14H             ;IF IT IS "T WE ARE IN TUNE MODE
04C9 C2D204             JNZ PRTDRIVE        ;IF NOT IN TUNE MODE GO ON
04CC AF         HOLD    XRA A               ;OTHERWISE OUTPUT LOW LEVEL TO SILENCE PRINTER
04CD D311               OUT PRINTER
04CF C30004             JMP RECEIVE         ;GO BACK FOR NEW START
04D2 FE13       PRTDRIVE CPI 13H            ;SEE IF FORMAT IS REVERSED
04D4 C2D604             JNZ NORMAL          ;IF NOT GO TO NORMAL
04D7 78                 MOV A,B             ;GET PRINTER DRIVE DATA
04D8 2F                 CMA                 ;COMPLEMENT IT FOR REVERSED MODE
04D9 47                 MOV B,A             ;PUT IT BACK
04DA 78         NORMAL  MOV A,B ;GET DATA
04DB D311               OUT PRINTER         ;AND DRIVE PRINTER
04DD C30004             JMP RECEIVE         ;THEN START OVER AGAIN
                ;
                ;TRANSMIT ROUTINE JUST ECHOES TO PRINTER, AN EXTERNAL SWITCH CAUSES
                ;DATA TO BE ROUTED TO THE FSK MODULATOR.  A CTRL C RETURNS TO
                ;RECEIVE MODE
                ;
04E0 0000       TRANSMIT IN KBDW            ;THIS ALTERNATE ADDRESS FOR KBD WAITS FOR DATA
04E2 FE03               CPI 3H              ;CTL C IS SIGNAL FOR RETURN TO RECEIVE MODE
04E4 CA0004             JZ RECEIVE
04E7 CD2000             CALL PRINT          ;PRINT ROUTINE IN ROM CONVERTS ASCII TO BAUDOT
                                            ;AND DRIVES PRINTER
04EA C3E004             JMP TRANSMIT        ;JUST DO THIS IN A LOOP
04ED            SIGCNTR DS 1                ;STORAGE FOR SIGCOUNTER BYTE
04EE            FORMAT  DS 1                ;STORAGE FOR TUNE/NORMAL/REVERSE FORMAT BYTE
04EF                    END
0>
```

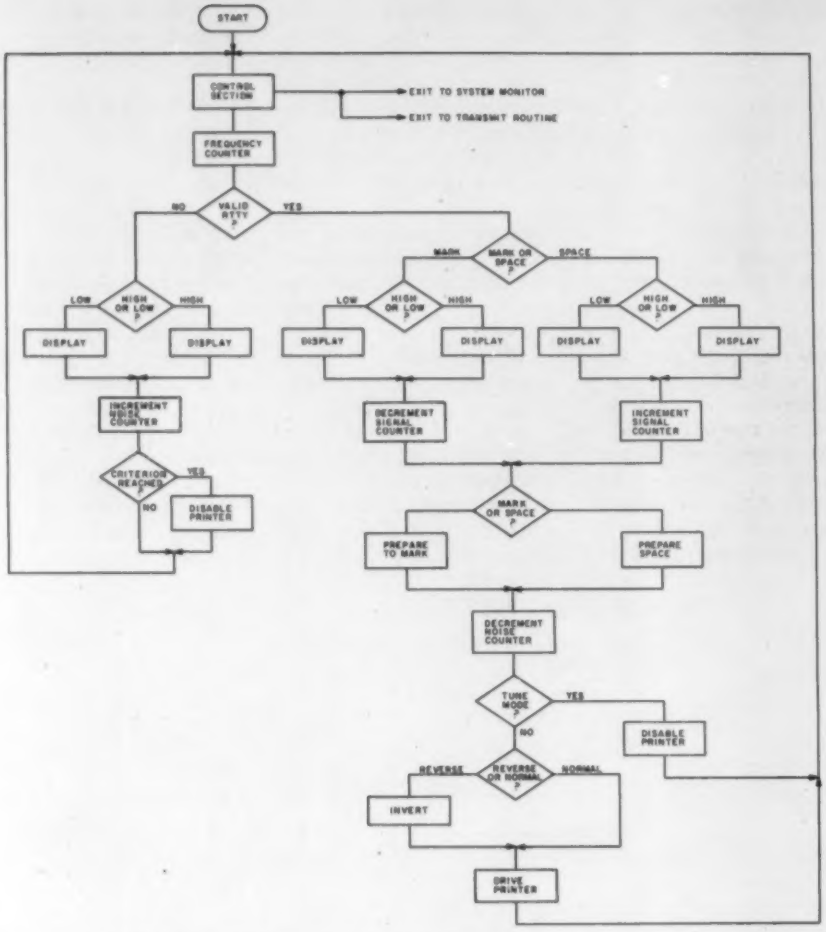

Fig. 6. Flowchart for complete TU program. Note the 6-way partition of the data for driving the tuning display. The noise counter squelches the printer when there is too much noise present. The signal counter acts as a post-detection low-pass filter.

needed is a driver for the teleprinter loop. Fig. 9 shows how I do it. A high-voltage transistor can be used for the switch if one is available. The piggyback circuit shown allows the use of relatively low-voltage "experimenter grab bag" power transistors to switch the high-voltage loop current.

For initial setup, an oscilloscope is convenient to allow determination of the proper audio level. I usually use a simple audio monitor connected right at the computer input port. With this arrangement, I can tell by ear when the audio level is adequate. Tuning is simply a matter of watching the LED display and making corrections when the low mark or high space lights begin to flash.

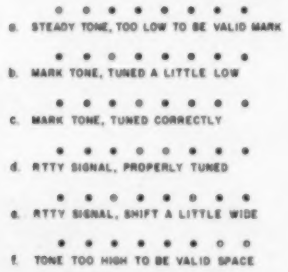
a. STEADY TONE, TOO LOW TO BE VALID MARK
b. MARK TONE, TUNED A LITTLE LOW
c. MARK TONE, TUNED CORRECTLY
d. RTTY SIGNAL, PROPERLY TUNED
e. RTTY SIGNAL, SHIFT A LITTLE WIDE
f. TONE TOO HIGH TO BE VALID SPACE

Fig. 7. Some of the possible combinations seen on the row of LEDs that serve as a tuning indicator. It is very easy to see which way the receiver dial should be tuned to maintain good copy. ○ = on; ● = off.

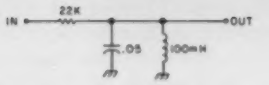

Fig. 8. A simple 2200-Hz filter. A lower-value resistor will widen the passband. Selecting capacitors from the junk box is the easiest way to tune the filter.

As I said at the start, one of the advantages of software is the ease of modification. Just sitting down to type this manuscript made me think of four or five changes, and I just had to try them before getting back to the typewriter. I'm sure anyone who tries this method of copying RTTY will come up with other changes. I intend to do some experimenting with different amounts of averaging in the signal counter and different criteria in the noise counter. It also would be possible to add more control signals to instantly modify the criteria and allow for different shifts. Enough information is extracted to allow the generation of control signals for afc. I would enjoy hearing from readers who undertake some of these improvements. ■

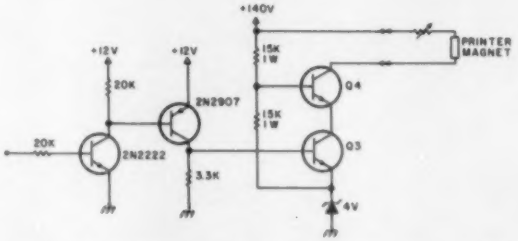

Fig. 9. A TTL-to-60-mA loop interface circuit. Q_3 and Q_4 could be replaced by a single high-voltage transistor. This piggyback circuit is a useful one for switching high voltages with low-voltage transistors. In my station, I use two unmarked TO-220-type power transistors from a "40 for $1.98" special pack.

ENTER A WHOLE NEW WORLD
WITH KILOBAUD MICROCOMPUTING!
. . . AND GET YOUR FIRST ISSUE FREE!

☐ Send me my first issue of **MICROCOMPUTING** free and start my subscription into the new world of **MICROCOMPUTING.**
☐ One year (12 issues) at half the cover price—$15.
☐ I prefer the additional savings of 3 years (36 issues) for $45. I understand that I'll still receive my first issue free.
☐ Payment Enclosed ☐ Bill Me Later
Bill my ☐ Master Charge ☐ BankAmericard ☐ Visa

Card # _____ Exp. Date _____
Signature _____
Name _____
Address _____
City _____ State _____ Zip _____

Offer good in U.S.A. and possessions only. Canadian subscriptions add $2.00 per year.
All foreign, one year only—$23 payable in U.S. currency only.
MICROCOMPUTING Subscription Department ●
P.O. Box 997 ● Farmingdale NY 11737 197B

ENTER A WHOLE NEW WORLD
WITH KILOBAUD MICROCOMPUTING!
. . . AND GET YOUR FIRST ISSUE FREE!

☐ Send me my first issue of **MICROCOMPUTING** free and start my subscription into the new world of **MICROCOMPUTING.**
☐ One year (12 issues) at half the cover price—$15.
☐ I prefer the additional savings of 3 years (36 issues) for $45. I understand that I'll still receive my first issue free.
☐ Payment Enclosed ☐ Bill Me Later
Bill my ☐ Master Charge ☐ BankAmericard ☐ Visa

Card # _____ Exp. Date _____
Signature _____
Name _____
Address _____
City _____ State _____ Zip _____

Offer good in U.S.A. and possessions only. Canadian subscriptions add $2.00 per year.
All foreign, one year only—$23 payable in U.S. currency only.
MICROCOMPUTING Subscription Department ●
P.O. Box 997 ● Farmingdale NY 11737 197B

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY CARD
FIRST CLASS PERMIT NO. 17 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

kilobaud
MICROCOMPUTING T.M.

Subscription Department • Box 997
Farmingdale NY 11737

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY CARD
FIRST CLASS PERMIT NO. 17 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

kilobaud
MICROCOMPUTING T.M.

Subscription Department • Box 997
Farmingdale NY 11737

ENTER A WHOLE NEW WORLD with KILOBAUD MICROCOMPUTING

. . . and get your first issue FREE!

Hardly a day passes without the computer having some effect on millions around the world. The world of microcomputing is changing every day, and there's one way you can keep up to speed in this dynamic field: Subscribe to Kilobaud **MICROCOMPUTING. MICROCOMPUTING** magazine is the forerunner in small business and home computing, loaded with articles on the most popular microcomputers available: the TRS-80, Apple, PET, Heathkit, Imsai and Altair, to name a few. In addition, the articles cover a whole range of subjects, from business applications to educational uses, from product reviews to the latest in software.

As a special limited offer to new subscribers, we'll send you your first issue absolutely free! You'll receive 13 issues for the price of 12. And we're offering you a year's subscription at half the newsstand price . . . only $15 (it's $30 a year on the newsstand), and the only difference between a subscriber copy and a copy of **MICROCOMPUTING** on the newsstand is $1.25. Send in the card today and we'll deliver your first copy in 4-6 weeks.

ENTER A WHOLE NEW WORLD WITH KILOBAUD MICROCOMPUTING And Get Your First Issue Free!

☐ Send me my first issue of **MICROCOMPUTING** free and start my subscription into the new world of **MICROCOMPUTING.**
☐ One year (12 issues) at half the cover price—$15.
☐ I prefer the additional savings of 3 years (36 issues) for $45. I understand that I'll still receive my first issue free.
☐ Payment Enclosed ☐ Bill Me Later
Bill my ☐ Master Charge ☐ Visa

Card #_____ Exp. Date _____
Signature_____
Name _____
Address _____
City _____ State _____ Zip _____

Offer good in U.S.A. and possessions only. Canadian subscriptions add $2.00 per year. All foreign, one year only—$23 payable in U.S. currency only.

MICROCOMPUTING Subscription Department ●
P.O. Box 997 ● Farmingdale NY 11737 197B

ENTER A WHOLE NEW WORLD WITH KILOBAUD MICROCOMPUTING And Get Your First Issue Free!

☐ Send me my first issue of **MICROCOMPUTING** free and start my subscription into the new world of **MICROCOMPUTING.**
☐ One year (12 issues) at half the cover price—$15.
☐ I prefer the additional savings of 3 years (36 issues) for $45. I understand that I'll still receive my first issue free.
☐ Payment Enclosed ☐ Bill Me Later
Bill my ☐ Master Charge ☐ Visa

Card #_____ Exp. Date _____
Signature_____
Name _____
Address _____
City _____ State _____ Zip _____

Offer good in U.S.A. and possessions only. Canadian subscriptions add $2.00 per year. All foreign, one year only—$23 payable in U.S. currency only.

MICROCOMPUTING Subscription Department ●
P.O. Box 997 ● Farmingdale NY 11737 197B

Baudot Hard Copy For Your SWTPC

—noisy, but cheap

Tie a 6800 to a five-level Teletype™.

Garry Caudell K4HBG
3125 Robin Lynn Drive
Ashland KY 41101

In an earlier article (March, 1978), I discussed the use of a simple search program. In this article, I'll explain hardware and software to tie an SWTPC 6800 to a Baudot Teletype™.

Everyone probably knows the disadvantages of the old Baudot machines, such as being slow, having a limited character set, etc. However, on the plus side, they are cheap and compatible with ham radio operation. If you want cheap (but slow) hard copy, or if you want to use the CRT terminal as a glass Teletype, keep reading.

The simplest way to get hard copy is to use the standard SWTPC MP-S board. All you need to build is the clock divider (see Fig. 2). Unfortunately, this board uses an ACIA (6850) chip, and there is no way to tell it that you don't need all eleven bits when you really need only seven (five data bits plus start and stop bits). If you are willing to slow down the already slow printer, it will think that the extra bits are just long stop bits. Trying to copy this way would not work on anything that was sent at near-synchronous speed. The program would need to be changed to accommodate an ACIA (see listing 2 in Fig. 4).

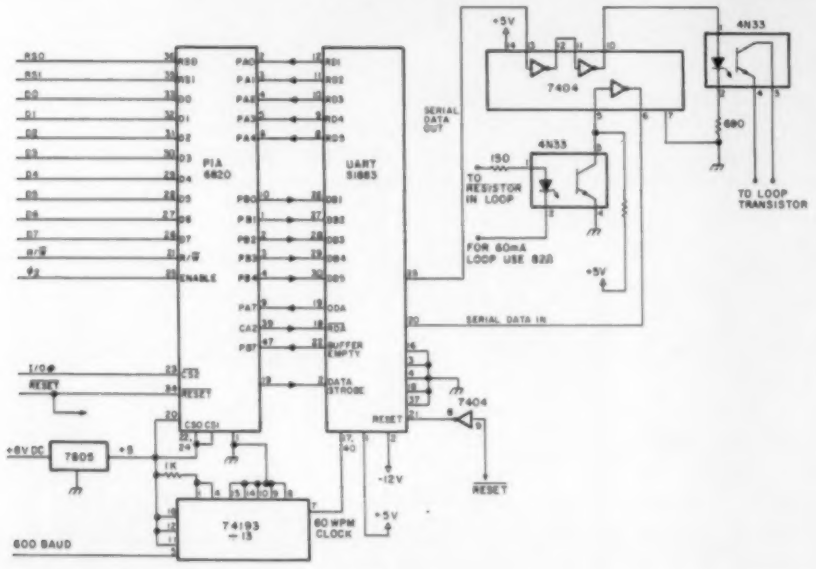

Fig. 1.

The circuit I used to interface my SWTPC 6800 computer to my Model 15 Teletype is an expansion of the circuit used by Mark J. Borgerson in his article in *73* (November, 1976). It has a PIA (6820) controlling a UART (S-1883). All connections into the PIA are identical to those used by the MP-L board.

The clock for the UART is derived from the 600-baud clock divided by 13. If you are using the 1.843-MHz crystal recommended by Motorola for the MC14411 baud generator chip, this comes out slightly high. If you are using the crystal which SWTPC rec-

Release Yourself

A broken tile, a rusty sword, the timeworn remnants of a medieval tapestry: Nothing sparks the imagination more than these fragile reminders of another place, another time, another way of life . . . nothing, that is, save the prospect of living it. That's why Santa Paravia and Fiumaccio is fast becoming a national fad among avid computer gamers and computer professionals alike. Why not get in on the fun today?

This superb simulation casts up to six lords and ladies as competitors in a race for the rule of their respective 15th century Italian city-states.

Each player begins with 1,000 Florins, a small parcel of land, a suitable complement of serfs, and a prewritten obituary and time of death. Life was short back then, so you'd better move quickly . . . from this point on you're on your own.

HARVEST

The winter ended, the grain steward reports the minimum grain amount necessary to feed your people; depending on how much of your reserves were eaten by rats, you may need to purchase additional grain. Underfeeding will cause many serfs to die, and will also severely lower the birth rate. If you fared the winter well, you may be in a position to sell surplus grain or to overfeed your people, which will cause a higher birth rate and attract serfs from less fortunate neighboring towns—something you should consider if you plan to purchase additional land for farming.

You can also speculate in land and grain at this time. The price may vary from year to year, but an average increase is certain.

TAXES

You must now decide the levels of taxation for your community. As in real life, the consequences of your decisions are far-reaching: Set the customs tax too high, and businesses will suffer; a high income tax won't sit well with the wealthy; and an overburdening sales tax has got to cut down receipts at your markets. Experiment, and you're sure to find a policy that will work well with your present economy—but changes will surely be needed as your community grows.

You've also got to decide a policy for justice. Will you be very fair (costs money, but is great for the economy) or outrageous (taking bribes, selling justice to the highest bidder)? A lenient stance will attract more serfs, while outrageous justice will soon have them fleeing to more pleasant surroundings.

MAP PHASE

The computer will now draw a detailed map of your area. From this map you will be able to determine the adequacy of your defenses, the ratio of workers to acreage, the number of woolen mills and market places, and the size of your castle and cathedral.

PUBLIC WORKS

Your treasury laden with the fruits of a year's labor, you can now purchase a woolen mill or two, or invest in more market places. Maybe you'll decide to increase the size of your castle. If you feel that more clergy support might hasten your rise to the throne, build another wing on your cathedral. If your land area has grown quickly, this might be the time to arm another unit of serfs for your regions' defense. Your computer will now look back at what you've accomplished in the last year, and decide if you merit a higher title.

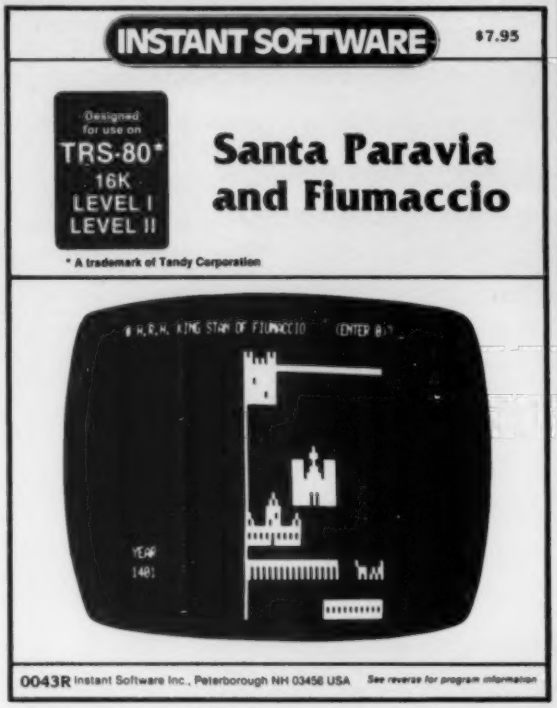

OBITUARY

At this point, the computer will check to see if you've reached "the fullness of time." If so, it will print the year and cause of your death, and your highest rank obtained. Although the computer will no longer offer your turn, the statistics of your reign will be kept in the comparison table until the game's end. Since it's whoever reaches the throne first, or achieves the highest title before death who wins . . . you could still wind up the winner. In any case, you're sure to end the game a little wiser—and chomping at the bit to play again.

Available for the 16K level I and level II TRS-80 microcomputer. Order No. 0043R. $7.95. *(See pg. 91 for order blank)*

Instant Software™ Inc.

Peterborough, N.H. 03458—603-924-7296

ommends, it will be slightly low. In either case, it is as close as the rest of the baud rates, if you follow SWTPC recommendations. (I don't know why SWTPC did this.) This circuit works well and gives one less variable, as compared to using a tunable oscillator (one less confusion factor when trying to get the thing working).

The A-side of the PIA ties to the receive data side of the UART, with bit 7 used for a data ready indication. CA2 is used to clear the UART.

The B-side of the PIA is used as an output to drive the UART, with bit 7 used as an input to poll the UART for a buffer empty signal. CB2 is used to strobe the UART to tell it when to transmit data.

I found it useful to connect the UART reset to the SWTPC reset (through a 7404 inverting gate). This may not be necessary, as most UART circuits do not require a reset, but simply ground this pin. I felt that if the UART did need a reset, this would be well worthwhile to include.

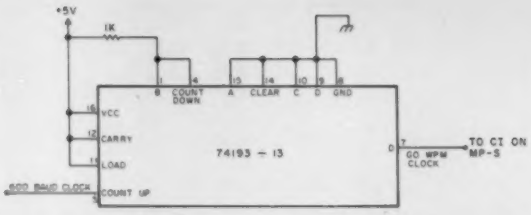

Fig. 2. Build this only if you are going to use the MP-S board. Don't jumper any baud rate on the board.

Data in and data out are buffered by the 7404 gates and by 4N33 optical couplers.

In my system, the output is in series with the base of my loop-keying transistor. This allows the printer to

Fig. 3. Program listing 1.

```
00100                    NAM   OUTEEE
00110                *****************************************************
00120                *
00130                *     PROGRAM TO CONVERT ASCII TO BAUDO
00140                *
00150                *     G. O. CAUDELL
00160                *
00170                *     JULY 1977
00180                *
00190                *****************************************************
01000                    OPT   O
01010                    OPT   S
01020                    ORG   $3F00
01030 3F00
01040 3F00 03      TABLE FCB   $00,$03,$19,$0E,$09,$01,$0D,$1A
      3F01 03
      3F02 19
      3F03 0E
      3F04 09
      3F05 01
      3F06 0D
      3F07 1A
01050 3F08 14            FCB   $14,$06,$0B,$0F,$12,$1C,$0C,$18
      3F09 06
      3F0A 0B
      3F0B 0F
      3F0C 12
      3F0D 1C
      3F0E 0C
      3F0F 18
01060 3F10 16            FCB   $16,$17,$0A,$05,$10,$07,$1E,$13
      3F11 17
      3F12 0A
      3F13 05
      3F14 10
      3F15 07
      3F16 1E
      3F17 13
01070 3F18 1D            FCB   $1D,$15,$11,$08,$02,$04,$16,$04
      3F19 15
      3F1A 11
      3F1B 08
      3F1C 02
      3F1D 04
      3F1E 16
      3F1F 04
01080 3F20 04            FCB   $04,$2D,$31,$34,$29,$04,$3A,$2B
      3F21 2D
      3F22 31
      3F23 34
      3F24 29
      3F25 04
      3F26 3A
      3F27 2B
01090 3F28 2F            FCB   $2F,$38,$2B,$1A,$2C,$23,$3C,$3D
      3F29 38
      3F2A 1A
      3F2B 2C
      3F2C 23
      3F2D 3D
      3F2E 3C
      3F2F 3D
01100 3F30 36            FCB   $36,$37,$33,$21,$2A,$33,$35,$27
      3F31 37
      3F32 33
      3F33 21
      3F34 0A
      3F35 35
      3F36 35
      3F37 27
01110 3F38 26            FCB   $26,$38,$2E,$3E,$2F,$2E,$32,$39
      3F39 38
      3F3A 2E
      3F3B 3E
      3F3C 2F
      3F3D 2E
      3F3E 32
      3F3F 39
01120 3F40 86 FF   CINT  LDA A #$FF     LOAD FLAG
01130 3F42 B7 3F83       STA A LAST+1   STORE FOR LATATE
01140 3F45 39            RTS
01150 3F46 81 5E   OUTEEE CMP A #$5E    IS IT LOWER CASE
01160 3F48 22 5F         BHI   EXIT     YES -- GET OUT
01210 3F4A FF 3FA5       STX   SAVX+1   SAVE INDEX REGISTER
01220 3F4D CE 3F00       LDX   #TABLE   POINT INDEX REG. AT START OF
01230 3F50 84 7F         AND A #$7F     GET ID OF PARITY
01240 3F52 E7 A6         STA B XSAVB+1,X  SAVE B
01260 3F54 6D 33         TST   XLAST+1,X  TEST CASE FLAG
01268 3F56 2C 0C         BGE   CKCR     GO CHECK FOR CARRIAGE RETURN
01290 3F58 C6 7F   INT   LDA B #$7F
01300 3F5A 8D 5B         BSR   XINT
01310 3F5C C6 1F         LDA B #$1F     LOAD BAUDOT LETTERS
01320 3F5E E7 B6         STA B XSEND+1,X  STORE B SO IT CAN BE SENT
01330 3F60 6F 83         CLR   XLAST+1,X  CLEAR CASE FLAG  (LAST+1)
01340 3F62 8D 4A         BSR   BAUDO    GO SEND BAUDOT LETTERS
01350 3F64 81 8D   CKCR  CMP A #$8D     IS IT CARRIAGE RETURN
01360 3F66 26 02         BNE   CKLF     GO CHECK LINE FEED
01370 3F68 86 5B         LDA A #$5B     POINT TO BAUDO CARRIAGE RETUR
01390 3F6A 81 0A   CKLF  CMP A #$0A     IS IT LINE FEED
01400 3F6C 26 04         BNE   CKSP     GO CHECK FOR SPACE
01410 3F6E 86 5C         LDA A #$5C     POINT TO BAUDO LINE FEED
01420 3F70 26 0A         BNE   CKSHF
01430 3F72 81 20   CKSP  CMP A #$20     IS IT SPACE
01440 3F74 26 02         BNE   CKCNTRL
01470 3F76 86 5D         LDA A #$5D     POINT TO BAUDO SPACE
01472 3F78 81 1F   CKCNTR CMP A #$1F    IS IT A CONTROL CHARACTER
01474 3F7A 23 28         BLS   SAVX
01480 3F7C 84 3F   CKSHF AND A #$3F     CONVERT TO SIX BIT ASCII
01490 3F7E A7 AB         STA A XLOOKUP+1,X  STORE IN LOOKUP+1
01500 3F80 84 20         AND A #$20
01510 3F82 81 FF   LAST  CMP A #$FF     COMPARE LAST
01520 3F84 27 16         BEQ   ASEND    IF SHIFT IS OK GO SEND CHAR
01540 3F86 23 0C         BLS   LTRS     GO TO LETTERS
01550 3F88 C6 20   FIGS  LDA B #$20     LOAD FIGS FLAG
01560 3F8A E7 83         STA B XLAST+1,X  STORE IN LAST+1
01570 3F8C C6 1B         LDA B #$1B     LOAD BAUDO LETTERS
01580 3F8E E7 B6         STA B XSEND+1,X  STORE IN SEND+1
01590 3F90 8D 1C         BSR   BAUDO    GO SEND IT
01600 3F92 20 06         BRA   ASEND
01605 3F94 6F 83   LTRS  CLR   XLAST+1,X  LEAR CASE FLAG  (LAST+1)
01610 3F96 C6 1F         LDA B #$1F     LOAD BAUDO LETTERS
01620 3F98 E7 B6         STA B XSEND+1,X  STORE IN SEND+1
01630 3F9A 8D 12         BSR   BAUDO    GO SEND IT
01640 3F9C 8D 0C   ASEND BSR   LOOKUP
01650 3F9E 20 04         BRA   SAVX
01660 3FA0 E7 B6   BSEND STA B XSEND+1,X  STORE IN SEND+1
01670 3FA2 8D 0A         BSR   BAUDO
01680 3FA4 CE 0000 SAVX  LDX   #$0000
01690 3FA7 C6 00   SAVB  LDA B #$00     RESTORE B
01700 3FA9 39            EXIT  RTS
01710 3FAA E6 00   LOOKUP LDA B 0,X     CONVERT CHARACTER TO BAUDO
01720 3FAC E7 B6         STA B XSEND+1,X  STORE IN SEND+1
01730 3FAE F6 800E BAUDO LDA B PIA
01740 3FB1 C4 80         AND B #$80     IS UART READY
01750 3FB3 27 F9         BEQ   BAUDO    NO GO BACK AND WAIT
01760 3FB5 C6 03   SEND  LDA B #$00     LOAD BAUDO CHARACTER
01770 3FB7 F7 800E XINT  STA B PIA      TICKLE THE UART
01780 3FBA C6 34         LDA B #$34     TO LET IT KNOW
01790 3FBC F7 8007       STA B PIA+1    TO DO SOMETHING
01800 3FBF C6 3C         LDA B #$3C
01810 3FC1 F7 8007       STA B PIA+1
01820 3FC4 39            RTS
07000              0082  XLAST EQU   LAST-TABLE
07010              00B5  XSEND EQU   SEND-TABLE
07020              00AA  XLOOKU EQU  LOOKUP-TABLE
07030              00A7  XSAVB EQU   SAVB-TABLE
09000              800E  PIA   EQU   $800E
99999                    END
TABLE  3F00
CINT   3F40
OUTEEE 3F46
INT    3F58
CKCR   3F64
CKLF   3F6A
CKSP   3F72
CKCNTR 3F78
CKSHF  3F7C
LAST   3F82
FIGS   3F88
LTRS   3F94
ASEND  3F9C
BSEND  3FA0
SAVX   3FA4
SAVB   3FA7
EXIT   3FA9
LOOKUP 3FAA
BAUDO  3FAE
SEND   3FB5
XINT   3FB7
XLAST  0082
XSEND  00B5
XLOOKU 00AA
XSAVB  00A7
PIA    800E

TOTAL ERRORS 00000
```

Fig. 4. Program listing 2. If you reassemble the entire program, NOPs (lines 1290-1295) can be omitted.

```
00100                          NAM    PATCH
01202                          OPT    L
01290 3F58 01          INT     NOP
01295 3F59 01                  NOP
01300 3F5A 8D 61               BSR    XINT
01310 3F5C C6 1F               LDA B  #$1F     LOAD BAUDOT LETTERS
01320 3F5E E7 B6               STA B  XSEND+1,X  STORE B SO IT CAN BE SENT
01330 3F60 6F 83               CLR    XLAST+1,X  CLEAR CASE FLAG  (LAST+1)
01340 3F62 8D 4A               BSR    BAUDO    GO SEND BAUDOT LETTERS


01722                          OPT    L
01728          8008C   ACIA    EQU    $8008C
01730 3FAE C6 02       BAUDO   LDA B  #$02     LOAD TEST FLAG
01740 3FB0 F5 8008C BIT        BIT B  ACIA     IS ACIA READY
01750 3FB3 27 FB               BEQ    BIT      NO GO BACK
01760 3FB5 C6 00       SEND    LDA B  #$00     LOAD BAUDOT CHARACTER
01770 3FB7 CA E8               ORA B  #$E8     SET EXTRA BITS TO MARK
01780 3FB9 F7 8008D            STA B  ACIA+1   SEND IT
01790 3FBC 39                  RTS


01800 3FBD C6 03       XINT    LDA B  #$03
01810 3FBF F7 8008C            STA B  ACIA
01820 3FC2 C6 55               LDA B  #$55
01830 3FC4 F7 8008C            STA B  ACIA
01840 3FC7 39                  RTS

TOTAL ERRORS 00000
```

operate either from my ST-5 or the computer, without doing any switching. Similarly, the input is a resistor in the loop which allows either the keyboard or the ST-5 input to the computer.

Construction

I am sorry to say that I do not have a nice printed circuit board to build this gadget on. Mine is handwired on a piece of vectorboard which is the same size as the SWTPC I/O boards and has the same plug arrangement. For no good reason, I put it on slot 3.

Program

The program to convert ASCII to Baudot (see listing 1) is noteworthy only because of the ease of relocating it. If you have a block-move program, only the memory locations in lines 1130, 1210, and 1220 have to be changed. From here on, relative or indexed addressing is used.

The first part of the program (1040-1110) consists of a lookup table to convert Baudot to ASCII. In the table, the conversion is accomplished by pointing the index register at the start of the table and using the ASCII character (6-bit form) as an offset. Line feed and carriage return are handled as exceptions. No other control characters are allowed (bell might have been useful).

Space is handled as an exception because some machines are set up for unshift on space. In the program, space is handled as a letters character only.

The CINT (1120-1140) subroutine is used to restore the flag so that the PIA will be initiated after a reset.

OUTEEE (1150) is the point to branch to in order to output a character in "A" accumulator (just like MIKBUG). The first thing it does (lines 1150-1160) is reject any lowercase ASCII. Next, it stores the index register and points the index register to the start of the conversion table (lines 1210-1220).

In line 1230, the program makes sure that we are talking about 7-bit ASCII and then saves the "B" accumulator (line 1240).

The test in line 1260 is to see if the PIA has been initialized or not. It does this by checking to see what is stored in LAST+1 (line 1510). If it sees a negative value ($FF), it will go through the INT portion (1290-1340) which will initialize the PIA, clear the last flag, and put the printer in letters shift.

If it sees a nonnegative value, it will jump around this section. All this means that, if you have reset the computer, you need to restore the $FF in LAST+1. This is the purpose of the CINT routine.

Lines 1350-1470 check for carriage return, line feed, and space. If it finds them, it substitutes values for them so they can be printed. Line 1472 rejects all other control characters. Line 1480 converts the character to 6-bit ASCII, and then it is stored to be sent later (1490).

In 6-bit ASCII, if the character is less than hex 20, it is a letter of the alphabet, so we should be in letters shift.

If it is greater than hex 20, we should be in figures shift. Line 1500 reduces the character to either a hex 20 or a zero value. This is compared to the value in LAST+1 (line 1510) to determine if the printer is in the correct shift. If it is in the correct shift, the program jumps ahead to send the character; otherwise, the appropriate shift is sent (1550-1630).

ASEND (1640) branches to send the character then to SAVX (1680) to restore index register and "B" accumulator and return.

Lookup (1710) does the actual conversion and stores the Baudot character in SEND+1. In lines 1730-1750, the UART is tested to see if it is ready for a new character. 1760-1770 sends the character to the UART. 1780-1820 strobes the UART to tell it that the character can be sent.

Software to input a character is listed in the November article and will not be repeated here.

These two programs do not represent a complete system for RTTY operation, but rather a set of subroutines to be incorporated in such a system. A complete system would need a software FIFO and some form of sense switch operation, so you would automatically switch from the input program to the output program when your transmitter is keyed.

The program listed here can be used to give hard copy on your existing program.

The procedure for finding the correct places and the patching procedures were outlined in my earlier (March, 1978) article.

I would like to say that I am not sure how much of this is my own work and how much was Doug Schwab WA4ZV1's. Anyhow, thanks to Doug, and thanks to the repeater gang. ■

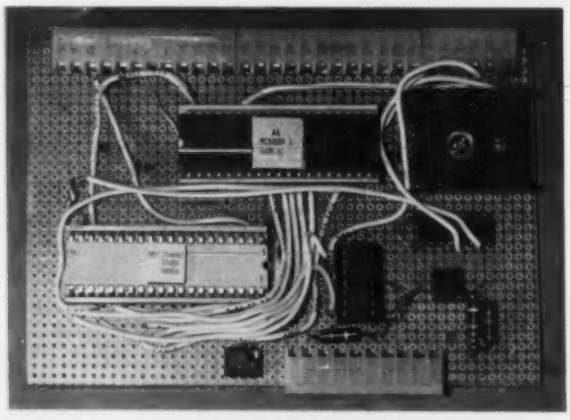

Home-brew I/O board.

Reference

Mark J. Borgersen, "Baudot to ASCII," *73 Magazine*, November, 1976.

FOR BEST PRICE AND FAST DELIVERY
CALL
1-800-325-3636
TOLL FREE
HAM RADIO CENTER
8340-42 Olive Blvd. P.O. Box 28071 St. Louis, MO 63132
H2

FAST SCAN ATV
ALL YOU NEED IN ONE BOX

Show the shack, home movies, computer games, etc. Connect to the ant. terminals of any TV set, add a good 450 antenna, a camera, and you are there . . .

- 10 Watts peak RF output. Specify 434.0 or 439.25 MHz
- Subcarrier sound with plenty of mic gain for distance pick-up.
- 8 MHz bandwidth, high resolution necessary for computer alphanumerics and color.
- Tuneable converter covers 420 to 450. (Covers CH 2, 3)
- Contains AC to 12VDC regulated 3 AMP power supply.
- Only $399.00 direct mail. Check, Money Order, VISA. Send S.A.S.E. for catalog of ATV Modules and PC Boards.

HITACHI HV-62U TV CAMERA . . . . . $239 ppd.

- Better than 500 line resolution. 7 watts on 117VAC.
- Small 4x25/8x8 inches. Can run on 12vdc @ 230ma.
- 10,000: 1 automatic light compensation. Lens included.

Send SASE for catalog of ATV and UHF products VISA or MC orders call (213) 447-4565.

P.C. ELECTRONICS
Maryann WB6YSS
2522 PAXSON
ARCADIA, CA 91006
Tom W6ORG

EXTEND
YOUR RANGE...

With the **RPT-1B Repeater.** Backed by Standard Communications' years of experience in producing quality repeaters for the commercial and amateur market, this superior 10 watt VHF repeater operates on a single pair of channels in the 143-149 MHz range. It contains separate transmitter and receiver assemblies for the re-transmission of signals and a COR/TIMER for control of the switching/timing/monitoring functions of the system. In addition, an optional private channel unit may be installed as an accessory. It may be operated in either a repeat or duplex mode. Priced under $850 from your dealer.

Write today for a FREE Catalog Sheet or see your nearest Standard Communications Dealer.

Standard Communications
S18
P.O. Box 92151, Los Angeles, California 90009

DEALER DIRECTORY

Fontana CA

We carry the following: ICOM, Midland, Amcom, DenTron, KLM, Swan, Drake, Ten-Tec, Wilson, SST, MFJ, Hy-Gain, Lunar, Nye-Viking, B&W, Redi-kilowatt, CushCraft, Mosley, Big Signal, Pipo, etc. Full Service Store **Fontana Electronics, 8628 Sierra Ave., Fontana CA 92335, 822-7710.**

Santa Clara CA

Bay area's newest Amateur Radio store. New & used Amateur Radio sales & service. We feature Kenwood, ICOM, Wilson, Yaesu, Atlas, Ten-Tec & many more. **Shaver Radio, 3550 Lochinvar Avenue, Santa Clara CA 95051, 247-4220.**

Denver CO

Experimenter's paradise! Electronic and mechanical components for computer people, audio people, hams, robot builders, experimenters. Open six days a week. **Gateway Electronics Corp., 2839 W. 44th Ave., Denver CO 80211, 458-5444.**

New Castle DE

Paul WA3QPX, Rob WA3QLS—Serving amateurs in southern New Jersey, Delaware, and Maryland with the largest stock of amateur equipment and accessories in Delaware. **Delaware Amateur Supply, 71 Meadow Road, New Castle DE 19720, 328-7728.**

Columbus GA

KENWOOD—YAESU—DRAKE

The world's most fantastic amateur showroom! You gotta see it to believe it! **Radio Wholesale, 2012 Auburn Avenue, Columbus GA 31906, 561-7000.**

Tell them you saw their name in 73

Preston ID

Ross WB7BYZ, has the Largest Stock of Amateur Gear in the Intermountain West and the Best Prices. Call me for all your ham needs. **Ross Distributing, 78 So. State, Preston ID 83263, 852-0830.**

Terre Haute IN

Your ham headquarters located in the heart of the midwest. **Hoosier Electronics, Inc., 43B Meadows Shopping Center, P.O. Box 1001, Terre Haute IN 47802, 238-1456.**

Littleton MA

The ham store of N.E. you can rely on. Kenwood, ICOM, Wilson, Yaesu, DenTron, KLM amps, B&W switches & wattmeters, Whistler radar detectors, Bearcat, Regency, antennas by Larsen, Wilson, Hustler, GAM. **TEL-COM Inc. Communications & Electronics, 675 Great Rd., Rt. 119, Littleton MA 01460, 486-3040.**

Laurel MD

We stock Drake, Icom, Ten-Tec, Swan, Tempo, Dentron, DSI, KDK, Wilson, Midland and others. Call toll free 800-638-4486. **The Comm Center, Inc., Laurel Plaza, Rte. 198, Laurel MD 20810.**

St. Louis MO

Experimenter's paradise! Electronic and mechanical components for computer people, audio people, hams, robot builders, experimenters. Open six days a week. **Gateway Electronics Corp., 8123-25 Page Blvd., St. Louis MO 63130, 427-6116.**

Camden NJ

X-Band (& other frequencies) Microwave Components & Equipment. Laboratory Grade Test Instruments, Power Supplies, 1000's in stock at all times, BUY & SELL all popular makes—HP, GR, FXR, ESI, Sorensen, Singer, etc. **Lectronic Research Labs, 1423 Ferry Ave., Camden NJ 08104, 541-4200.**

North Arlington NJ

Collins, General Radio, Tektronix, Hewlett Packard. Radio sales/service. Cash or trade for tubes or gear. **Ted W2KUW, DCO, INC., 10 Schuyler Avenue, No. Arlington NJ 07032 998-4244.**

Syracuse NY

We Deal, We Trade, We Discount, We Please! Yaesu, Kenwood, Drake, ICOM, Ten-Tec, Swan, DenTron, Midland, CushCraft, KLM, Hy-Gain, etc. Complete 2-way service shop! **Ham-bone Radio (div. Stereo Repair Shop) 3206 Erie Blvd. East, Syracuse NY 13214, 446-2266.**

Syracuse-Rome-Utica NY

Featuring: Yaesu, ICOM, Drake, Atlas, DenTron, Ten-Tec, Swan, Tempo, KLM, Hy-Gain, Mosley, Wilson, Larsen, Midland Southwest Technical Products. You won't be disappointed with equipment/service. **Radio World, Oneida County Airport-Terminal Building, Oriskany NY 13424, 337-2622.**

Cleveland OH

Need service on your late model or old time equipment? We service all makes and models. Rates $19.96 hr. Call or write. **Communications World, Inc., 4788 State Rd., Cleveland OH 44109, 398-6363.**

Scranton PA

ICOM, Bird, CushCraft, VHF Engineering, Antenna Specialists, Barker & Williamson, CDE Rotators, Ham-Keys, Belden, W2AU/W2VS, Shure, Regency, CES Touch-Tone pads, Radio Amateur Callbooks. **LaRue Electronics, 1112 Grandview St., Scranton PA 18509, 343-2124.**

Souderton PA

Tired of looking at ads ??? Come and try our new and used equipment yourself—personal advice from our staff's 60 years combined ham experience. **Electronic Exchange, 136 N. Main St., Souderton PA 18964, 723-1200.**

Houston TX

Experimenter's paradise! Electronic and mechanical components for computer people, audio people, hams, robot builders, experimenters. Open six days a week. **Gateway Electronics Inc., 8932 Clarkcrest, Houston TX 77063, 978-6575.**

Port Angeles WA

Mobile RFI shielding for elimination of ignition and alternator noises. Bonding straps. Components for "do-it-yourself" projects. Plenty of free advice. **Estes Engineering, 930 Marine Drive, Port Angeles WA 98362, 457-0904.**

DEALERS

Your company name and message can contain up to 25 words for as little as $150 yearly (prepaid), or $15 per month (prepaid quarterly). No mention of mail-order business or area code permitted. Directory text and payment must reach us 45 days in advance of publication. For example, advertising for the August issue must be in our hands by June 18th. Mail to 73 Magazine, Peterborough NH 03458. ATTN: Aline Coutu.

Reader Service—see page 211

Instant Software™ New Releases

Math? Model Rocketry? TRS-80* Utilities? There's something for everyone in this batch of new releases . . . which ones have *you* been waiting for?

Ask for Instant Software at your local computer store, use the handy order blank on page 91, or just get out your credit card and call Toll Free 1-800-258-5473.

TRS-80*

Level II

FINANCIAL ASSISTANT Compute the figures for a wide variety of business needs. Included are:

- **Depreciation**—This program lets you figure depreciation on equipment in five different ways.
- **Loan Amortization Schedule**—Merely enter a few essential factors, and your TRS-80 will display a complete breakdown of all costs and schedules of payment for any loan.
- **Financier**—This program performs thirteen common financial calculations. Easily handles calculations on investments, depreciation, and loans.
- **1% Forecasting**—Use this simple program to forecast sales, expenses, or any other historical data series.

All you need is a TRS-80 Level II 16K. **Order No. 0072R $7.95**

TRS-80 UTILITY 1 Ever wonder how some programmers give their programs that professional look? Instant Software has the answer with the TRS-80 Utility 1 package. Included are:

- **RENUM**—Now you can easily renumber any Level II program to make room for modification, or to clean up the listing.
- **DUPLIK**—This program will let you duplicate any BASIC, assembler, or machine-language program, verify the data, merge two or more programs into one data block, and even copy Level I programs on a Level II machine.

For TRS-80 Level II 16K. **Order No. 0081R $7.95.**

INSTANT SOFTWARE
$7.95
Designed for use on TRS-80* 16K LEVEL II
TRS-80* Utility I
• DUPLIK—Cassette Duplication
• RENUM—Program Renumbering
* A trademark of Tandy Corporation
0081R Instant Software Inc. Peterborough NH 03458 USA See reverse for program information

TRS-80 UTILITY 2 Let Instant Software change the drudgery of editing your programs into a quick, easy job. Included in this package are:

- **CFETCH**—Search through any Level II program tape and get the file names for all the programs. You can also merge BASIC programs, with consecutive line numbers, into one program.
- **CWRITE**—Combine subroutines, that work in different memory locations into one program. This works with BASIC or machine-language programs and gives you a general checksum.

This package is just the thing for your TRS-80 Level II 16K. **Order No. 0076R $7.95**

HOUSEHOLD ACCOUNTANT Let your TRS-80 help you out with many of your daily household calculations. Save time and money with these fine programs:

- **Budget and Expense Analysis**—You can change budgeting into a more pleasant job with this program. With nine sections for income and expenses and the option for one- and three-month review or year totals, you can see where your money is going.
- **Life Insurance Cost Comparison**—Compare the cost of various life insurance policies. Find out the difference in price between term and whole life. This program can store and display up to six different results.
- **Datebook**—Record all those important dates in your life for fast, easy access. The program has all major holidays already included.

All you need is TRS-80 Level II 16K. **Order No. 0069R $7.95**

MODEL ROCKET ANALYZER AND PRE-FLIGHT CHECK Let your TRS-80 help you enjoy the fast-growing hobby of model rocketry. The complementary programs included are:

- **Model Rocket Flight History Prediction**—This program will compute the flight characteristics for almost any model rocket. Engine and body tube data included covers Estes, Centuri, Flight Systems, A.V.I. Astroport, C.M.R., and Kopter products.
- **Weather Forecaster**—Before you launch your rocket, get an up-to-the-minute weather forecast. Just enter your location, elevation, average temperatures for January and July, and barometric pressure. You'll be the short-range weather forecaster for your local area.

For a successful launch, you'll need TRS-80 Level II 16K. **Order No. 0024R $7.95**

TEACHER Now you can have the benefits of computer-assisted instruction right in your own home. The programs allow you to input any number of questions and answers. Using this data, the computer will prepare several types of tests, quiz students, provide up to three "hints" per question—even offer graphic rewards for younger children, all at the user's discretion. Perfect for parents, teachers, or anyone faced with learning a lot of material in the shortest possible time. Furnished with blank data cassette.

Teacher requires a 16K Level II TRS-80. **Order No. 0065R $9.95.**

PET**

TURF AND TARGET Whether on the field or in the air, you'll have fun with Turf and Target package. Included are:

- **Quarterback**—You're the quarterback as you try to get the pigskin over the goal line. You can pass, punt, hand off, and see the results of your play using the PET's superb graphics.
- **Soccer II**—Play the fast-action game of soccer with four playing options. The computer can play itself, play a single player, two players with computer assistance, and two players without help.
- **Shoot**—You're the hunter as you try to shoot the bird out of the air. The PET will keep score.
- **Target**—Use the numeric keypad to shoot your puck into the home position as fast as you can.

To run and score all you'll need is a PET with 8K. **Order No. 0097P $7.95**

ARCADE I This package combines an exciting outdoors sport with one of America's most popular indoor sports:

- **Kite Fight**—It's a national sport in India. After you and a friend have spent several hours maneuvering your kites across the screen of your PET, you'll know why!
- **Pinball**—By far the finest use of the PET's exceptional graphics capabilities we've ever seen, and a heck of a lot of fun to play to boot.

Requires an 8K PET. **Order No. 0074R $7.95.**

ARCADE II One challenging memory game and two fast-paced action games make this one package the whole family will enjoy for some time to come. Package includes:

- **UFO**—Catch the elusive UFO before it hits the ground!
- **Hit**—Better than a skeet shoot. The target remains stationary, but you're moving all over the place.
- **Blockade**—A two-player game that combines strategy and fast reflexes.

Requires 8K PET. **Order No. 0045P $7.95.**

Apple***

MATH TUTOR I Parents, teachers, students, now you can turn your Apple computer into a mathematics tutor. Your children or students can begin to enjoy their math lessons with these programs:

- **Hanging**—Perfect your skill with decimal numbers while you try to cheat the hangman.
- **Spellbinder**—Cast spells against a competing magician as you practice working with fractions.
- **Whole Space**—While you exercise your skill at using whole numbers, your ship attacks the enemy planet and destroys alien spacecraft.

All programs have varying levels of difficulty. All you need is Applesoft II with your Apple II 24K. **Order No. 0073A $7.95**

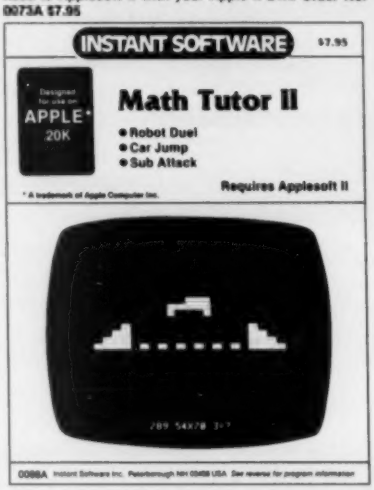
INSTANT SOFTWARE
$7.95
Designed for use on APPLE* 20K
Math Tutor II
• Robot Duel
• Car Jump
• Sub Attack
Requires Applesoft II
* A trademark of Apple Computer Inc.
0098A Instant Software Inc. Peterborough NH 03458 USA See reverse for program information

MATH TUTOR II Your Apple computer can go beyond game playing and become a mathematics tutor for your children. Using the technique of immediate positive reinforcement, you can make math fun with:

- **Car Jump**—Reinforce the concept of calculating area while having fun making your car jump over the ramps.
- **Robot Duel**—Practice figuring volumes of various containers while your robot fights against the computer's mechanical man.
- **Sub Attack**—Take the mystery out of working with percentages as your submarine sneaks into the harbor and destroys the enemy fleet.

All you need is Applesoft II with your Apple II and 20K. **Order No. 0095A $7.95.**

*A trademark of Tandy Corporation
**A trademark of Apple Computer Inc.
***A trademark of Commodore Business Machines Inc.

Instant Software™ Has It All...

TRS-80*

Level I

KNIGHT'S QUEST/ROBOT CHASE/HORSE RACE This varied package of one-player games will give you hours of fun.

- **Knight's Quest**—Battle demons to gain treasure and become a full-fledged knight.
- **Robot Chase**—Destroy the deadly robots without electrocuting yourself.
- **Horse Race**—Place your bet and cheer your horse to the finish line.

These programs require a TRS-80 Level I 16K. **Order No. 0003R $7.95.**

SPACE TREK III Let yourself go to the far ends of the solar system—and beyond. This package includes:

- **Stellar Wars**—Shoot down the Tie fighters and destroy the Death Star.
- **Planetary Lander**—Land your spacecraft and plant your flag across the solar system.

These one-player games require a TRS-80 Level I 4K. **Order No. 0031R $7.95.**

DESTROY ALL SUBS/GUNBOATS/BOMBER This package of three programs is fun for the whole family. Included are:

- **Destroy All Subs**—Hunt down enemy subs while avoiding mines and torpedoes. A one-player game.
- **Gunboats**—One or two players can try to blow each others ships out of the water.
- **Bomber**—Carefully release your bomb to destroy the moving submarine. A one-player game.

To enjoy these programs, you'll need a TRS-80 Level I 4K. **Order No. 0021R $7.95.**

FUN PACKAGE I Why call it "Fun Package?" Judge for yourself! This entertaining package includes:

- **Rocket Pilot**—Flying it is easy—it's the landing that's tough!
- **Paper, Rock, Scissors**—Play the time-honored game just as you remember it played against your TRS-80.
- **Hex I**—Just when you master this puzzle game, the computer will increase the difficulty.
- **Missile Attack**—Use your missiles to protect your city from jet attack.

Requires a Level I 16K TRS-80. **Order No. 0037R $7.95.**

DOODLES AND DISPLAYS I Here's a mixed bag of programs that's sure to entertain:

- **Doodle Pad**—Draw pictures and save them on cassette tapes.
- **Symmetrics**—Turn your TRS-80 into a kaleidoscope.
- **Video Display**—Follow the bouncing cursor as your TRS-80 draws its own pictures.
- **Math Curves**—Bring those Geometry lessons to life as the computer draws six different geometrical curves.
- **Rug Patterns**—A never ending stream of symmetrical patterns that's sure to spark your imagination.

All you'll need is a 16K Level I TRS-80. **Order No. 0030R $7.95.**

BUSINESS PACKAGE I Keep the books for a small business with your TRS-80 Level I 4K. The six programs included are:

- **General Information**—The instructions for using the package.
- **Fixed Asset Control**—This will give you a list of your fixed assets and term depreciation.
- **Detail Input**—This program lets you create and record your general ledger on tape for fast access.
- **Month and Year to Date Merge**—This program will take your monthly ledger data and give you a year to date ledger.
- **Profit and Loss**—With this program you can quickly get trial balance and profit and loss statements.
- **Year End Balance**—This program will combine all your data from the profit and loss statements into a year end balance sheet.

With this package, you can make your TRS-80 a working partner. **Order No. 0013R $29.95.**

BUSINESS PACKAGE III This package can change your TRS-80 into a full working partner for any businessman:

- **Inventory**—Maintain a computer based inventory for a constant inventory system.
- **Discount and Commission Percentages**—Let your computer figure out mark up and discount calculations, sales tax and more. This is a perfect time saving package for any small business.

For the TRS-80 Level I 4K. **Order No. 0061R $7.95.**

CAVE EXPLORING/YACHT/MEMORY These three programs are not only fun, but stimulating as well:

- **Cave Exploring**—Search for fabulous treasures as you explore the magic cave. For one player.
- **Yacht**—A two player game of strategy and chance. The computer rolls the dice and keeps score.
- **Memory**—Two players can pit their memories in this program based on a popular television show. You'll need a TRS-80 with Level I and 16K. **Order No. 0010R $7.95.**

CAR RACE/RAT TRAP/ANTIAIRCRAFT Enjoy these challenging, fun-filled programs:

- **Car Race**—You and a friend can race on a choice of two tracks.
- **Rat Trap**—Trap the rat in his maze with your two cats. For one player.
- **Antiaircraft**—Aim and shoot down the enemy airplane. Requires Level I 4K TRS-80. **Order No. 0011R $7.95.**

STATUS OF HOMES/AUTO EXPENSES Two long-awaited programs that have got to save you money at work or in the home:

- **Status of Homes**—This program will allow you to keep track of all the expenses involved in building one house or an entire subdivision.
- **Auto Expenses**—Find out *exactly* what it costs you to drive your car or truck.

These programs require a TRS-80 Level I 4K. **Order No. 0012R $7.95.**

HEX PAWN/SHUTTLE CRAFT DOCKING/SPACE CHASE/SEA BATTLE This four-game package is sure to provide hours of fun for the whole family.

- **Hex Pawn**—Turn your TRS-80 into a model of artificial intelligence by playing a simple game.
- **Shuttle Craft Docking**—Land your shuttle craft on the starship—even through varying gravity fields!
- **Space Chase**—Seek out and destroy the enemy delta that's hidden in the star field.
- **Sea Battle**—You must find and destroy the enemy fleet.

This package requires a TRS-80 Level I 16K. **Order No. 0041R $7.95.**

DEMO I This package is just the thing to show your friends what your TRS-80 can do. Included are:

- **Computer Composer**—Compose and play music using only a standard AM radio.
- **Horse Race**—Place your bet and cheer your pony to the winner's circle.
- **E.S.P.** Test your powers of extrasensory perception.
- **Hi-Lo/Tic-Tac-Toe**—Guess the secret number or get three in a row.
- **Petals Around the Rose**—Can you figure out the secret behind the five dice?
- **Slot Machine**—Turn your computer into a one-armed bandit. These programs require a TRS-80 Level I 4K. **Order No. 0020R $7.95.**

PERSONAL FINANCE I Let your TRS-80 handle all the tedious details the next time you figure your finances:

- **Personal Finance I**—With this program you can control your incoming and outgoing expenses.
- **Checkbook**—Your TRS-80 can balance your checkbook and keep a detailed list of expenses for tax time.

This handy financial control package for the home requires only a TRS-80 Level I 4K. **Order No. 0027R $7.95.**

Level II

SPACE TREK IV Trade or wage war on a planetary scale. This package includes:

- **Stellar Wars**—Engage and destroy Tie fighters in your attack on the Death Star. For one player.
- **Population Simulation**—A two-player game where you control the economy of two neighboring planets.

You decide, guns or butter, with your TRS-80 Level II 16K. **Order No. 0034R $7.95.**

DOODLES AND DISPLAYS II Wait until your children get a hold of this package:

- **Doodle Pad**—Draw pictures and save them on cassette tapes.
- **Symmetrics**—An electric kaleidoscope that changes from black to white and back again. It's almost hypnotic!
- **Drawing**—like Doodle Pad but for the serious artist. Over 40 user commands.
- **Random Pattern Display**—The computer does the drawing, but those itchy fingers can tamper.
- **Math Curves**—Bring those Geometry lessons to life. Six different geometrical curves on the screen of your TRS-80.
- **Rug Patterns**—Yes, it does design rug patterns and, with a choice of user or computer control, it can do a whole lot more.

For the Level II 16K TRS-80. **Order No. 0042R $7.95.**

RAMROM PATROL/TIE FIGHTER/KLINGON CAP Buck Rogers never had it so good. Engage in extraterrestrial warfare with:

- **Ramrom Patrol**—Destroy the Ramron ships before they capture you.
- **Tie Fighter**—Destroy the enemy Tie fighters and become a hero of the rebellion.
- **Klingon Capture**—You must capture the Klingon ship intact. It's you and your TRS-80 Level II 16K battling across the galaxy. **Order No. 0028R $7.95.**

CARDS This one-player package will let you play cards with your TRS-80—talk about a poker face!

- **Draw and Stud Poker**—These two programs will keep your game sharp.
- **No-Trump Bridge**—Play this popular game with your computer and develop your strategy.

This package's name says it all. Requires a TRS-80 Level II 16K. **Order No. 0083R $7.95.**

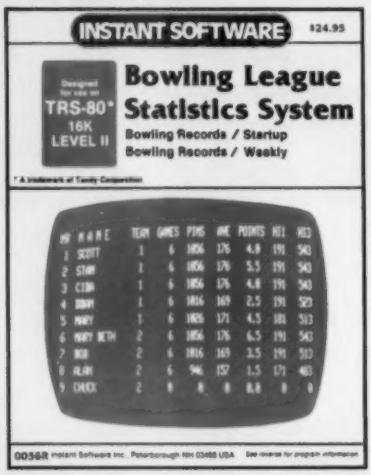
INSTANT SOFTWARE
$24.95
Designed for use on TRS-80* 16K LEVEL II
Bowling League Statistics System
Bowling Records / Startup
Bowling Records / Weekly
* A trademark of Tandy Corporation
0058R Instant Software Inc., Peterborough NH 03458 USA See reverse for program information

BOWLING LEAGUE STATISTICS SYSTEM This package is the answer to the prayers of harried bowling league scorekeepers. The Bowling League Statistics System will keep a computerized list of league data, team data, and data for each bowler. It is extremely flexible and has a total of 16 different options to let you modify the program to suit your league's rules. The program is very easy to use and has extensive "built in" aids to help you along. Requires TRS-80 Level II 16K. **Order No. 0058R $24.95.**

Level I and II

BACKGAMMON/KENO Why sit alone when you can play these fascinating games with your TRS-80?

- **Backgammon**—Play against the computer. Your TRS-80 will give you a steady challenging game that's sure to sharpen your skills.
- **Keno**—Enjoy this popular Las Vegas gambling game. Guess the right numbers and win big.

You'll need a TRS-80 Level I or II. **Order No. 0004R $7.95.**

OIL TYCOON Avoid oil spills, blowouts and dry wells as you battle to become the world's richest oil tycoon. Two players become the owners of competing oil companies as they search for oil and control their companies. Requires a TRS-80 4K Level I or II. **Order No. 0023R $7.95.**

BOWLING Let your TRS-80 set up the pins and keep score. One player can pick up spares and get strikes. For the TRS-80 Level I 4K, Level II 16K. **Order No. 0033R $7.95.**

AIR FLIGHT SIMULATION Turn your TRS-80 into an airplane. You can practice takeoffs and landings with the benefit of full instrumentation. This one-player simulation requires a TRS-80 Level I 4K, Level II 16K. **Order No. 0017R $7.95.**

GOLF/CROSSOUT Have fun with these exciting one-player games. Included are:

- **Golf**—You won't need a mashie or putter—or a caddie, for that matter, to enjoy a challenging 18 holes.
- **Crossout**—Remove all but the center peg in this puzzle and your neighbors will call you a genius.

You'll need a TRS-80 Level I 4K, Level II 16K. **Order No. 0009R $7.95.**

HAM PACKAGE I This versatile package lets you solve many of the commonly encountered problems in electronics design. With your Level I 4K or Level II 16K TRS-80, you have a choice of:

- **Basic Electronics with Voltage Divider**—Solve problems involving Ohm's Law, voltage dividers, and RC time constants.
- **Dipole and Yagi Antennas**—Design antennas easily, without tedious calculations.

This is the perfect package for any ham or technician. **Order No. 0007R $7.95.**

BASIC AND INTERMEDIATE LUNAR LANDER Bring your lander in under manual control. The Basic version is for beginners; the Intermediate version is more difficult with a choice of landing areas and rugged terrain. For one player with a TRS-80 Level I 4K, Level II 16K. **Order No. 0001R $7.95.**

SPACE TREK II Protect the quadrant from the invading Klingon warships. The Enterprise is equipped with phasers, photon torpedoes, impulse power, and warp drive. It's you alone and your TRS-80 Level I 4K, Level II 16K against the enemy. **Order No. 0002R $7.95.**

ELECTRONICS I This package will not only calculate the component values for you, but will also draw a schematic diagram, too. You'll need a TRS-80 Level I 4K, Level II 16K to use:

- **Tuned Circuits and Coil Winding**—Design tuned circuits without resorting to cumbersome tables and calculations.
- **555 Timer Circuits**—Quickly design astable or monostable timing circuits using this popular IC.
- **LM 381 Preamp Design**—Design IC preamps with this low-noise integrated circuit.

This package will reduce your designing time and let you build those circuits fast. **Order No. 0008R $7.95.**

SANTA PARAVIA AND FIUMACCIO Become the ruler of a medieval city-state as you struggle to create a kingdom. Up to six players can compete to see who will become the King or Queen first. This program requires a 16K TRS-80 Level I & II. **Order No. 0043R $7.95.**

PET**

QUBIC-4/GO-MOKU Play two ancient games on your modern PET. The two programs included are:

- **Qubic-4**—Play a multi-dimensioned game of tic-tac-toe.
- **Go-Moku**—Line up five of your men while blocking the PET's moves.

These one player games require 8K of memory. **Order No. 0038P $7.95.**

TREK-X Command the Enterprise as you scour the quadrant for enemy warships. This package not only has superb graphics, but also includes programming for optional sound effects. A one-player game for the PET 8K. **Order No. 0032P $7.95.**

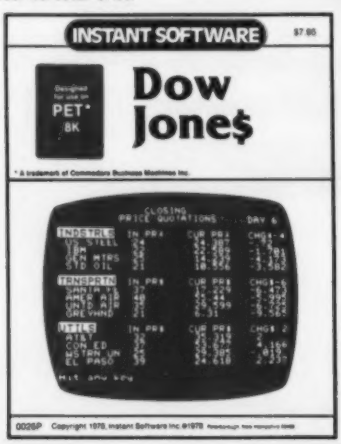

DOW JONE$ Up to six players can enjoy this exciting stock market game. You can buy and sell stock in response to changing market conditions. Get a taste of what playing the market is all about. Requires a PET with 8K. **Order No. 0026P $7.95.**

DUNGEON OF DEATH Battle evil demons, cast magic spells, and accumulate great wealth as you search for the Holy Grail. You'll have to descend into the Dungeon of Death and grope your way in the suffocating darkness. If you survive, glory and treasure are yours. For the PET 8K. **Order No. 0064P $7.95.**

MORTGAGE WITH PREPAYMENT OPTION/FINANCIER These two programs will more than pay for themselves if you mortgage a home or make investments:

- **Mortgage with Prepayment Option**—Calculate mortgage payment schedules and save money with prepayments.
- **Financier**—Calculate which investment will pay you the most, figure annual depreciation, and compute the cost of borrowing, *easily and quickly.*

All you need to become a financial wizard with an 8K PET. **Order No. 0006P $7.95.**

CASINO I These two programs are so good, you can use them to check out and debug your own gambling system!

- **Roulette**—Pick your number and place your bet with the computer version of this casino game. For one player.
- **Blackjack**—Try out this version of the popular card game before you go out and risk your money on your own "surefire" system. For one player.

This package requires a PET with 8K. **Order No. 0014P $7.95.**

CASINO II This craps program is so good, it's the next best thing to being in Las Vegas or Atlantic City. It will not only play the game with you, but also will teach you how to play the odds and make the best bets. A one player game, it requires a PET 8K. **Order No. 0015P $7.95.**

CHECKERS/BACCARAT Play two old favorites with your PET.

- **Checkers**—Let your PET be your ever-ready opponent in this computer-based checkers program.
- **Baccarat**—You have both Casino- and Blackjack-style games in this realistic program.

Your PET with 8K will offer challenging play anytime you want. **Order No. 0022P $7.95.**

TANGLE/SUPERTRAP These two programs require fast reflexes, and a good eye for angles:

- **Tangle**—Make your opponent crash his line into an obstacle.
- **Supertrap**—This program is an advanced version of Tangle with many user control options.

Enjoy these exciting and graphically beautiful programs. For one or two players with an 8K PET. **Order No. 0029P $7.95.**

DIGITAL CLOCK Don't let your PET sit idle when you are not programming, put it to work with these two unique and useful programs:

- **Digital Clock**—Turn your PET into an extremely accurate time-piece that you can use to display local time, time in distant zones, or as a split time clock for up to nine different sporting events.
- **Moving Sign**—Let the world know what's on your mind. This program turns your PET into a flashing graphic display that will put your message across. **Order No. 0083P $7.95.**

PENNY ARCADE Enjoy this fun-filled package that's as much fun as a real penny arcade—at a fraction of the cost!

- **Poetry**—Compose free verse poetry on your computer.
- **Trap**—Control two moving lines at once and test your coordination.
- **Poker**—Play five card draw poker and let your PET deal and keep score.
- **Solitaire**—Don't bother to deal, let your PET handle the cards in this "old favorite" card game.
- **Eat-'Em-Ups**—Find out how many stars your gobbler can eat up before the game is over.

These six programs require the PET with 8K. **Order No. 0044P $7.95.**

MIMIC Test your memory and reflexes with the five different versions of this game. You must match the sequence and location of signals displayed by your PET. This one-player program includes optional sound effects with the PET 8K. **Order No. 0039P $7.95.**

PERSONAL WEIGHT CONTROL/BIORHYTHMS Let your PET help take care of your personal health and safety:

- **Personal Weight Control**—Your PET will not only calculate your ideal weight, but also offer a detailed diet to help control your caloric intake.
- **Biorhythms**—Find out where your critical days are for physical, emotional, and intellectual cycles.

You'll need only a PET with 8K memory. **Order No. 0005P $7.95.**

BASEBALL MANAGER This pair of programs will let you keep statistics on each of your players. Obtain batting, on-base, and fielding averages at the touch of a finger. Data can be easily stored on cassette tape for later comparison. All you need is a PET with 8K. **Order No. 0062P $14.95.**

Apple***

BOWLING/TRILOGY Enjoy two of America's favorite games transformed into programs for your Apple:

- **Bowling**—Up to four players can bowl while the Apple sets up the pins and keeps score. Requires Applesoft II.
- **Trilogy**—This program can be anything from a simple game of tic-tac-toe to an exercise in deductive logic. For one player.

This fun-filled package requires an Apple with 20K. **Order No. 0040A $7.95.**

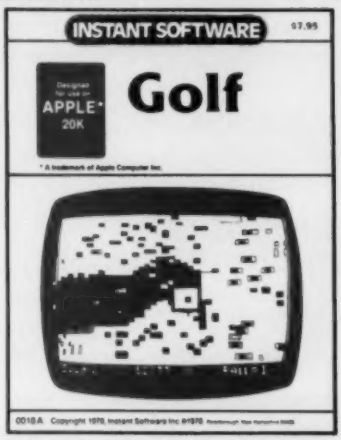
INSTANT SOFTWARE
$7.95
Designed for use on APPLE* 20K
Golf
* A trademark of Apple Computer Inc.
0018A Copyright 1978, Instant Software Inc 8/1978

GOLF Without leaving the comfort of your chair, you can enjoy a computerized 18 holes of golf with a complete choice of clubs and shooting angles. You need never cancel this game because of rain. One or two players can enjoy this game on the Apple with Applesoft II and 20K. **Order No. 0018A $7.95.**

DATA TAPES Use these high quality data tapes to record business or personal data. Four tapes per package. **Order No. 0067 $7.95.**

*A trademark of Tandy Corporation

** A trademark of Commodore Business Machines Inc.

*** A trademark of Apple Computer Inc.

Cut along dotted line and mail today

Ordered by _____

Address _____

City _____ State _____ Zip _____

☐ Check ☐ Money Order ☐ VISA ☐ AMEX ☐ Master Charge

Card No. _____ Expiration date _____

Signed _____ Date _____

Order your Instant Software today!

Quantity	Order No.	Program name	Unit cost	Total cost
		Shipping and handling		$1.00
			Total order	

Instant Software Inc. Dept. 73-ISF3
Peterborough, N.H. 03458

The 9-Element Duoband DX Attention-Getter

—when you call, they listen

From the folks who brought you the "Towerless 'Tower.' "

Robert H. Walker K4FK
400 Tivoli Ave.
Coral Gables FL 33143

Roy D. Mazzagatti N4OG
18551 S.W. 204th St.
Miami FL 33187

Photos by WA4KIL

Hy-Gain's "tiger on 20," the popular 204BA 4-element monoband yagi, exhibits the excellent performance which can be obtained from a relatively small close-spaced yagi array. For over a decade, the one at K4FK has been performing flawlessly and giving no maintenance problems. Originally, the antenna was up 77 feet on a Rohn tower. A move to a new QTH in 1971 limited us to mounting it on a telescoping TV mast at heights between 12 and 20 feet (see Walker and Mazzagatti, "The Towerless 'Tower,' " *73 Magazine*, June, 1978). Even at such low heights, the 204 has proven itself competitive in pileups.

With the recent upturn in the sunspot cycle, we decided to try interlacing a 15 meter yagi with the 204BA on the Hy-Gain boom. According to *The ARRL Antenna Book*, "It is generally accepted that interaction, if any, is very minimal between bands which are not harmonically related." Would this hold true in practice? Our empirical experimentation has essentially validated that quotation. The result has been a much more versatile antenna, with no degradation in 20 meter performance.

We began by constructing one 15 meter element and placing it near the boom. The swr on 20 meters immediately jumped to 1.7 to 1 from 1.3 to 1. Moving the 15 meter element along the boom and rotating it in and out of the plane of the 20 meter elements produced no further changes. As soon as the 15 meter element was placed within a yard of the boom, the swr climbed. We moved it further away, and the swr returned to normal. We tried the same experiment using a 10 meter ele-

Photo A. A most unorthodox 204BA. Nine elements and two gamma matches radically alter its appearance!

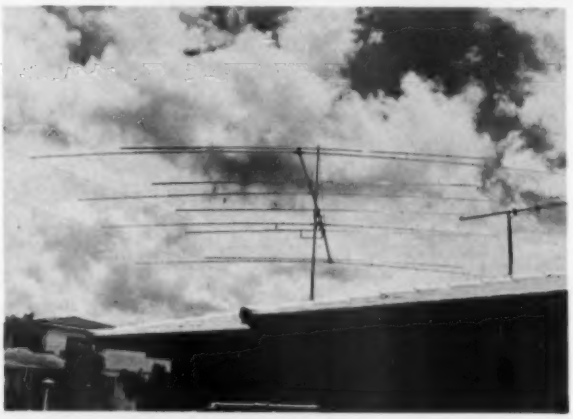

Photo B. A view of the "business end." The result is usually heard around the world.

FOR BEST PRICE AND FAST DELIVERY

CALL

1-800-325-3636

TOLL FREE

HAM RADIO CENTER

amo

H2

Radio World

CENTRAL NEW YORK'S FASTEST GROWING HAM DEALER

Featuring Yaesu, Icom, Drake, Atlas, Ten-Tec, Swan, Dentron, Pace, Palomar, Alda, Midland, Wilson, KDK, MFJ, Microwave Module, Standard, Tempo, Astron, KLM, Hy-Gain, Mosley, Larsen, Cushcraft, Hustler, Mini Products, Universal and Tristao Towers. *We service everything we sell!* Write or call for quote. **You Won't be Disapointed.** We are just a few minutes off the NYS Thruway (I-90) Exit 32

CALL TOLL-FREE 1-800-448-7914

ONEIDA COUNTY AIRPORT TERMINAL BUILDING
ORISKANY, NEW YORK 13424

Bob WA2MSH Warren K2IXN

NY STATE RESIDENTS CALL 315-337-2622 or 315-337-0203

The only thing we can't disguise is the professional quality of amateur antennas.

Amateur Radio spoken here!

FREE decal just for fun!

Name _____

Address _____

City _____ State _____ Zip _____

the antenna specialists co.

a member of The Allen Group Inc.
12435 Euclid Ave. Cleveland, Ohio 44106
Export: 2200 Shames Drive, Westbury, L.I., New York 11590
Canada: A. C. Simmonds & Sons, Ltd.

R-X Noise Bridge

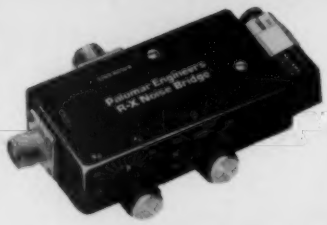

- Learn the truth about your antenna.
- Find its resonant frequency.
- Adjust it to your operating frequency quickly and easily.

If there is one place in your station where you cannot risk uncertain results it is in your antenna.

The Palomar Engineers R-X Noise Bridge tells you if your antenna is resonant or not and, if it is not, whether it is too long or too short. All this in one measurement reading. And it works just as well with ham-band-only receivers as with general coverage equipment because it gives perfect null readings even when the antenna is not resonant. It gives resistance and reactance readings on dipoles, inverted Vees, quads, beams, multiband trap dipoles and verticals. No station is complete without this up-to-date instrument.

Why work in the dark? Your SWR meter or your resistance noise bridge tells only half the story. Get the instrument that really works, the Palomar Engineers R-X Noise Bridge. Use it to check your antennas from 1 to 100 MHz. And use it in your shack to adjust resonant frequencies of both series and parallel tuned circuits. Works better than a dip meter and costs a lot less. Send for our free brochure.

master charge VISA

The price is $49.95 in the U.S. and Canada. Add $2.00 shipping/handling. California residents add sales tax.

Fully guaranteed by the originator of the R-X Noise Bridge.

ORDER YOURS NOW!

Palomar Engineers

Box 455, Escondido, CA. 92025

Phone: [714] 747-3343

Reader Service—see page 211

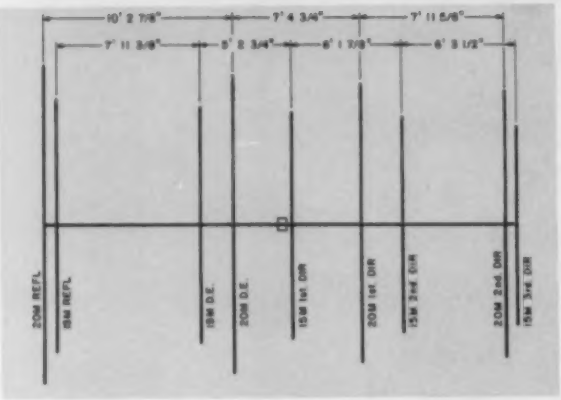

Fig. 1. Element spacing.

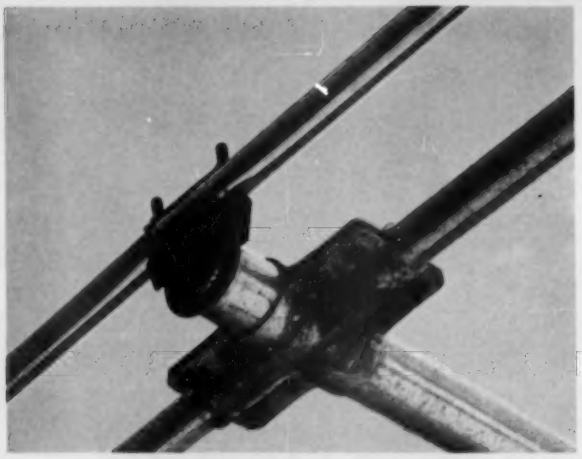

Photo C. Despite using just one muffler clamp per element, there has been no difficulty maintaining alignment.

ment, and, interestingly enough, this had no effect on the 20 meter swr. Bringing a Hy-Gain DB10-15A 3-element trap duobander close to the 204 produced a similar effect to that produced by the 15 meter element alone. Obviously, there was some interaction. Was it sufficient to reduce the 20 meter efficiency?

We tested for any 20m degradation by mounting three 15m elements on the boom and then using the beam normally on 20m over a period of several weeks. The additional elements did not increase the interaction over that introduced by the initial element, and we could detect no difference in the beam's 20 meter operation. If the 15 meter beam would function correctly, there appeared to be no reason why we couldn't interlace it with the 204BA. It would be desirable to provide an easily-adjusted matching system for each of the yagis, however.

One thing which we had noticed over the years of using the antenna at extremely low heights was how profoundly its capacitive coupling to the building was reflected in impedance excursions during rotation. Most annoying—rotate the array a few degrees, and then retouch the transmitter tuning. The better the antenna and feedline are matched, the less pronounced this effect becomes.

20 Meter Modifications

Hy-Gain's beta match is an inductive "hairpin" type of matching device. We decided to replace it with a more easily adjusted gamma match. Commercially manufactured coaxial capacitor-style gamma matches are much easier to install and maintain than are those which require a separate air variable capacitor in a waterproof enclosure. Viking Instruments* and Gotham Antennas** both market such a gamma match. We settled on the Gotham unit because it is a lower-Q device, which makes adjustment easier and less critical. Additionally, the Gotham gamma match is mechanically stronger and doesn't tend to fill with water and short out, as did two of our Viking matches.

The Hy-Gain driven element is split at the center for use with the beta match. We made it into a one-piece element by wrapping heavy-duty aluminum foil over the plastic center insulators and out over the element. An ohmmeter check showed that once the driven element halves were installed in the element-to-boom bracket, continuity was excellent. The aluminum foil should be covered with electrical tape and waterproofed by coating the tape with a sealant such as a popular uncured silicone rubber compound. For good measure, we attached a piece of coax braid between the two element halves as well.

Make sure you obtain good continuity between the driven element and the boom as well, if you plan to attach your feedline braid to the bracket which mounts the gamma match to the boom. Otherwise, attach the braid to the center of the driven element, not to its mounting bracket. It's also a good idea to run a bolt through the gamma tube itself for attaching the coax center conductor rather that relying on the U-bolt as the instructions suggest.

The length of the driven element wasn't altered from Hy-Gain's CW specification. The beta match, being an inductive device, probably requires a slight shortening of the driven element. Our method of making the driven element into an electrically one-piece element effectively lengthens it slightly. Therefore, resonance does not noticeably change. One additional benefit occurs as a result of this conversion. The 204BA will now display better bandwidth characteristics across the entire 20 meter band.

15 Meter Construction

Fig. 1 shows the spacing of both sets of elements along the boom. We had originally constructed the antenna with the 20 meter reflector mounted at one end of the boom, and the remainder of the elements spaced according to Hy-Gain's instructions. This left 2 inches of boom unused beyond the 20 meter second director. We chose to mount the 15 meter third director in this area to maximize its spacing. If you don't have room to do this on your particular 204BA, you can move that director inside of the 20 meter second director

Element	Length
Reflector	23' 5-1/2"
Driven Element	22' 6-1/2"
1st Director	21' 6-1/2"
2nd Director	21' 1-3/8"
3rd Director	20' 8-1/4"

Fig. 2. 15 meter element lengths.

*Viking Instruments, 73 Ferry Rd., Chester CT 06412.

**Gotham Antennas, 2051 N.W. 2nd Ave., Miami FL 33127

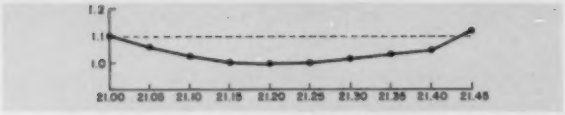

Fig. 3. Swr curve across the 15 meter band.

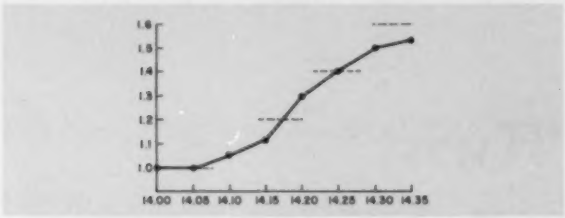

Fig. 4. Swr curve across the 20 meter band.

without affecting performance.

The boom of our 1968 vintage 204BA measures 26 feet, 2 inches. We needed to use it all if we were to mount 5 elements. Also, we had to locate some of the 15 meter elements very close to existing 20 meter elements. For these reasons, we dispensed with the usual aluminum element-to-boom mounting plates such as those used by W8ZCQ in his article, "Working 15m with a 20m Beam," *73 Magazine*, June, 1978.

Photo C shows how a single 2-inch muffler clamp can be used to mount each element. If you can't get muffler clamps with a long U-bolt, you may have to use hardware-store U-bolts with the saddles from your muffler clamps. The U-bolt must be long enough to come up through the element. We have had no trouble with elements slipping or otherwise coming out of alignment, and the array has withstood winds gusting to 56 mph.

Each 15 meter element is constructed of two 12-foot lengths of 3005 aluminum tubing. Make the center of each element from a single 1-inch diameter run. Cut a single run of 7/8-inch tubing into two 6-foot lengths. These are inserted into the ends of the center section. The ends of the center section should be Xed with a hacksaw so that hose clamps can pull it down snugly over the end sections. Our 1-inch tubing has a wall thickness of .041 inches, while our 7/8-inch tubing has a wall thickness of .035 inches. This combination produces a nicely telescoping assembly.

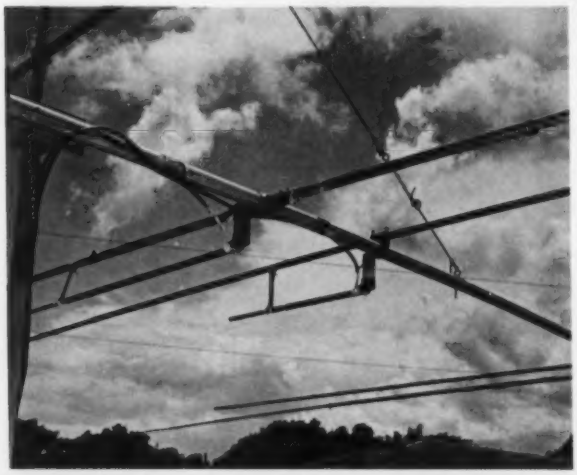

Photo D. White material on the gamma matches and over the electrical tape is GE Silicone Seal.™ It also protects the aluminum foil on the 20 meter driven element.

Adjustment

The gamma matches are adjusted in the normal manner, 20 meters first, and then 15. A good starting point for the shorting strap is a distance of 10 percent of the total length of the driven element, out from the center of the driven element. Preset in this fashion, both sections displayed an swr of less than 1.8 to 1 prior to any additional adjustment. Slide the coaxial capacitor part of the gamma match in and out until lowest swr is obtained. Then move the shorting strap a half inch and readjust the coaxial capacitor. By alternating these adjustments, you should easily find a combination which yields an swr of 1.2 to 1, or less.

It is ideal, of course, to adjust the gamma matches with the antenna in its final operating position. Most of us cannot accomplish this. We have found that the swr changes only slightly once the antenna is installed if it has been carefully adjusted either on top of a ladder or pointed vertically into the air with its reflector resting on the ground.

Performance

Figs. 3 and 4 show the swr curves on the 15 and 20 meter bands, respectively. It is quite permissible (although purists may disagree) to use the gamma matches to "fudge" the resonant frequencies a bit, if desired. Our matches were adjusted for lowest swr at 21.125 and 14.025 MHz. The 20 meter performance remains, as far as we can observe, absolutely unchanged except for the previously mentioned improvement in bandwidth. We have no way to measure the forward gain on 15 meters. However, "if you point it at 'em and give 'em a call . . . you usually get a reply." The front-to-back ratio on 15 meters runs about 20 to 25 dB and the front-to-side is just about 40 dB.

Some Thoughts

We were so pleased with this project that we decided to try to add 10 meters as well. Predictably, the interaction was so bad that we had to forego our attempts to triband the 204BA. The 10 meter elements didn't affect the performance on either 15 or 20 meters. We were just unable to make the 10 meter section perform as a beam. One set of adjustments gave us a slight bit of gain—off the reflector! Another set provided an omnidirectional pattern with signal levels about three S-units under a dipole. In no case did it make any difference whether the 10 meter elements were insulated from the boom or not. We would very much like to hear from anyone who successfully adds both 10 and 15 meter elements to a 204BA. That would surely be a most impressive tribander!

Parts Availability

In cooperation with Gotham Antennas, we are offering a complete kit to interlace five 15 meter elements with an existing 204BA. Elements, hardware, both gamma matches, and instructions are included. Please send an SASE for details.■

Bibliography

1. *The ARRL Antenna Book*, 1974 edition.
2. McCoy, Lewis G., "Why a Beam Antenna?", *QST*, January, 1972.
3. Orr, William I., *Beam Antenna Handbook*, 1976 edition.
4. Umberger, Dan, "Working 15m with a 20m Beam," *73 Magazine*, June, 1978.

Here's a "Twist"

—an OSCAR antenna with a difference

Introducing the 8XY/2M.

Dave Ingram K4TWJ
Eastwood Village No. 1201 S.
Rt. 11, Box 499
Birmingham AL 35210

If you are one of the many amateurs who has experienced communication via our OSCAR orbital satellites, you know the challenge and enjoyment of satellite operations. The various aspects of OSCAR communications have something to catch nearly everyone's fancy: convenient operating times, orbital calculations and tracking systems, duplex style operating, unobtrusive antenna setups, low TVI levels, etc. Amateurs with limited time available to enjoy on-the-air operations truly appreciate the pinpoint-accurate communication times synonymous with satellite passes. What else could one ask?

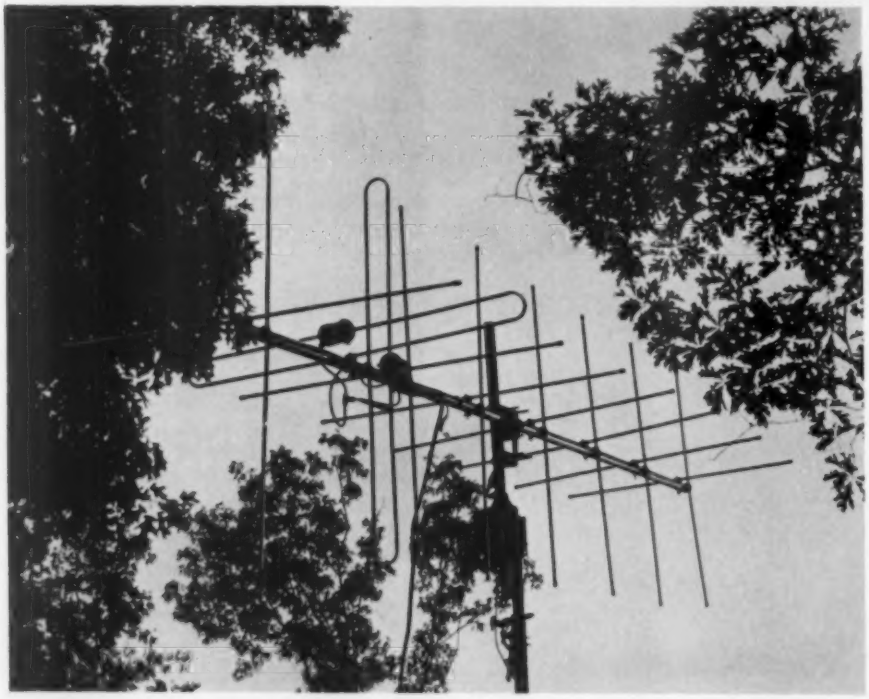

The Spectrum International 8XY/2M OSCAR antenna is mounted on a 30-foot push-up mast which is tilted 30 degrees. This "skyward tilt" bypasses elevation rotor needs.

As with any station setup, the antenna system plays a major role in its performance. Quite simply, it's what's "up top" that counts! A poor skywire can undermine the most elaborate amateur setup, while an efficient antenna can make a mediocre setup perform like a million dollars. OSCAR setups are no exception to this rule. If you plan to fully enjoy OSCAR, you'll definitely benefit from using an antenna designed for satellite operations. Such an antenna is the 8XY/2M 8-element, 2-meter "Twist" antenna distributed by Spectrum International.

I found that assembling the 8XY/2M antenna was a refreshing change from the usual time-consuming task of rigging clamps and measuring element mounting locations. This gem went through smoothly in an hour's time, with heavy-duty bolts and wing nuts making hand-assembly a snap. Not a single tool was required until transmission lines were connected to

the driven elements. Each element of the S.I. "Twist" is ¼-inch aluminum tubing which is precut and capped with color-coded tips to aid assembly. The boom is also predrilled and color-coded to ensure quick, foolproof assembly. *All* hardware for the antenna is *preassembled*, and an extra element-mount is included in case one becomes lost or broken. The massive boom-to-mast clamp could support a triband beam. Very nice! I must admit that this was the first time I've enjoyed (sort of) constructing an antenna.

The 8XY/2M antenna can be fed four different ways to obtain either vertical, horizontal, right-hand circular, or left-hand circular signal polarization. A ready-to-install phasing harness for circular polarization is available from Spectrum International, or you can fabricate your own harness from details supplied in various antenna books. Since I didn't care to kill time building a harness, I used the S.I. unit—and I'm glad I did.

If a fixed polarization is desired, the harness can be mounted at the antenna proper. If various polarizations are desired (for operating various modes of OSCAR), two transmission lines can be run from the antenna's driven elements and the phasing harness placed at the operating position. A coax switch can then be used to select the required polarization.

My Spectrum 8XY/2M antenna replaced a 2-month-old, 3-element array previously used for satellite work, and a significant signal improvement was realized. Suddenly, I was able to easily access the satellite and "stay into" the transponder for a longer period of time during each pass. I also noticed that my signal wasn't as prone to the heavy fades which were apparently due to polarization shifts during passes. This gain alone was worth the change to Spectrum's 8XY/2M antenna, as it allowed me to successfully operate slow scan TV via satellite.

When OSCAR 8 was placed in orbit, I decided to remove a few director elements from the 8XY/2M to reduce my erp to this new "bird." This antenna change worked very well, but a couple of days later, OSCAR 8 lost sensitivity and I had to replace the removed elements. Hopefully this satellite problem is merely an overloading situation which will soon be rectified.

I truly feel that the 8XY/2M antenna was a prime factor in my operations of successfully transmitting the first SSTV pictures via OSCAR 8 during orbit 102. Since I have only one small TV rotor to use with the 8XY/2M, I bent the rotor-to-boom mast approximately thirty degrees. This tilt allows the antenna to "look skyward," and bypass elevation rotor requirements.

In conclusion, I think amateur satellite communication and Spectrum's 8XY/2M are an ideal combination which all amateurs would thoroughly enjoy experiencing. There's no better way of renewing one's interest in amateur radio than by trying a new aspect of communication.

The 8XY/2M antenna is available from Spectrum International, Inc., P.O. Box 1084, Concord MA 01742. This 16-element array (8 elements vertical, 8 elements horizontal) is in the $45 to $50 price class. ■

NEW!

ok®

PRB-1 DIGITAL LOGIC PROBE

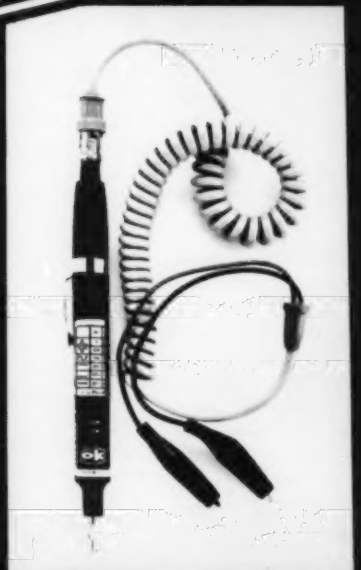

Compatible with DTL, TTL, CMOS, MOS and Microprocessors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels, using LED's to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt pocket portable (protective tip cap and removable coil cord)

$36.95*

- DC to > 50 MHZ
- 10 Nsec. pulse response
- 120 K Ω impedance
- Automatic pulse stretching to 50 Msec.
- Automatic resetting memory
- Open circuit detection
- Automatic threshold resetting
- Compatible with all logic families 4-15 VDC
- Range extended to 15-25 VDC with optional PA-1 adapter
- Supply O.V.P. to ± 70 VDC
- No switches/no calibration

* ADD $2.00 FOR SHIPPING
(N. Y. CITY AND STATE RESIDENTS ADD TAX)

OK MACHINE & TOOL CORPORATION ⌐05
3455 Conner St., Bronx, N.Y. 10475 (212) 994-6600 / Telex 12509

Reader Service—see page 211

A Fortified 2m Whip

—won't bend in the breeze

Donald A. Habeck W9AMM
5973 Sugarbush Lane
Greendale WI 53129

Are you in need of a good 2 meter mobile antenna? How about an antenna for your base station? Or, do you just plain have the feeling that your station has become too commercialized and that a portion of your setup should be home-brewed? Then, why not try this antenna project? In actual checks, it was found to compare favorably with the commercially-made antennas tested. Whether you decide to use the antenna for mobile or base station operation, you'll be pleasantly surprised with its performance. The antenna is easy to construct and tune, and, best of all, it's inexpensive.

Photo A. The coil protective cover has been removed in this picture to show details of the base coil.

Design

One unique feature of this antenna is the construction of the whip. It consists of a 1/4"-diameter fiberglass rod with a shield of copper braid. This design was selected because it provided rigidity to minimize deflection during high winds or mobile operation. Research has shown that deflection of the flimsy-type whip causes degradation of the vertically polarized signal. In some instances, the efficiency of a 5/8-wave antenna actually becomes less effective than a 1/4-wave antenna.

The fiberglass rod is from the pennant-topped-type whip that is made for mounting on bicycles. Many retail stores have given away these whips as promotional items. They also are readily available from department stores and bicycle shops for approximately $1.25.

The impedance matching coil is 3 turns of no. 14 tinned copper wire wound on a wood thread spool from your XYL's sewing basket. It is tapped 1-1/8 turns from the ground end. A small ceramic trimmer capacitor across the coil provides a precise match in conjunction with the base coil tap. The impedance matching circuit is protected from the weather by enclosing it in an empty plastic container. Fish food had come in the container we used.

Construction and Assembly

Since no tricky construction or special tools are needed, no problems should be encountered. The fiberglass rod is prepared by drilling the 1/16"-diameter hole from the bottom as indicated in the diagram. Another 1/16"-diameter hole is drilled on the side of the rod at point A. This should be drilled at a slight angle towards the bottom to make the routing of the coil tap wire easier. The depth of this hole is only to the extent of meeting with the hole previously drilled from the bottom. When drilling these holes in the fiberglass rod,. it is important to use a sharp drill and not allow the drill to heat up. It is best to cut the whip to proper length after the coil form is secured in place.

Prepare the coil form and other parts as indicated. Check that the hole in the spool is of the proper

diameter to permit the spool to slide on the rod. The notches filed into the coil form prevent the coil from slipping. The hole for the coil tap is displaced 1/8 of a turn from the alignment of the bottom notch.

After the coil form is prepared, feed the 20-AWG tap wire through the tap-wire hole and out the bottom of the spool. Slide the form over the fiberglass rod and carefully route the tap wire through the drilled hole at point A and downward through the rod, out the bottom. Allow sufficient length for the tap wire to be soldered later in the PL-259 connector. Apply epoxy glue to the appropriate rod area, slide the coil form into its proper position on the rod, and take up any slack in the top wire. The final position of the coil form should be such that the tap-wire holes in the spool and the rod line up with each other and the rod extends sufficiently below the bottom of the spool to accept the UG-176 adapter. To hold the tap wire securely in position, apply a small amount of epoxy to the tap-wire opening in the spool and at the bottom of the whip.

Two holes must be drilled in the cover of the coil protector. A 1/4" hole in the center will permit it to be slipped over the bottom of the whip. With the cover in position on the whip, use the notch of the coil form for determining the position of the second hole. This is a 1/8" hole and should be drilled in the correct position to allow the ground end of the coil wire to pass through the cover and be soldered to the PL-259 connector. After both holes are drilled in the cover, epoxy the cover (threads towards the coil form) to the bottom of the wood spool. Position the feedthrough hole in the cover so that the tap occurs at 1-1/8 of a turn when the coil is added.

With epoxy applied to the bottom of the fiberglass rod, slide the UG-176 reducer onto the rod and up against the container cover. Check that none of the other parts has slipped from its proper position. At this point of construction, it is best to allow the epoxy to harden before proceeding.

After the epoxy hardens, the UG-176 reducer can be screwed into the PL-259 and the tap wire soldered in the center pin. Measure 42½ inches from the top of the coil form and cut the whip to length.

The next step is to slide the copper braid shield over the fiberglass rod. Tinned braid is recommended. However, if this is not readily available, the shield from RG-8/U coax cable will work fine. If the braided shield is too snug to readily slip over the rod, the diameter of the shield can be enlarged by squashing the braid together a little bit at a time. If the diameter of the shield has to be enlarged to any extent, be sure to allow for the shrinkage in length that will occur. The braided shield is slipped over the full length of the rod down to the coil form. The shield can be snugged to the rod by running your hand tightly along the braid.

One end of the coil is secured by routing a 24" piece of 14-AWG wire through the hole in the cover and soldering it to the side of the PL-259 connector. With the one end secured, the 3-turn coil can then be easily wound on the form and soldered to the whip shield. Solder the tap wire 1-1/8 turns from the coil bottom (ground) and the trimmer capacitor across the entire coil. Cut off the braid shield so that it extends 3/8" above the top of the rod; twist and

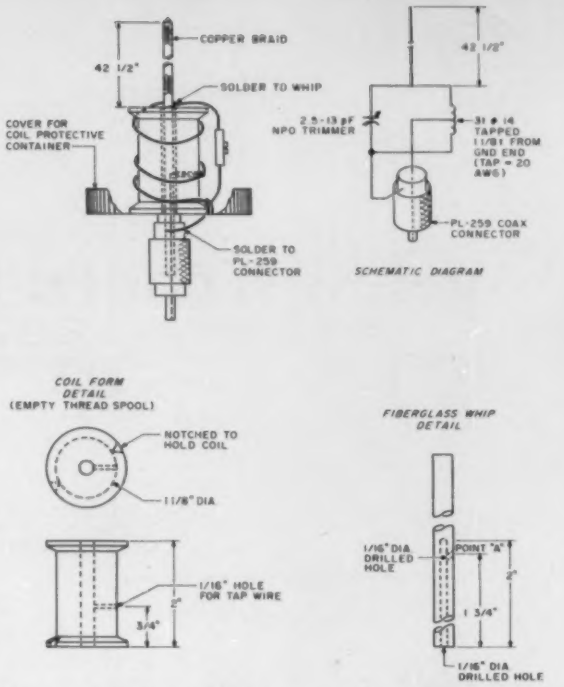

Fig. 1. A rigid 2 meter antenna for base or mobile operation.

solder. To protect the whip from the weather, shrink tubing, plastic electrical tape, or a protective spray can be used.

Mounting

For base station operation, I used a simple L-shaped aluminum bracket with an SO-239 connector, RG-58 coax, and four 19¼" ground radials. This arrangement is secured with U-bolts to the mast above a triband beam. For mobile operation, the bracket design is dependent on the type of car and individual desires. For my mobile operation, I mounted a simple bracket and connector arrangement directly to the luggage rack.

Tuning

The easiest method to tune the antenna is with a field-strength meter at a distance of approximately 2 to 3 feet. With the antenna connected and the transmitter keyed on an unused simplex channel, adjust the trimmer capacitor with a non-metallic screwdriver for a peak field-strength indication. The vswr will be minimum at this point. Numerous antennas have been built, and, on all occasions, vswrs of less than 1.2 to 1 were obtained. The antenna, of course, should be situated away from all objects and as high off the ground as practical during tuning procedures.

With a 5/16"-diameter hole drilled in the bottom of the plastic container to accommodate the whip, slide the container over the whip and screw it into its cover. If the container affects the tuning of the antenna, drill a hole in its side and retune the antenna with the container in position. With RTV, seal the top opening of the container, but not the bottom. The hole in the cover will help prevent any moisture from accumulating.

Do you want to generate conversation? Just mention on your local repeater the fact that you're using a home-brew antenna.■

Ageless Wonder: the Collinear Beam

—sure beats a dipole

Good results for a few dollars.

C. Stewart Gillmor W1FK
Spencer Road
Higganum CT 06441

Ever since the ready availability of aluminum tubing after the second World War, yagi beams have been popular with hams. More recently, quads have joined as popular antennas for the HF bands. These parasitic array antennas have a number of attractive features, including high gain, unidirectional radiation, and rotatability. Realization of their full potential, however, requires relatively expensive support equipment, including tower and rotor.

I have enjoyed using collinear wire beams, which give reasonably narrow bidirectional radiation patterns. These arrays are composed of elements arranged in a straight line. Each element is connected to the next by a phasing stub so that all elements operate in phase. The collinear antenna is often used at VHF and UHF in vertical orientation, but at HF it is only practical to erect horizontal collinear antennas. Collinear antennas have long been used in military applications, or in any situation where need exists for a rugged, directive HF antenna which can quickly be erected and which can deliver good performance. Especially for the Novice or for the ham on a budget, the collinear should be considered because it is easy to construct and it is inexpensive.

Many antenna texts discuss collinear antennas, but few provide complete design information. Particularly omitted is information on impedances. Collinear antennas may use elements of varying electrical length, but most common is the one-half wavelength element. Collinears may have as many as 6 elements. Because of mutual coupling and increasingly uneven current distribution obtained as one adds elements, most hams have built collinears with 2 or 3 elements. Highest gain is obtained if the antenna elements are spaced with 0.4 or 0.5 wavelengths of space between the ends of the elements, but this introduces construction problems. Less gain but much simpler design results from separating the elements only by use of an insulator.

I give design criteria below for 3-element 20 meter and 5-element 15 meter collinears, each of which requires less space to erect than an 80 meter dipole. I also give data on impedance characteristics at and near resonance to aid in selecting a suitable feedline. Many collinears are fed between the ends of the elements, where a very high impedance exists. In the antennas described below, feed occurs in the center of an element at a relatively low impedance, high current point. This permits a good match to 300- or 600-Ohm balanced lines. If one prefers, a 4:1, 6:1, or 9:1 ratio balun may be inserted so that the antennas may be fed directly with coax. My collinears are fed with balanced line, and a balun is introduced just outside the shack.

I was not able to find information on the impedances met when feeding collinears at current points, so I performed measurements on 3- and 5-element collinears suspended ¼ to 1 wavelength above ground. The impedances were measured on my Boonton 250-A "RX" meter. The impedance at resonance of the 3-element centerfed antenna was found to be 372 Ohms resistive; the 5-element antenna showed an impedance at resonance of 600 Ohms. Each of these antennas operates across an entire ham band with vswr of less than 1.5:1 (±1% of design frequency), using no matching device except a

Frequency	Dimensions			½-wavelength in feedline	
				coax V = 0.66	twinlead V = 0.82
	A	B	C		
21.2 MHz	11' 4"	22' 7½"	9' 6"	15' 4"	19' 0"
14.15 MHz	16' 6½"	33' 1"	14' 3"	22' 11½"	28' 6"

Table 1. Dimensions as measured for 15 and 20 meter collinears. A = halves of center element; B = outer elements; C = matching stubs.

properly chosen balun. The transmission line is chosen to be an integral number of half wavelengths. Of course, a balanced line tuner may be employed and the balun omitted. One can also tap up and down the transmission line for impedance matching purposes if this method is desired.

It is worth pointing out that the velocity of propagation of electromagnetic waves along transmission lines varies with the dielectric material used in constructing the line or cable. This velocity factor (V) must be included in calculating electrical wavelength in various types of lines. For example, open-wire line can be assumed to have a velocity factor of nearly 1.0 (or perhaps more exactly, 0.95 to 0.975). Thus, a wavelength in free space is nearly the same as one measured along open-wire line. The coax cable usually used by hams has a V of 0.66, and most 300-Ohm polyethylene balanced line ("twinlead") has a V of 0.82. This means, for example, that a wave of 15 meters length in free space has a physical length in coax of about (0.66 × 15m) = 10 meters and a physical length in 300-Ohm twinlead of about (0.82 × 15m) = 12.3 meters. In the designs below, I use 300-Ohm twinlead for the ¼-wave matching sections.

The 3-element collinear achieves a gain of about 3.3 decibels over a simple half-wave dipole and has a beamwidth to the half-power points (where the field strength voltage drops to 0.707 of its maximum value) in the horizontal plane of about ±18°. This is for a horizontally oriented antenna, of course, and the radiation is greatest at right angles to the axis of the array. The 5-element antenna achieves a gain of about 5.3 decibels and a beamwidth of about ±10° or so. Each antenna's horizontal radiation pattern is bidirectional with minor side lobes. I have designated the centerfed element halves as "A" in the drawing (Fig. 1) and in Table 1, the pairs of outer elements as "B", and the matching sections as "C", for the case of the 3- or 5-element centerfed collinear.

Construction Hints

All half-wave elements should be of equal length in a given antenna. One can erect the centerfed element and adjust it to exact resonance, if desired, then add the stubs and outer elements. Velocity factor V was found to be 0.95 for the 3-element collinear. The 5-element collinear resonated slightly higher than the calculated frequency; evidently a V of 0.95 overcorrects for end effects. I found V here to equal 0.975, and I give the actual determined dimensions for each antenna in Table 1.

I used home-brew nylon insulators which are 2 to 3 inches long and cut out of scrap. They are light and tough. One could also use Plexiglas™ or some other material or commercially-made ceramic insulators.

The phasing sections could be of open-wire line (remember, then, V would be about 0.95), but I chose 300-Ohm twinlead because the stubs tend to blow around in high winds and ladder line might twist up and short. (Also, I had a few scrap pieces of 300-Ohm twinlead in the shack.)

The antenna elements themselves I made of odds and ends of #16 and #14 hard-drawn copper wire, but almost anything will do here.

Care should be taken to fasten the phasing stubs to the insulators so that they do not fatigue and break off. Solder the stubs

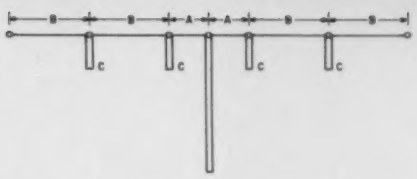

Fig. 1. Centerfed multi-element collinear wire beam. A = ¼ wavelength (ft.) = 246 (0.95)/f_{MHz}; B = ½ wavelength (ft.) = 492 (0.95)/f_{MHz}; C = ¼ wavelength (ft.) = 246 (0.82)/f_{MHz}.

closed at the ends. I suspended the collinears high in some maple trees using clothesline pulleys and ¼-inch nylon line. One has been up for two winters and has survived numerous ice storms and high winds. You might wish to silicone or wax the twinlead to minimize swr changes during rainstorms. I'm not fussy about these antennas, except that I make sure that I never erect an antenna near, over, or under a power line.

In Table 1, I have given actual dimensions for center frequencies of 14.15 MHz for the 3-element and 21.2 MHz for the 5-element antenna. I use these collinears for working into Europe with my Triton IV. The 15 meter collinear would make a dandy antenna for Novice DXing. If one has the space for an 80 meter dipole, then 2 or 3 hours invested in construction and erection of a multi-element collinear will probably result in surprise and pleasure that such a simple antenna brings such good results for only a few dollars. ■

The RF testing kit for professionals.

The WATT-KIT puts RF equipment testing all together. It is a convenient, all-purpose power-metering kit for RF coaxial cables and 7/8" transmission lines. The kit consists of the Model 1000-A Wattmeter, the SNIFFER adjustable signal sampler, and a spare UHF connector and patch cable. It's all contained in a carrying case that includes space for two Quick Match Connectors and six measuring elements. A 100 watt dry terminating load is also available.

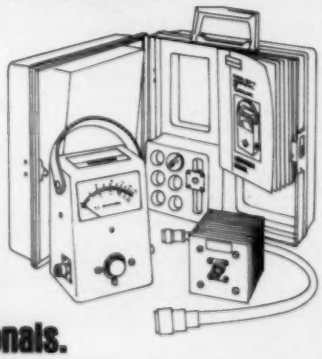

Wattmeters for professionals.

For the name of your local distributor call toll free 800-341-9678

D25

GS DIELECTRIC COMMUNICATIONS
A UNIT OF GENERAL SIGNAL
RAYMOND, MAINE 04071 • TEL 207-655-4555 • 800-341-9678

Three Baluns for a Buck

—go find yourself a junked TV

Better than mail-order.

Editor's note: This article was written while the author was in Iran. He has since returned to the United States.

Donald E. Lively W6SJQ
9 Wedgewood Drive
Millington NJ 07946

Activating an HF radio station in areas of the world where hamming is not too common calls for a certain amount of improvisation. This is particularly true if station logistics have not been carefully planned prior to leaving home base.

Material Selection and Preparation

The problem facing this station was that of acquiring a balun for a three-band dipole and then a three-element beam. Experiments with a home-made balun in the US using the ferrite core of a defunct TV flyback transformer had been quite successful on 80 and 40 meters. It was decided, therefore, to see if the same approach would do for 20, 15, and 10. It figured that a core material able to handle the TV horizontal retrace without significant loss should be fairly good for HF radio transmission. Actual measurements through the finished balun at 28 MHz and lower frequencies show less than a ½-dB attenuation.

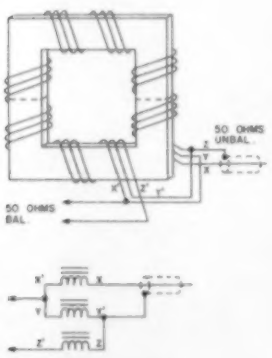

Fig. 1.

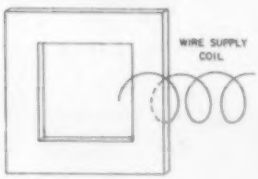

Fig. 2.

Initial Construction

Actual construction was started in the following fashion. A burned-out flyback was obtained from a TV service shop, and all of the windings, plus sealing compounds, were removed. After disassembly, two C-shaped core halves remained. These are normally mated at their highly polished surfaces and clamped together to form a solid O-shaped rectangle. To avoid any shorted turn effects from the clamping arrangement, and to make unobstructed space for windings around the full core circumference, the two core halves are held together with an epoxy compound. A very thin film of steel-filled epoxy is used for this purpose—hopefully this minimizes discontinuities in the magnetic circuitry of the core.

Some further core preparation is still needed before putting windings in place. This includes removal of any sharp edges with a fine file or abrasive cloth (to avoid scratching the enameled wire). The last step of preparation is to place two layers of plastic or glass tape over the core—this gives a very smooth surface for the winding process.

The actual winding calls for considerable care if a low swr is to be realized. Considerable experimentation took place to get best results—and two precautions turned out to be important in getting good balance and low loss: sym-

metrical placement of the turns and uniform "turn shape." The results of this care are uniformly distributed capacity within and between turns and equal inductance for each of the three trifilar windings.

The way the tight and uniform turns are achieved is to employ a modification of the "bobbin" technique (see Fig. 2) used on commercially-wound toroids. For this application, start with a single piece of about no. 20 gauge wire approximately 18 inches long. Thread the wire repeatedly through the core center until eight turns are in place. Distribute the turns evenly and clip all but about two inches on each end of the winding. Remove this temporary winding, straighten it, and measure its length. This will be the length of the permanent windings. Cut three lengths of no. 14 Formvar or similarly insulated copper wire and wind each one around a D-cell battery or similarly sized form to create the "wire supply coil" for the finished balun.

Next, take one of these coils and "screw" it onto the TV transformer core. Do this by spreading the turns and placing an end through the center hole, rotating the coil until it is all on the core. Straighten one end of the coil so that the 2" excess extends out from the core, then press tightly against the core this first turn of the "wire supply coil." Use your thumb to force each turn of the balun into shape against the core. Form each turn diagonally so that two turns are placed on each side. (Depending on where you wish to make your connection to the antenna and transmission line, you may start and finish at a corner or a side.)

Repeat the process for each of the next two windings. To keep the turns tight so that their final spacing can be evenly positioned, temporarily twist the two ends of each coil together. This will prevent any unwinding. Place a few drops of 5-minute epoxy glue at the point where windings start. When the windings are firmly set and evenly spaced, wire and solder them as shown in the diagram of Fig. 1. Be especially careful to make the connections between the windings symmetrical (to ensure equal inductance and coupling). Failure to do this will create a poor swr and increase loss. (An associate of mine has run tests on several commercial baluns and found that inattention to this matter accounts for fairly wide variations in performance, particularly at the higher frequencies.)

You are now ready to attach the leads on the balun which connect it to the feedline and antenna. Mount a coax fitting at one corner, and for the feedline, and the flexible leads (short lengths of coax outer conductor braid) for the dipole connection.

Final Adjustments

With a short length of coax, connect the balun through an swr bridge to a transmitter with variable output carrier. Connect the flexible leads to a dummy load, being careful to keep them straight, symmetrical, and evenly spaced. (Pieces of RG-58 outer covering can be used to protect the leads from the weather and to avoid shorts during the tests.) Next, set the rf source on 28 MHz and apply enough power to get a good reading on the swr meter in the forward direction. (Run the power high enough to ensure that the transmitter output "looks like" its transmission-line drive impedance—with some solid-state rigs, this may vary at very low power settings.)

Switch the swr meter to reverse and observe the reflected power level—it should read 1:1.2 or less. If it's higher, remove the rf power and try evening up any irregularities in the windings or significant spaces between adjacent wires in the individual turns. With careful dressing of the turns and connecting leads, this kind of performance can be realized.

The transformer (balun) is now ready for final assembly and mounting. Numerous schemes are appropriate. For my application, no enclosure was used, but just encapsulation in epoxy with a piece of vinyl tubing threaded through the center to tie the unit to the beam boom. (This was because an earlier model placed in a metal can arced to ground from a nearby lightning strike.) An appropriate form to contain the epoxy while it sets was made from the sides of a polyethylene detergent bottle. This material can be "welded" using a soldering iron to melt and join edges of individual pieces to form the desired shape of container.

Incidentally, the 30¢ cost refers to the wire—it has to be purchased locally. The epoxy is, of course, optional and is an added expense. The TV transformer core was a gift from a friendly Iranian TV repairman—a similar acquisition is no doubt possible anywhere.

The balun has worked fine and is superior to a mail-order kit which has been rebuilt numerous times but which has never given a satisfactory 10 meter swr when connected to a very load-match-sensitive Atlas 210X. ■

Newest, Low Cost
INLINE RF WATTMETER
USES **NO** EXTERNAL DELICATE SLUGS
COVERS 20 MHz THRU 1000 MHz
TELEWAVE MODEL 44

No Band Switching
20 MHz — 1 GHz
0 to 500 Watts
In 5 Ranges
Forward And
Reflected Power
Rugged Die-Cast
Metal Case
"N" Connectors
UHF on Special Order
VSWR Conversion
Chart on Rear

Shipped From Our Stock • Just $295 Complete
All M.O. & Cert. Check orders shipped next day Calif. Res. Add 6% Tax
ROSS DISTRIBUTING CORP. • (213) 919-3446
P.O. BOX 5003 • COVINA, CA 91723 R35
EG-73-7/8-79

So You Want to Raise a Tower

—do it safely, do it right

A simple guide to an important subject.

James Wyma WA7DPX
513 W. 10th St.
Casa Grande AZ 85222

Sooner or later every ham has the desire to put up a tower. The intent of this article is to save you from some of the problems you can have by improper installation of your tower. These problems can result in loss of your tower and antennas, loss of your ham shack (a falling tower can do a great deal of remodeling to your shack), and last, but not least, loss of your or someone else's life. The first two losses can be corrected; the third can't!

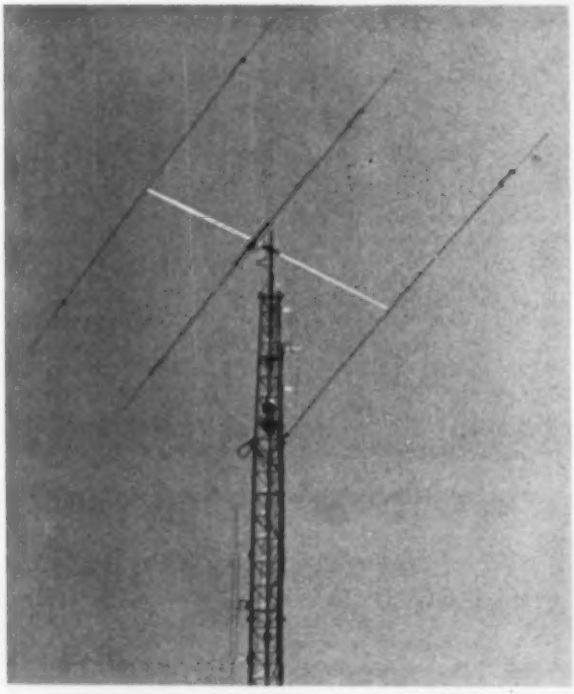

Photo A.

First off, let's establish some basics. There are only two *safe* ways to erect a tower: with a crane or with a gin-pole. If you have the money, the first is the easiest. The second method is the one used by those of us who have more time than money.

Assuming that you have decided on the second method, you will have to do some tower climbing. There is one very important principle involved in tower climbing. Simply stated, it is: "If you are unable to strap a safety belt on the tower, let loose with both hands and lean back comfortably for a short nap, then keep both your feet on the ground."

If your legs are shaking, your hands are white from hanging on, and all you can think of is "I'm going to die," then you have no business on a tower!

Try the technique that I use. Tell yourself that once you have climbed more than ten feet, you probably will be killed if you fall. If you don't like this approach, you should get someone else to do the climbing.

Once you have doubled your life insurance—or found some tower rigger to do the climbing—you now have to decide where to put it. The ideal place is right next to the window in your shack, but this doesn't always turn out to be possible. Considerations governing tower location are as follows:

1) The guy-line anchors should be kept within your property boundaries, if at

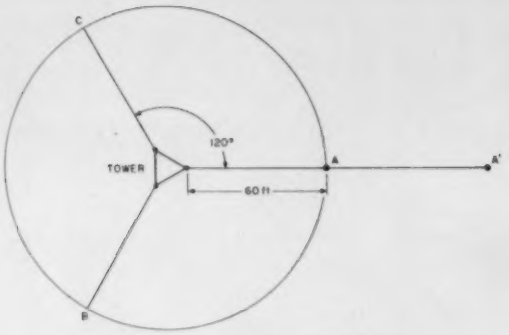

Fig. 1. Diagram for 60′ tower and guys.

all possible.

2) The anchors should be at a distance of at least two-thirds of the tower height away from the base of the tower, and, preferably, a distance equal to the tower height. Example: A 60′ tower should have guy supports at a distance of 40′ to 60′ from the base. Three guy lines are generally used.

3) The guy-line anchors should be at 120° spacing from each other. If available, a surveyor's transit should be used to site their locations. Fig. 1 demonstrates this. Note that it is not necessary to have all the anchors in a circle (i.e., equal distance from the base). This is shown by point A′ of Fig. 1. Every effort should be made to keep the anchors as close to 120° apart as possible. The more you deviate from this, the more vulnerable is the tower to twisting torque.

4) Guy lines should not be obstructed by power lines, trees, or parts of any building.

5) Be sure your community has no restrictions on tower erection; obtain a building permit if one is required.

6) Make sure there are no buried water, gas, or power lines in the areas where you plan to dig your base- and guy-anchor holes. Call the utility companies; they will locate them for you free of charge.

7) If at all possible, attach the tower to your house or shack. In most cases, this will classify it so that your home-owner's insurance will cover it. Check with your agent to see if this applies to your policy, and, if it does not, ask him about a separate liability policy. In most areas, a tower is considered an attractive nuisance for juveniles, and if a child is hurt on your tower, you are at fault even though it is on private property. If your tower falls on a neighbor's house, more than "Gee, I'm sorry about that!" is usually required to fix the damage.

8) Determine that the ground where your base and anchors will be is solid enough to hold them in place. Freshly-excavated ground should be avoided. (Quicksand, mud, and earthquake faults also should be avoided.)

Now that we have the basics out of the way, let's get started on putting this thing up. The tower foundation and the guying are the two most important parts of your whole installation. Don't take short cuts in either of these areas. A few bucks saved on cheap concrete or junky guy lines could cost you thousands of dollars in the long run.

The type of ground (clay, sand, soft dirt, or whatever) and the height of the tower will determine how much concrete you need for the base and guy-line anchors. A very good place to get this information is in the Rohn tower catalog. You can probably obtain a copy of it from Rohn or your Rohn dealer. This will give you a lot of valuable information on how and where to guy your tower and how big to make your holes for concrete. Under no circumstances should the base or anchors contain less than ¼ yard of concrete.

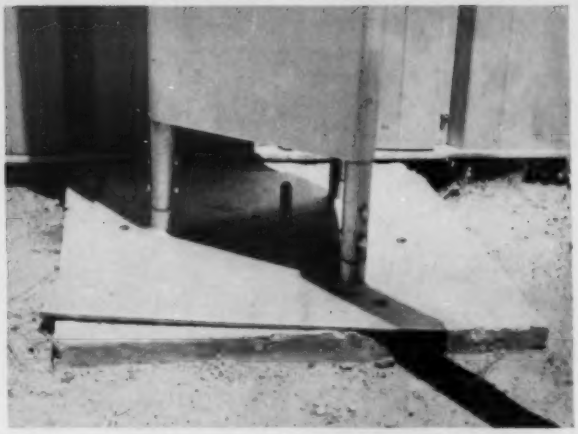

Photo B. The base plate is anchored to the tower foundation with one bolt.

The specific information in this article is pertinent to most towers, but it is specifically related to the Rohn 25G tower. This is one of the most popular ham towers and the one with which I have the most experience.

In Photo B, you can see what I prefer for the tower base. Note that the concrete sticks up above ground level. This is accomplished by making a frame out of 2 × 4s, with the 4″ side vertical. There are a number of reasons for doing this: looks, maintainability (grass trimming), and, most important, leveling. If your base plate isn't level, it will be nearly impossible to level the tower.

Speaking of the base plate, it is a good investment to make. At $40 to $45 per section, it is a very expensive practice to bury part of the tower in concrete. With my system, should you decide to move, the base plate can be taken with you. (Most people would rather not take a yard of concrete with them to get the tower section cemented in it.)

You will notice that the base plate is held in place by one 5/8″ x 18″ galvanized bolt in the center. If you are unable to find one at your hardware store, try your local power company. These bolts are used quite extensively for power-pole hardware.

After you have poured the concrete in your base hole and tamped the air out of it, the bolt is inserted. Don't wait too long to put the bolt in or your concrete won't hold it too well. If you are a pessimist, a 3″ flat washer welded to the end of the bolt before putting it in the concrete will add holding power.

Do not attempt to put the base plate in place until after the concrete has set. Also, be careful not to bump your cement form when pouring the concrete.

Two-inch pump rods were installed to stop cars from running into the tower.

Once the base has cured (at least a week, and preferably longer), the

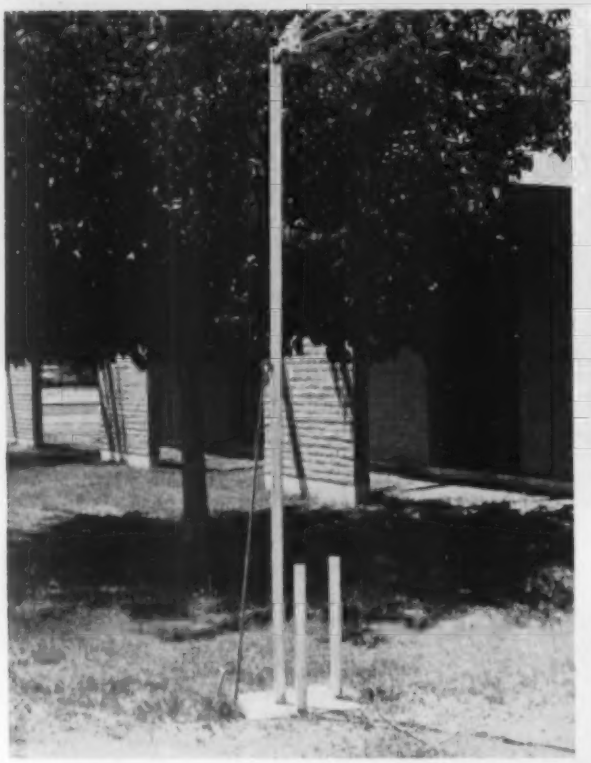

Photo C. Two types of guy-line supports are shown here.

Photo D. Guy lines are attached to equalizer plates, one of which is welded to the pump rod.

tower can be bolted to the base and set in place. Generally, the first two sections can be bolted together and set on the base without too much trouble.

Next, let's look at the guy-line supports. Photo C shows two types of guy-line supports. At the bottom of the picture is a Rohn guy anchor. This piece is cemented into the ground with just a few inches of shaft and the eye sticking out above the ground. (See your Rohn catalog for recommended installation of this device.)

Also in the picture is a pole with the lines attached to it. In this case, a 2"-diameter solid-steel pipe (a well pump rod) is used. If you check with a local pump repair company, you will find that pieces of rod that have been removed from wells are available for a couple of bucks each. Don't take your Volkswagen over to load up three lengths of this pipe, however. A 10' piece of pump rod weighs over 300 pounds!

If you are unable to find the pump rod, a piece of 3" or 4" pipe will do equally well, with the pipes filled with concrete for extra strength, if desired.

The use of the pole has several advantages over the use of the guy anchor. The main advantage is that the lines are above ground so that people won't trip on them or hang themselves on them.

The hole for the anchor was 2'×2'×2½' deep. This left 7½' of pipe above ground, and, in most cases, this is plenty. If a driveway is crossed, you may need to go higher than that. If so, I recommend you use concrete-filled 4" pipe rather than a pump rod. In any case, to make sure that they don't move, the pipes should be placed in the hole before pouring the concrete. The pipe also can be guyed with wire or rope attached to stakes in the ground.

Before calling your Redi-Mix company for a load of concrete, be sure that you have everything prepared. If the driver stands around while you put the pipe in the ground and guy it, you'll find that your bill will have a substantial charge for "stand-by" on it.

Photo D shows a close-up of how the guy lines are attached to the pipe. The piece of metal welded to the pipe is one of the equalizer plates in the Rohn EP-2534-3 package. When ordering, get 5 EP-2534-3 packages. There are 2 plates and hardware in each kit. Three sets will be used as standard equalizer plates, three of the remaining four plates will be welded to the pipes and the last plate always can be used as a paper weight.

Unless you are an extremely good welder, you should have the plates put on at your local welding shop. Tell the welder you want a *very* strong weld, to hold guy wires which will hold up a tower.

A few more points and tips: (1) All of the hardware shown comes with the equalizer plates, but, when ordering, be sure you get the correct plate for the number of guys that you will have. An EP-2534-3 is for two or three guys. An EP-2534-5 is for four or five guys. (2) When you set the guy-line pipe in the ground, be sure that the equalizer plate is facing toward the tower. It is very hard to rotate the pipe once the concrete has set. (3) If you want a little extra safety, you can weld a 12" × 12" plate to the bottom of the pump rod to make it harder to pull out of the concrete.

Once you have the base and guy supports poured in concrete, the next thing is to sit back and take a well-deserved break while the concrete cures. This will give you time to catch up on your reading of those back issues of *73*. After a couple of days, you can sand the rust off your guy pipes and spray them with Rust-o-leum, or some other rust-inhibiting paint. The silver paint seems to last the best of the colors I've tried.

Now that you are well rested and raring to go, we will start putting the tower up. We previously men-

NEW FROM *DSI!*

50 Hz — 500 MHz 8 DIGITS
1 Meg INPUT — 1 Hz RESOLUTION — 1 PPM TCXO

- AC—DC Operation
- BNC Inputs 1 Meg Direct 50 Ohms Prescaled
- 8 Large .4" LED Readouts
- Auto Decimal Point & Zero Blanking

$149.95

MODEL 500 HH
50 Hz — 500 MHz

MODEL 100 HH
50 Hz — 100 MHz
$99.95

The 100 HH and 500 HH hand held frequency counters represent a significant new advancement, utilizing the latest LSI design . . . and because it's a DSI innovation, you know it obsoletes any competitive makes, both in price and performance. No longer do you have to sacrifice accuracy, ultra small readouts and poor resolution to get a calculator size instrument. Both the 100 HH and 500 HH have eight .4 inch LED digits — 1 Hz resolution — direct in only 1 sec. or 10 Hz in .1 sec. — 1 PPM TCXO time base. These counters are perfect for all applications be it mobile, hilltop, marine or bench work. CALL TODAY TOLL FREE: (800—854-2049) Cal. Res. CALL (800—542-6253) TO ORDER OR RECEIVE MORE INFORMATION ON DSI'S FULL PRODUCT LINE OF FREQUENCY COUNTERS RANGING FROM 10 Hz TO 1.3 GHz.

COMPARISON CHART

MANUFACTURER	MODEL	SUG'STD. LIST PRICE	FREQUENCY RANGE	TYPE OF TIME BASE	ACCURACY OVER TEMPERATURE		SENSITIVITY			DIGITS		PRE-SCALE INPUT RESOLUTION	
					17° - 40°C	0° - 40°C	100 Hz - 250 MHz	50 MHz - 250 MHz	250 MHz - 500 MHz	No.	SIZE IN INCHES	.1 SEC	1 SEC
DSI INSTRUMENTS	100 HH	$ 99.95	50Hz-100MHz	TCXO	1 PPM	2 PPM	25 MV	NA	NA	8	.4	100 Hz	10 Hz
CONTINENTAL SPECIALTIES	MAX 50	$ 89.95	100Hz-50MHz	Non-Compensated	3 PPM @ 25°C	8 PPM	100 MV	NA	NA	6	.1	100 Hz	NA
DSI INSTRUMENTS	500 HH	$149.95	50Hz-550MHz	TCXO	1 PPM	2 PPM	25 MV	20 MV	30 MV	8	.4	100 Hz	10 Hz
CONTINENTAL SPECIALTIES	CSC-500	$149.95	1kHz-550MHz	Non-Compensated	3 PPM @ 25°C	8 PPM	500 MV	250 MV	250 MV	6	.1	NA	1 kHz
OPTOELECTRONICS	OPT-7000	$139.95	10Hz-600MHz	TCXO	1.8 PPM	3.2 PPM	NS	NS	NS	7	.4	1 kHz	100 Hz

100 HH ..... **$ 99.95**
500 HH **$149.95**
1 Year Limited Warranty Parts & Labor.
Factory Assembled in U.S.A.

DSI INSTRUMENTS, INC.
7924 Ronson Road, Dept. G
San Diego, California 92111

T-500 Ant. ..... **$ 7.95**
AC-9 Battery Eliminator ..... **$ 7.95**
NiCad Batt Pack **$24.95**

TERMS: MC - VISA - AE - Check - M.O. - COD in U.S. Funds. Orders outside of USA & Canada, please add $20.00 additional to cover air shipment. California residents add 6% Sales Tax.

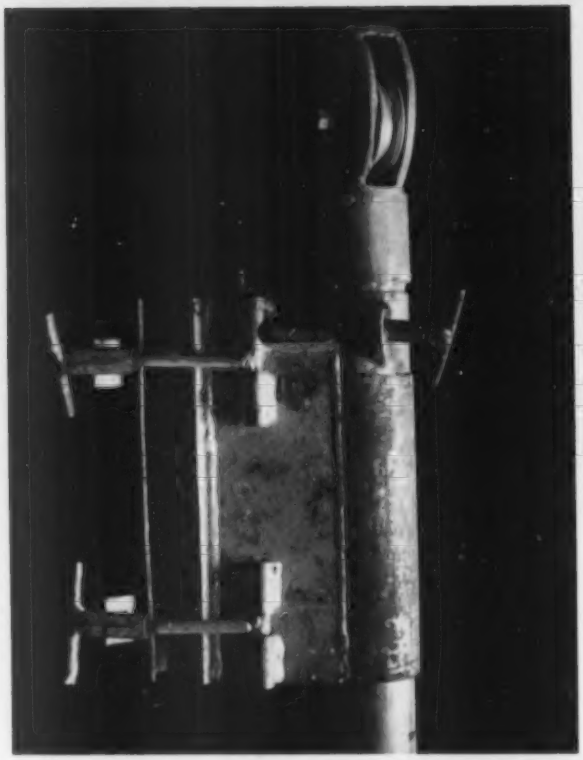

Photo E. This is what a gin-pole looks like.

Photo F. Clearing excess galvanizing from the tower legs will make joining easier.

tioned the gin-pole. Photo E shows a picture of the gin-pole, for those of you who don't know what one is. It consists of an aluminum pipe about 13' long, a clamping device, and a pulley at the top of the pole. (If you know someone who works at a radio shop, you may be able to borrow their gin-pole.)

While you are out scrounging around, you also will need a *good* safety belt (not a World War I surplus job). Remember, your life literally depends on the belt. If it goes, you go; if your belt breaks, you will be in for a big letdown. Another need is good rope. You will need a piece as long as twice the height of the tower, plus about 30'.

Before you get gung-ho to start putting up the tower, take a few minutes to inspect the tower sections. If any of the mating ends appear to be at all bent, check to be sure that they will mate with another section of tower. If severe damage is evident, turn in a claim to the trucking company and request replacements. While you're checking out the tower, locate the mounting hardware. You will find a plug in one of the lower legs of the tower. Pry it out, tilt the leg, and catch the nuts and bolts as they slide out. There should be two sizes of nuts and bolts, and three of each size. Be sure to count all the hardware to make sure you're not short, and then place it in the pouch of your safety belt.

Two other things can be done to make the tower sections easier to put together. The first is to take a 1½" piece of rod a foot or so long and grind a blunt point on it. Very gently drive this into the female (lower part of tower) ends of the tower sections. (Don't get carried away or you will split the tower legs open.) Photo F shows this being done. The second is to drive a drift punch through each of the bolt holes in the tower. Drive the punch in from both sides of the holes. The reason for these steps is to clear out any excess galvanizing that may be clogging the holes. (All Rohn towers are hot-dipped galvanized after they are assembled.) Under no circumstances should you use a drill to ream out the holes.

You now are ready to start putting up the tower sections. If you are doing the climbing, be sure that your ground man is reliable. Your life literally rests in his hands. If *you* say "whoa" and *he* "let's go," you have a big problem.

The man on the tower *always* calls the shots—he is the boss. If you can get hold of a pair of walkie-talkies, it will save you from laryngitis from yelling to each other. And let your ground man do as much of the physical work as possible.

The number one rule is safety. Tower work is no place to be horsing around. Before you take one foot off the ground, make the following point emphatically clear to everyone: If anything breaks, comes loose, or drops, don't try to stop it or catch it. Should anything go wrong, get your butt out of the way. A piece of mangled-up tower can easily be replaced. A mangled body is not so easily replaced.

The man on the tower should have the following equipment with him before he starts climbing: (1) Safety belt, boots, and gloves. (2) Two wrenches for *each* of the two bolt sizes on the tower. (A ratchet and socket help a lot.) (3) A drift punch and hammer. These are used to help align the bolt holes. (4) All of the nuts and bolts for all of the tower sections. (5) A small pulley which can be used to raise the gin-pole from one section of the tower to the next. (6) A work platform, if used.

Item six is not a requirement, but it can make the tower work a lot easier and save a lot of wear and tear on your feet and back. (See Photo G.) Once again, I wish to emphasize that very important point: If you can't relax while doing tower work, *stay on the ground*. There is no way

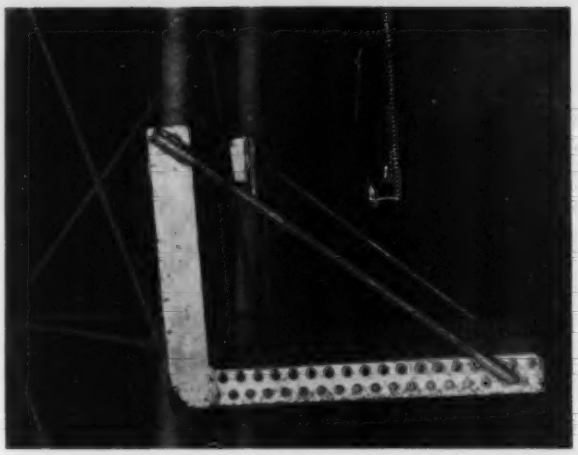

Photo C. A work platform can make tower erection much easier.

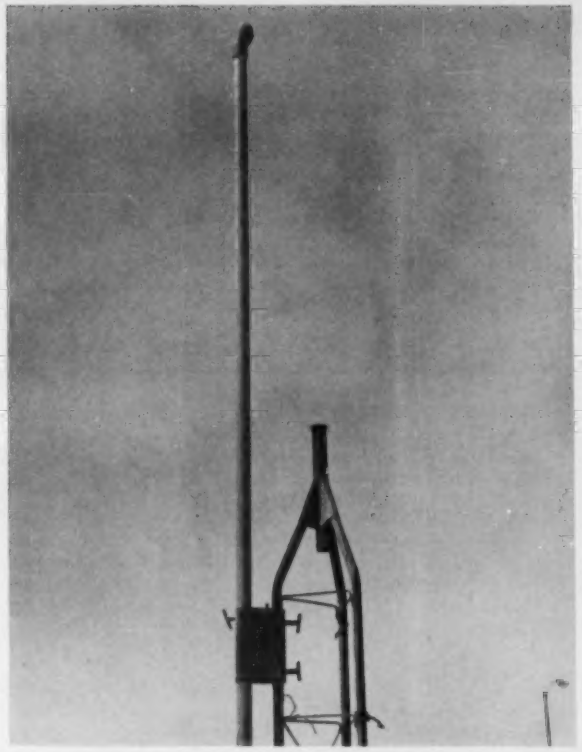

Photo H. The gin-pole is clamped in place at the top of the tower.

that you can hold on with one hand and work with the other. Tower work requires both hands and all of your attention.

Your first job is to place the gin-pole at the top of the first section. Carry the pole up the tower with the pole in the lowered position, or use the small pulley. Once you have it in place on the tower, you can raise the pole. Be sure to place the clamp on a tower leg so that sections can be pulled up without obstructions being in the way.

The clamp should be positioned so that it faces away from the tower. The pulley should be rotated so that it faces toward the inside of the tower. Do not use pliers to tighten any of the clamp screws on the gin-pole; hand-tight is sufficient on all three screws. Photo H shows a picture of the gin-pole clamped in place on the tower.

While you are mounting the gin-pole, your ground man should be tying the rope to the next section of the tower. The rope should be tied approximately two-thirds of the way up the section. If it is tied too high, you will have trouble placing the sections in place. Photo I shows how I tie the rope on. You will notice that this is a slip knot. Many people have looked at this and said, "It won't work." I have used this knot to send up over 500' of tower sections and never has it come loose.

Once you have the third section of tower in place, the first set of guy lines should be attached. I personally recommend that if you put up thirty feet or more of tower, it should be guyed. The Rohn catalog gives recommended guying heights for various tower heights. While you are working on the third section of tower, have your ground man getting the guy lines ready. Each line should be prepared as shown in Photo J *before* it is sent up to you. The loop should be about three inches long, and two cable clamps (minimum) should be used at each loop.

When you have the gin-pole ready (you can do this before moving the pole if you want), have the loop sent up to you on the gin-pole line. Each line should be taken to the turnbuckle it attaches to and measured to length before cutting. The turnbuckles should be screwed to the maximum *out* position before measuring. *Do not* try to pull the guy line tight when you are measuring it, but leave plenty of slack. The lines can't be tightened until all three lines are attached.

Leave a couple of feet extra so that the cable clamps can be fastened. When you cut the guy cable, be sure to tape both sides of the cut with electrical tape before you cut it. A small pair of bolt cutters does a good job of cutting the cable.

After the first line is attached, have the second one prepared and sent up. After all three guys are attached, the tower man should come down, because the next job is easiest when done by all hands—preferably with four men. Have one man on each of the guy lines, and the fourth man at the tower, with a two-foot or longer level. It is best to use a ladder, so that the level can be placed on the middle of the second section or higher (15' from the ground).

The level man should not stand on or hold onto the tower when he is leveling it. Each turnbuckle should be tightened until the tower is level. Take at least two perpendicular readings (90° from each other) on each leg to ensure that the tower is level. The first set of guys is very important. If the tower is not properly leveled at this point, you may never get it straight.

If you turn the turnbuckle all the way in and still need more tightening, then back it all the way out, loosen the cable clamps, pull the cable until it is tight, re-clamp, and start tightening the turnbuckle again. When properly tightened, the guy lines still should have a fair amount of slack. You should be able to shake the cable and have a small amount of ripple in it.

If the cables are too

Photo I. A good knot to use when lifting tower sections.

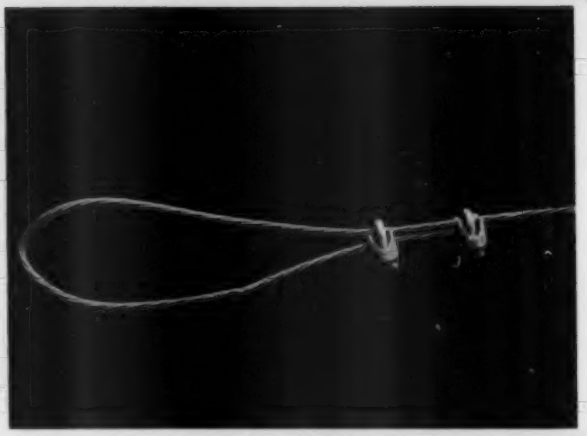

Photo J. The three-inch loop should be prepared before the guy line is lifted up to the tower.

tight, you stand a good chance of losing your tower. The theory is that of the reed in the wind. A reed will bend in the wind and not be broken, but a rigid plant will snap off because it is unable to give. A properly-guyed tower will have a small amount of sway to it. And remember that if you put up your tower in winter, you will need *less* slack than you would in the summer!

Continue to put additional sections of tower and guy lines on until the tower is completed. Additional sections of tower are leveled in the same manner. The only exception is that, rather than using a level, the level man should look up each leg of the tower. A section that is not level will stand out very noticeably. If you're not sure, have several people sight up the tower and level until the general consensus is that it is straight.

When all sections of tower have been installed and leveled, the turnbuckles should be safety-wired. This prevents movement of the lines from working the turnbuckles loose. The method I prefer to use is the "figure-8" safety wiring. This can be seen in Photo K.

Another feature you may want to add to your tower is a skirt on the bottom section. Remember, your tower is classified as an "attractive nuisance." The skirting I used can be seen in Photo L. The best way to make this is to take a section of tower to a local air conditioning contractor and ask him to make you a piece of metal 8' long to cover the tower. You can have him attach it to the tower, or do it yourself. The best way to attach it is to use pop rivets. Be sure to leave space at the top and bottom of the section so that the mounting bolts can be installed.

The only remaining part of the job is the antenna and feedline installation. Since there are so many types of antennas and mountings, I will not attempt to go into installation of them. If you intend to use a rotor, contact your Rohn dealer. He probably can fix you up with a rotor mount and thrust bearings that are made for the tower.

Two words of caution on feedlines: (1) There seems to be quite a bit of unjacketed Heliax® available that has been removed from commercial service. If you run across any of it, take it if it is given to you, proceed to your nearest scrap metal yard, and sell it for the value of the copper. Under no conditions do you want to use it on your tower. When you place two dissimilar metals together and place them in an electromagnetic field, you have created a fantastic TVI generator. This is the reason that it was removed from commercial service. And (2), watch for kinks in the outer shield. If it is kinked, there is a 98% chance that the cable is ruined. If you need a good attenuator, it is fine. However, most people find it to no advantage to have a 3-dB attenuator in their feedline.

If you are planning to buy a complete tower, you can buy a package that has the tower, guy lines, turnbuckles, equalizer plates, and cable clamps. This could save you some time and money. Check with your Rohn dealer about the package tower before you buy all the pieces individually.

Be sure that the tower you buy will handle the wind loading and weight for the antenna system that you plan to use. If you plan to use the pump-rod guying technique, be sure to order two extra equalizing plate kits. Also, check to see that there is sufficient guy line to meet your guying needs. The packages are set up for the ideal guying, but there is a very good chance that your installation will need more cable.

I hope that this article has given you some insight into the proper methods of erecting a tower. I claim neither to have covered every possible condition you may encounter nor that this is the only way to put up a tower. All I can say is that these are some of the most acceptable methods I've tried in 15

ALL NEW

FT-101ZD

HIGH-PERFORMANCE HF TRANSCEIVER

Today's technology, backed by a proud tradition, is yours to enjoy in the all-new FT-101ZD transceiver from YAESU. A host of new features are teamed with the FT-101 heritage to bring you a top-dollar value. See your dealer today for a "hands on" demonstration of the performance-packed FT-101ZD.

Diecast front panel, plus heavy duty case
Built-in, fully adjustable, VOX circuitry
Built-in RF speech processor for more "talk power" when you need it
Built-in, threshold adjustable, noise blanker
Equipped for SSB and CW operation. Choice of wide or narrow bandwidth for CW (with optional CW filter installed)
Continuously variable IF bandwidth: 300 Hz to 2.4 KHz
Digital plus analog frequency readout. Digital display resolution to 100 Hz
Rugged 6146B final amplifier tubes with RF negative feedback
RF and AF gain controls located on concentric shafts for operator convenience
Full band coverage: 160 through 10 meters, plus WWV/JJY (receive only)
TX, RX, or transceive frequency offset from main dial frequency
For WARAC Flexibility
Select switches for use with FV-901DM synthesized scanning VFO (option). FV-901DM provides scanners plus 40 frequency memory bank.

SPECIFICATIONS

TRANSMITTER

PA Input Power:
180 watts DC
Carrier Suppression:
Better than 40 dB
Unwanted Sideband Suppression:
Better than 40 dB @ 1000 Hz, 14 MHz
Spurious Radiation:
Better than 40 dB below rated output
Third Order Distortion Products:
Better than −31 dB
Transmitter Frequency Response:
300-2700 Hz (−6 dB)
Stability:
Less than 300 Hz in first 30 minutes after 10 min. warmup; less than 100 Hz after 30 minutes over any 30 min. period
Negative Feedback: 6 dB @ 14 MHz
Antenna Output Impedance:
50-75 ohms, unbalanced

GENERAL

Frequency Coverage:
Amateur bands from 1.8-29.9 MHz, plus WWV/JJY (receive only)
Operating Modes:
LSB, USB, CW
Power Requirements:
100/110/117/200/220/234 volts AC, 50/60 Hz; 13.5 volts DC (with optional DC-DC converter)
Power Consumption:
AC 117V: 75 VA receive (65 VA HEATER OFF) 285 VA transmit; DC 13.5V: 5.5 amps receive (1.1 amps HEATER OFF), 21 amps transmit
Size:
345 (W) × 157 (H) × 326 (D) mm
Weight:
Approximately 15 kg.

COMPATIBLE WITH FT-901DM ACCESSORIES

RECEIVER

Sensitivity:
0.25 uV for S/N 10 dB
Selectivity:
2.4 KHz at 6 dB down, 4.0 KHz at 60 dB down (1.66 shape factor); Continuously variable between 300 and 2400 Hz (−6 dB); CW (with optional CW filter installed): 600 Hz at 6 dB down, 1.2 KHz at 60 dB down (2:1 shape factor)
Image Rejection:
Better than 60 dB (160-15 meters); Better than 50 dB (10 meters)
IF Rejection:
Better than 70 dB (160, 80, 20-10 m); Better than 60 dB (40 m)
Audio Output Impedance:
4-16 ohms
Audio Output Power:
3 watts @10% THD (into 4 ohms)

arma
amateur radio manufacturer's association

Price And Specifications Subject To Change Without Notice Or Obligation

YAESU
The radio.

379X

YAESU ELECTRONICS CORP., 15954 Downey Ave., Paramount, CA 90723 ● (213) 633-4007
YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246

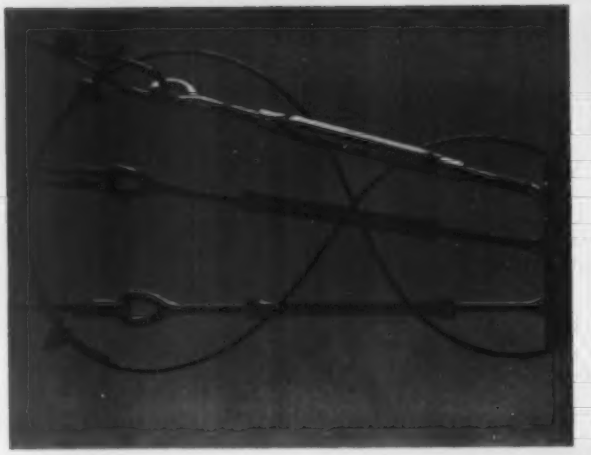

Photo K. A "figure-8" safety wiring for turnbuckles.

years of putting up ham and commercial towers.

If you have any suggestions or questions, I will be glad to respond to them. If you wish and expect a reply, send an SASE. Good luck, and remember the final words of Harry Splash, the tower rigger: "I knew that I should have replaced that worn strap on my safety belt!"

Note: Thanks to Deborah Coyle for proofreading and typing this article, and to Sue (WB7CXE's YL) for help with the photo work. ■

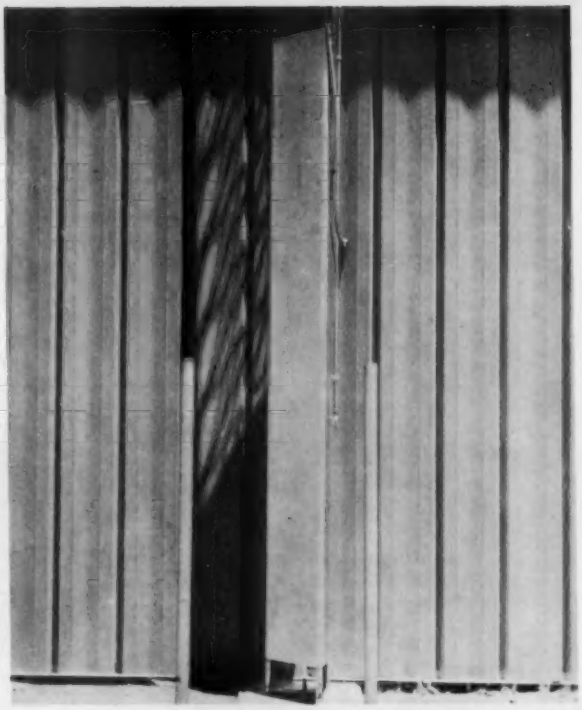

Photo L. A skirting at the bottom of the tower lessens the "attractiveness" of your "attractive nuisance."

TUBES & LINEAR PARTS

Eimac®

IN STOCK

	List	Special
3-400Z	$90	$81
3-500Z	$90	$81
8873	$135	$129
8874	$135	$129
8875	$135	$129
8877	On Quote	

All are new, factory fresh w/ full warranty

SK-400, SK-410, SK406
SK-416, SK-510, SK516
SK2210, SK2216, SK640
and much more in stock
finger stock too!

VARIABLE CAPACITORS

40-310pf	7KV Air	$24.00
2.2-30pf	15KV Vac	$20.00
5-100pf	15KV Vac	$47.50
11-300pf	10KV Vac	$60.00
4.1-465pf	5KV Vac	$60.00
18-1000pf	3KV Vac	$70.00
10-1000pf	5KV Vac	$80.00

VACUUM RELAYS

Type	New	Surplus
HC1 Kilovac	$99.95	$49.95
HC3 Kilovac	$119.95	$49.95
RF2B Jennings	$89.50	$22.00

π-INDUCTOR, SWITCH ASSY'S

B&W 852	$79.95
B&W 850A	$79.95
B&W 851	$57.50

RF SWITCHES

SP6T Millen	$22.50

PLATE CHOKES

2.5mH 100mA	$.99
2.5mH 300mA	$1.69
B&W 800	$10.25

RTTY CORNER

Mod 28ASR	$499
Mod 28KSR	$225
TTY Paper (3ply) case	$6
TTY Perf Tape case	$15
TT292 Typing Reperf	$150

Hard to Find Tubes & Parts-Call or Write

Quantities Limited to Stock on Hand

Please allow for shipping charges. AZ residents add sales tax.

Specials Good thru 7/31/79

Amateur Radio Center
11 S. Morris, Mesa, AZ 85202
(602)833-8051

ABT

Call Toll Free 1-800-243-7765

FREE • Monthly Computerized Used Equipment List
• Courteous, Personalized Service

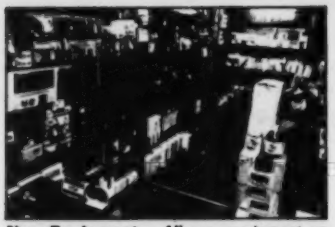

New Equipment — All new equipment on display is operating for actual "on the air" QSO's. We really know our gear!

Used Equipment — We recondition and guarantee all our used equipment. We make sure it satisfies you!

Service Shop — You've probably heard of our fine service reputation — using Cushman CE4B signal generators, Hewlett Packard oscilloscopes, Bird wattmeters — we fix it right!

Inventory Warehouse — Our large volume assures you the best prices!

ICOM IC-701

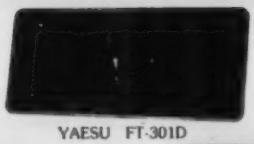

YAESU FT-301D

ATLAS RX-110

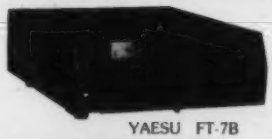

YAESU FT-7B

YAESU FT-101ZD

TEN TEC OMNI-D

KDK 2016A

CUSHCRAFT ANTENNAS

AUTHORIZED DEALER . . .

FOR OVER 50 MAJOR LINES.

NEW AND USED EQUIPMENT *"Get on our used equipment mailing list."*

TRADES WELCOME *"The best allowances anywhere"*
"We buy good used SSB gear"

OUR EVERYDAY LOW PRICES *"remain the same for cash or trade-ins!"*

SAME DAY U.P.S. SHIPPING *"Just a phone call away"*

COMPLETE RADIO SERVICE SHOP *"Mail Order Repair Service"*

- Fast Efficient Service
- Most Repairs Done and Shipped Within 7 Days
- We Repair All Brands
- Amateur Extra/First Class Licenses
- All Work Guaranteed
- Free Shipping Both Ways If Work Is Done
- Send Us Your Defective Equipment U.P.S. Collect

OUR FINE REPUTATION SPEAKS FOR ITSELF . . .
"YOU SHIP IT — WE FIX IT"

OPEN MON.-FRI. 10-6 • THURS. 10-8 P.M. • SAT. 10-4
EASY DIRECTIONS: Rt. 15 South — 2 blocks past McDonald's (Berlin Turnpike)

"We can match most any other quote!"

"We want your used gear!" We will buy or trade.

T34

Call or Write for your super quote today!

master charge

VISA

THOMAS COMMUNICATIONS

95 Kitts Lane, Newington, Conn. 06111
"Near ARRL Headquarters"
Connecticut Residents Call: **203-667-0811**

Available for Kenwood TR 7400, Midland 13-510, Yaesu 227R, or KDK FM-144

At your Ham Radio Dealer or Call or Write ✓C115

CES COMMUNICATIONS ELECTRONICS SPECIALTIES, inc.

399 W. Fairbanks Ave., Winter Park, Fla. 32789
305/645-0474

TODAY'S MOST VERSATILE SCANNER

Scan a few channels or all 800 - for example - you can program CES Model 800 to scan Repeater and Simplex Channels or all 2 Meter Bands - Other features include: Instantaneous Addition or Deletion of Channels • Scan Resume delay assures hearing return calls • Resume and Hold provides complete control of scanning action • Hold Control activated by mic's P.T.T. switch • Scan entire band in 5 KHz steps and retain programmed memory • Selectable automatic scan resume after 10 secs. on channel. Slow Scan of memory to locate specific channels.

DOVETRON

MPC-1000C

Multipath Correction
In-Band Diversity &
AFSK Tone Keyer

Amateur Net: $545.00

Standard features include CONTINUOUSLY tuneable Mark and Space channels (1000 Hz to 3200 Hz), Dual Mode (MARK or FSK) Autostart and internal high level neutral loop keyer (20 to 60 ml). Both EIA and MIL FSK outputs are provided for direct interface to microprocessor and video terminal peripherals.

MPC-1000CR

Signal Regeneration &
Speed Conversion

Amateur Net: $645.00

A front panel switch permits internal TSR-200 Signal Regenerator-Speed converter assembly to electronically "gear-shift" between 60, 67, 75 and 100 WPM. All incoming and outgoing signals are regenerated to less than 0.5% bias distortion. Also available with DIGITAL Autostart (TSR-200D): Amateur Net: $695.00

MPC-1000R/-TSR-500

Dual UART Regeneration,
Speed Conversion, 200
Char. Memory, Word Correction & DIGITAL
Autostart

Amateur Net: $895.00*

The MPC-1000R/TSR-500 provides Preloading and Recirculation of the 200 character FIFO Memory, a keyboard-controlled Word Correction circuit, Variable Character Rate, Tee Dee Inhibit, Blank/LTRS Diddle, a Triple Tone-Pair AFSK Tone Keyer and a Character Recognition/Speed Determination DIGITAL (DAS-100) Autostart mode.

*The MPC-1000R is also available without a TSR assembly and functions as a MPC-1000C with a Triple Tone-Pair AFSK Tone Keyer. This "Basic-R" permits future expansion with a TSR-100, TSR-200, TSR-200D or TSR-500 by simply lifting the lid and plugging in the appropriate TSR assembly: Amateur Net (Basic-R): $595.00

Your QSL will bring complete specifications, or call: 213-682-3705.

✓D23

DOVETRON

627 FREMONT AVENUE
(P. O. BOX 267)
SOUTH PASADENA, CA. 91030

- Special Saturday night activities
- Swap shop inside and out
- ARRL talks and topics
- Forums and meetings
- Commercial exhibits
- Hourly prizes
- Major awards

Now in its 14th year
September 7, 8 and 9, 1979

MELBOURNE HAMFEST

Meet us at the air-conditioned Melbourne auditorium. Hamfest headquarters at the Ramada Inn, US1. Talk-in on 25/85. Tickets are $3.50 per person.

For full information contact:
Platinum Coast Amateur Radio Society
PO Box 1004
Melbourne FL 32901

1-800-485-0942

VINEYARD AMATEUR RADIO

We sell Ten-Tec, Alda, SST, Wilson, Lunar, Mirage, and many others for less.

★ INTRODUCING ★

The RM-101 and TM-820 rcvr mod kit.

Improves overload, crossmod, and sensitivity (noise fig.)

BEST OF ALL, the kit sells for $14.95, (half of the cost of other kits)

Drop us a card or call for the low prices

VAR **Vineyard Amateur Radio**
4407 Vineyard Rd.
Oxnard, CA 93030

✓V75

SCANNERS • SCANNERS • SCANNERS

YOU'VE SEEN THE REST, NOW BUY THE BEST

HAM SCAN-2

Kenwood 7400A, KDK 2015R, KDK 2016A, Tempo VHF/1, Midland 13-510, others

- **Features one channel of memory, without need of resetting dials to zeros as required by others.**
- **Unit mounts totally inside of rig, no external boxes.**
- **Scanning rate 200 kHz nom, not 50 kHz, with a 3 second pause on all active channels before resuming scan.**
- **Mike-mounted switch provides 3 functions; scan start/stop, remote frequency incrementing, and transmit interlocking when in active scan mode.**
- **Totally assembled, and tested $59.95 $1.50 shp.**

Order HAM SCAN-2 and please specify type of rig

Technical Clinic

P.O. BOX 536
STERLING HTS. MI 48078 ✓T84
Phone Orders Call: (313) 286-4836

✓ *Reader Service—see page 211*

FREE!
RADIO AMATEURS
WORLD ATLAS
with purchase of famous
CALLBOOK
MAP LIBRARY!

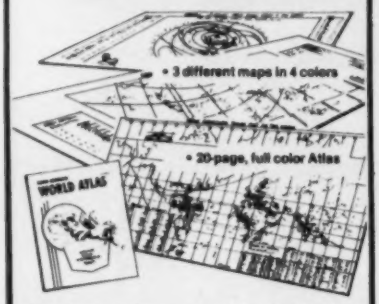

Here's an offer you can't refuse! You receive three, information-packed, Amateur Callbook maps, folded, plus the World Atlas for only $3.75 plus $1.50 shipping and handling. If purchased separately, total value of map/atlas offer would be $6.25, plus shipping. You save $2.50 and get these invaluable radio amateur aids!

1. **Prefix Map of the World,** folded. World-wide prefixes. Shows 40-zone map on one side, 90-zone map on the other. Size 40" x 28"
2. **Map of North America,** folded. Includes Central America and Caribbean to the Equator. Shows call areas, zone boundaries, prefixes, etc. Size 30" x 25"
3. **Great Circle Chart of World,** folded Centered on 40°N, 100° W. Shows cities, latitude, longitude, great circle bearings and more! Size 30" x 25"

Plus special FREE bonus!
The Callbook's own **Radio Amateur World Atlas, FREE** with the purchase of the 3 maps. Contains eleven full color maps of the world, looking at things from the radio amateurs point of view.

Callbook Map Library	$3.75
Shipping	$1.50
Total	$5.25

Special Limited Offer!
Amateur Radio
Emblem Patch
only $2.50 prepaid

Pegasus on blue field, red lettering. 3" wide x 3" high. Great on jackets and caps. Sorry, no call letters.
ORDER TODAY!

Order from your favorite electronics dealer or direct from the publisher. All direct orders add $1.50 for shipping. Illinois residents add 5% Sales Tax.

RADIO AMATEUR **callbook** INC.
R1
Dept. B
925 Sherwood Drive
Lake Bluff, Ill 60044

Touch-n-go
with
DRAKE 1525EM
Push Button Encoding Mike

- Microphone and auto-patch encoder in single convenient package with coil cord and connector. Fully wired and ready for use.
- High accuracy IC tone generator, no frequency adjustments.
- High reliability Digitran® keyboard.
- Power for tone encoder obtained from transceiver through microphone cable. No battery required. Low current drain.
- Low output impedance allows use with almost all transceivers.
- Four pin microphone plug: directly connects to Drake UV-3 without any modification in transceiver. Compatible with all previous Drake and other 2 meter units with minor modifications.
- Tone level adjustable.
- Hang-up hook supplied.
- Complete instructions supplied for use with any transceiver.

SPECIFICATIONS:

• **Microphone Element Type:** Low impedance dynamic • **Frequency Response:** 300-5000 Hz • **Output Impedence:** 500 ohms • **Microphone Output Level:** −72 dBm per microbar. Approx 3mV (−47dBm) with average voice level • **Tone Encoder:** Single integrated circuit dual tone synthesizer • **Encoder Audio Level:** Adjustable from approx 1mV to 5mV with internal potentiometer • **Encoder Frequency Tolerance:** Better than ±1% from −20°C to +50°C • **Encoder Supply Voltage:** 7.5 to 15 Volts (Obtained through microphone cable from transceiver) • **Encoder Current Drain:** 5 to 20 mA depending on supply voltage • **Encoder Keyboard:** High reliability Digitran® keyboard • **Microphone Hanger:** Hook supplied • **Dimensions:** 2.6" x 3.5" x 1.7" (6.6 x 8.9 x 4.3 cm) • **Weight:** 8 oz. (.227 kg)

Drake 1525EM, microphone with tone encoder and connector for UV-3, TR-33C, TR-72, TR-22C, ML-2 ..... **$49.95**

Drake 7073DM as above but without tone encoder **$19.00**

To receive a FREE Drake Full Line Catalog, please send name and date of this publication to:

DRAKE®
D11

R. L. DRAKE COMPANY
540 Richard St., Miamisburg, Ohio 45342 • Phone: (513) 866-2421 • Telex: 288-017

Prices and specifications subject to change without notice or obligation.

COMPLETELY FREE-STANDING, TELESCOPING TOWERS.

TELE-TOW'R

PUT IT RIGHT WHERE YOU WANT IT. With one hand, raise the tower from 21' to as high as 55'. Find exactly the right receiving level from CB, Ham or TV. When you want to adjust your antenna, install a new one, or pull maintenance, crank it down again. No more climbing up in the sky to repair or replace antennas. With the exception of our breakover models, this is the most convenient tower you can buy.

BREAKOVERS—THE ULTIMATE IN CONVENIENCE—Our breakovers not only telescope, they lie down for you. One man can crank it down, then lay it down, so your feet never have to leave the gound, even on our tallest towers.

TOTALLY FREE-STANDING. No guy wires, no brackets. Our towers are designed to withstand 60 mile winds, with 50 pounds rotor and antenna with a vertical area of 6 square feet.

TOWER CONSTRUCTION. We make it out of the finest materials available. Our steel is thicker and heavier, our cables are thicker and stronger—our towers themselves are two or three times heavier than comparable towers on the market. Weight runs about 165 pounds for our 40' towers 350 pounds for 55'. Several design innovations are used to make Tele'Tow'r the strongest, most reliable tower.

ONE-PIECE PRICE. When you buy one of these towers you get the whole tower ready to install. No accessory charges, no extra costs for guy wire, base plates, etc. And even our complete one-piece price is considerably lower than any comparable tower on the market.

Concrete sleeves available for Model 40s and Model 55s. By using sleeves you can move tower to another location and all you leave is the sleeve in concrete.

40' MODELS
Model 40 (extends 21' to 40')
Breakover Model 40
(extends from 23' to 40' with breakover at ground level)

55' MODELS
Model 55 (extends from 21' to 55')
Breakover Model 55
(Extends from 23' to 55' with breakover at ground level)

TELE-TOW'R MFG. CO., INC.

P.O. Box 3412 • Enid, Oklahoma 73701
405-233-4412

✔T52

SST T-4
ULTRA TU'NER DELUXE

ULTRA TUNER DELUXE Matches any antenna—coax fed or random wire on all bands (160-10 meters). Tune out the SWR on your antenna for more efficient operation of any rig. Home, mobile, portable—only 9"x2¼"x8" • 300 watt RF **output** capability • **SWR meter** with 2-color scale • **Antenna Switch** selects between two coax fed antennas, random wire, or tuner bypass • Efficient **Airwound inductor** • 208 pf. 1000V. Capacitors • Attractive bronze finished enclosure.

only $64.95

SST T-2 ULTRA TUNER

Tunes out SWR on any antenna—coax fed or random wire (160-10 meters). Any rig—up to 200 watts RF output. Rugged, yet compact: 5¼" x 2¼" x 2¼".

only $37.95

SST T-3 MOBILE IMPEDANCE TRANSFORMER

Matches 52 ohm coax to the lower impedance of a mobile whip. Taps between 3 and 50 ohms. 3-30 MHz. 300 watts output. 2¼"x2"x2¼".

only $19.95

SST T-1 RANDOM WIRE ANTENNA TUNER

All bands (160-10 m.) with any wire • 200W **output** • Any transceiver • Home or portable • Neon tune-up indicator.

only $29.95

SST DL-1 KARL'S DUMMY LOAD. 1000W PEP 1.5:1 1-225 MHz. Sealed. 3-1/8"x4-3/8".

only $17.95

SST CL-1 24 HR. CLOCK. Giant red **LED** numerals. Month and day also at push of button. Beautiful for your desk. 110VAC.

only $22.95

SST B-1 BAL'UN for balanced lines. 300W.

only $5.00

Call (213) 376-5887 to order C.O.D., VISA, or Master Charge.

To Order:
Send a check or money order—or use your M.C. or VISA. Add $3 shipping and handling. Calif. residents, add sales tax.

Guarantee: All SST products are unconditionally guaranteed for 1 year. In addition, they may be returned within 10 days for a full refund (less shipping) if you are not satisfied for any reason.

SST ELECTRONICS ✔S10
P.O.BOX 1 LAWNDALE, CALIF.
90260 (213) 376-5887

MESSAGE MEMORY KEYER

"BRAND NEW"

Model # TE201

$69.95

Features:
- Advanced CMOS message memory
- Two (50 char. each) message storage
- Repeat function
- Records at any speed—plays back at any speed
- Longer message capacity. Example: send CQ CQ CQ DX de WB2YJM WB2YJM K—then play second message on contact—de WB2YJM OSL NY NY 579 579 Paul Paul K
- Use for daily QSOs or contests

PLUS:
- State-of-the-art CMOS keyer
- Self completing dots and dashes
- Both dot and dash memory
- Iambic keying with any squeeze paddle
- 5-50 wpm
- Speed, volume, tone, tune and weight controls
- Sidetone and speaker
- Low current drain CMOS battery operation—portable
- Deluxe quarter-inch jacks for keying and output
- Keys grid block and solid state rigs
- WIRED AND TESTED FULLY GUARANTEED—LESS BATTERY

"BRAND NEW"

Model # TE144

59.95

- State-of-the-art CMOS circuitry
- Self completing dots and dashes
- Both dot and dash memory
- IAMBIC keying with any squeeze paddle
- 5-50 wpm
- Speed, weight, tone, volume tune controls & sidetone and speaker
- Semi-automatic "bug" operation & straight keying—rear panel switch
- Low current drain CMOS battery operation—portable
- Deluxe quarter inch jacks for keying and output
- Keys grid block and solid state rigs
- Wired and tested—fully guaranteed—less battery

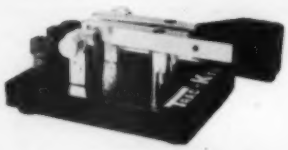

TRAC - KEY

FEATURES:
- Twin paddle squeeze key
- Extra heavy base—non skid feet
- Adjustable contact spacing
- Touch tension—comfort keying
- Smooth friction free paddle movement
- Handsome crinkle finish base and inch red paddles
- Five way binding posts
- Use with Trac CMOS keyer or any keyer

$25.95

plus $2.50 s/h
NY res. add tax

AT YOUR DEALER OR SEND CHECK OR MONEY ORDER.

TRAC ELECTRONICS, INC
1106 RAND BLDG. ✔T18
BUFFALO NY 14203

✔ Reader Service—see page 211

NEW!! THE SPACE CASE

...What better way to give your circuit designs a professional look. House them in top quality enclosures...

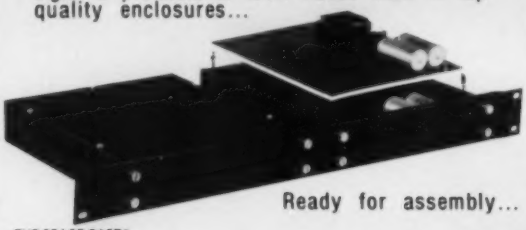

Ready for assembly...

THE SPACE CASE®

C-1 1¾" x 7" x 8" $24.50
C-3 3" x 7" x 8" $29.50

• 6061-T6 Black Anodized Aluminum • ⅛" Sides, ¼" Front and Rear, 18 Guage Top and Bottom Panels • Circuit Card Guides • Pre-Drilled For Ease of Assembly • All Necessary Hardware

RACK PANELS

P-1 1¾" x 19" $12.50
P-3 3½" x 19" $14.50

• Fits Any Standard Size Rack

B-5 5V (Complete) $40.50
B-12 ± 12V (Complete) $45.00
B-B Bare Board $25.00
T-5 5V Transformer $12.00
T-12 ± 12V Transformer $12.00

• Powerbuses Accepts Up To 25, 14 Pinpacks • Provisions Made For Either 5V at 800 ma. or ± 12 V at 230 ma. By Simple Transformer Change • Complete With All Parts.

S100

Charge to VISA or MASTER CHARGE or mail us a check or money order. Include list price plus $3.00 shipping and handling.

CALL OR WRITE FOR FREE LITERATURE
(216) 494-6050

SCOTT MANUFACTURING

P.O. BOX 2304 NORTH CANTON, OHIO 44720

TELREX "Tri-Band" — $415.00

ELECTRICAL	TB5EM
Gain in DB reference ½ wave dipole	8.5 dbd
Front to back ratio	28 db
V/S/W/R at resonant point	1.3/1
Maximum Power Input	4 KWP
Nominal Input Impedence	52 ohm
Beamwidth to ½ power Input	60° 3 bands
Frequency range	10, 15, 20
Side Nulls	35 db

MECHANICAL	
Number of Elements	Five
Alum. Boom: Dia. & Lgth. approx.	2.2.5"x18 ft.
Turning Radius approx.	20 ft.
Wind Load at 100 mph (approx.)	210 lbs.
Wind Area	7 sq. ft.
Longest Element	36 ft.
Net Weight (approx.)	49 lbs.
Shipping weight (domestic pack)	60 lbs.
Length of shipping carton	13 ft.

M35

MADISON
ELECTRONICS SUPPLY, INC.
1508 McKINNEY • HOUSTON, TEXAS 77002
713/658-0268

W5GJ, W5MBB, K5AAD, N5JJ, AG5K, W5VVM, W5EGP, WA5TGU, WB5AYF, K5BGB.

MASTERCHARGE • VISA

DLA!

A Breakthrough In Technology!

MICROPROCESSOR CONTROLLED SYNTHESIZED HANDIE

FT-207R

144-148 MHz Range
3 Watts Output

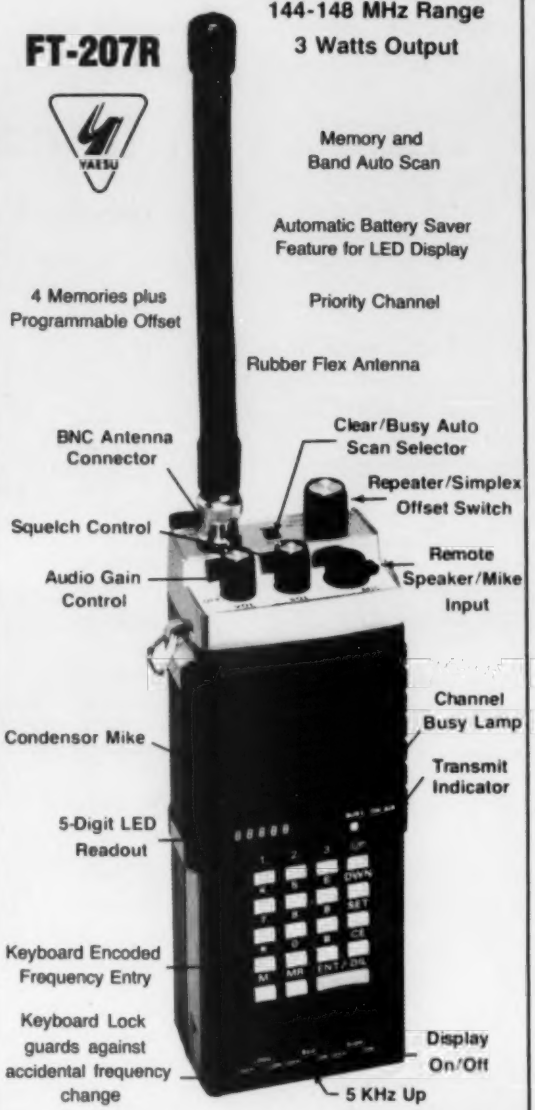

- Optional Equipment:
  Tone Squelch, Speaker/Mike, Nicads, Battery Charger

The Yaesu FT-207R Synthesized Handie has all the features you could want in a very compact package

T44

TOWER ELECTRONICS
24001 Alicia Pky., Mission Viejo, CA 92691
(714) 768-8900

"The Southwest's full-line Yaesu Distributor"

The Revolutionary Organic Antenna

—product of NASA research

Arm yourself!

Author's Note: To prevent possible adverse heating effects in the arm tissue, it is important that power input to antenna described in this article be limited to 10 mW.

James C. Gaddie
Russell T. Wolfram
(SRI International)
Ames Research Center
Moffet Field CA 94035

A human arm may be made to act as an antenna for a communications system. It has been done by using an energy coupler made of two strips of copper foil fastened to a strap and wrapped around the wrist. Apparently, the wrist strap can efficiently transfer radio-frequency energy to or from the arm.

Reprinted from NASA Tech Briefs, Summer, 1978.

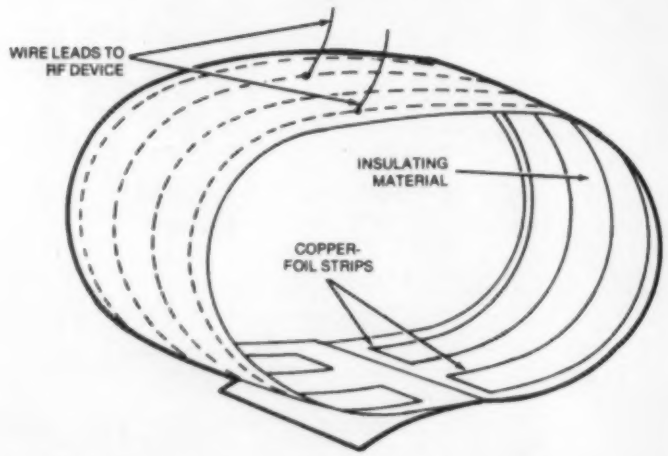

Fig. 1. Wrist-strap coupler of radio-frequency energy consists of two strips of copper fastened to an insulating material. Wires at the midpoints of the strips lead to the radio-frequency device that can act as a transmitter or receiver.

A prototype of the antenna coupler was built and found suitable for both sending and receiving very-high-frequency signals. The goal of the developers is to build a body-worn communications system for the deaf blind, and it was with this purpose in mind that the prototype unit was built and tested. Other potential applications for the compact coupler include body-worn two-way local communications systems for police and as part of a portable personal communications system that could communicate via satellite.

The copper-foil strips of the wrist-strap coupler shown in Fig. 1 are rectangular, 5 in. (13 cm) long and ½ in. (1.3 cm) wide. They are placed 7/16 in. (1.1 cm) apart and are fastened to the underside of a wrist strap made of an electrically insulating material. A thin insulating

ASCII MORSE RTTY

strip is also placed over the straps as a protective cover. Such an insulator can be added to the wrist strap because the copper strips need not be in direct contact with the skin for the rf signals to be coupled to or from the arm.

For connecting the coupler to a transceiver, or receive- or transmit-only unit, a small wire is attached to the edge of each copper strip at a point equidistant from the ends of the strip. Each wire is then routed through a hole in the insulating material to the upper surface of the strap. In addition, a fastener must be attached to the strap so that it can be pulled snugly against the wrist.

Radio-frequency energy couples to or from the arm through the electrical capacity between the arm and the copper strips. Electrical impedance characteristics of the antenna are shown in Fig. 2. The radiated field strength, with the strap driven by a 170-MHz, 10-mW transmitter, was found to be slightly greater than that from a well-designed loop antenna built with a 16- by 11- by 3-mm ferrite core and driven by the same transmitter.■

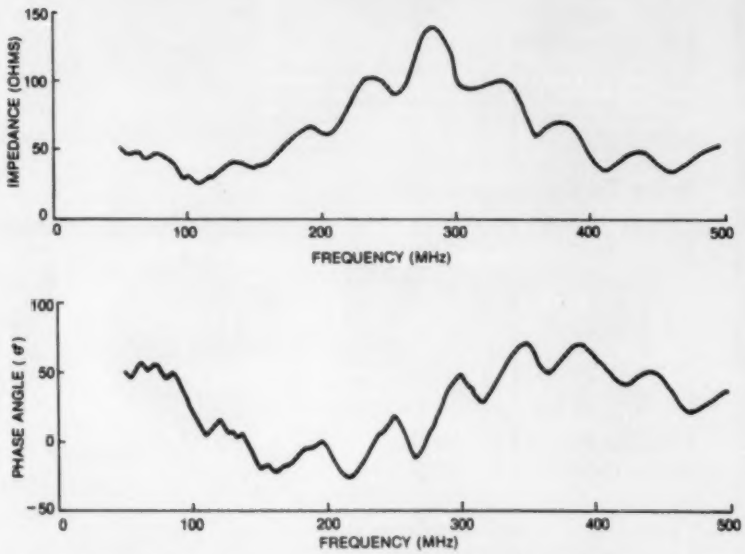

Fig. 2. Electrical impedance characteristics of the wrist-strap antenna coupler were measured with a General Radio 1710 rf network analyzer. Varying the widths of the copper strips will produce somewhat different characteristics.

1-800-633-3410 TODAY!

CALL LONG'S TOLL FREE

LONG'S HAM BUYERS GUIDE

Prices in this catalog subject to change without notice. Prices good only while supply lasts.

NEW!

KENWOOD TS-180S solid state HF transceiver

Covers: 160 - 10 meters, digital frequency control with 4 memories and manual scanning, 200W PEP/160W DC 160 - 10 meters and 160W PEP/140W DC on 10 meters, adaptable to new bands, IF shift, tunable noise blanker, dual RIT (VFO and memory/fix), SSB, CW, and FSK, 13.8 VDC operation, and built-in digital display to show VFO freq. and difference between VFO and M-1 memory freq.

Price To Be Announced

ORDER NOW!

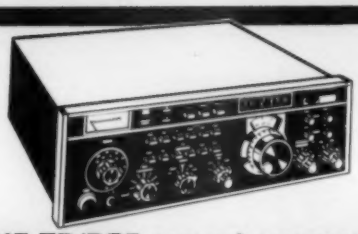

YAESU FT-101ZD High performance HF transceiver

Covers: 160 thru 10 meters plus WWV, modes: LSB, USB, and CW, built-in power supply, input power: 180 WDC, digital and analog frequency readout, 6146B final tubes, RF speech processor, variable IF bandwidth, noise blanker, heater switch, VOX, attenuator 10 dB or 20 dB selectable, operation from 100-234 volts, and TX and RX frequency offset.

895.00 List. Call for quote.

DRAKE TR/DR7 general coverage digital R/O transceiver

Covers 160 thru 10 meters, reception from 1.5-30 MHz continuous, 0-30 MHz with optional Aux-7, modes: USB, LSB, CW, RTTY, AM, true passband tuning, RIT, built-in RF wattmeter/VSWR bridge, SSB 250W PEP, CW 250W, AM 80W. Power supply required for AC operation.

1395.00 List. Call for quote.

VISA

Long's Electronics

master charge

MAIL ORDERS P.O. BOX 11347 BIRMINGHAM, AL 35202 • STREET ADDRESS 2808 7TH AVENUE SOUTH BIRMINGHAM, ALABAMA 35233

CALL LONG'S TODAY!

1-800-633-3410 TOLL FREE

YAESU CPU-2500RK
2m FM transceiver

With 800 PLL channels, automatic scan over entire 2m band, 4 memories, tone burst, 25W hi/3W lo @ 13.6 VDC at 8 amps continuous, freq. coverage 144-148 MHz. Comes with a keyboard mic that allows remote input of memory or dial freqs., up/down scanning control, aux. repeater split selection to 4 MHz, and 2 tone input for autopatch or control link.

585.00 List. Call for quote.

SAVE NOW!

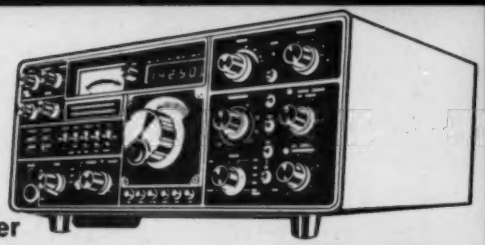

YAESU
FT-901DM
HF transceiver

An all mode HF total communications system. Freq. coverage: 160 thru 10 meters, 200W PEP, RF speech processor, built-in VFO, reject tuning, variable IF band width tuning, LED freq. display with memory, built-in Curtis Keyer, 6146B final tubes, AC/DC power supply built-in audio peak freq. tuning.

1459.00
List. Call for quote.

NEW!

YAESU FT-207R
Synthesized
Handie Talkie

Covers 144-148 MHz, has 10 KHz steps, 3 watt output, 4 memories plus programmable offset, priority channel, memory band and auto scan, keyboard encoded frequency entry, 2 tone input from keyboard, keyboard lock, odd splits can be programmed from keyboard, automatic battery saver feature for LED display, and a rubber flex antenna.

PRICE
TO BE ANNOUNCED
List. Call for quote.

YAESU FT-202R
2m handheld
FM transceiver

1 watt output minimum, 6 channel capability, flexible helical whip antenna, equipped with toneburst, compact size and light weight, S-meter and battery condition indicator, operated on 8 AA NiCad or 7 AA dry cell batteries. 3 pr. Xtals incl.

199.00 List. Call for quote.

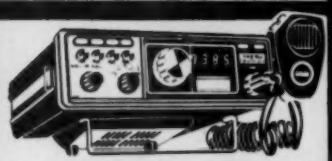

YAESU FT-227RA
2m FM transceiver

This has 4 memory channels, a remote scan from mic, can select to scan clear or busy channel, a frequency coverage of 144 to 148 MHz, 800 channels, power requirements: 13.8 VDC @ 2.5 amps continuous, RF output: 10W hi/1W lo, toneburst ± 600 KHz repeater offset.

399.00 List. Call for quote.

YAESU FT-202R
ACCESSORIES

YB-1 AA rechargeable NiCad battery, 1.2V (FT-202R requires 8 batteries) ..... **2.29 ea.**
NC-1 NiCad charger for the FT-202R, 110 VAC charging current: 45 milliamps mA. for 8-10 hrs. **39.00**
PA-1 DC power adapter steps down 13.8V to 10V for the FT-202R. **39.00**
VCC-202 vinyl carrying case for the FT-202R **9.85**
LCC-202 leather carrying case for the FT-202R **34.95**
TC-202 top cover for the LCC-202 **3.95**

Call today!

YAESU SP-901P speaker patch

Round out your station with the SP-901P speaker/phone patch. It matches the FT-901 and the -101ZD. The unit has full metering and level controls.

74.00 Call today!

YAESU FRG-7000
communications receiver

For the short wave listener, this unit has full coverage 0.25-29.9 MHz, modes: AM, SSB, & CW, digital freq., display, digital GMT/local clock, CPU clock timer, AM noise limiter, built-in power supply for AC. Listen to the world!

655.00 List. Call for quote.

YAESU FRG-7
communication receiver

A solid state, synthesized, high performance unit with continuous coverage (500 KHz to 29.99 MHz) featuring: drift canceling circuit, RF attenuator, noise blanker, AC/DC or internal battery modes: USB, LSB, CW, & AM, power requirement: 100/110/117/200/220/234 VAC, 50/60 Hz, 13.5 VCD, battery UM-1x8.

370.00 List. Call for quote.

YAESU QTR-24 world clock

A great addition to your ham shack! Now you can tell world time at a glance. It is battery powered and automatically retains the correct time.

35.00 Call today!

VISA

Long's Electronics

master charge

MAIL ORDERS P.O. BOX 11347 BIRMINGHAM, AL 35202 • STREET ADDRESS 2808 7TH AVENUE SOUTH BIRMINGHAM, ALABAMA 35233

FOR YOUR BOOKS, TAPES & MAPS CALL TOLL

ARRL Publications

ARRL Radio Amateur's Handbook Newly revised & jampacked with everything from basics to latest developments. I.N. 10081 ..... 9.75

ARRL Radio Amateur's License Manual The most up to date compilation of rules & regulations. Covers from Novice to Extra Class. I.N. 10012 ..... 4.00

ARRL Antenna Handbook Complete instructions for building antennas of all types. I.N. 10028 ..... 5.00

ARRL World Map I.N. 10099 ..... 3.50

LCF Calculator Slide rule type calculator to compute resonant frequency, etc. A great aid! I.N. 10082 ..... 3.00

Electronic Data Book All you need to know about Filter design, RF circuit data, antennas and feedling info & more. I.N. 10027 ..... 4.00

Learning to Work With Integrated Circuits Build a digital voltmeter/freq. counter while learning about IC's. I.N. 10080 ..... 2.00

Single Sideband for the Radio Amateur Covers theory and practical how-to-built ideas. I.N. 10017 ..... 3.00

FM and Repeaters for the Radio Amateur Learn all about FM and repeaters from this handy book. I.N. 10014 ..... 5.00

Solid State Design for the Radio Amateur Packed with information for practical use of solid state devices. I.N. 10061 ..... 7.00

Solid State Basics Pure solid state information and practical basics for today's ham. I.N. 10037 5.00

Specialized Communication Techniques for the Radio Amateur Covers ATV, SSTV, FAX, RTTY, satellite communications and more. I.N. 10028. 3.00

ARRL Radiogram Message Pads I.N. 10007 .75 ea.

ARRL Special Operating Kit Consists of ARRL Ham Radio Guide, full color U.S. area call map, ARRL log book, 70 ARRL radiograms. I.N. 10063 8.50

ARRL Ham Radio Operating Guide Brush up on good operating practices with this ready reference source. I.N. 10025 ..... 4.00

Getting to Know Oscar from the Ground Up. Explains all about the use of amateur satellites, how to use them and where to find them. I.N. 10059 ..... 3.00

80 meter DXing Handbook. Contains 4 sections on propagation, antennas, station equipment, and operating practices. It's filled with solid practical experience..I.N. 26307 ..... 4.50

The Amateur Radio Vertical Antenna Handbook. The first book for amateurs solely about vertical antennas, it is full of information. I.N. 26316 5.00

The Challenge of 160 The unique operating characteristics are explained and there are tips on building simple equipment. I.N. 26312 4.95

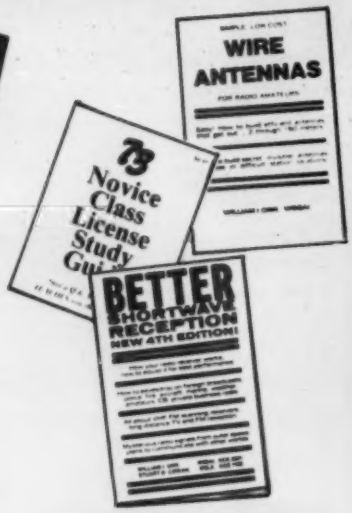

Hints and Kinks New ideas written by hams themselves. This is full of practical ideas and tips that they have used successfully. I.N. 10029 4.00

Radio Frequency Interference A new book to help everyone understand RFI. It covers all from good neighbor relations to simple technical cures for RFI. Helps identify and solve problems. I.N. 10083 ..... 3.00

ARRL Code Kit Upgrade your Novice or Tech License with these 2 60 min. cassettes with speeds of 5, 7½, 10, & 13 wpm. Instruction book included. I.N. 10048 ..... 8.00

ARRL Log Books spiral bound books.
Large I.N. 10015 ..... 1.75
Small I.N. 10020 ..... .75

Tune in the World with Ham Radio Learn all about amateur radio with a text and a morse code cassette. For the beginner studying for the Novice exam. I.N. 10031 ..... 7.00

Understanding Amateur Radio A must guide for the newcomer, it explains in simple language elementary principles of electronics & tells how to build low cost equipment. I.N. 10016 ... 5.00

Radio Publications, Inc.

Beam Antennas Handbook by Wm. Orr, W6SAI I.N. 26200 ..... 4.95

Wire Antennas by Wm. Orr, W6SAI I.N. 10058 4.95

All About Cubical Quad by Wm. Orr, W6SAI I.N. 26201 ..... 4.75

The Truth About CB Antennas by Wm. Orr, W6SAI. I.N. 26202 ..... 5.95

EIMAC's Care and Feeding of Power Grid Tubes I.N. 26205 ..... 4.95

The Antenna Handbook I.N. 26207 ..... 6.95

VHF Handbook by Wm. Orr, W6SAI. I.N. 26203 5.95

Better Short Wave Reception by Wm. Orr, W6SAI. I.N. 26204 ..... 4.95

Ameco Books

Communicate with the World with Ham Radio NP-1. I.N. 24825 ..... 6.95

Ameco 7-01 Question and Answer Guide for the Novice Exam 1.00

Question & Answer for Advanced Class Exam 16-1 I.N. 24809 ..... 1.50

Question & Answer for Extra Class Exam 17-1 I.N. 24801 ..... 1.50

Radio Amateur Theory Course 102-01 I.N. 24812 4.95

Radio Electronics Made Simple I.N. 24800 2.50

Logbook I.N. 24807 ..... 1.50

Commercial Radio Operator Theory Course 15-01 I.N. 24808 ..... 6.95

Commercial Q&A License Guide Ele. 4 10-01 I.N. 24805 ..... 1.95

Commercial Q&A License Guide Ele. 3 9-01. I.N. 24804 ..... 2.95

Commercial Q&A License Guide Ele. 1, 2, & 9. 8-01. I.N. 24803 ..... 1.50

Other Great Books

Collins Radio Co. SSB Amateur Single Sideband I.N. 10092 ..... 4.95

73 Magazine VHF Antenna Handbook I.N. 26303 ..... 4.95

73 Magazine Novice Class Study Guide. I.N. 26300 ..... 4.95

73 Magazine General Class Study Guide I.N. 26301 ..... 4.95

The Beverage Antenna Handbook. I.N. 0000 5.00

K3CHP DX QSL Guide I.N. 26313 ..... 3.95

Amateur TV in a Nutshell I.N. 26322 ..... 5.00

How to Make Better QSL's. I.N. 26304 ..... 4.95

The Complete Handbook of Slow Scan TV. I.N. 30518 ..... 9.95

Remember, you can Call Toll Free: **1-800-633-3410** in the U.S.A. or call **1-800-292-8668** in Alabama for our low price quote. Store hours: 9:00 AM til 5:30 PM, Monday thru Friday.

VISA

Long's Electronics

master charge

MAIL ORDERS P.O. BOX 11347 BIRMINGHAM, AL 35202 • STREET ADDRESS 2808 7TH AVENUE SOUTH BIRMINGHAM, ALABAMA 35233

FREE 1-800-633-3410 OR ORDER BY MAIL TODAY

Tab Books

Novice Class Study Guide I.N. 30517 ..... **5.95**
General Class Study Guide I.N. 30519 ..... **7.95**
Advanced Class Study Guide I.N. 30522 ..... **5.95**
Extra Class Study Guide I.N. 26302 ..... **5.95**
A Beginners Guide to Microprocessors I.N. 30502 ..... **5.95**
57 Programs and Games in Basic I.N. 30501 **7.95**
The "Compulator" Book I.N. 30509 ..... **7.95**
Ham Radio Incentive Licensing Guide I.N. 30503 **4.95**
Programming Microprocessors I.N. 30508 **6.95**

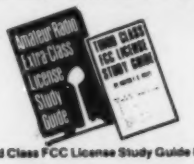

Third Class FCC License Study Guide I.N. 30514 **6.95**
First Class FCC License Study Guide I.N. 30542 **7.95**
Electronics Data Handbook I.N. 30549 ..... **5.95**
Impedance I.N. 30520 ..... **5.95**
Basic Digital Electronics I.N. 30527 ..... **4.95**
Basic Electronic Problems Solved I.N. 30545 **4.95**
Tower's International FET Selector I.N. 30500 **6.95**
Second Class FCC Encyclopedia I.N. 30535 **7.95**
How to Use AF and RF Signal Generators I.N. 30512 ..... **5.95**
Electronics Unraveled I.N. 30531 ..... **5.95**
Master Transitor/IC Substitution Handbook I.N. 30510 ..... **7.95**
RF and Digital Test Equipment You Can Build I.N. 30521 ..... **5.95**
Commercial FCC License Handbook I.N. 30542 **7.95**
IC Projects for the Amateur and Experimenter I.N. 30543 ..... **5.94**
How to Read Electronic Circuit Diagrams I.N. 30546 ..... **6.95**

Getting the Most Our of Your Electronic Calculator I.N. 30528 ..... **4.95**
How to Install Everything Electronic I.N. 30552 **7.95**
The 2 Meter FM Repeater Circuit Handbook I.N. 30537 ..... **6.95**
Modern Applications of Linear IC's I.N. 30530 **9.95**
Mobile Radio Handbook I.N. 30534 ..... **4.95**
Basic Electricity and Beginning Electronics I.N. 30536 ..... **5.95**
Practical Solid State DC Power Supplies I.N. 30515 ..... **6.95**
Electronic Conversions, Symbols, and Formulas I.N. 30524 ..... **5.95**
Tower's International Transitor Selector I.N. 30507 ..... **6.95**
Electronic Test Equipment and How to Use It I.N. 30526 ..... **4.95**

Master Handbook of 1001 Practical Electronic Circuits I.N. 30523 ..... **9.95**
Master Handbook of Ham Radio Circuits I.N. 30506 ..... **8.95**
Complete Short Wave Listeners handbook I.n. 30532 ..... 6.95
Master OP-AMP Applications Handbook I.N. 30505 ..... **9.95**
C.E.T. License Handbook I.N. 30513 ..... **8.95**
Effective Trouble Shooting with EVM and Scope I.N. 30525 ..... **5.95**
Handbook of Electronic Tables I.N. 30548 **4.95**
Homebrew HF/VHF Antenna Handbook I.N. 30504 ..... **5.95**
How to Be a Ham I.N. 30533 ..... **3.95**

Radio Amateur Callbook

Map Library A complete set of maps, prefix world map, great circle chart, map of N. America, and world atlas I.N. 10005 ..... **3.75**
Callbook binders
U.S. callbook red I.N. 10054 ..... **6.00**
DX callbook blue I.N. 10055 ..... **6.00**
DX Callbooks I.N. 10001 ..... **14.95**
U.S. Callbooks I.N. 10000 ..... **15.95**
Prefix map of North America I.N. 10004 .. **1.25**
Zone prefix map of the World I.N. 10022 .. **1.25**
Great circle chart of the World I.N. 10003 **1.25**

RSGB Books

Oscar - Amateur Radio Satellites The comprehensive book on amateur satellites illustrated with pictures and charts I.N. 10059 **8.50**

VHF-UHF Manual If you have any interest above 30 MHz, then get this book. It covers everything in this field. I.N. 26208 ..... **13.95**

TRAINING PACKAGES TAPES

Crack the code and ace your exam by studying the new way with our selection of cassettes. Just drop them into a cassette player and study anywhere easily and quickly. You'll have great results.

73 cassettes
Novice Theory Tapes prepare you for the FCC novice exam. Clearly presented material can be reviewed many times. I.N. 26306 ..... **15.95**

Code Tapes
5 word per min. Blitz Tape I.N. 26308 ..... **4.95**
6 word per min. Blitz Tape I.N. 26309 ..... **4.95**
13 word per min. Blitz Tape I.N. 26310 ..... **4.95**
20 word per min. Blitz Tape I.N. 26311 ..... **4.95**

Teco Code Practice Tape are guaranteed for life.
Novice tape I.N. 31461 ..... **3.95**
5 wpm tape I.N. 31450 ..... **3.95**
7½ wpm tape I.N. 31451 ..... **3.95**
10 wpm tape I.N. 31452 ..... **3.95**
13 wpm tape I.N. 31460 ..... **3.95**
15 wpm tape I.N. 31454 ..... **3.95**
17 wpm tape I.N. 31455 ..... **3.95**
20 wpm tape I.N. 31456 ..... **3.95**
22 wpm tape I.N. 31457 ..... **3.95**
25/30 wpm tape I.N. 31458 ..... **3.95**
35/40 wpm tape I.N. 31459 ..... **3.95**

Ameco Code Tapes
Junior Code Course #100-T Covers start to 8 wpm I.N. 24819 ..... **4.95**
Advanced Code Course #103-T From 8 to 18 wpm. I.N. 24821 ..... **4.95**
Senior Code Course #101-T Double length covering the Junior and Advanced Courses start to 18 wpm. I.N. 24820 ..... **8.95**
Extra Class Code Course #104-T Covers from 13 wpm to 22 wpm includes FCC type exam. I.N. 24822 ..... **4.95**
General Class QSO tapes #105-QT 12, 13, 14, & 15 wpm. I.N. 24827 ..... **4.95**
Extra Class QSO tape #106QT 19, 20, 21, & 22 wpm. I.N. 24826 ..... **4.95**

Katronics
QSO Code Tapes Covers 7½, 10, 13, & 15 wpm. Be ready for the new FCC exams! I.N. 28906 **4.95**

Remember, you can Call Toll Free: **1-800-633-3410** in the U.S.A. or call **1-800-292-8668** in Alabama for our low price quote. Store hours: 9:00 AM til 5:30 PM, Monday thru Friday.

VISA

Long's Electronics

master charge

MAIL ORDERS P.O. BOX 11347 BIRMINGHAM, AL 35202 • STREET ADDRESS 2808 7TH AVENUE SOUTH BIRMINGHAM, ALABAMA 35233

1-800-633-3410 TODAY!

CALL LONG'S TOLL FREE

200 WATTS PEP

KENWOOD TS-120S All solid state HF SSB transceiver

No tune up needed on this extremely small unit with miniaturized circuits and solid state construction. It has built-in digital display, cooling fan, IF shift, built-in protection for the final transistor, VOX, noise blanker, 25 KHz marker. The freq. range is 80 to 10 meters and WWV, modes: SSB and CW, power requirements: receive - 0.7A 13.8 VDC, transmit- 18A 13.8 VDC. Size: 3⅞"H x 9¼"W x 13½"L. Weight: 11.7 lbs.

699.95 List. Call for quote.

KENWOOD VFO-120

This unit allows the operator to work split frequencies, find a clear frequency while holding the original one. It has new features as the T-F set switch which prevents mis-operation in double split frequency operation and aids in quick setting of transmit frequencies.

159.95 List. Call for quote.

KENWOOD PS-30 power supply

Designed to match the TS-120S, this unit supplies regulated 13.8 VDC at 15 A continuous, 20A intermittent load with complete ease and safety due to the use of generous heat sinks and an automatic reset electronic overload trip.

139.00 Call for quote.

KENWOOD AT-120 antenna tuner

For use with the TS-120S. Frequency range 3.5 thru 29.7 MHz, input impedance: 50 ohms, output impedance: 20-300 ohms unbalanced (coax fed), max. power: 150 watts, tuning range: 1.0—1-10:1, SO-239 connectors. SWR meter, insertion loss less than 0.5 dB at optimum match. 6"W x 2⅝"H x 6¼"D.

99.95 List. Call for quote.

KENWOOD SP-120 speaker

A good-looking compact speaker matching the TS-120S styling and designed for home station use. Low distortion speaker unit for clear reproduction of audio.

39.00 Call today!

KENWOOD TR-7625 25W transceiver

The unit has memory channel with simplex or repeater operation ±600 KHz transmitter offset, mode switch for switching the transmit freq. up or down, full 4 MHz coverage on 2m (144.00-147.995), 800 channels, 5 KHz offset switch, MHz selector switch, digital freq. display, unlock indicator for transceiver protection.

425.00 List. Call for quote.

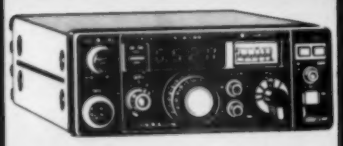

KENWOOD TR-7600 2m FM transceiver The radio that remembers

Full 4 MHz coverage (144-148), 800 channels, 10 W RF output/1 W low, memory channel with repeater or simplex offset, 13.8 VDC at 3 amps continuous.

375.00 List. Call for quote.

KENWOOD MC-45 touch tone mic

The touch tone circuit provides PTT with only ½ second hang time. It is an omnidirectional, dynamic mic with 500 ohm impedance, very good frequency response, and adjustable tone output level. Power requirement: 8 VDC, 20 mA. Complete with connector and coiled cord. Compatible with the TR-7600 and TR-7625 with no modification.

49.95 Call today.

DON'T WAIT!

KENWOOD R-300 all band communications receiver

Listen to foreign broadcasts or ham operators from around the world! It has a 3-way power supply (AC/batteries/external DC). In case of an AC power failure, it automatically switches to DC so is ideal for emergency use. The receiver frequencies (180 KHz to 30 MHz) are all covered by 6 bands. There is a 500 KHz marker on the receiver.

279.00 List. Call for quote.

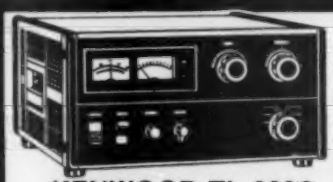

CALL NOW!

KENWOOD TL-922A 2000W linear amplifier

Features: 2 3-500Z final tubes, time delay fan circuit, frequency range: 160 thru 15 meters, drive power: 80W or more for full output, RF input power: SSB 2000W PEP, CW & RTTY: 1000W DC, power requirements: 120/220/240 VAC 50/60 Hz.

1199.00 List. Call for quote.

VISA

Long's Electronics

master charge

MAIL ORDERS P.O. BOX 11347 BIRMINGHAM, AL 35202 • STREET ADDRESS 2808 7TH AVENUE SOUTH BIRMINGHAM, ALABAMA 35233

CALL LONG'S TODAY!

1-800-633-3410 TOLL FREE

MFJ-484 Grandmaster memory keyer

Featuring speed control, 4 LEDs to show memory in use, record and playback, iambic operation, dot-dash memories, repeat messages with pauses, built-in memory saver, weight control, tone control, tune function, solid state keying, uses 110 VAC or 12-15 VDC. Automatically switches to external batteries when AC power is lost.

139.95 list

MFJ-721 CW/SSB filter

Featuring selectable bandwidth, 8 pole active filter, switchable automatic noise limiter, plugs into phone jack, 2 watts for speaker, simulated stereo reception, inputs for 2 rigs, speaker and phone jacks, aux 2W amplifier, 20 dB gain, 80 Hz bandwidth, requires 9-18 VDC 300 ma max.

59.95

MFJ-941B Versa Tuner II

Features SWR and dual range wattmeter, antenna switch, built-in balun, 300W RF output. Matches everything from 1.8 thru 30 MHz, uses 1 antenna, increases the usable bandwidth, has SO-239 connectors.

79.95

MFJ-8044 IC deluxe keyer

Sends iambic, automatic, semi-automatic or manual. Dot and dash memories, totally RF proof, solid state keying, front panel controls, weight control, tone control, function switch, 3 conductor phone jack for key, phono jacks for keying outputs. Squeeze key optional.

69.95 Call today

CUSHCRAFT AMS-147 FM mobile 2m mag mount antenna

A ⅝ wave length antenna with 3 dBi gain, low SWR operation over 146-148 MHz FM band. Move center freq. 1-5 MHz. Matched to 50 ohms. Complete with coax & connector.

34.95 Call for yours today

CUSHCRAFT ARX-2 2m antenna

Three ½ waves in phase and a 1/8 wave matching stub. Extremely low angle of radiation for better signal coverage. Tuneable over a broad freq. range. Matched to 52 ohm coax.

39.95 Call today

B&W 595 coax switch

Features 6 outputs a power rating of 2KW PEP, VSWR of less than 1.2:1 up to 150 MHz, grounds all unused antennas IN 27305. Add 1.10 shipping & handling.

21.50 Call today

B&W 375
5 position coax switch

Features 5 outputs, power rating of 2KW PEP, VSWR less than 1.2:1 up to 150 MHz, with wall mount and dial plate, grounds all unused antennas IN 27306. Add 1.10 shipping & handling.

19.75 Call today

B&W 593
3 position coax switch

This switch features 3 outputs, a power rating of 2 KW PEP, VSWR of less than 1.2:1 up to 150 MHz & grounds all unused antennas IN 27315. Add 1.10 shipping & handling.

17.50 Call today

B&W 375 coax switch

Featuring power rating 1000W AM and 2000W SSB, connectors are UHF type, dial plate supplied, has 5 outputs. Grounds all unused antennas & has VSWR of less than 1.2:1 up to 150 MHz IN 27300. Add 1.10 shipping & handling.

19.75 Call today

B&W 550 A
5 position coax switch

Featuring power rating of 1000W AM 2000W SSB UHF type connectors 5 outputs. VSWR is less than 1.2:1 up to 100 MHz with very little insertion loss IN 27301. Add 1.10 shipping & handling.

17.50 Call today

B&W 550A-2
2 position coax switch

This unit features 2 outputs a power rating of 2 KW PEP VSWR less than 1.2:1 up to 100 MHz B&W wall mount and DP-2 dial plate available IN 27303. Add 1.10 shipping & handling.

14.95 Call today

DENTRON Big Dummy load

Now you can tune-up off the air with the Big Dummy! A full power dummy load, it has a flat SWR, full frequency coverage from 1.8 to 300 MHz and a high grade of industrial cooling oil furnished with the unit. Fully assembled. Cut out the QRM factor now!

29.50 Call today!

HY-GAIN HB-MAG 287 Hy-bander foldover antenna

A magnetic mount antenna with the unique fold over for mounting on hatchback cars. ¼ wave, ratchet foldover adjusts through a 180 degree arc and hold its position at speed up to 120 mph. Less than 1.4:1 VSWR, 144-148 MHz, power rated to 150W, 3 dB gain, DC grounded.

19.95 Call today!

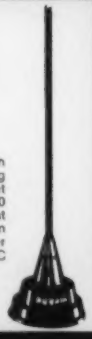

BENCHER BY-1 iambic paddle

The Ultimate iambic paddle. Features solid silver contact points, full range adjustment, non-skid feet and heavy steel black textured base. Item No. 31700. Add 1.35 shipping & handling.

39.95

BENCHER BY-2 iambic paddle

The By-2 has all the features of the BY-1 but comes with chrome base. Add 1.35 shipping & handling. Item No. 31701.

49.95

VISA

Long's Electronics

master charge

MAIL ORDERS: P.O. BOX 11347 BIRMINGHAM, AL 35202 • STREET ADDRESS: 2808 7TH AVENUE SOUTH BIRMINGHAM, ALABAMA 35233

DDRR Dipole for VHF

— experiment!

Seeking selectivity.

Dave Atkins W6VX
130 N. Westgate Ave.
Los Angeles CA 90049

Selectivity in an antenna is becoming increasingly important as the bands compress under the load of more and more stations. Reception is where this is most desirable. Front-end overload, we have learned, will cause big problems to a communications circuit when off-channel signals are strong. Directional-type antennas, of course, are the answer unless we need to cover everything around us. The DDRR, or directly driven ring radiator, developed by its inventor, J.M. Boyer (with patents assigned to Northrop), has high selectivity. Because of this, it also is a low-noise device. This makes two good reasons for its superior performance. (*73 Magazine* for August and September, 1976, goes into detail of its design and advantage. There have been many other articles written about it over the years.) Two drawbacks are noted when the chips are down. One is the size of the ground plane for the monopole design; the other is the cost of the conductor material for low-frequency use. Tuning can be another problem where its use for high-power transmission is contemplated. Very high voltage and current are the prices of the trade-off for high selectivity.

What Is It?

Boyer suggests the DDRR dipole in his September (part two) article. This version does without the big ground plane, as would any dipole. So here we have a quarter-wave open transmission line formed into a shape which "leaks" and radiates rf. I first built one of these for ten meters and made it so it operated on its highest frequency (no added capacitance) and at a fixed frequency. A/B checks with the spaced rings mounted vertically compared very well with those of a horizontal folded dipole at the same height and with the same orientation. Pretty good for an antenna on ten meters which is 30 cm "long" and 84 cm in diameter (see *73*, April, 1965, "Double Hula," Peter Lovelock).

The Two Meter DDRR Dipole

To make the two meter model, I dug out an old ¼-inch tubing coil from a long-forgotten final and annealed it in the fireplace, then cleaned and polished the surface after stretching it between a car bumper and a stout post. 33 inches comes to a half wave. This is then folded on a one-inch-diameter rod or mandrel at exact center. The quarter-wave line is formed on a can to make a circular double ring or transmission line of about 5 inches diameter. This will resonate above the 148 MHz end of the band. I made a simple tuning arrangement of a 4-inch piece of #20 (0.8 mm) Teflon™-covered flexible wire. This is formed into a U to slide into the open ends of the line. When

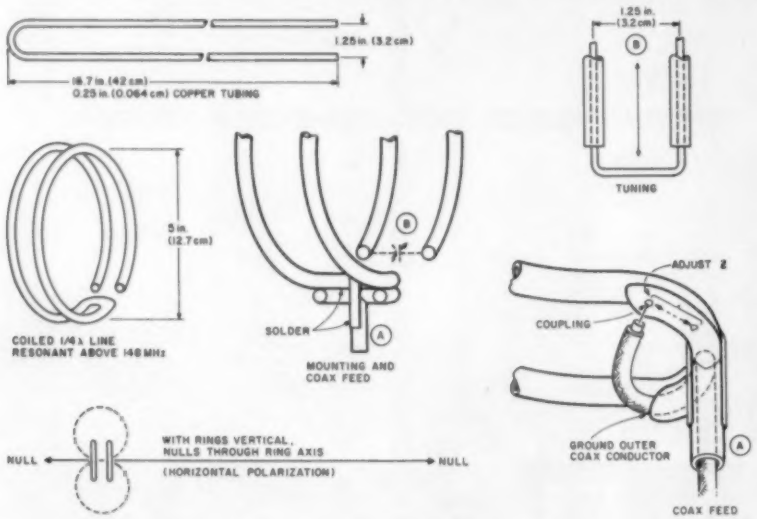

Fig. 1. Two meter DDRR dipole.

CALL TOLL FREE

1-800-228-4097

Communications Center

443 N 48th Street
Lincoln, Nebraska 68504
In Nebraska Call (402)466-8402

C58

Antenna Sale!

HY-GAIN

		Regular	Special			Regular	Special
TH6DXX	Super Thunderbird	$299.95	$239.95	18HT	Hy-Tower 80-10M vertical	299.95	239.95
TH3MK3	3 el. 10-15-20M beam	229.95	179.95	18AVT/WB	80-10M Trap vertical	99.95	79.95
TH3JR	3 el. 10-15-20M beam	149.95	129.95	14AVQ/WB	40-10M Trap vertical	69.95	57.00
Hy-Quad	2 el. 10-15-20M Quad	229.95	179.95	12AVQ	20-10M Trap Vertical	39.95	32.95
205BA	5 el. "Long John" 20M beam	289.95	229.95	14RMQ	Roof Mounting kit (verticals)	33.95	29.95
155BA	5 el. "Long John" 15M beam	169.95	139.95	5BDQ	80-10M Trap doublet	89.95	69.95
105BA	5 el;"Long John" 10M beam	119.95	99.95	2BDQ	80-40M Trap doublet	49.95	39.95
204BA	4 el. 20M beam	219.95	179.95	66B	6 el. 6M beam	119.95	99.95
204MK5	5 el. conversion kit	99.95	79.95	203	3 el. 2M beam	15.95	
153BA	3 el. 15M beam	79.95	69.95	205	5 el. 2M beam	17.95	
103BA	3 el. 10M beam	54.95	44.95	208	8 el. 2M beam	25.95	
402BA	2 el. 40M beam	209.95	169.95	214	14 el. 2M beam	31.95	
BN-86	Balun for beam antennas	15.95	15.95	LA-1	Deluxe lightning arrestor	59.95	49.95
TH2MK3	2 el. 10-15-20M beam	149.95	119.95				

MOSLEY

		Regular	Special
Classic 33	3 el. 10, 15, 20 Mtr. beam	304.75	209.95
Classic 36	6 el. 10, 15, 20 Mtr. beam	392.75	269.95
TA-33	3 el. 10, 15, 20 Mtr. beam	264.00	189.95
TA-36	6 el. 10, 15, 20 Mtr. beam	392.75	269.95
TA-33 Jr.	3 el. 10, 15, 20 Mtr. beam	197.00	149.95
TA-40KR	40 Mtr. Add On	119.95	89.95

CUSHCRAFT

ATB-34	4 ele. 10, 15, 20 Mtr. beam	289.95	219.95	A147-11	11 ele. 146-148 Mhz. beam	36.95	30.95
ATV-4	10, 15, 20, 40 Mtr. Vertical	89.95	69.95	A147-22	22 ele. Power Pack	109.95	89.95
ATV-5	10, 15, 20, 40, 80 Mtr. Vertical	109.95	89.95	A144-10T	2 Mtr. "Twist" 10 ele.	42.95	34.95
ARX-2	2 Mtr. Ringo Ranger	39.95	32.95	A144-20T	2 Mtr. "Twist" 20 ele.	62.95	52.95
AR-6	6 Mtr. Ringo	36.95	32.95	A147-20T	2 Mtr. beam	62.95	52.95
ARX-220	220 Mhz. Ringo Ranger	39.95	32.95	A430-11	432 Mhz. 11 ele. beam	34.95	29.95
ARX-450	435 Mhz. Ringo Ranger	39.95	32.95	A432-20T	430-436 Mhz. Beam	59.95	49.95
A144-11	11 ele. 144-146 Mhz. beam	36.95	30.95				

HUSTLER

		Regular	Special
3-TBA	3 ele; 10, 15, 20 Mtr. beam	259.95	189.95
4-BTV	10-40 Mtr. Vertical	99.95	79.95
5-BTV	10-80 Mtr. Vertical	134.95	99.95
RM-75	75 Meter Resonator	16.95	14.50
RM-75S	75 Meter Super Resonator	31.95	27.50
G6-144B	2 Mtr. Base Colinear	79.95	59.95
G7-144	2 Mtr. Base Colinear	119.95	89.95

WILSON

System One	5 ele. 10, 15, 20, Mtr. Beam	$299.95	$239.95
System Two	4 ele. 10, 15, 20 Mtr. Beam	249.95	199.95
System Three	3 ele. 10, 15, 20 Mtr. Beam	199.95	159.95
WV-1	10-40 Mtr. Vertical	79.95	69.95

TAYLOR

HQ 1040AV	10-40 Mtr. Trap vertical	59.95	49.95

ROTORS

HamIII $125.00 — T2X Tailtwister $199.95 — Alliance HD 73 $109.95

Call for prices on rotor cable, Coax, Towers, and Accessories. All prices do not include shipping.

18HT

We carry all major brands of ham radios AT DISCOUNT PRICES

BANKAMERICARD

Yaesu — Kenwood — Drake — ICOM — Dentron — Ten-Tec — Swan — Tempo — Midland — E.T.O. — Wilson

master charge

Reader Service—see page 211

pushed in, the frequency should more than cover the 2 meter band. See detail B in Fig. 1.

A length of small-diameter coax may be coupled tightly to the closed end of the open line. Mine was fed through a separate matching U-shape of the same tubing soldered to the closed end of the line. A good match was obtained by varying the size of the link (see drawing). A 50-Ohm match comes at an area of less than that formed by the 180 degree half turn at the closed end of the line. The ¼-inch line thus formed needs no insulators for support.

Mounting of the completed antenna may be done in several ways. Mine was to make a pedestal a few inches long and to feed the coax through. This was mounted breadboard fashion on a piece of hardwood. A BNC coax connector was fastened to this piece. A tuning arrangement was made to slide the Teflon tuning U in or out to cover the band of interest. The selectivity curve was measured using a signal generator, a counter, and an FM receiver. The antenna frequency was left fixed and the receiver and generator were moved together across the antenna frequency.

While vertical polarization is the way most of our present two meter signals leave the antenna, things happen that make the polarization somewhat different at the receiving end. By orienting the receiving antenna, it is often possible to null out an interfering signal. By going a step further, I made the mounting adjustable in azimuth and elevation. This also can be done in various ways—mine is a breadboard way to test the idea. Aiming it works well and can reduce multipath *and* QRM.

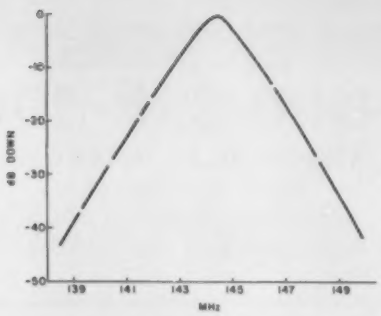

Fig. 2. Two meter DDRR dipole antenna selectivity.

Conclusions

While the amount of selectivity afforded by the DDRR will not come up to that of a multipole filter, it is worthwhile in that it is ahead of the front end—aiding in the signal-to-noise problem. An undesired signal off to one side is noise, too.

Do not try transmitting with the device with the tuning method described except with very low power. It will not pass the smoke test.

Broadband antennas are very convenient (discones, rhombics, and tribanders), but who needs all these unwanted signals going up and down the feedline? Phased DDRR elements could improve selectivity as well as gain.

A selective antenna should make a big difference to you.■

AHF ANTENNAS
INTRODUCES OUR NEW EXCLUSIVE
MOBILE ANTENNA
★ GREATER FIELD STRENGTH
★ GREATER TUNING RANGE
★ ALL NON-CORROSIVE PARTS
★ ALL THREADS U.S. STANDARD 3/8 × 24
★ MADE ENTIRELY OF QUALITY MATERIALS
OUR FINEST KIT only $85.00
Radiator, Mast, 10 Meter Adaptor, and 1 ea. 75, 40, 20 and 15 Meter Coils
(Parts may be purchased separately)
Common 2 - 4 - 6 and 8 MHz MARINE frequency coils also available
2 to 30 MHz Custom Frequency Coils, made to order
Contact your favorite dealer or Write for brochure
AHF / ANTENNAS
2814 S. Baywater Ave.
San Pedro Ca. 90731
Phone (213) 831-5444
Dealerships available

50 144 REPEATERS 220 450 Mhz
BASIC AUTO PATCH
*Access, #Disable and adjustable Timer. COMPLETELY ASSEMBLED—$75.00.
Now with courtesy beep and beacon capability
EXTENSION BOARD
Antifalsing, 3 digit sequential Touch Tone™ decoder with automatic reset, Antifalsing Ring detector, reverse auto patch capability for basic auto patch and two, two-watt audio amplifiers.
COMPLETELY ASSEMBLED—$140.00
Available Separately:
COR Identifier: All on one board, programmable, Fully adjustable, time out (.5-7 min.), hang time (0-1 min.), identifier (1-10 min.), tone, speed, volume, L.E.D. outputs, low current drain CMOS logic, plugs for easy installation and removal plus much more. $79.95 COMPLETELY ASSEMBLED
Hi Pro Mk I REPEATERS
Basic Repeater $499.95 COMPLETELY ASSEMBLED
2M 130-175 MHz Basic Repeater for 2 meters with all the features of the HI Pro Mkl less the power suply and front panel controls and accessories.
50 MHz $789.95 450 MHz 799.95
144 + 220 MHz $699.95
PA Res. add 6% tax
PLUS SHIPPING
M36
Maggiore Electronic Laboratory
845 WESTTOWN RD.
WEST CHESTER, PA. 19380 PHONE 215 436-6051

THE BIG SIGNAL
UNADILLA "W2AU" Baluns
U9
Still Only $14.95
DEMANDED BY PROFESSIONALS WORLD-WIDE OVER 12 YEARS
• The Original Lightning Arrest
• 650# Strength
• Stainless Hardware
• Sealed
• GUARANTEED
ASSISTANCE? Call: HUGH GUNNISON, WA2ZOT Toll-Free 800-448-1666 [NYS Collect 315-437-3953]
FOR HIGHEST ANTENNA EFFICIENCY
1:1 OR 4:1 2,000 W PEP
FULL · POWER, QUALITY HAM ANTENNA PARTS AT YOUR DEALER
• BALUNS · TRAPS · INSULATORS
• QUAD PARTS · ANTENNA KITS
• BOOM/MAST MOUNTS · WIRE
• CABLE · CONNECTORS
WRITE FOR FULL CATALOG [Enclose 30¢ Stamps]
MICROWAVE FILTER COMPANY INC
UNADILLA/REYCO DIVISION [Dept. 73]
6743 KINNE STREET, EAST SYRACUSE, NEW YORK 13057
DEALERS WANTED - OVER 300 WORLD-WIDE

Reader Service—see page 211

TET®

ANTENNA SYSTEMS

Multi Band Beam Super DX Series

NEW HIGH PERFORMANCE TRI-BAND BEAMS AS GOOD AS FULL-SIZE MONO BAND ANTENNAS.
These beams employ hybrid system which is a combination of separated full-size driven element for each band individually and Hi-Q trap parastic elements. These feature result high radiation efficiency, high power rating and excellent VSWR in entire band width.

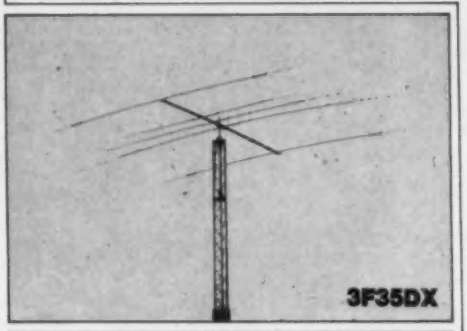

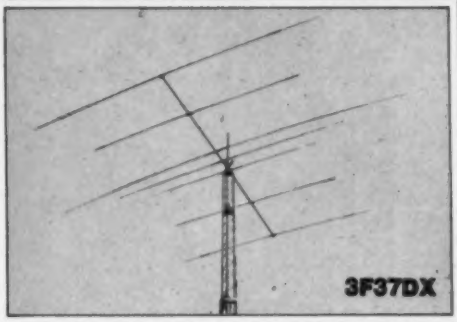

MODEL		3F37DX	3F35DX
BAND		14 21 28	14 21 28
ELEMENTS		7	5
ELEMENTS PER BAND	20m	3	3
	15m	5	3
	10m	5	3
ANTENNA GAIN	20m	8.5dB	8.0dB
	15m	10dB	8.5dB
	10m	10dB	8.0dB
FRONT BACK RATIO		25dB	20-25dB
MAX. POWER INPUT		3kw	3kw
VSWR		1.5 or less	1.5 or less
IMPEDANCE		50Ω	50Ω
MAX. ELEMENT L.		10.5m	10.5m
BOOM LENGTH		7.5m	5.0m
BOOM DIAMETER		50mm	50mm
TURNING RADIUS		5.3m	5.25m
WIND RATING		40m/sec.	40m/sec.
SUITABLE MAST		50mm	50mm
WEIGHT		23kg	17kg

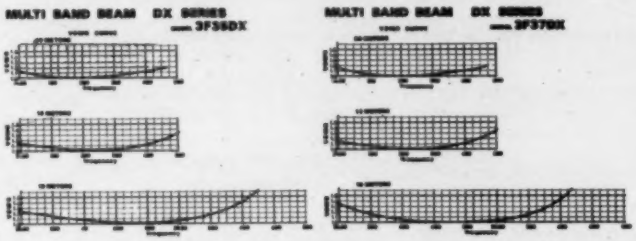

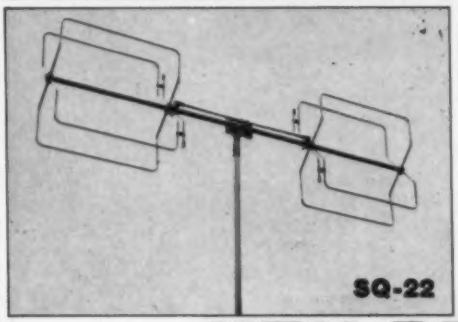

"SWISS QUAD VHF SERIES"

SQ-22 TWO METER DUAL QUAD

ANTENNA GAIN AND FRONT TO BACK RATIO ARE WELL IMPROVED WHEN TWO ELEMENTS ARE DRIVEN AT ONE TIME WITH PHASE DIFFERENCE COMPARED TO A SINGLE DRIVEN ELEMENT SUCH AS A CONVENTIONAL QUAD OR YAGI. THE SQ-22 PROVIDES THE OWNER WITH SUCH FEATURES SIMPLE ASSEMBLY AND LIGHT WEIGHT.

KEN PRO ROTATORS

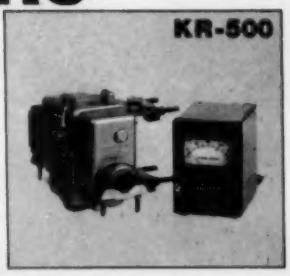

425 Highland Parkway, Norman, Oklahoma 73069
Tel (405) 360-6410

✔T55

TET U.S.A.

✔ Reader Service—see page 211

Social Events

Listings in this column are provided free of charge on a space-available basis. The following information should be included in every announcement: sponsor, event, date, time, place, city, state, admission charge (if any), features, talk-in frequencies, and the name of whom to contact for further information. Announcements must be received two months prior to the month in which the event takes place.

LOUISVILLE KY
JUN 29-JUL 1

The Louisville Area Computer Club will hold its 4th annual Computerfest™ 1979 from June 29 through July 1, 1979, at the Bluegrass Convention Center, Louisville, Kentucky. Activities include a flea market, seminars, and exposition, as well as activities for the entire family. Seminar and exposition admission is $4.00. Pre-registered Ramada Inn guests ($29.00, single; $34.00, double) receive free admission. For advance mail information, write Computerfest '79, Louisville Area Computer Club, PO Box 70355, Louisville KY 40270, or phone Tom Eubank, Chairman, at (502)-895-1230.

BATESVILLE AR
JUN 30-JUL 1

The Arkansas Army MARS meeting will be held on June 30-July 1, 1979, at the Independence County Fairgrounds, Batesville, Arkansas. There will be a fish fry on Saturday and a pancake breakfast on Sunday. Camping and motel rooms will be available. For further information, contact Robert Glines WB5KUI/ADN2MH, Box 97, Floral AR 72534, or phone (501)-345-2880.

BELLEFONTAINE OH
JUL 1

The Champaign Logan Amateur Radio Club, Inc., will hold its annual hamfest on Sunday, July 1, 1979, at the Logan County Fairgrounds, South Main Street and Lake Avenue, Bellefontaine, Ohio. There will be free admission and door prizes. Trunk and table sales are $1.00, and there will also be a bid table. Talk-in on 146.52. For more information, contact John L. Wentz W8HFK, Box 102, West Liberty OH 43357, or Frank Knull W8JS, 402 Lafayette Ave., Urbana OH 43078.

DUNKIRK NY
JUL 1

The Northwestern New York Repeater Association and the Northern Chautauqua Amateur Radio Club will hold their Lake Erie International Hamfest on Sunday, July 1, 1979, at the fairgrounds in Dunkirk, New York. A large flea market area and plenty of free parking will be provided. Tickets are $4.00 at the gate or $3.00 in advance. RV hookups are available. For information on advance sales or for a map showing easy directions from I-90, write to Dick Brinkerhoff WB2HEF, 123 5th St., Dunkirk NY 14048.

HARRISBURG PA
JUL 4

The Harrisburg RAC will hold its annual Firecracker Hamfest on Wednesday, July 4, 1979, at the Shellsville VFW picnic grounds, I-81 north, Exit #27 or #28, Racetrack Exit, Harrisburg, Pennsylvania. Look for the large balloon. Admission is $3.00, with no charge for tailgating. Tables will be available in the pavilion. Talk-in on .52/.52.

WELLINGTON OH
JUL 7

The Northern Ohio Amateur Radio Society will hold its second annual NOARSFEST on Saturday, July 7, 1979, at the Lorain County Fairgrounds, one mile west of Rte. 58 on Rte. 18, Wellington, Ohio. Admission tickets are $1.50 in advance and $2.00 at the gate and are good for all prize drawings. Children under 12 are admitted free. Gates open for the sellers and dealers at 6:00 am and to the public from 7:00 am to 5:00 pm. Indoor dealer tables are $4.00 each by advance registration. Drawing-only tickets are available by mail or at the gate for $1.00 each. Flea market spaces are $1.00 each. There will be over 100 prizes, including a DenTron HF-200 transceiver, a Ten-Tec 509, a DenTron GLA-1000, a Wilson Mark II, and an Opto-electronics counter. There will be plenty of food and free parking. Featured will be a large indoor exhibit hall for dealers and a huge blacktopped midway for flea market and trunk sales. There will be free camping outside the gates on Friday night, but no hookups. For advance registration, information, or tickets, write NOARSFEST, PO Box 354, Lorain OH 44052.

INDIANAPOLIS IN
JUL 8

The Indianapolis Amateur Radio Association will sponsor the Indianapolis Hamfest on Sunday, July 8, 1979, at the Marion County Fairgrounds, on the southeast corner of Indianapolis at the intersection of Interstates 74 and 465, Indianapolis, Indiana. There will be commercial exhibitors and dealer displays for a fee of $30.00 per booth. The commercial building will be open from 12:00 noon until 9:00 pm on Saturday and will reopen at 7:00 am on Sunday. Camper hookup facilities are available on the fairgrounds for overnight parking if you arrive on Saturday. A food and drink vendor will have a setup outside, while a professional caterer will have facilities inside. For more information, write to the Indianapolis Hamfest, PO Box 1002, Indianapolis IN 46206.

OAK CREEK WI
JUL 14

The South Milwaukee Amateur Radio Club will hold its annual Swapfest '79 on Saturday, July 14, 1979, at American Legion Post #434, 9327 S. Shepard Avenue, Oak Creek, Wisconsin. Admission is $2.00 and includes a happy hour with free beverages. Prizes include a $100 first prize, a $50 second prize, and a variety of other prizes. Activities will begin at 7:00 am and continue until 5:00 pm. Parking, a picnic area, hot and cold sandwiches, and liquid refreshments will be available on the grounds. Overnight camping is also available. Talk-in on 146.94. More details, including a map, may be obtained from the South Milwaukee Amateur Radio Club, Inc., Robert Kastelic WB9TIK, Secretary, PO Box 102, South Milwaukee WI 53172.

BEAVER PA
JUL 15

The Beaver Valley Amateur Radio Association will hold its 2nd annual hamfest on Sunday, July 15, 1979, from 9:00 am to 5:00 pm at Brady's Run Park on Rte. 51 west from Beaver, Pennsylvania. Shelters 12 and 17 will be used. There will be free space for vendors. Tickets are $3.00. Talk-in on .52 and directions on 146.25/.85. For information, write WB3FKE, 3414 47th Street, New Brighton PA 15066.

TERRE HAUTE IN
JUL 15

The 33rd annual WVARA Hamfest will be held on July 15, 1979, at the Vigo County Fairgrounds, one mile south of I-70 on US 41, Terre Haute, Indiana. Overnight camping will be available. There will be a free flea market, a covered flea market at $2.00 for a 12' x 12' space with some tables and ac available, XYL bingo, food, refreshments, and valuable prizes. Advance ticket sales are $1.50 or 4 for $5.00. Tickets at the gate are $2.00 or 3 for $5.00, with children under 12 free. Talk-in on .25/.85 and .52. For tickets and information, send an SASE to WVARA Hamfest, PO Box 81, Terre Haute IN 47808.

ALLENTOWN PA
JUL 15

The Delaware-Lehigh ARC, Inc., the BGYE, Inc., and the Lehigh Valley ARC, Inc., will hold their Tri-Club Hamfest on July 15, 1979, from 8:00 am to 4:00 pm at the Allentown Police Academy pistol range on Lehigh Parkway South at Allentown, Pennsylvania. Admission is $2.00 for lookers and $4.00 for sellers. Talk-in on .34/.94 and .52.

WILKES-BARRE PA
JUL 15

The Broadcasters Amateur Radio Club will hold its 2nd annual hamfest on July 15, 1979, from 9:00 am to 4:00 pm at Pocono Downs Racetrack, Rte. 315, four miles north of Wilkes-Barre, Pennsylvania. Setup begins at 8:00 am. Admission is $2.50, with no additional fee for sellers. XYLs and children are free. The event is all indoors. Talk-in on 147.66/.06 or 146.52. For more information, write John Soha W3KU, 62 S. Franklin Street, Wilkes-Barre PA 18707, or phone (717)-823-3101.

CANTON OH
JUL 15

The fifth annual Hall of Fame Hamfest will be held on Sunday, July 15, 1979, at Stark County Fairgrounds, Canton, Ohio. Tickets are $2.50 in advance and $3.00 at the gate. Mobile check-in on .19/.79 or .52/.52. For information, contact Max Lebold WA8SHP, 10877 Hazelview Ave., Alliance OH 44601.

GUANAJUATO MEX
JUL 19-21

The first annual ARARM-LMRE will be held in Guanajuato, Mexico, from July 19-21, 1979. Guanajuato is located 230 miles north of Mexico City. Registration will be US $13.00. A package will be available for US $40.00 and will include 2 banquets, 1 dinner dance, sight-seeing, theater, and gifts. Drawings will be held, with a grand prize being an SSTV setup. A total of 500 prizes will be given away. The US $40.00 includes registration. Hotels are available with prices ranging from US $10.00 and up for a double room. English-speaking guides are available from the University of Guanajuato. Talk-in on 147.63/.03, 146.10/.70, and 149.22/.82. HF/SSB frequencies will also be operating, and we

Continued on page 182

YOU HAVEN'T READ THEM ALL. . .

Rush my subscription so that I can read them all, and if I'm not completely satisfied with what I read, or the service I receive on the first or any issue, I'll receive a full refund on **all** remaining issues.

☐ One year $15 (50% off) ☐ Three years $45* (50% off)
☐ Payment enclosed ☐ Bill Me
Bill my ☐ Master Charge ☐ Visa

Credit Card # **Expiration Date**

Signature

Name **(print or type, please)**

Address

City **State** **Zip** 197

Canadian subscriptions add $2 per year. All other foreign subscriptions $26 one year only payable in U.S. funds. Please allow four to six weeks for delivery of first copy.

73 Magazine / P.O. Box 931 / Farmingdale NY 11737

YOU HAVEN'T READ THEM ALL. . .

Rush my subscription so that I can read them all, and if I'm not completely satisfied with what I read, or the service I receive on the first or any issue, I'll receive a full refund on **all** remaining issues.

☐ One year $15 (50% off) ☐ Three years $45* (50% off)
☐ Payment enclosed ☐ Bill Me
Bill my ☐ Master Charge ☐ Visa

Credit Card # **Expiration Date**

Signature

Name **(print or type, please)**

Address

City **State** **Zip** 197

Canadian subscriptions add $2 per year. All other foreign subscriptions $26 one year only payable in U.S. funds. Please allow four to six weeks for delivery of first copy.

73 Magazine / P.O. Box 931 / Farmingdale NY 11737

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY CARD
FIRST CLASS PERMIT NO. 17 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

73 magazine
Subscription Department ● Box 931
Farmingdale NY 11737

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY CARD
FIRST CLASS PERMIT NO. 17 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

73 magazine
Subscription Department ● Box 931
Farmingdale NY 11737

IF YOU'VE READ ONE,

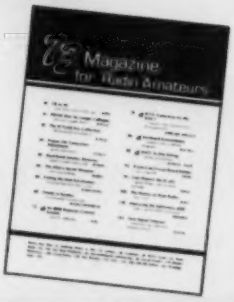

YOU HAVEN'T READ THEM ALL!

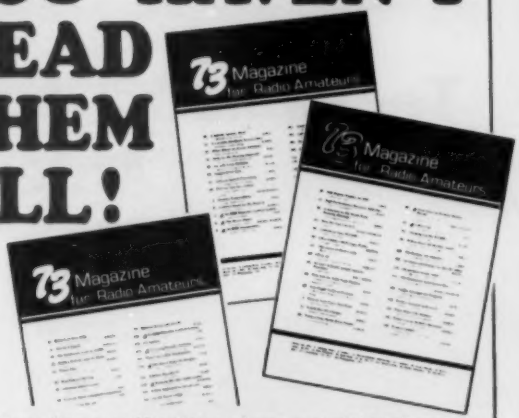

Ever notice how other magazines published in the field of radio electronics are just like the ones before them—same old subjects, same predictable view, same old editorials?

Each issue of **73** is an entirely **new** book: over 194 pages including over 25 articles of new material each month, separate and special, unlike all that have come before it. **73** led the way in developing the use of solid-state circuitry and was the first to promote SSTV, radioteletype, computer applications for radio communications, and single sideband, to name a few. In addition, the staff of **73** is working on another scoop that you won't want to miss.

In one issue you might find building projects and information on antennas, moonbouncing, and mountaintopping. In the next issue you might read about computers, radioteletype, traffic handling, and satellites.

This is a hefty magazine, with more articles each month than any two of the other ham magazines combined, and we pay more for an article than any other ham magazine.

You get what **we** pay for!

The only thing that every issue of **73** has in common is quality, and we take pride in delivering them to you, pride in providing the latest developments in the field, pride in helping you enjoy your hobby, and pride in covering subjects the rest of the ham media ignore.

So try a year with us at **73**; you'll be surprised at the amazing variety. You've got nothing to lose, but plenty to gain. If, after you've read your first copy, or even your 11th, you're not completely satisfied with **73**, if you don't feel that **73** is as good a magazine as you can buy anywhere, we'll refund your money on all remaining issues. So start your subscription by dropping the attached postage-paid card in the mail today. You pay only $15—50% off the current newsstand price for 12 issues, or save $45 on a three year subscription. Please allow 60 days for shipment of first copy.

Rush my subscription so that I can read them all, and if I'm not completely satisfied with what I read, or the service I receive on the first or any issue, I'll receive a full refund on **all** remaining issues.

☐ One year $15* (50% off) ☐ Three years $45* (50% off)

☐ Payment enclosed ☐ Bill Me
Bill my ☐ Master Charge ☐ Visa

Card# _____ Exp. date _____

Signature _____

Name _____
(please print or type)

Address _____

City _____ State _____ Zip _____

*Canadian subscriptions add $2 per year. All other foreign subscriptions: $26 one year only, payable in U.S. funds. Please allow 4-6 weeks for delivery of first copy.

197

73 Magazine ● Subscription Dept. Box 931 ● Farmingdale NY 11737

Rush my subscription so that I can read them all, and if I'm not completely satisfied with what I read, or the service I receive on the first or any issue, I'll receive a full refund on **all** remaining issues.

☐ One year $15* (50% off) ☐ Three years $45* (50% off)

☐ Payment enclosed ☐ Bill Me
Bill my ☐ Master Charge ☐ Visa

Card# _____ Exp. date _____

Signature _____

Name _____
(please print or type)

Address _____

City _____ State _____ Zip _____

*Canadian subscriptions add $2 per year. All other foreign subscriptions: $26 one year only, payable in U.S. funds. Please allow 4-6 weeks for delivery of first copy.

197

73 Magazine ● Subscription Dept. Box 931 ● Farmingdale NY 11737

Tennamatic: An Auto-Tuning Mobile Antenna System

—works all of 40 and 75

Farewell to fading.

B. F. Brown W6TWW
1241 Arroyo Seco Dr.
Campbell CA 95008

Would you like to operate your mobile station over the entire 40 and 75 meter phone bands with a vswr not exceeding 1.15 to 1? With a Tennamatic, you can convert a high-Q narrow-bandwidth mobile antenna into a wide-bandwidth system. This means that you can use transceivers having solid-state finals and obtain full output power on any frequency in the 40 or 75 meter phone bands without any manual tuning operations. All you have to do is select frequency, start talking, and the Tennamatic will tune your mobile antenna system to resonance automatically, ensuring maximum field strength. Of course, if your transceiver has tubes in the final, you will still have to retune it when you QSY. Specifications for the Tennamatic are listed in Table 1.

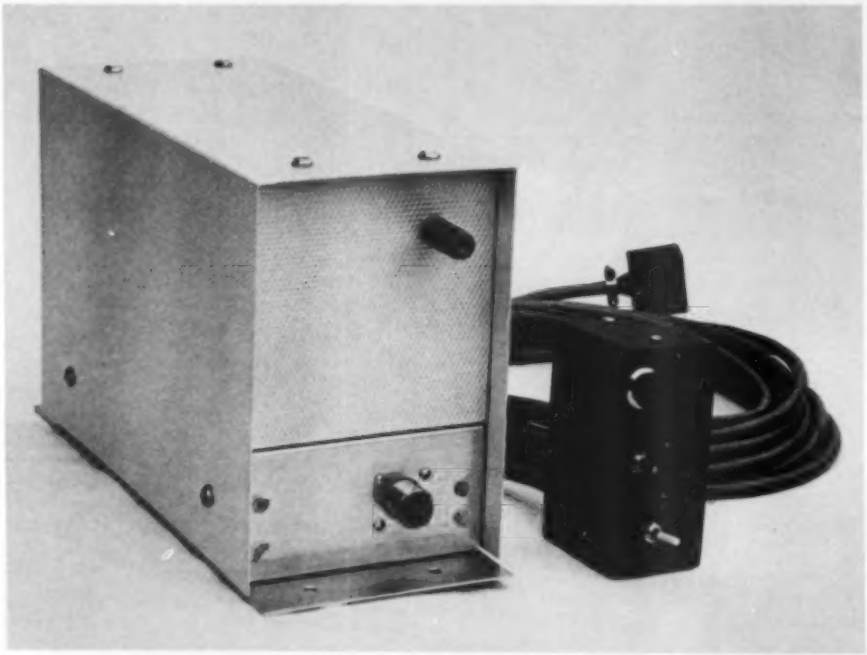

The neat packaging of the Tennamatic can be duplicated easily. The control head, tuner cover, and end pieces are 0.040-inch soft aluminum cut in a paper cutter and folded in a vise using wood blocks. The chassis is described in the text.

History

About two years ago, I met Don Johnson W6AAQ, and I adopted his "big DK" mobile antenna system. He subsequently described it in his October, 1976, *73 Magazine* article entitled "Build a Weird 2 Band Mobile Antenna." His antenna neatly solved the problem of needing to change antenna loading coils when band-hopping between 40 and 75 meters. It also proved to be an exceptionally efficient radiator compared to the commercials, but it was still limited to only a few kHz of usable bandwidth on each band, and I wanted full band coverage.

To obtain full band coverage, I added a motor-driven roller inductor at

the base of the antenna and a control switch at the driver's seat, allowing me to QSY the antenna resonant frequency. This worked beautifully for about six months until I ran off a freeway one day while watching a field strength meter as I was peaking the antenna. Luckily, no damage was done, but the experience convinced me that for safety's sake I had to get out of the loop. This conclusion required me to design a servo system.

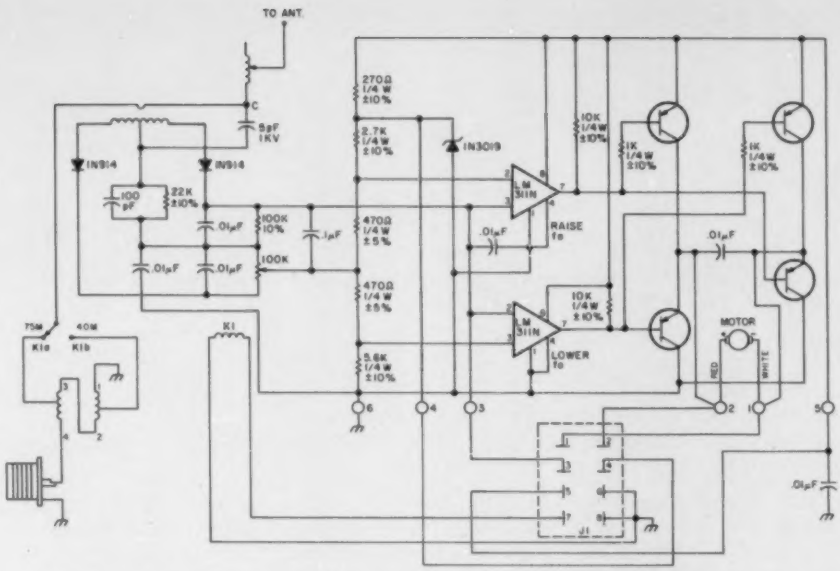

Fig. 1. Tuning unit schematic. The output transistors and motor are discussed in the text. The jack is a male chassis-type Jones plug.

Design Requirements

I decided that the tuner would be required to tune automatically over all of the 40 and 75 meter phone bands and use easily-obtainable parts. The parts count was to be minimized to keep reliability high, complications associated with limit switches were to be avoided, and the power handling capability had to be at least 350 Watts PEP. It had to be easy to duplicate, present a pleasing appearance, and the control head had to be capable of being mounted on the side of an Atlas and be visually compatible. Last of all, the servo system had to be uniquely simple, have a 3- or 4-kHz deadband so it would not hunt or jitter around in the voice pass band, provide constant motor torque while tuning, and operate reliably over a plus ten-to-fifteen-volt supply voltage range.

The System

These design requirements led to a system consisting of two units. One unit is a control head and the other is the tuning unit. The tuning unit contains a phase detector and a servo system which drives a permanent-magnet dc gear motor. The motor turns a roller inductor taken from a surplus T21/ARC-5 or T22/ARC-5 command transmitter. The tuning unit also contains a toroidal impedance-matching transformer which ensures a good impedance match between the antenna and coaxial line. The control head has directional indicators, an automatic/manual operation switch, an automatic/manual indicator, a manual slewing switch, and an impedance-match selector switch. The units are shown in the photographs.

The Circuit

The circuit which I designed is depicted in Fig. 1. To understand its operation, it is best to start with an explanation of the servo system and work backwards toward the input. The system that I selected is known as a "bang bang" servo system in aerospace circles. It is either off or on in one direction of rotation or the other and provides full motor torque when on. Fig. 2 is a simplified diagram of the servo. It uses two LM311N voltage comparator integrated circuits connected as a window comparator. The circuit states listed in Fig. 2 simply say that if the input voltage (V_{in}) is a positive voltage between the upper and lower threshold voltages, the outputs of both comparators will be at supply voltage. If V_{in} either exceeds the upper threshold voltage or is less positive than the lower threshold voltage, one or the other comparator's output will be low. The low-state output is about one-half volt positive.

Referring back to Fig. 1, it will be seen that the comparator outputs are connected to diagonally-opposite transistors. When a comparator switches on and its output goes low, it turns on the associated transistors, resulting in one side of the motor being clamped to ground while the other side is clamped to the positive supply, turning the motor on. The upper comparator drives the motor in the direction which reduces inductance, raising the antenna system resonant frequency. The lower comparator drives the motor in the opposite direction, increasing inductance and lowering the antenna system resonant frequency.

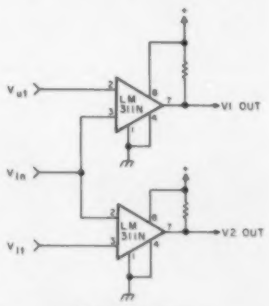

Circuit states

$V_{in} < V_{ut}$: V1 out is high
$V_{in} > V_{lt}$: V2 out is high
$V_{in} > V_{ut}$: V1 out is low
$V_{in} < V_{lt}$: V2 out is low

Fig. 2. Window comparator servo simplified diagram.

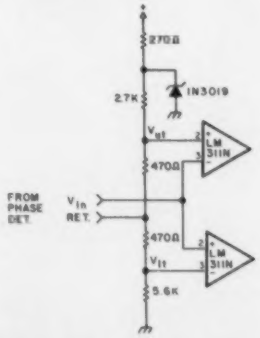

Fig. 3. Window comparator regulated-voltage divider.

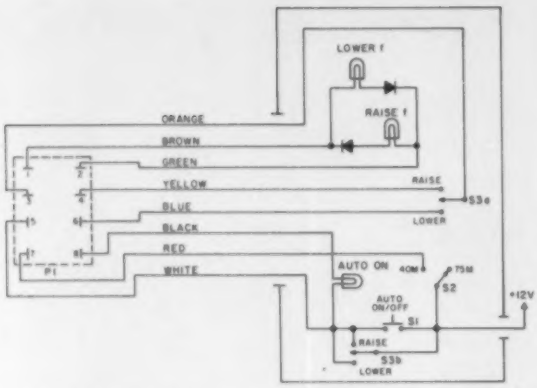

Fig. 4. The control head assembly connects to the Jones-type plug, P1, through 20 feet of TV rotator cable. The diodes are Radio Shack part number 276-1101.

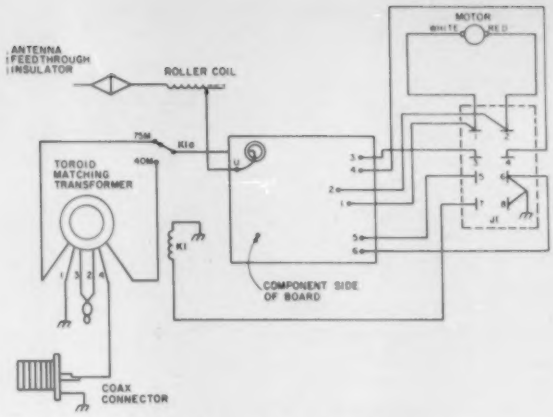

Fig. 5. Tuner unit wiring diagram.

Fig. 3 shows the input circuit to the voltage comparators. The comparators must operate with their inputs positive with respect to ground, making it necessary to reference the phase detector to a point above ground. This reference point is the junction of the two 470-Ohm resistors. The output of the phase detector is connected to V_{in} and will be a voltage which will swing positive or negative with respect to the reference point, causing the comparator inputs to swing above V_{ut} or below V_{lt}, depending upon the off frequency condition existing at the time. The voltage divider is zener regulated to hold the switching thresholds constant. The voltage drops across the two 470-Ohm resistors set the width of the deadband to 3 kHz on 75 meters and 4 kHz on 40 meters.

The phase detector compares the phase relationship between the current flowing in the antenna circuit and the voltage from the antenna circuit to ground. When the input frequency is higher than the antenna system resonant frequency, the phase detector produces a dc output voltage across the two 100k load resistors which is positive with respect to the slider on the trimpot. Conversely, if the input frequency is lower than the antenna system resonant frequency, the output dc voltage is negative.

The trimpot is adjusted in operation to cause the phase detector to find exact resonance. It compensates for the inductive reactance inserted by the toroidal antenna impedance-matching transformer. The reduced output from the low side of the phase detector caused by the trimpot results in need for incremental downward QSY on 75 meters with pauses to allow the servo system to catch up. Even so, a QSY from 4000 kHz to 3800 kHz takes less than 30 seconds.

The impedance-matching transformer is necessary with the DK antenna because of its low input impedance at resonance. The taps are set at the 10-Ohm point for 40 meters and at the 14-Ohm point for 75 meters. These low input impedance values are excellent indicators of the low-loss characteristics and high performance of the antenna. Relay K1, a Potter and Brumfield KT11D 12 V dc 5-Ampere contact relay, selects the appropriate tap and is controlled by a manual switch on the control head.

Fig. 4 depicts the schematic of the control head. All of the switches, diodes, and 12 V dc indicator lamps are from Radio Shack. Switch S1 provides for switching the tuner into the automatic or manual mode and is a push-on/push-off switch. S3 provides capability to

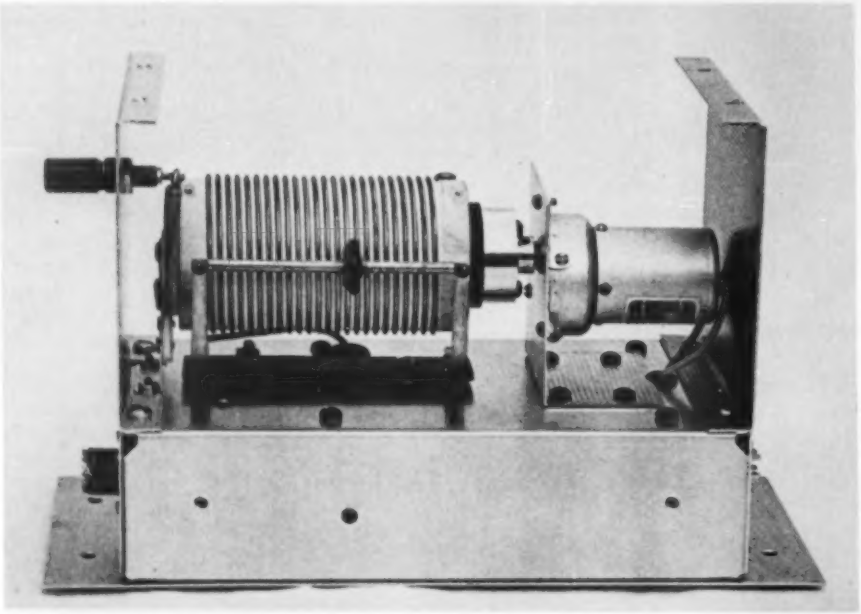

Mounting details of the roller inductor, gear motor, and shaft coupler illustrate the mechanical simplicity of the unit.

manually slew the tuner up or down in frequency. It is a DPDT center-off-type switch. I have found that I use it rarely in operation, but it is nice to have in case you need it. It is needed during the installation adjustments. S2 operates the antenna-matching transformer tap-selector relay. No power on/off switch is provided, as power is taken directly from the transceiver. This prevents inadvertently leaving power on the tuner unless, of course, you forget to turn the transceiver off when you leave the car.

Construction

The photographs of the tuner reveal how simple the unit is to duplicate. It is built on a standard 2" × 4" × 8" aluminum chassis, and the motor bracket, end panels, cover, and bottom plate are easily constructed in the home workshop. Several W6s have built the tuner and made Plexiglas™ covers so that they can see the roller coil go into operation when they QSY. The layout I selected results in minimum antenna-circuit wire length and should be duplicated as closely as possible.

Don't get innovative by trying to reduce conductors in the control cable. You can quickly get into trouble because the voltage comparators are sensitive to rf and to ground loops and will go "ape" if you unknowingly build in a ground loop as a result of a circuitry change. Also, keep some spacing between the control cable and the coaxial line, as rf pickup in the control cable can lead to erratic operation. The wiring diagram is shown in Fig. 5. The only precaution here is to note the direction of the antenna wire as it goes through the hole in the toroidal phase-sensing transformer. If it goes through from the wrong side of the printed circuit board, the tuner will drive away from resonance.

Antenna-Matching Transformer

A T-106 red toroidal core, obtained from either G.R. Whitehouse or Amidon Associates, both of which advertise in several amateur magazines, is the heart of the transformer. Fig. 6 provides all necessary details for construction. The sleeve for securing the taps is a model airplane copper gas line obtained from a hobby shop and cut to length with a hacksaw. Should you desire to use an antenna other than the big DK, you must determine the antenna input impedance in Ohms at resonance with an antenna noise bridge and then determine the correct tap position from Table 2. If you don't use the DK, you will still have to change loading coils when changing bands.

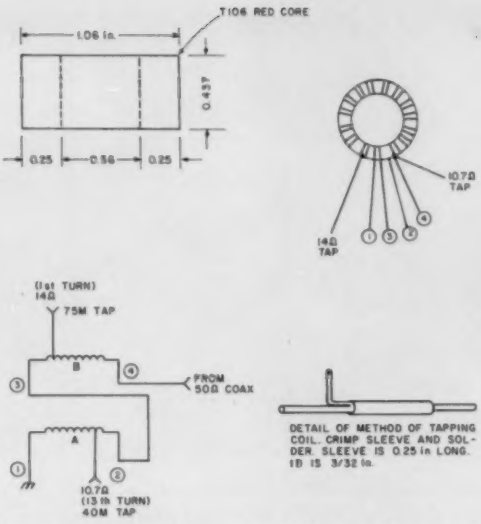

Fig. 6. Toroidal impedance-matching transformer details. Notes: Cut two wires 24" long and wind in parallel for a bifilar winding. Each winding is to have 14 turns. Taps and wires 1 and 4 are to be 2" long. Wires 2 and 3 are to be twisted and soldered and not to exceed ½" long. All wire should be AWG #18 enamel. Dip it in General Cement Red Glypt and hang up to dry before use.

Phase-Detector Transformer

Construction details of this transformer are depicted in Fig. 7. When winding the transformer, be sure that the wires remain parallel to each other without any crossovers. Also, count each pass through the hole as a turn.

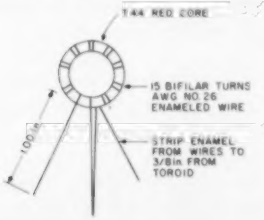

Fig. 7. Phase-detector transformer details. Note: Cut two wires 12" long and wind in parallel for bifilar winding. Connect the opposite ends together as shown for center tap.

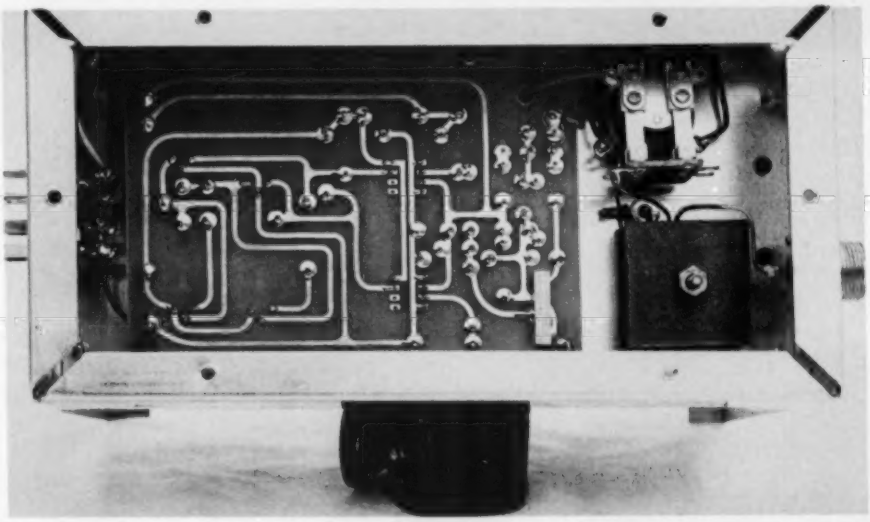

The under chassis view further illustrates the mechanical as well as the electrical simplicity of the unit. The toroidal antenna impedance-matching transformer is hidden by the masonite clamping pieces. The prop under the chassis is a photographic lens case.

This neat installation of the tuning unit in the left rear window of my station wagon permits a short lead-in from the ball mount outside.

Frequency range:	75m—200 kHz 40m—300 kHz
*Slewing rate:	75m—6 kHz/sec. 40m—40 kHz/sec.
Minimum Δf:	75m—requires 3 kHz QSY to activate tuner 40m—requires 4 kHz QSY to activate tuner
Maximum Δf:	75m—50 kHz (QSY of 200 kHz in four increments of 50 kHz requires less than 30 seconds.) 40m—200 kHz (QSY of 200 kHz requires less than 5 seconds.)
Vswr:	typically 1.15 to 1 or better after tuning completed
Modes:	automatic/manual
Input voltage:	10 to 15 V dc, negative ground
Input current:	420 mA at 13.8 V dc while tuning; 125 mA at 13.8 V dc after tuning completed
Power rating:	350 Watts PEP

*Table 1. Tennamatic specifications. *Full carrier inserted. On SSB, the slewing rate is slightly slower due to speech pauses.*

Remember that it is impossible to wind a half turn on a toroid. This transformer need not be dipped in General Cement Red Glypt, although you may do so if you wish.

Gear Motor

The gear motor which I used and recommend is a Magna-Torc™ permanent-magnet 24 V dc motor with a type B gear reduction unit. Operated in the Tennamatic, this motor will turn the roller inductor at approximately one revolution per second. The motor is manufactured by the Hansen Manufacturing Co., Princeton, Indiana 47670. It may also be obtained from Hartfield, Kennan, and Freytag, PO Box 328, Fremont CA 94536. The motor is expensive at about $21.50 per copy; however, it is the smallest and neatest solution to the drive-motor problem and well worth it.

Others who have built this tuner have found various surplus motors or used window crank-up motors obtained from auto wrecking yards. These high-current motors are quite bulky, do not allow neat packaging of the system, and also require the addition of relays to the output of the tuner, since the transistors can not drive them directly. These surplus motors do have the advantage of being cheap, however.

Shaft Coupler

The shaft coupler mates the gear motor drive shaft to the thumbwheel on the end of the roller inductor. It is made of aluminum turned out on a lathe and is simply bolted with three 6-32 machine screws to the thumbwheel. Fig. 8 provides the dimensional details. One of the photographs shows how it looks when the motor and roller coil are coupled together.

Printed Circuit Board

Fig. 9 depicts the printed circuit board. Be sure that you watch the polarity of the phase-detector diodes when you insert them. Also, it is a very good idea to use integrated circuit sockets instead of soldering the integrated circuits directly into the board. The four output transistors can be Poly Paks green-body PNP power-tab transistors, part number 92CU2227, or Radio Shack PNP power-tab transistors, part number 276-1641. Both types are rated at 35 Watts with suitable heat sinking. Heat sinking is not required in this application.

If you use the Poly Paks transistors, bend the tabs at right angles to the body of the transistors to ensure that they clear other components mounted on the board. Make the bend about a quarter inch from the body of the transistor. Test them carefully for leakage before you solder them because I have found that about 25% of them are too leaky to work properly in this circuit. They will cause the directional indicator lights to light even when the system is at resonance. I've had no trouble with Radio Shack transistors.

The photograph of the underside of the chassis shows the printed circuit board as installed in the tuner. The trimpot was mounted on the foil side of the board because, when three-quarter-inch stand-

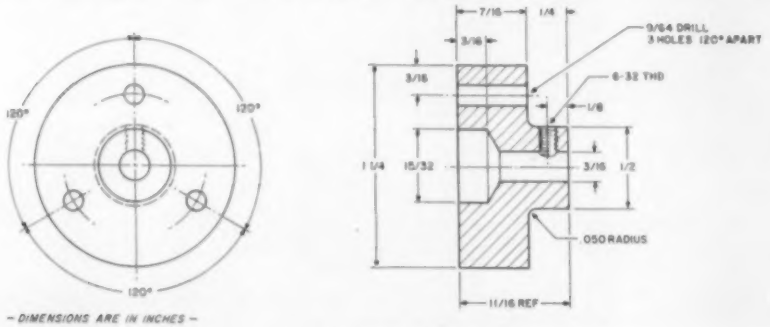

Fig. 8. Shaft coupler.

offs for supporting the board are used, the screwdriver access hole in the side of the chassis falls midway in the side.

I have a few extra printed circuit boards available at $5.00 each for those who prefer not to make their own.

Installation

Mount the tuning unit as close as possible to the base of your antenna. Connect the base of the antenna to the tuning unit with insulated AWG #12 or #14 wire. Do not under any circumstances use coax to connect the antenna to the tuner! Make sure that you ground the tuning unit to the car body by means of sheet metal screws or a short bonding strap. Use 50-Ohm coaxial cable to connect the tuning unit to your transceiver. RG-58A/U is satisfactory, and the length is not critical.

One photograph shows how I mounted the tuner in my station wagon. After mounting the control head to the transceiver (I used Velcro® fastening tape), connect the control head power lead to the transceiver so that the transceiver power switch will control application of power to your Tennamatic.

DK Antenna Adjustment

After installation of your Tennamatic, your DK antenna (or other antenna) must be retuned to be resonant on approximately 4025 and 7325 kHz. For this adjustment, the roller inductor must be slewed to minimum inductance using the manual slewing switch. Next, you must determine the antenna resonant frequency on both 75 and 40 meters using your vswr bridge or field-strength meter. Resonance will be lower than it was before the Tennamatic was installed. Don't overlook changing the impedance-matching tap when you change bands looking for resonance.

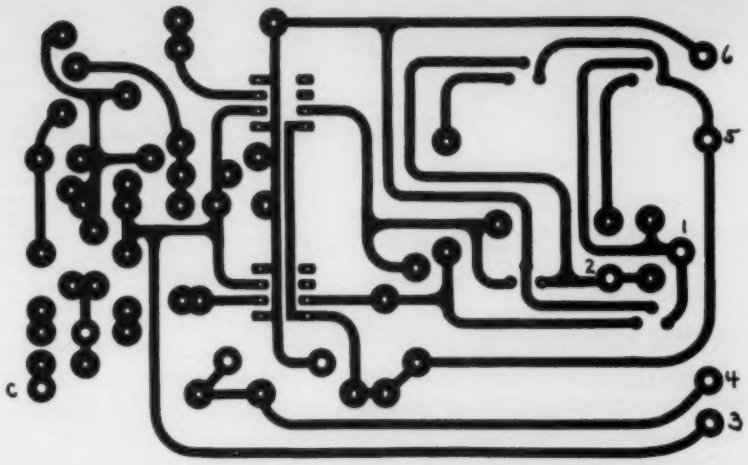

Fig. 9(a). PC board.

Now that you know where the antenna system resonances are, you can proceed to raise them by removing turns from the loading coil, shortening the whips, or by a combination of both methods. If the two resonances are as low as 3900 kHz and 7150 kHz approximately, you may find it better to remove a turn or two from the bottom of the loading coil and one or more turns from the top of the loading coil in order to minimize the amount that must be trimmed off the whips. Remove turns only one at a time. Be sure to check the resonant frequency on each band after each adjustment because they interact, and it is essential that you do not go too far. By the time resonance is approaching the upper band edge on 75 and 40 meters, you should have determined the number of kHz per inch of frequency change you get with each inch cut off. The kHz-per-inch figure will be different for each whip. After reaching 3995 kHz and 7295 kHz, cut off an additional increment from each whip determined by dividing 30 kHz by the number of kHz per inch for each band. This will complete the antenna tuning procedure.

Tuner Trimpot Adjustment

This adjustment is made to cause the tuner to tune for maximum field strength (coincident with minimum vswr). When adjusted on 40 meters, it will also be correct on 75 meters. Adjust as follows:

1. Make sure your vehicle is at least fifteen feet away from other vehicles, trees, buildings, or metallic objects.

2. Turn the trimpot fully counterclockwise, and

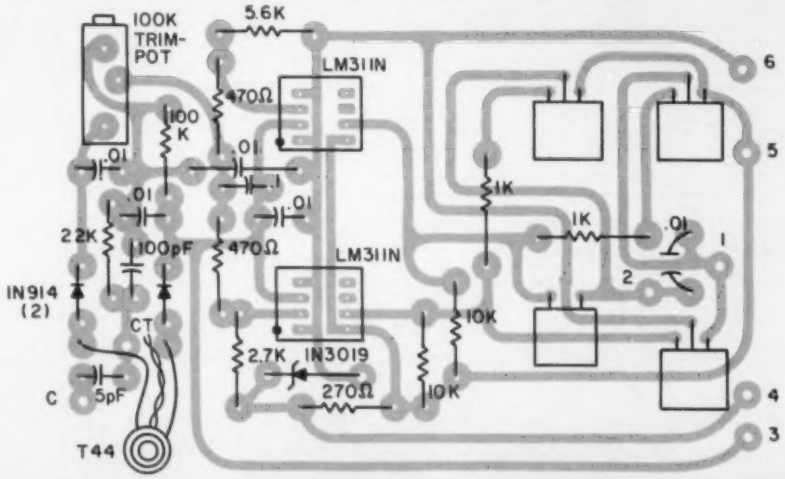

Fig. 9(b). Component locations viewed through the foil side of the board. When installing the LM311N integrated circuits, line up the dot on the IC with the dot shown on the outline of the board. The T-44 phase-sensing transformer may be glued to the board. The four output transistors are mounted against the board.

Antenna input impedance	Winding A turn number	Winding B turn number
3.13	7	
4.08	8	
5.17	9	
6.38	10	
7.72	11	
9.18	12	
10.78	13	
12.5	14	
14.34		1
16.33		2
18.43		3
20.66		4
23.02		5
25.51		6
28.13		7
30.87		8
33.74		9
36.73		10
39.86		11

Table 2. Transformer taps required for various antenna input impedances to match 50-Ohm coaxial line.

then preset it six turns clockwise.

3. Turn on your transceiver. Place it in the tune mode with carrier inserted on the 40 meter band.

4. While watching a field-strength meter or vswr indicator, tweak the trimpot until you observe maximum field strength or minimum vswr. The Tennamatic must be in the automatic mode for this adjustment. Your unit is now ready to operate.

Operating Results

With a year and a half of operating experience, the Tennamatic has demonstrated that high-Q mobile antennas are extremely sensitive to the environment around them. For example, a dense fog will lower the antenna system resonant frequency on 75 meters by as much as 25 kHz, but the Tennamatic will compensate by rolling the inductor to less inductance. I leave it in the automatic mode at all times while driving, and, as long as I am talking, it will compensate quickly for the detuning caused by passing trucks, cars, trees, freeway overpasses, bridges, and residential power line drops as you drive under them. The result is that most of the characteristic mobile fade, which I now realize is due to antenna detuning, is eliminated. The result is such a strong steady mobile signal that I frequently have to convince my contact that I am really mobile!

There is one thing that the Tennamatic cannot compensate for. That is another 75 or 40 meter mobile parked up to twenty feet away. The mutual coupling between antennas, reflected signal, and phase shifts cause it to go "ape." So, if you build one, don't proudly try to demonstrate it when parked near another mobile.

Acknowledgement

I would like to acknowledge with my thanks the numerous suggestions made by Don Johnson W6AAQ as this project proceeded through the breadboard, prototype, final design, and evaluation phases. I also wish to express my grateful appreciation for the photography provided by Jerry Fulstone WA6EJV. ■

ALL BAND TRAP ANTENNAS!

PRETUNED - COMPLETLY ASSEMBLED - ONLY ONE NEAT SMALL ANTENNA FOR UP TO 6 BANDS! EXCELLENT FOR CONGESTED HOUSING AREAS - APARTMENTS LIGHT - STRONG - ALMOST INVISIBLE!

FOR ALL MAKES & MODELS OF AMATEUR TRANSRECEIVERS - TRANSMITTERS - GUARANTEED FOR 2000 WATTS SSB 1000 WATTS CW. FOR NOVICE AND ALL CLASS AMATEURS!

COMPLETE AS SHOWN with 90 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 30 ft. 300 lb. test dacron end supports, center connector with built in lightning arrester and static discharge - molded, sealed, weatherproof, resonant traps 1"X6"- you just switch to band desired for excellent worldwide operation - transmitting and recieving! WT. LESS THAN 5 LBS.

160-80-40-20-15-10 bands 2 trap— with 90 ft. RG58U - connector - Model 777BU . . .$59.95
80-40-20-15-10 bands 2 trap — 102 ft. with 90 ft. RG58U - connector - Model 998BU . . .$54.95
40-20-15-10 bands 2 trap — 54ft. with 90 ft. RG58U coax - connector - Model 1001BU . . .$53.95
20-15-10 bands 2 trap — 26 ft. with 90 ft. RG58U coax - connector - Model 1007BU $52.95

SEND FULL PRICE FOR POST PAID INSURED DEL. IN USA. (Canada is $5.00 extra for postage - clerical - customs - etc.) or order using VISA Bank Americard - MASTER CHARGE - AMER. EXPRESS. Give number and ex. date. Ph 1-308-236-5333 9AM - 6PM week days. We ship in 2-3 days. ALL PRICES WILL INCREASE $5.00 SEPT. 1 - SAVE - ORDER NOW! All antennas guaranteed for 1 year. Money back trial! Made in USA. FREE INFO. AVAILABLE ONLY FROM.

WESTERN ELECTRONICS ✔W18 Dept. A7-7 Kearney, Nebraska, 68847

FOR BEST PRICE AND FAST DELIVERY
CALL
1-800-325-3636
TOLL FREE
HAM RADIO CENTER
8340-42 Olive Blvd. P.O. Box 28271 St. Louis, MO 63132
✔H2

JAN CRYSTALS
HOLD THE FREQUENCY

- CB
- CB standard
- 2 meter
- Scanners
- Amateur Bands
- General Communication
- Industry
- Marine VHF
- Micro processor crystals

Send 10¢ for our latest catalog. Write or phone for more details.

JAN CRYSTALS
master charge
VISA
easy to charge
✔J2
2400 Crystal Drive
Ft. Myers, Florida 33907
all phones (813) 936-2397

✔ Reader Service—see page 211

KENWOOD

TECH TALK 7B79

TS-120S

ALL SOLID-STATE HF TRANSCEIVER

TS-120S

What's unique about the PLL circuit in the TS-120S?

A single-conversion PLL (phase-locked loop) system is employed in the TS-120S. Only one crystal is required, instead of a heterodyne crystal element for each band, resulting in simplification of circuitry, and a marked improvement in overall stability. The single-conversion PLL system also improves the spurious characteristics during transmission and reception, and makes IF shift operation and mono-dial indication available on any model.

The VCO frequency is obtained from the PLL circuit by synthesizing the VFO and CAR frequencies and reference oscillating frequencies of 10 MHz and 500 kHz supplied by the counter. Bandswitching is accomplished by changing the preset value of the programmable divider in the PLL. Therefore, when switching bands, the frequency (except, of course, the 1-MHz and 10-MHz order digits) remains the same. The frequencies for each band and PLL stage are shown in the table.

FREQUENCY COMPOSITION OF THE TS-120S PLL SYSTEM

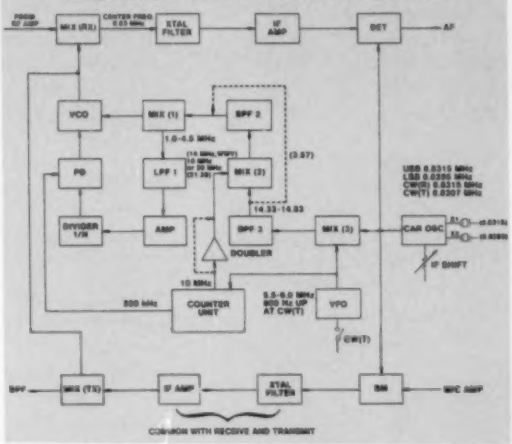

First, MIX (3) mixes the CAR and VFO frequencies, using a double balanced mixer to reduce spurious signals. The output of MIX (3), after passing through a bandpass filter (BPF 3) is applied to the input of MIX (1) on the 3.5 and 7.0-MHz bands. On the 14-MHz and WWV bands, MIX (2) mixes the output of MIX (3) with a 10-MHz signal from the counter-unit oscillator. On the 21 and 28-MHz bands, MIX (2) mixes the output of MIX (3) with a 20-MHz signal from a doubler connected to the counter-unit oscillator.

The output of MIX (2) – or MIX (1) on the 3.5 and 7.0-MHz bands – is mixed with the VCO output at MIX (1), providing output frequencies shown in the table. The output passes through a lowpass filter (LPF 1) and is amplified, and the resulting digital signal is divided by a programmable divider, producing a 500-kHz output.

"Information" from the band switches is converted into BCD signals in the counter and the division ratio as shown in the table is preset. The loop-filter consists of transistors mounted on the outside to minimize signals. A Motorola MC4044P functions as the phase comparator. Five VCO circuits with high-output transistors cover all of the bands.

If the output of the phase comparator unlocks, VCO output is switched off to prevent emission at unwanted frequencies and, at the same time, the digital display blanks to warn the operator.

What is the concept of the TS-120S digital counter for displaying frequencies?

The TS-120S digital counter employs a VFO frequency counting system. First, the VFO frequency is mixed with a 5-MHz signal obtained from the reference oscillator chain and is converted to 0.5 to 1 MHz. This signal passes through a lowpass filter, is amplified, buffered, and shaped into a digital (square) wave, passes through a 0.1-second gate circuit, and is applied to a four-digit counter. The signal is counted from 10 Hz to 100 kHz and is fed to a preset counter to derive the carrier output.

The 100-kHz order digit presets at 5 to display the operating frequency on the 3.5, 28.5, 29.5, and WWV bands, and at 0 for display on 7.0, 14.0, 21.0, 28.0, and 29.0 MHz. The 1-MHz and 10-MHz order digits are determined by a matrix operating with bandswitch information.

The counter outputs are switched by the multiplexer and converted from BCD to seven-segment information by the decoder to light the fluorescent display tubes. The large digits have good luminous intensity and a dark filter, providing fatigue-free viewing over long operating periods. The display can be read easily, even in the car and other sunlit locations.

The reference oscillator produces a 10-MHz signal and performs time-base division, and generates gate pulses, latch pulses, and reset pulses, which are applied to the counter. The PLL circuit produces 10-MHz and 500-kHz outputs. The marker circuit produces a 100-kHz signal which synchronizes the 25-kHz multivibrator to obtain a marker signal as accurate as the reference frequency.

The 1/10 division at the first stage of the count-down chain utilizes low-power Schottky TTL, and other divisions use CMOS ICs for low power consumption and minimum spurious emission. With the IF shift circuit, the CAR frequency is independent of both transmitting and receiving frequencies.

When the VFO frequency is counted, the operating frequency is indicated as accurately as the reference oscillator frequency, provided that the 10-MHz reference is calibrated to WWV.

True operating frequencies are displayed accurate to three digits (100-Hz order), regardless of CW transmitting and receiving frequencies or the position of the band switch or mode switch. When the VFO is tuned to the extent that the 1-MHz and 10-MHz orders are switched (beyond the band edge), these digits are blanked out.

FREQUENCIES FOR EACH BAND AND PLL STAGE

BAND	RANGE (MHz)	VCO (MHz)	MIX (1) INPUT (MHz)	MIX (1) OUTPUT (MHz)	DIVIDER RATIO	DCBA
WWV	14.5-15.0	23.33-23.83	24.33-24.83	1.0	1/2	1110
3.5	3.5- 4.0	12.33-12.83	14.33-14.83	2.0	1/4	1100
7	7.0- 7.5	15.83-16.33	14.33-14.83	1.5	1/3	1101
14	14.0-14.5	22.83-23.33	24.33-24.83	1.5	1/3	1101
21	21.0-21.5	29.83-30.33	34.33-34.83	4.5	1/9	0111
28	28.0-28.5	36.83-37.33	34.33-34.83	2.5	1/5	1011
28.5	28.5-29.0	37.33-37.83	34.33-34.83	3.0	1/6	1010
29	29.0-29.5	37.83-38.33	34.33-34.83	3.5	1/7	1001
29.5	29.5-30.0	38.33-38.83	34.33-34.83	4.0	1/8	1000

William Epperhart, Jr. WB2DTY
7 Sampson Street
Oyster Bay NY 11771

Add Solid-State Braking to the T²X

—a worthwhile improvement

Tame your Tailtwister.

The T2X "Tailtwister" rotor by CDE is quite a piece of machinery. It's a heavy-duty rotor capable of turning an antenna system with 26 square feet of wind load, has a coast-down pre-brake action, and has a wedge brake system that keeps the rotor from slipping when not in use. As an added safety feature, power is not delivered to the directional controls until the wedge brake has been released.

In order to get the rotor to turn, you must press the brake release switch on the control unit, holding it down while pressing either the clockwise or counter-clockwise direction switch. Once the antenna reaches its destination, the direction switch must be released first, followed by the brake release switch after the antenna has coasted to a stop. If you should let go of the brake release switch before releasing the direction switch, or if both switches are released simultaneously, the wedge brake will immediately engage, bringing the system to an abrupt stop, placing undue strain on the rotor, mast, antenna system, and the tower itself.

Holding onto the brake release switch until the rotor has had plenty of time to coast to a stop is much easier in theory than in actual practice. What this means is that sooner or later you could have troubles, unless you can guarantee that the wedge brake won't be constantly slamming into the gears of a moving rotor.

One solution to this problem is to electronically delay the engagement of the wedge brake for a small period of time after the rotor has stopped turning. The circuit I designed to accomplish this consists of four ICs, one optoisolator, a small power supply, and a solid state relay. All the parts, with the exception of the power transformer, filter capacitor, and bridge rectifier, are mounted on a 5¼" x 2¾" perfboard using standard wire-wrapping techniques. The entire circuit fits in the rotor control unit, and no modifications to either the rotor or the outside appearance of the control unit are required.

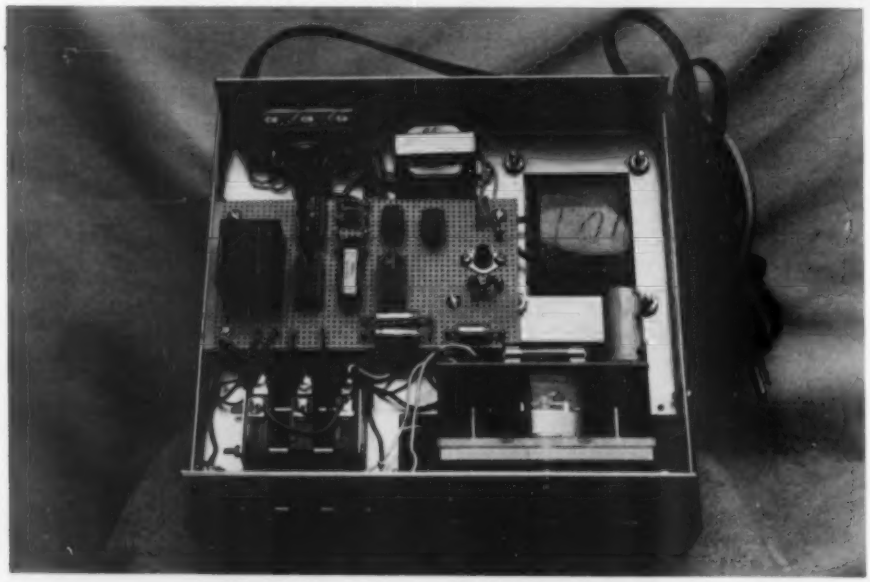

The power to the rotor's brake solenoid and directional circuitry is switched by a Grayhill Solid State Relay, which takes the place of the brake release switch in the original schematic—see Figs. 1(a) and 1(b). The SSR is ideal for this application for a number of reasons:

1. Its zero voltage turn-on and zero current turn-off characteristics plus its 3000-volt-per-microsecond transient protection allow it to switch a 110-V-ac inductive load at 4 Amps without the contact arcing found in a mechanical relay.
2. It will switch with 5 V dc of control voltage and draw less than 5 mA of current, making it compatible with TTL.
3. It physically separates

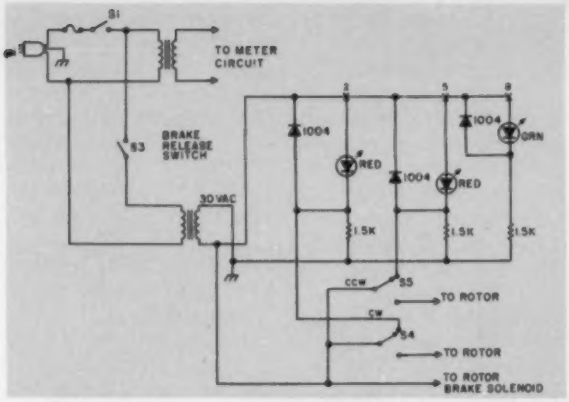

Fig. 1(a). Detail of control unit (original version). All resistors ¼ Watt. "X" denotes wiring connection to the control unit PC board.

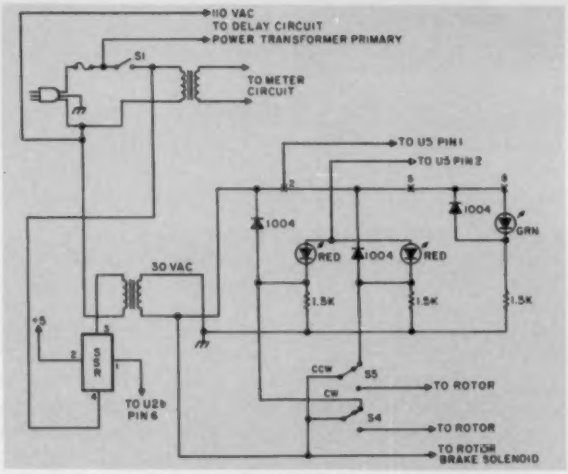

Fig. 1(b). Detail of control unit (modified version). All resistors ¼ Watt. "X" denotes wiring connection to the control unit PC board.

the digital control circuitry from the load by means of optoisolation, protecting the logic from any spikes that might be generated by the brake solenoid.

4. Its small size (1 cubic inch) enables it to be mounted directly on the perfboard, producing a very compact modification in the rotor control unit.

The rest of the circuitry on the perfboard (Fig. 2) determines the amount of time the SSR will remain energized. When the brake release switch (S_3) on the front panel is closed, the reset (pin 4) on the NE555 timer goes low, as does pin 6 on the 7409, turning on the SSR, releasing the wedge brake, and applying power to the rotor's directional controls. When the switch is released, the 74121 (which is triggered on the negative-going edge of its input pulse) applies a one-shot to the NE555, which in turn goes high at its output. This keeps pin 6 of the 7409 low, allowing the SSR to remain energized for approximately five more seconds. The five-second delay is determined by the RC combination of the 3.3-megohm resistor and the 1-uF capacitor on the NE555 and can be lengthened or shortened by increasing or decreasing the values of these components.

The input to the digitial circuitry is physically separated from the rotor's direction control voltage by an optoisolator (U_5) whose diode is wired in series with the LED directional indicators on the control unit—see Fig. 1(b). By the way, the optoisolator drops the total current in each directional LED by only 1 mA and therefore does not affect the original brightness of the indicators. If either one of the rotor's directional controls is pressed while the wedge brake is released, current will flow through the diode of the optoisolator. This causes the output of the optoisolator to go low (Fig. 2), resetting the NE555 and keeping the SSR energized.

Releasing the directional switch triggers the 74121 which pulses the NE555 and holds the SSR on for another five seconds. As a result, it is no longer necessary to hold down the brake release switch once the circuit has been energized. The wedge brake will not engage unless all three front panel switches have remained open for five seconds. Closing any one of the switches during the five-second delay resets the timer and repeats the cycle upon release of the switch.

In building this circuit, I used a 1k resistor network in place of mounting separate pull-up resistors, but there is room to mount the ¼-Watt resistors separately on the perfboard if you don't have a network handy. It should be noted also that I have connected the primary of the digital logic power supply transformer—Fig. 1(b)—before the rotor control unit "Off/On Switch" (S_1) so that power is supplied to the ICs continuously. Although you might prefer to make the connection after the switch, this will tend to energize the brake solenoid as soon as power is applied to the box. Powering the ICs constantly (the digital logic draws considerably less than 100 mA) not only prevents this,

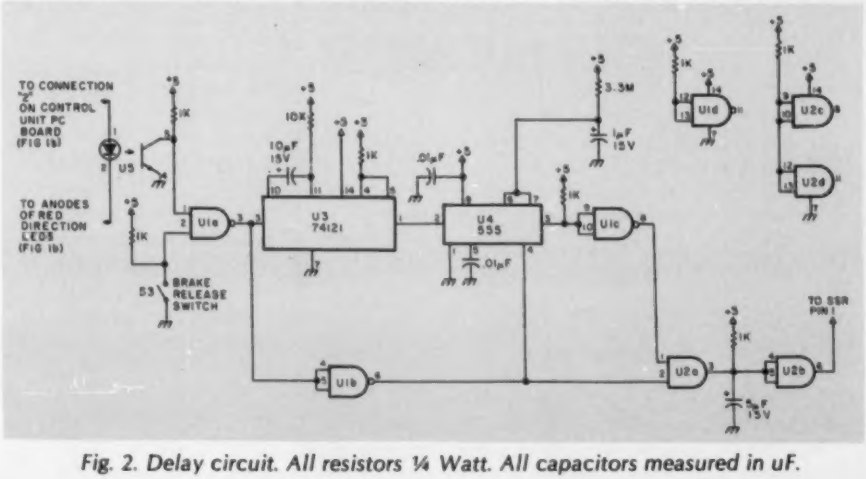

Fig. 2. Delay circuit. All resistors ¼ Watt. All capacitors measured in uF.

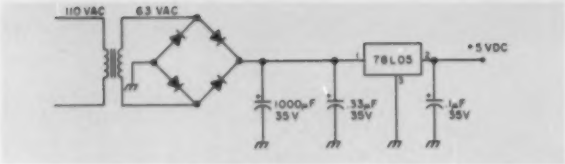

Fig. 3. Power supply.

but also is better for the ICs in the long run since they are not subjected to surges that accompany the application of voltage to the unit.

When connecting the wire-wrap wire to the SSR "control" pins, use the wire-wrap tool to make the connection, but make sure you solder the wire to the pins. Normally, solder is not necessary with the wire-wrapping technique, but the pins on the relay are round as opposed to the square wire-wrap pins, so solder should be used to ensure a solid connection.

Since all of the circuitry, with the exception of the power transformer, bridge rectifier, and 1000-uF filter capacitor (Fig. 3), is built on the perfboard, the digital logic can be checked for any wiring errors before connecting it to, or mounting it in, the rotor control unit. The 78L05 voltage regulator will handle up to 35 volts on its input (although it runs much cooler with the 6.3-volt supply used in this project) so you can temporarily power the perfboard with the output of a standard 12-V-dc supply. Attach a logic probe or voltmeter to pin 6 of the 7409 (since the 7409 has an open collector output, pin 6 must be connected to pin 1 of the SSR and pin 2 on the SSR must be connected to +5 V dc in order to get the proper readings). You should get a high-level logic state on the probe or a little under 5 volts on the voltmeter. Grounding pin 1 or pin 2 on the 7400 should change the reading to a low-level logic state (under 1 volt on the voltmeter). When you remove the ground, the reading should stay low for about 5½ seconds before returning to its original state.

If the circuit checks out correctly, disconnect the leads on the brake release switch (S_3) and solder them to the "load" pins on the SSR. Now you can mount the board on the bottom side of the control unit's chassis and hook up the power supply as shown in the schematics in Figs. 1(b) and 3. Connect a lead from one contact on the brake release switch to pin 2 of the 7400 and a lead from the other contact to ground. Unsolder the leads from connection points 2 and 5 on the control unit's printed circuit board (the board is numbered) and connect them both to pin 2 (the cathode) on the optoisolator (U_5). Connect a lead from pin 1 on the optoisolator (U_5) to connection point 2 on the printed circuit board. Connection point 5 is not used. This completes the modification of the rotor control unit.

Although I made this modification on the Tailtwister rotor, the schematic for the control unit is very similar to the schematic of the Ham II and Ham III rotors. I have not modified these rotors, but this circuit should work with them and is worth checking into. The only real difference between the Ham II/Ham III schematics and the Tailtwister schematic is that the Tailtwister has the three front panel LEDs (two red ones for direction indication and one green one for an indication that the wedge brake has been released). These could be added quite simply if desired—see Figs. 1(a) and 1(b)—using three 1.5k ¼-Watt resistors and three HEP1004 (1N34A-type) diodes. Although the direction indicators are not really necessary, the brake release LED does indicate the status of the wedge brake and I would recommend that you install it if you plan to use the brake delay circuit. It should be a simple matter to mount the extra components on the perfboard.

In all, the addition of an electronic brake delay circuit makes a good rotor better and may save you from the headache of rotor troubles at a later date. ■

Parts List

ICs

1 SN7400 (U_1)
1 SN7409 (U_2)
1 SN74121 (U_3)
1 NE555 (U_4)
1 IL 1 or equiv. optoisolator (U_5)
1 uA78L05 5-volt voltage regulator

Resistors

7 1k, ¼-Watt, 10%
1 10k, ¼-Watt, 10%
1 3.3 megohm, ¼-Watt, 10%

Capacitors

1 1000 uF, 35 volts
1 10 uF, 15 volts
1 5 uF, 15 volts
1 1 uF, 15 volts
1 .33 uF, 35 volts
1 .1 uF, 35 volts
2 .01-uF disc ceramic

Miscellaneous

1 Power transformer, 6.3 V at 300 mA (Radio Shack 273-1384)
1 Bridge rectifier (Radio Shack 276-1151 or equiv.)
1 SSR Grayhill Inc., 561 Hillgrove Ave. La Grange IL 60525, Part no. 70S2-04-B-04-F ($21.00)

Sockets

2 8-pin wire-wrap sockets
3 14-pin wire-wrap sockets
1 Transistor socket for voltage regulator (Radio Shack 276-548)

MEMPHIS, TENNESSEE

NO MONKEY BUSINESS!

(A) Complete Service Facilities
(B) Good Deals on most Brands
(C) Shipping within 24 Hours
(D) All inquiries handled by Active Hams with over 20 years experience in ham radio

CALL TOLL FREE
1-800-238-6168

IN TENNESSEE, CALL 901-452-4276
MONDAY – SATURDAY 8:30-5:30
FOR YOUR SPECIAL.

Write: 3202 Summer Ave., Memphis, Tennessee 38112

Reader Service—see page 211

LX303

ALL THE MOST WANTED FEATURES AT A MOST WANTED PRICE...

BIG ½" HIGH LCD DISPLAY
USE INDOORS OR OUT
200 HOUR 9V BATTERY LIFE
AUTO ZERO, POLARITY, OVERRANGE INDICATION
100 mV DC F.S. SENSITIVITY
19 RANGES AND FUNCTIONS

Removable cover stores test lead set furnished as part of the unit.

Available accessories include AC adapter, padded vinyl carrying case, 40KV DC probe, 10 Amp DC shunt.

X10 DCV probe (optional accessory) for protecting input up to 10KV.

$74.95

HICKOK

Here is the handfull of accuracy you've been waiting for. Handsomely encased. Compact. Efficient. Only 8 ounces. Hickok's exciting, new LX 303, 3½ digit Mini-Multimeter with high quality components, one year guarantee and rugged Cycolac* case offers features previously found only in expensive units. . .at a price under $75.00! So why wait any longer? The amazing LX 303 is here, NOW! Another American made test equipment breakthrough from Hickok, The Value Innovator. Order today!

See your local Hickok distributor or order below

SPECIFICATIONS:

DC VOLTS (5 RANGES): 0.1mV to 1000V; Accuracy ±0.5% rdg ±0.5% f.s.; Input imped: 10MΩ; Max. input 1kV except 500V on 200mV range.
AC VOLTS (40Hz to 5kHz): 0.1V to 600V; Accuracy: ±1.0% rdg ±0.5% f.s. (–2dB max. at 5kHz); Max. input: 600V.
RESISTANCE (6 LOW POWER RANGES): 0.1Ω to 20MΩ; Accuracy: ±0.5% rdg ±0.5% f.s. (±1.5% rdg on 20MΩ range); Input protected to 120V AC all ranges.
DC CURRENT (6 RANGES): .01mA to 100mA; Accuracy: ±1.0% rdg ±0.5% f.s.
DIMENSIONS AND WEIGHT: 5-7/8" x 3-3/8" x 1-3/4", 8 oz.; **POWER:** 9V battery (not included) or Hickok AC adapter; **READ RATE:** 3/sec.

ADVANCE ELECTRONICS
54 West 45th Street, New York, NY 10036 212-687-2224

TO ORDER CALL TOLL FREE
800-223-0474

PLEASE SEND ME

_____	Hickok LX303 Digital Multimeters	@ 74.95 ea.
_____	RC-3 AC Adapter, 115VAC (220VAC avail.)	@ 7.50 ea.
_____	CC-3 Deluxe Carrying Case	@ 7.50 ea.
_____	VP-10 X10 DCV Probe Adapter	@ 14.95 ea.
_____	CS-1 10A DC Current Shunt	@ 14.95 ea.
_____	VP-40 40 KV DC Probe	@ 35.00 ea.

Payment encl. ☐ Bill my: Master Charge ☐ VISA ☐
Account # _____ Exp. Date _____

Name _____
Address _____
City _____ State _____ Zip _____
Add $3.00 Postage and Handling, NY residents add sales tax. DEPT. 73

Compact Beams for 20 or 15

—build these when your quad bites the dust

Light, neat, rugged.

Jerrold A. Swank W8HXR
657 Willabar Drive
Washington Court House
OH 43160

My tower is just 11 feet from my neighbor's property line. The further I stay away from his television antenna, the better, lest I cause him TVI. I, therefore, have long wanted a 20 meter beam that, while a monobander, would not have a spread so long as to go outside my yard.

I do not like the regular 20 meter quad, as it is too big and floppy and somewhat unsightly, besides being easily damaged by the wind. I did not want to buy a triband beam, since I cannot operate 15 or 10 meters. I have only a three-band rig.

At one time, I had a 15 meter quad up for a couple

of years, and it worked fine, but since I cannot now work 15, I wanted to make a 20 meter beam out of my quad.

Everyone told me that this plan would not work, including one nationally-known antenna expert on quads. They said that bending back the ends of the elements would make it act like a transmission line.

I could have used loading coils, but most of all I did not want to have to buy an expensive beam. I had my quad put away and also had some parts of quad arms from another quad which I had once cut from 20 to 15 in my DX days. It was heavier, but a fellow ham had cut it down to 6½ feet to make a CB quad. Three of the arms had been broken when it fell while being taken down after he became a ham.

I decided to telescope one arm into a larger arm, and found that this would give me 11 feet per arm. I put epoxy on the smaller arms, or spreaders, and put them together. I was thus able to make four good arms and still have two usable short spreaders 6¼ feet long, by inserting aluminum tubing in one of the best broken arms. The 15 meter spreaders were still a full 8 feet long.

The reason I am telling you all of this is to make you think about ways of getting material for your beam. It would be possible to use bamboo or even wooden arms. If the arms are not hollow, you could tape the wire to the wooden arms. I actually tried this at first with the arms I am using, and then decided to see if the proximity of the aluminum spider would change the tuning of the beam elements. I found that it made no difference, so I removed the taped wires and fed the wires through the center of the fiberglass tubing.

I might mention a few booby traps I found as I went along. The first was that the stored tubing had been stopped up by insects and egg sacs. I used a 5/8 λ two meter mobile whip with the ball removed to poke out some of the debris. I then put my mouth to the small end, holding fingers over the hole which had been cut for wire in the old quad, and blew.

This worked with one arm, but not with two others. I tried poking wire through, but the wire was not stiff enough. I finally banged the large end on the concrete floor of my patio, and finally 8 cocoons fell out. I know now that I should have cleaned out the 15 meter quad arms before putting the two arms together. It would have been easier to handle them.

I then tried to push some #14 stranded wire through, but it kept catching on the end of the smaller inside arm. I took some #18 tinned wire and poked it through from the small end of the tubing, and it didn't buckle as it did when trying to force it the other way. I ran it through, twisted the end to the #14 Belden 8000, and pulled it back through.

I put a length of nylon tubing over the wire to keep it from being shorted to the bolts which held the clamps on the fiberglass arms.

I had cut the wire by formula to 16½ feet for the 14,200 MHz. I thus had 5½ feet left after reaching the end of the 11-foot arm. This I had to bend back. I put one of the short arms into the spider after placing the other 11-foot arm in the clamps. This I used in the upper arm of the spider. The lower arm of the spider was not used.

I could have left the upper arm unused and put the 6½-foot arm in the downward position. This I

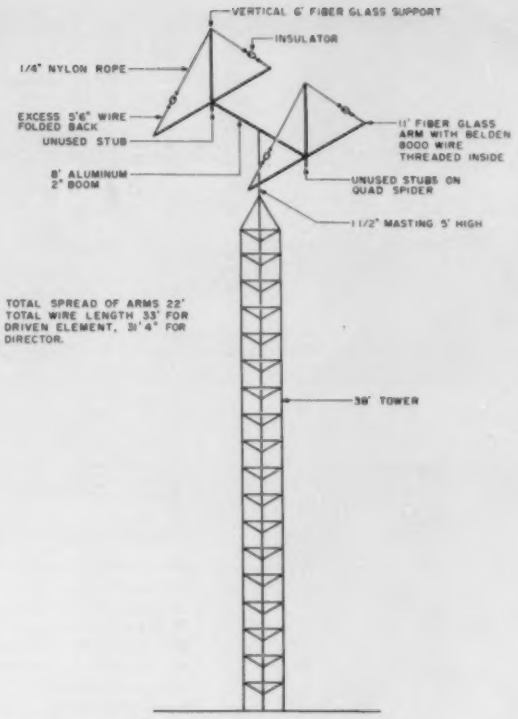
VERTICAL 6' FIBER GLASS SUPPORT
INSULATOR
1/4" NYLON ROPE
EXCESS 5'6" WIRE FOLDED BACK
UNUSED STUB
8' ALUMINUM 2" BOOM
11' FIBER GLASS ARM WITH BELDEN 8000 WIRE THREADED INSIDE
UNUSED STUBS ON QUAD SPIDER
1 1/2" MASTING 5' HIGH
TOTAL SPREAD OF ARMS 22'
TOTAL WIRE LENGTH 33' FOR DRIVEN ELEMENT, 31'4" FOR DIRECTOR.
38' TOWER

Fig. 1. Small light 20 meter beam.

decided against for two reasons. It would have brought the 5½ feet of excess wire back toward the metal tower, and by using the upward position, it furnished a support for the ends of the 11-foot arms. They did not sag, but I felt that they would be subject to more wind vibration if turned down.

I pounded a 3-foot length of 1½-inch pipe into the ground and placed the 8-foot boom with the attached spiders and center T-fixture in the pipe. This gave me a position for attaching the arms and stringing the ¼-inch nylon rope supports. The patio was too short, and the egg crate roof was so low that I could never have gotten the completed beam out. Even in the yard I was short of space, but I managed, even with shrubs and trees.

I drilled a ¼-inch hole in the tops of the vertical arms and threaded ¼-inch nylon rope through. I pulled enough through to reach the ends of the wire, and then tied a knot each side of the vertical arms to keep the rope from slipping. I used a 6-inch length of 7/8-inch PVC pipe with holes drilled in the ends for insulators. I probably did not need the insulators with about 7 feet of nylon rope and a fiberglass support, but habit made me use them. I would probably not use them again, so I suggest you don't bother.

I fastened a Kirk balun to the lower quad spider arm, and it made a fine installation. However, after spending several hours trying to figure out why the swr was about 10:1, I opened up the balun and found that one of the wires, after 20 years of use, had finally broken. I just put it up without a balun. I think a balun might have helped in some ways, but it seems to work well, anyway. I had used a hose clamp to attach the balun to the arm, and it was a neat job. If you use a balun, try this.

I used 31 feet, 4 inches for the director, which is 95%

FOR BEST PRICE AND FAST DELIVERY

CALL

1-800-325-3636

TOLL FREE

HAM RADIO CENTER

8340-42 Olive Blvd. P.O. Box 28271 St. Louis, MO 63132

✓H2

Radio Shack DEALER

MICRO MANAGEMENT SYSTEMS

Up To 15% Discount on TRS-80's

MICRO-COMPUTER SPECIALIST

LARRY OWENS

COMPUTER CENTER

MINI MALL—DOWNTOWN SHOPPING CENTER

CAIRO, GEORGIA 31728

912-377-7120

✓M95

TRS-80 OWNERS

Send-Receive RTTY & CW

- Auto. send & receive: RTTY & CW.
- Complete hardware & software.
- Connects to TRS-80 User Port & key/headphone jacks.
- 10 message memories - 255 char. ea.
- Keyboard buffer-allows typing ahead.
- Uses built-in PLL or external TU.
- Morse trainer-random 5 letter words.
- Includes hardware, cassette & manual.
- Requires Level II Basic & 16K RAM.

$99. kit

$129. wired

- PET version available, 69.95 kit / 99.95 wired

Write or call for detailed brochure

MACROTRONICS, inc.

FORMERLY MICROTRONICS ✓M48

P.O. Box 747 (S) Keyes, CA 95328 (209) 634-8888 / 667-2888

MasterCard VISA

California residents add 6% tax

★★★★★★★★★★★★★★★★★★★★

Bearcat® 250

Only $269.00 plus $5.00 U.P.S. shipping.

Quantity discounts available!

Order toll free (800) 521-4414

or (313) 994-4444. Circle C5 on reader's service card for a free catalog or write us at Box 1002, Ann Arbor, Michigan 48106

COMMUNICATIONS ELECTRONICS™ ✓C5

★★★★★★★★★★★★★★★★★★★★

---

electronic calculators

LIST	HAM NET	TEXAS INSTRUMENTS ELECTRONIC CALCULATORS
$299.95	$269.95	T.I.-59, 960 STEP PROGRAMMABLE SCIENTIFIC
124.95	112.45	T.I.-58, 480 STEP PROGRAMMABLE SCIENTIFIC
99.95	83.95	T.I.-57, 150 STEP PROGRAMMABLE SCIENTIFIC
49.95	44.95	T.I.-56, 32 STEP PROGRAMMABLE SCIENTIFIC
99.95	83.95	T.I. PROGRAMMER, CONVERTS DECIMAL,OCTAL,HEX
99.95	83.95	T.I. MBA, SUPER PROGRAMMED FINANCIAL
LIST		**HEWLETT-PACKARD ELECTRONIC CALCULATORS**
$750.00	$675.00	H.P.-67, 224 STEP PROG SCIENTIFIC PRINT/VISUAL
450.00	405.00	H.P.-67, 224 STEP PROG SCIENTIFIC
275.00	247.50	H.P.-19C, 98 STEP PROG SCIENTIFIC PRINT/VISUAL
175.00	157.50	H.P.-29C, 98 STEP PROG SCIENTIFIC
175.00	157.50	H.P.-10 BASIC HAND HELD PRINTER/VISUAL
325.00	292.50	H.P.-91, PREPROGRAMMED SCIENTIFIC PRINT/VISUAL
100.00	90.00	H.P.-33E, 49 STEP PROG SCIENTIFIC
80.00	72.00	H.P.-32E, PREPROGRAMMED SCIENTIFIC WITH STAT
60.00	54.00	H.P.-31E, PREPROGRAMMED SCIENTIFIC
495.00	445.50	H.P.-92, PREPROGRAMMED FINANCIAL PRINT/VISUAL
120.00	108.00	H.P.-38E STEP PROGRAMMABLE SUPER FINANCIAL
75.00	67.50	H.P.-37E, PREPROGRAMMED FINANCIAL

WE STOCK ALL HEWLETT-PACKARD CALCULATOR SOFWARE AND ACCESSORIES

SEND ME THE CALCULATOR(S) INDICATED BELOW. COMPLETE WITH INCLUDED ACCESSORIES, INSTRUCTIONS, AND MANUFACTURERS WARRANTY. I UNDERSTAND THAT IF I AM NOT COMPLETELY SATISFIED, I MAY RETURN IT WITHIN 10 DAYS FOR A COMPLETE REFUND (LESS SHIPPING).

MODEL(S) _____ QUANTITY _____ AMOUNT ENCLOSED $_____

WE HONOR _____ VISA _____ MASTERCHARGE _____ MONEY ORDERS _____ COD

ADD $2.00 FOR POSTAGE AND HANDLING. PLEASE ALLOW 10 DAYS FROM DATE OF RECEIPT OF ORDER FOR DELIVERY. TEXAS RESIDENTS ADD 5% SALES TAX.

CARD NUMBER _____ EXPIRATION DATE _____

FULL NAME _____ CALL _____

STREET _____ CITY _____ STATE _____ ZIP _____

MORE LITERATURE MODEL(S) _____

**********DEALER INQUIRIES INVITED**********

Hartwells Office World, Inc. ✓H26

MAIL TO: 6810 LARKWOOD
HOUSTON, TEX 77074
ATTN: STEVE, WA5OEN
PHONE: A.C. (713) 777-2673

PASS FCC EXAMS

The Original FCC Tests-Answers Exam manual that prepares you at home for FCC First & Second class Radiotelephone licenses. You get the complete set of 15 newly revised multiple-choice examinations - covering all areas tested on the actual FCC exam. Also included—helpful study tips, short cuts, and "Self-Study Ability Test." These updated FCC Tests-Answers take the mystery out of preparing for current FCC exams. Practical proven Material. $9.95 postpaid. Unconditional Moneyback Guarantee.

COMMAND PRODUCTIONS

RADIO ENGINEERING DIVISION ✓C106

P.O. BOX 26348-F SAN FRANCISCO, CA 94126

Please rush me Tests-Answers for FCC First and Second Class Commercial License. My $9.95 is enclosed.

Name _____

Address _____

City _____ State ___ Zip _____

✓ Reader Service—see page 211

of the 33-foot length of the driven element. I used a director instead of a reflector because it requires less boom length for the same gain and needed less extra wire pulled back toward the support. There was about 4 feet, 8 inches to pull back on each end.

I checked the swr on the ground, and it was 2½:1 from about 14.200 MHz to 14.350 MHz, except that it dropped to 2:1 in the area of 14.250 MHz. I figured that this would improve when it was up in the air, and it did. At the height of 43 feet, it dropped to 1.5:1 at 14.250 MHz and 2:1 at 14.350 and 14.200 MHz.

I have no rotator yet, so I

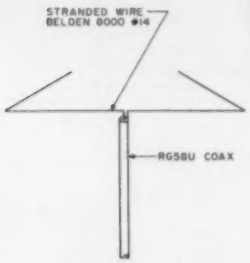

Fig. 2. Schematic of one element.

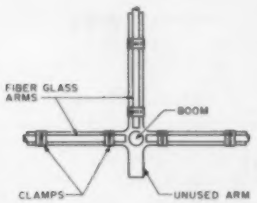

Fig. 3. Closeup of spider.

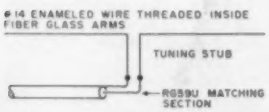

Fig. 4. Schematic of 15 meter driven element.

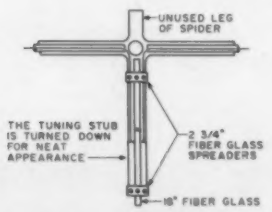

Fig. 5. Closeup of spider.

wanted to face the beam SW. It needed to be attached to a mast to raise it about 5 feet above the 38-foot tower. I had 8 feet of 1½-inch heavy wall aluminum tubing, and I inserted a similar length of 1¼-inch steel tubing inside to make a stiff mast. I drilled a hole and inserted a metal screw to hold the tubing together.

I had planned that we drill the mast for the T-fixture when it was up in the air, but my friend, Bill Burns WA8IEJ, who was going to raise it for me, wanted to drill it on the ground. I think he regretted it when he carried it to the tower. I had told him the beam weight was about 12 pounds, I thought. I had easily carried it on the ground.

While he was carrying it up in one arm and climbing with the other, he stopped to rest a couple of times, and he said it was more like 25 pounds with the attached masting. I recommend that you wait until it is on the tower and drill it before lifting the mast up to the desired height. I let it stick out 5 feet above the tower, which gives me enough inside the tower to attach a rotator.

I later wished I had done one more thing. I should have slipped the wire through a short piece of Teflon™ or nylon tubing as it comes out of the end of the fiberglass arm. This would help prevent the chafing of the wire by the sharp edge of the tubing and might keep the wire from breaking. It probably will last at least a couple of years, though. There is not much pull on the wire, since I did not draw it up very tight, so perhaps it will last longer.

It makes a lot neater arrangement than a 20 meter quad, and up in the air it looks nice.

I used a quarter wavelength of RG-59/U as a matching section from the driven element to the RG-8/U coax lead-in. I guessed that the beam impedance would be about 20 Ohms, and this would raise it to 40 Ohms. This would give an swr of 1.25:1, so the 1.5:1 final measurement was not far off.

When I got a chance to test it, I first called CQ and a California station came back and said that I had a "really strong signal" in his location. Next, I went in a pileup and got a reply, after only two calls, from P29JS in Papua, New Guinea. He said I was 5 x 9. It was a new country for me. The band was going out, so I went to bed.

The next night I tried to talk to a friend, Dale WD8VTD in Jamestown, Ohio, about 19 miles away, but he was off the side of my beam and we were really weak. While I was listening for him, Hans SM6CVX called me and wanted to know my Ohio county. When I told him Fayette, he wanted a QSL card. He gave me 5 x 7 and he was 5 x 8 here. I guess that my front-to-back is probably about 12-15 dB, so it seems I can work Europe off the back OK.

I usually work 40 meters from about 0600 to 0900 GMT, so I don't get on 20 until late. Thus I work mostly Pacific stations.

Last night I called Harry VK3XI and he came back on the first call. He said the band was going out and my beam must be pretty good, as he would not otherwise have been able to work me. He was 5 x 7 here.

I am running just about 800 Watts PEP, so I am very pleased with the results. I think I could have done well with just a 15 meter quad alone and a 1½-inch boom, but I used what I had. My 15 meter quad boom was only 1½ inches x 5 feet long, so I wanted a longer boom. There is no reason why you can't make your own beam from scratch with bamboo or even 1 x 2 wood and a plywood spider. The fact that there is a support for the arms, and the shortened length, bring up many possibilities for a light, cheap beam or even a dipole.

The director is not connected to the boom. The boom is 8 feet long and 2 inches in diameter—a very husky beam.

After seeing my 20 meter compact beam, Kenny Long WB8NGX wanted a 15 meter like it, and I had four arms left, so I decided to build one for him. I used lightweight spiders and a boom from a Kirk 15 meter quad, and of course, I didn't need such a long wire. I only used about 22 feet of wire for a 15 meter beam, so I decided to thread the wire just to the ends of the arms and bend them back an inch, both to hold them taut and to allow for corona prevention. I then had only about 1 foot, 5 inches left in the center.

I pulled this out along another short fiberglass arm, about 18 inches long. See Fig. 5. Then I fastened the wire to the binding posts on a short fiberglass strip. I bolted this to the arm and then added another strip for a spreader. This kept the wire from touching the metal of the spider arm. This was for the driven element.

For the director, I had only about 5 inches left on each side. I used a short piece of PVC tubing bolted to the arm to hold this piece. This wire was not broken, nor was it grounded to the boom. The boom is 6 feet long.

The beam is a very light, neat, and rugged affair. I guessed that it weighed about 7 pounds. I carried it over to Kenny Long's house on the top of a car, not even tied down. We held it down by hand, sticking our arms out the windows. ■

SPECTRONICS, INC.

1009 Garfield St., Oak Park, Illinois · 60304

(312) 848-6777

DIPOLES, ROTORS, ACCESSORIES

At Warehouse-To-You Savings

KLM

KLM 144-148-11 2 meter beam..... $47.95 c
KLM 144-148-14 2 meter beam..... 65.95 d
KLM 144-148-16 2 meter beam..... 72.95 d
KLM 219-226-7 220 MHz beam..... 28.95 b
KLM 219-226-9 220 MHz beam..... 29.95 b
KLM 219-226-11 220 MHz beam..... 32.95 c
KLM 219-226-14 220 MHz beam..... 49.95 d
KLM 420-470-6 UHF beam ..... 19.95 b
KLM 420-470-14-UHF beam ..... 31.95 c
STANDARD BALUNS for abv beams. 24.95 b

Larsen

LM150K 2M 3db, mob ant w/cable .. $31.95 c
NM0150 2M adapt ant TAD/TAE mt .. 27.10 b
NLA150K 3/8" hole, 3db mob w/cable 33.75 c
LMQ-K ¼ wave w/cable 136-512 MHz . 9.55 b
LM220K 220 MHz, 3db mob w/cable . 32.00 c
LM440K UHF 5db mob w/cable..... 30.00 c
MMLM150 2M Mag mt 3db gain ant.. 40.75 d
PQ ¼ wave port and w/PL259 conn... 5.25 a

MOR-GAIN

HALF-SIZE FULL PERFORMANCE
Multi-Band HF Communications Antennas

MOR-GAIN HD Dipoles.....
* One half the length of conventional half-wave dipoles
* Multi-band. Multi-frequency
* Maximum efficiency - no traps, loading coils, or stubs
* Fully assembled and pre-tuned - no measuring, no cutting
* All weather rated - 1 KW AM, 2.5 KW CW or PEP SSB
* Proven performance - more than 10,000 have been delivered
* Permit use of the full capabilities of today's 5-band rigs
* One feedline for operation on all bands

40-10HD/A 40/20/15/10 Mtrs (36) .... $63.25 c
80-40HD/A 80/40 Mtr bands (69) ..... 61.25 c
75/40HD/A 75/40 Mtr bands (66) ..... 56.75 c
75-10HD/A 75/40/20/15/10 Mtr (66).... 78.25 c
80-10HD/A 80/40/20/15/10 Mtr (69).... 80.25 c

B&W

MODEL 595
$21.50

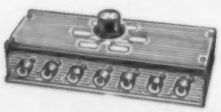

Our most popular switch. 6 position, grounds all except selected output circuit. Can be mounted on wall, on desk, or almost anywhere. Good to 150MHz. Wt. 2 lbs.

375 6 position, axial lead, gnd..... $19.75 a
376 5 pos, PROTAX, gnd pos ..... 19.75 a
550A 5 pos,Radial, no gnding ..... 17.50 a
550A2 2 pos, Radial, economy sw ... 14.95 a
590 5 pos, axial, panel mtg..... 18.50 a
590G same as above w/gnd unused . 18.50 a
592 2 pos axial, panel mtg ..... 17.25 a

"SLINKY" Dipole Antenna

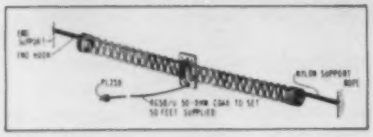

A lot of performance in a little space, on 80/75, 40 and 20 meters. Only one setting needed for full band coverage—low VSWR throughout. Can be set at any length from 24-40' an 80/75 meters, 12-35' on 40, 6-18' on 20. Band change takes less than a minute. Handles 1000 watts CW, 2000 PEP on SSB. With 50' RG-58/U coax $43.95

NEW! B&W PORTABLE WHIP ANTENNA

Simple, dependable whip is designed especially for apartment dwellers and renters who cannot install a permanent antenna. Tunes the 2, 6, 10, 15, 20 and 40-meter Amateur bands. Offers VSWR of 1.1:1 when properly adjusted to operating frequency. Ideal for use as a portable emergency antenna, too. Amounts to almost any horizontal support with a simple clamp bracket.

Weighs less than 2 pounds including five base-loading coils (not used for 6-2 meters), coax line and counterpoise. Whip is 22½" long disassembled, extends to 57". Mount is 14" long. Power rating: 360 watts SSB or CW.

Quick Mounting
$32.50
Model 370-10 $32.50

SOUTH RIVER

HDT TRIPODS

- **Galvanized steel.**
- **Lag Screws incl.**
- **UPS Shippable.**

HDT-10KD 10' tripod, hvy duty ..... $49.95 g
HDT-5 5' tripod, galvanized..... 24.95 f
HDT-3 3' tripod, galvanized ..... 15.95 c
ST-SN Stainless chimney mt (pair) .. 17.50 c
PFM71 Hvy duty self sup roof mt ..... 8.95 c
2791 Guy wire wood screw hooks (3).. 1.54 a
2751 "thread x 7/8" turnbuckle (3) .... 3.46 b
2871 50' #8 alum ground wire..... 4.35 b
2876 100' #8 alum ground wire..... 8.19 c
GND-4CP 4' copper plated grnd rod... 3.39 c
S-1625P 2½ ft. x 1¼" mast ..... 3.95 c
A-125-5P 5 ft. x 1¼" alum mast..... 11.50 c

WHEN ORDERING FROM SPECTRONICS, REMEMBER:

ALL PRICES are subject to change without notice. When any item carries a special sale price lower than shown in the catalog, you will automatically receive a refund if you overpaid with your order.

C.O.D. ORDERS require payment to be made by cash, certified check, or money order only. We will gladly quote you the exact amount that the delivery-man will ask for.

SHIPPING CHARGES must be added to your order. Please refer to the chart on the order blank page and add to your total.

ALL ORDERS sent F.O.B. Oak Park, Illinois.

Famous "W2AU" Balun

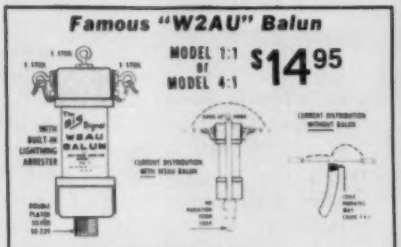

1. **HANDLES FULL 2 KW PEP AND THEN SOME.** Broad Banded 3 to 40 Mc.
2. **HELPS TVI PROBLEMS** By Reducing Coax Line Radiation
3. **NOW ALL STAINLESS STEEL HARDWARE.** SO239 Double Silver Plated
4. **IMPROVES F/B RATIO** By Reducing Coax Line Pick-Up
5. **REPLACES CENTER INSULATOR.** Withstands Antenna Pull of Over 600 Lbs.
6. **BUILT IN LIGHTNING ARRESTER.** Helps Protect Balun — Could Also Save Your Valuable Gear
7. **BUILT-IN HANG-UP HOOK.** Ideal for Inverted Vees, Multi-Band Antennas, Dipoles, Beam and Quads

NOW BEING USED BY ALL BRANCHES OF THE U.S. ARMED FORCES, FAA, RCA, CIA, CANADIAN DEFENSE DEPT. PLUS THOUSANDS OF HAMS THE WORLD OVER

Comes in 2 models. 1:1 matches 50 or 75 ohm unbalanced (coax line) to 50 or 75 ohm balanced load. 4:1 model matches 50 or 75 ohm unbalanced (coax line) to 200 or 300 ohm balanced load.

Model 1:1.....$14.95 Model 4:1.....$14.95

DIPOLE HEADQUARTERS

CABLE

8U FOAM, hi dens braid 50 ft..... $11.95 c
8U FOAM, hi dens braid 100 ft..... 22.00 e
RG58A/U stranded center 50 ft ..... 6.95 c
RG58A/U stranded center 100 ft ..... 9.95 d
RG58 3 ft w/PL259 each end..... 3.35 b
RG58 5 ft w/PL259 each end..... 4.39 b
RG58 50 ft w/PL259 each end..... 9.95 c

COPPER WIRE

#14 stranded, 100 ft spool..... 5.95 c
#14 solidcopper enameled 100'..... 5.95 c

INSULATORS

Egg Ins, porcelain per pair ..... .99 a
DOG BONE, porcelain set of 3 ..... 1.25 a
HY GAIN #155 center insulator..... 5.95 b
HY GAIN Cycolac end ins per pair.... 3.95 b
MOSLEY dipole center insulator ..... 5.75 a

CONNECTORS

PL259 UHF male, 2 per pkg ..... 1.59 a
SO239 UHF female chassis mt ..... .69 a
UG175 Adapts RG58 to PL259, pkg 2.... .59 a
UG176 Adapts RG59 to PL259, pkg 2.... .59 a
PL258 UHF double female ..... .99 a
DM-SP UHF double male ..... 1.69 a
M359 90 deg UHF elbow conn..... 2.10 a
UG88U BNC male for RG58 ..... 1.49 a
1094 BNC female ..... 1.10 a
M358 UHF "T" connector..... 2.95 a
UG255 UHF female to BNC male ..... 3.49 a
UG273 BNC female to UHF male ..... 2.45 a

ESTIMATED WEIGHT CODING

After the price of each item you will find a letter, i.e., 19.95 a. To make it easier to figure shipping costs, these letters indicate the approximate weight of the item as follows:

a. Less than 1 lb.
b. 1-3 lbs.
c. 4-6 lbs.
d. 7-10 lbs.
e. 10-20 lbs.
f. 20-30 lbs.
g. 30-40 lbs.
h. 40-50 lbs.

★ will be sent truck collect.

tune in ...at half price!

☐ Yes . . . Please send me 1 year of 73 Magazine at the half-price rate of $15.*

☐ Please send me 3 years at half price for $45.*

*Savings based on newsstand cost.

☐ Payment Enclosed (mail form in envelope)

☐ Bill Me

Mr./Ms. _____

Address _____

City _____

State _____ Zip _____

Canadian subscriptions add $2 per year. All other foreign subscriptions $26 one year only payable in U.S. funds. Please allow four to six weeks for delivery of first copy.

B97

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY MAIL

FIRST CLASS PERMIT NO. 17 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

73 magazine

Subscription Department ● Box 931

Farmingdale NY 11737

HF & VHF BEAMS and VERTICALS

At Warehouse-To-You Savings

SPECTRONICS, INC.

1009 Garfield St., Oak Park, Illinois · 60304

S81 (312) 848-6777

the antenna specialists

2 MTR DUCKIES

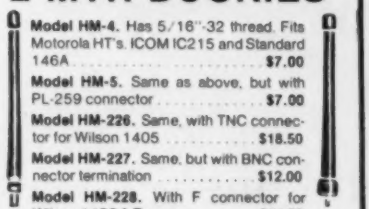

Model HM-4. Has 5/16"-32 thread. Fits Motorola HT's. ICOM IC215 and Standard 146A $7.00

Model HM-5. Same as above, but with PL-259 connector $7.00

Model HM-226. Same, with TNC connector for Wilson 1405 ..... $18.50

Model HM-227. Same, but with BNC connector termination $12.00

Model HM-228. With F connector for Wilson 1402 & Tempo $11.50

HM180 2mtr, 3db trunk lip ant..... $33.50 b
HM179 2mtr, 3db hole mount ant.... 29.00 b
HM20 2mtr, 3db for marine use..... 39.00 b
HM176 440MHz 5db trunk lip ant .... 33.00 b
HM175 440MHz 5db hole mount ant . 29.00 b
HM224 220MHz 4db trunk lip ant .... 33.50 b

NEW! ASP-694 ¼-Wave Magnetic Antenna

Low profile magnetic antenna with cable and connector. Tunable 108-512 MHz. Can be converted to gain antenna later. Wt.: 3 lbs.

Model ASP-694 ..... $21.00

cushcraft

AR2 2meter Ringo base ant..... $24.95 b
ARX2 2mtr Ringo Ranger base ant .. 39.95 c
AR220 220MHz Ringo base ant..... 24.95 b
ARX220 220MHz Ringo Ranger..... 39.95 c
AR450 UHF Ringo base ant ..... 24.95 b
ARX450 UHF Ringo Ranger bse ant . 39.95 c
AR6 6 meter Ringo base ant ..... 36.95 c
ARX2K Adapts 2M Ringo to Ranger . 16.95 b
A147-4 4 ele 2M FM beam ant ..... 24.95 b
A147-11 11 ele 2M FM beam..... 36.95 c
A147-20T 10 ele 2M vert/horz twist... 62.95 d
A144-7 7 ele 2M CW/SSB beam..... 26.95 c
A144-11 11 ele 2M CW/SSB beam.... 36.95 d
A144-10T 10 ele Twist OSCAR ant ... 42.95 c
A144-20T 20 ele Twist OSCAR ant ... 62.95 d
A220-7 7 ele 220MHz beam..... 26.95 c
A220-11 11 ele 220MHz beam ..... 34.95 c
A449-6 6 ele UHF FM beam ..... 24.95 c
A449-11 11 ele UHF beam..... 34.95 c
A432-11 11el 432MHz SSB/CW beam 34.95 c
AFM4D 144-148MHz Four Pole..... 69.95 c
AFM24D 220MHz Four Pole..... 64.95 c
AFM44D 435-450MHz Four Pole..... 64.95 c
ASQ-2 2M Squalo horiz ant ..... 19.95 b
LAC-1 Coax lightning arrester..... 4.95 a
LAC2- Coax lightning arrester..... 4.95 a
ATB34 ★ 4 ele 20-10mtr beam ..... 219.95 ★
ATV3 20-10mtr trap vertical ..... 49.95 e
ATV4 40-10mtr trap vertical ..... 69.95 e
ATV5 80-10mtr trap vertical ..... 89.95 e
A50-3 3 element 6 meter beam ..... 39.95 d
A50-5 5 element 6 meter beam ..... 59.95 e
A28-3 ★ 3 element 10 meter beam .. 69.95 ★
A432-20T 432MHz 20 ele twist..... 59.95 d

2M BASE ANT. PACKAGE

Here's what you get:

- Cushcraft AR2 Ringo South River.
- PFM71 Roof mount.
- A125-5P 5' alum mast.
- Lag bolts.
- 50' 8U foam coax.
- PL259 coax conn.

$59.95

Wt. 16 lbs.

FINCO

The most rugged 6 & 2 meter beams we've seen yet!!

A 2-10 10 ele, 2M beam ..... $44.95 d
A 2-5 5 ele, 2M beam, 9.5db gain..... 27.95 c
A 2-2 10 ele, 2M dual polarization.... 46.50 e
A62 6&2M antenna on one boom .... 74.95 e
A6-5 5 element 6M beam, 11db ..... 46.50 e
A6-3 3 ele 6M beam, 7db gain ..... 30.00 d
A 1¼ 220MHz 10 ele, 13.8db ..... 32.95 d

HUSTLER

$9.95 "BUCK-BUSTER" SF-2 ANTENNA

Fits all Hustler deluxe mobile mounts. 3/8"x24 base. 5/8" wave two meters, 3.4 db gain. SWR at resonance: adj. to 1.5:1 or better. Bandwidth: 6 MHz, 2:1 or better SWR. 100 watts max.

$79.95 NEW 4-BTV VERTICAL

One setting covers 10, 15, 20, 40M. Space restricted or unlimited, you get top signal reports, consistent contacts and complete coverage. Add 5th band with a 75M resonator. Use one feedline, any length. Requires no switching or matching devices. 15 lbs.

MO1 Mobile mast ..... $22.95 c
MO2 Mobile mast ..... 22.95 c
RM10 10 Meter resonator ..... 6.95 b
RM15 15 meter resonator ..... 7.95 b
RM20 20 Meter resonator ..... 8.95 b
RM40 40 Meter resonator ..... 14.95 b
RM75 75 Meter resonator ..... 16.95 b
RM80 80 Meter resonator ..... 17.95 b
RM10S 10M resonator 2KW PEP .... 11.95 b
RM15S 15M resonator 2KW PEP .... 12.95 b
RM20S 20M resonator 2KW PEP .... 13.95 b
RM40S 40M resonator 2KW PEP .... 16.95 b
RM75S 75M resonator 2KW PEP .... 31.95 b
RM80S 80M resonator 2KW PEP .... 31.95 b
CG144 5.2db 2mtr ant 3/8 x 24 stud ... 26.95 b
CGT144 Same but trunk lip mount... 42.95 c
SF2 3db 2mtr ant 3/8 x 24 stud ..... 9.95 b
SF220 3db 220MHz ant 3/8 x24 stud .. 11.95 b
4BTV 40-10mtr vertical ..... 79.95 e
G6-144 2mtr base ant 6db..... 79.95 d
BM1 Bumper mount 3/8 x 24 thread... 15.95 d
RSS2 Mobile resonator spring ..... 5.95 a
QD1 Quick disconnect 3/8 x 24..... 16.95 a

hy-gain

VERTICAL ANTENNAS

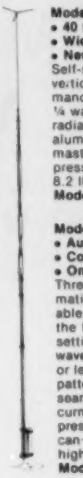

Model 14AVQ/WB
- 40 thru 10 meters
- Wide band performance
- New Hy-Q traps

Self-supporting, automatic band switching vertical antenna. Omni-directional performance. Favorable L/C ratio. High Q. True ¼ wave resonance on all bands. Low angle radiation pattern. Taper swagged seamless aluminum construction. 12' double-grip mast bracket. Full circumference compression clamps at tubing joints. Weight: 8.2 lbs.

Model 14AVQ/WB $57.00

Model 18AVT/WB
- Automatic band switching
- Completely Self-Supporting
- Omni-Directional Performance

Three beefed-up Hy-Q traps permit automatic switching. 5 band capability. Favorable L/C ratio. Top loading coil. Across the band performance with one furnished setting for each band (10 thru 40). True ¼ wave resonance on all bands. SWR of 2:1 or less at band edges. Low angle radiation pattern. Extra heavy duty tapered swaged seamless aluminum tubing with full circumference, corrosion resistant compression clamps at tubing joints. Antenna can be mounted without guide wires. 25' high. Weight: 10.7 lbs.

Model 18 AVT/WB $79.95

BN86 Ferrite balun for 80-10mtrs... $15.95 a
155 Center insulator for doublet..... 5.95 a
156 End insul. for doublet (pair) ..... 3.95 a
18HT ★ HyTower 80-10M vertical .. 239.95 ★
18V Economy 80 tru 10M vertical .... 24.95 c
12AVQ 20-10mtr trap vertical..... 39.95 c
14AVQ 40-10mtr trap vertical..... 57.00 d
18AVT/WB 80-10mtr trap vertical .... 79.95 d
2BDQ Trap doublet for 80 & 40mtr... 39.95 d
5BDQ Trap doublet for 80-10mtrs.... 69.95 e
TH3 MkIII ★ 3 ele 20-10 tribander .. 179.95 ★
TH6DXX ★ 6 ele 20-10M tribander.. 239.95 ★
TH3 Jr 3 ele tribander (750W PEP) .. 129.95 e
HY QUAD ★ 2 ele quad 20-10 mtrs . 189.95 ★
103BA 3 element 10Mtr beam ..... 54.95 e
153BA ★ 3 element 15mtr beam..... 79.95
204BA ★ 4 element 20mtr beam ... 179.95 ★
402BA ★ 2 element 40 mtr beam... 169.95 ★
64B ★ 4 element 6 meter beam 39.95
270 6db fiberglass 2M antenna..... 39.95 e
203 3 element 2 meter yagi..... 15.95 b
205 5 element 2 meter yagi..... 17.95 c
208 8 element 2 meter yagi..... 25.95 c
214 14 element 2 meter yagi..... 31.95 d

Mosley

TA33 ★ 3 el triband beam 2KW PEP . $189.95
TA33Jr ★ 3ele triband 1KW PEP ... 149.95 ★
TA36 ★ 6ele triband 2KW PEP .... 269.95 ★
CL33 ★ 3 ele Classic..... 209.95 ★
CL36 ★ 6 ele Classic..... 269.95 ★
TA40KR 40mtr adpt for TA33/36 ..... 92.95 e
MPK3 2KW conv kit for TA33Jr ..... 67.65 e

CDE

HAM IV Rotor with control box .... $149.95 f
T2X Tailtwister xtra hvy dty..... 219.95 f
CD45 Medium duty rotor..... 119.95 f
AR22XL Light duty rotor..... 59.95 e
Mast adaptor for Ham II/T2X..... 29.95 d
South Center meter kit ..... 3.00 a

"Weeping Willow" Vertical for 40

—go out on a limb and build one

A vote for the bends.

Art Pightling WA6OYS
240 Louisiana Place
Oxnard CA 93030

There are two things which I look for in a vertical antenna: simplicity (no traps or hats) and availability of parts. A quarter-wave vertical for forty meters fits both of these criteria, but it is often overlooked when antenna construction is contemplated.

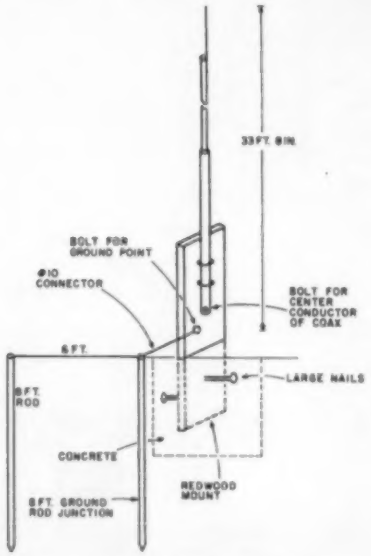

Fig. 1. Forty meter vertical.

There are also two schools of antenna construction: the oak (make it so rigid and strong that it just cannot be destroyed by wind, earthquakes, snow, ice, or whatever) and the willow (able to bend, flex, and take all of the above and spring back). Since the "oak" method never did work for me, this antenna is of the "willow" configuration. It is made of lengths of concentric tubing and ends in a whip.

To determine how much tubing we will need, we have to figure out how long a quarter wave is at forty meters. Using $\lambda/4(\text{feet}) = 246/f\ (\text{MHz})$ and then converting the fraction of a foot which remains to inches, we get $\lambda/4 = 33'10''$ for a center frequency of 7.265 MHz. Any center frequency can be chosen by placing that frequency in place of f in the formula.

Construction

Now let's get down to business. The aluminum tubing is available locally in most areas in concentric sizes from 2" to 3/8". I had a 3'×1-1/2"-o.d. piece of tubing on hand, so this was the logical place to start. Now, all we need is 30'10" more. Five 8' sections of tubing were used: 1-1/4", 1", 3/4", 1/2", and 3/8" o.d. After slotting the ends with a hacksaw and clamping the ends with hose clamps, I had 30' of tubing in 6' sections with approximately 2' of each inside the lower tube. An 18" whip was clamped to the top, and the already-on-hand 3'× 1-1/2" tube was attached to

CALL TOLL FREE

1-800-228-4097

Hy-Gain 3806

2-Meter Hand-Held Amateur Transceiver

SPECIALLY PRICED ONLY $119.95

- Low cost, 6-channel hand-held provides superb voice transmission over short to medium distances
- Sharply tuned on-frequency selectivity in the RF amplifier stages plus FET's in the 1st and 2nd mixers for virtual immunity to out-of-band signals intermodulation distortion and cross-modulation
- Separate microphone and speaker elements for enhanced audio
- Internally adjustable mic preamp—a Hy-Gain exclusive
- Specially gasketed case seals out water, dirt and corrosive salt air
- Watertight, high-impact ABS plastic case—ribbed for non-slip grip
- Top-mounted controls for instant access

Accessories:

Model No.	Description	Price
3807	Nicad Battery Pack	$31.95
1104	Touch Tone Pad	$44.95
1106	AC Battery Charger	$ 9.95
1107	Cigarette Lighter Adaptor Cord	$ 9.95
1108	Antenna Adaptor Cord	$ 9.95
1110	Carrying Case (Leather)	$17.85
1111	Carrying Case (Vinyl)	$ 9.95
269	Rubber Duck Antenna	$ 5.95
	Crystal Certificates	$ 3.95

PLEASE ENCLOSE $2.50 FOR SHIPPING AND HANDLING PER UNIT

CALL TOLL FREE

1-800-228-4097

for Quality Ham Radio Products at Discount Prices

YAESU	DENTRON	TAYLOR	E.T.O. ALPHA
KENWOOD	HY-GAIN	SWAN	VHF ENGINEERING
DRAKE	MOSLEY	TEMPO	BERK-TEK CABLE
ICOM	CUSHCRAFT	TEN-TEC	CONSOLIDATED TOWER
STANDARD	WILSON	MIDLAND	SAY
EDGECOM	HUSTLER	CDE	SHURE
KDK	LARSEN	AUTEK	TELEX
PANASONIC	BENCHER	MIRAGE	ROBOT SSTV
	ROBOT	AEA	BENCHER

Our Mail Order Hours (CST)

M-F 8 am to 12 Midnight
Saturday 8 am to 6 pm
Sunday 12 Noon to 8 am

Call and Talk to

Don	WBØYEZ	Ken	WDØEMR
Denny	WØQR	Eli	KAØCEJ
Bill	WBØYHJ	John	WBØMTS
Joe	WAØWRI	Blaine	WBØQLH
Jim	KAØCRK	Bob	WBØRQZ

BANKAMERICARD

✔CS8

Communications Center

443 N. 48th, Lincoln, Nebraska 68504 In Nebraska Call (402)466-8402

master charge

the bottom. Now we have either a very long trout rod or a slightly-oversize quarter-wave antenna for forty meters.

Ground is an important part of a quarter-wave antenna, so ground mounting was chosen. A piece of redwood 3′×4″×1/2″ was found and painted to match my fence. Holes were drilled in appropriate place for U-bolts to hold the vertical to the redwood, and a test fitting showed that the antenna could be securely fastened to the redwood. A couple of large nails were driven into the bottom part of the redwood mount to give the concrete more to grab on to. A 24″-deep hole was dug in an inconspicuous corner of my yard and filled with a 60-pound bag of concrete. The prepared hunk of redwood was then placed in the wet concrete and propped up so that it would be straight when the concrete set. A bolt was put into the bottom of the antenna so that the center conductor of the coax feed could be connected. Another bolt was placed in the redwood mount to serve as a junction point for the ground system. (This bolt must be insulated from the radiating element.)

The Ground System

Some of us have a good ground (swamp or salt marsh) and others don't (rock or sand). My worst-case ground was 120 #18 wire radials, each a little more than a quarter-wavelength long, splayed out sunburst-style around the base of the antenna. The ground system which I wound up with was three radials, six feet long, terminating at 8′ ground rods. These three radials were joined at the antenna base on another 8′ ground rod. I used #10 wire to interconnect the ground rods and the *short* run to the bolt which was previously placed for ground connection on the redwood mount. To be sure, there was a difference in vswr obtainable, but the simpler ground system was satisfactory for my area.

Adjustment

Connect one foot or less of 52-Ohm coax to the antenna, connecting the center conductor to the vertical radiator and the ground braid to the ground connection on the redwood. Connect the vswr meter and the transmitter. Take a reading at the low end of the band, one at the middle, and one at the top. This should be enough to give you an idea of whether to shorten or lengthen the element. If you have built the antenna as described, you will probably have to shorten it a bit. This is best at the top sections. Do your fine tweaking with the whip. You have to take the antenna down each time you want to adjust it, so, by all means, take notes to help you make as few adjustments as possible. When this was done, an swr of 1.2 to 1 was obtained at 7.265 MHz and the swr did not go above 1.6 to 1 in the forty meter band. This was quite acceptable to me. The swr on the top end of fifteen meters was around 2 to 1—not bad for a bonus band.

This antenna has performed well at this QTH and was used when I was net control for the infamous swap net. Using only an FT-101 "barefoot," I was quite well heard in all of southern California, Arizona, and northern California as well. The antenna is also good for DX on forty and fifteen meters because of its low angle of radiation.■

3 YEARS WARRANTY!
EXACT Replacements for
SYLVANIA
ECG Transistor-Diodes-ICs

ECG#		ECG#		ECG#		ECG#	
100	.94	153	5.95	220	1.72	280	.88
101	.99	154	5.75	221	1.90	290	.95
102	.99	165	6.95	222	1.99	291	1.99
102A	.99	171	1.37	223	2.75	292	2.25
103	1.05	172A	.72	224	5.95	293	1.00
103A	1.11	175	1.82	225	4.34	294	1.14
104	1.09	176	2.06	226	1.67	295	2.02
105	2.27	177	.49	228	1.39	297	1.13
106	.95	178	5.69	229	1.66	298	1.13
107	.79	180	5.86	230	3.60	299	2.02
108	.89	181	4.65	231	3.98	300	2.60
121	2.15	182	3.35	232	.76	302	2.60
123	.69	184	3.83	233	.74	305	2.60
123A	.79	194	1.37	234	.72	307	2.57
124	1.53	195	1.70	235	2.45	308	7.85
126	1.16	196A	1.48	236	5.75	308K	3.27
127	4.80	197A	1.48	237	5.07	310	7.85
128	1.37	198	1.59	238	7.95	311	2.13
129	1.56	199	1.59	239	3.02	312	1.13
130	1.95	190	1.85	241	1.71	313	1.00
131	1.58	191	2.07	242	1.90	314	7.85
132	1.01	193	.99	276	9.72	315	2.01
133	1.14	193	1.04	278	1.38	316	2.74
152	1.43	194	.82	279	5.85	317	24.20
153	1.85	195A	2.67	280	5.08	318	20.60
154	1.85	196	1.98	281	8.35	319	1.11
155	2.02	197	1.89	282	4.24	320	26.00
157	1.43	198	1.89	283	4.52	321	7.85
158	1.58	199	.59	284	7.35	322	1.80
159	.88	210	1.37	285	7.89	323	3.53
160	1.43	211	1.98	286	5.75	324	3.53
161	.96	218	3.08	287	.69	325	27.50
162	5.75	219	4.36	288	.74	326	.96

- R-U-S-H, All Orders Shipped Same Day Received
- FREE Freight on all prepaid orders
- EXCLUSIVE 3 YEAR CONDITIONAL WARRANTY!
- NO Min. Order-Quantity Discounts Available
- Exact ICs & Diodes In Stock
- Longer Hours Mon-Sat 9a-10p, Sun 1-7p
- Call or write today—to place your order (518)-465-3367

Communications & T.V. Unlimited
Dept 73, 17 Washington St., Rensselaer, N.Y. 12144
DISTRIBUTOR INQUIRIES INVITED
T.V.-C.B.-AMATEUR RADIO-STEREO-MONITORS-
ELECTRONIC PARTS ✓C105

AUXILIARY POWER
for Emergency or Portable Operation

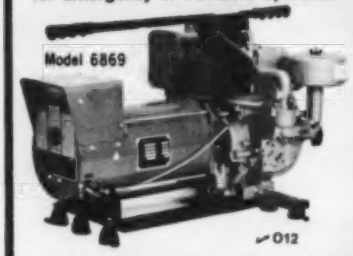

✓O12

Light wt. Alternator. Stand-by power for Ham Equipment, household needs during power outages or operation in remote areas. Operates lighting, refrigerators, heating systems or other appliances including freq. sensitive loads such as TV sets, induction motors and fluorescent lights. Solid-State voltage regulation. 3750W rating; 25% surge capacity. 120/240V at 31.3/15.6A. 8 HP/3600 RPM B&S engine. Alternator draws just enough engine output to meet load resulting in up to 25% fuel savings. Low interference. Advanced design. Drip-proof construction protects windings from rain and dirt & long life. One year warranty by manufacturer. 30"L x 18"W x 19"H. 128 lbs. Shipped via Truck **PREPAID** (No extra charges) **$659.95**

Electric Start	$110.00
Battery Charging	11.00
Spark Arrest Muffler	21.00

Models available with 1350 to 7000 watt ratings. Write for our quote and additional information.

Mastercharge or VISA accepted

OUTDOOR OUTFITTERS
705 Elm Ct. Waukesha, WI 53186
Ph. 1-414-542-7772 ● Ken, N9KS - Mgr.

new COAX SWITCHES
from Barker & Williamson

Model 593

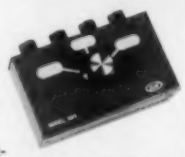

- ***Single Pole*** 3 Position with grounding of all unused positions
- ***Crosstalk*** (measured at 30 MHz) is -45db between adjacent outlets and 60 db between alternate outlets

Model 594

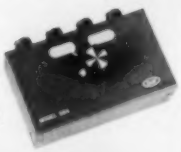

- ***2 Pole 2 Position***
- ***Crosstalk*** 45db (measured at 30 MHz)

Specifications for both switches

- ***Power*** 1 KW-2 KW PEP
- ***Impedence*** 50-75 ohms
- ***VSWR*** 1.2:1 up to 150 MHz
- ***Dimensions*** 1¾" high, 5" wide, 3" deep
- ***Weight*** 1 lb.
- ***Mount*** Wall or desk

✓B23 Available at your B&W dealer

B&W
Barker & Williamson, Inc.
10 Canal St. Bristol, Pa. 19007
Telephone: (215) 788-5581

✓ Reader Service—see page 211

IT'S ABOUT TIME...

...Someone offered a 2 Meter FM Transceiver with all of the features you want at a price you can afford.

- 25 Watts
- Fully Synthesized
- 144-148 MHz
- 5 KHz Steps
- Provisions for non-standard splits
- Full 1 year warranty
- 2-5/8(H) x 6-5/8(W) x 10-3/4(D)

1979 FM-28
only $295.00

NOW AVAILABLE WITH $$$$SSSCAN

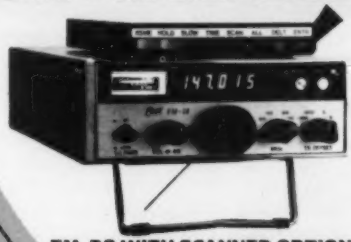

FM-28 WITH SCANNER OPTION
$395.00

- Scan capability 144-147.995 MHz
- Scan entire band or memory
- Up to 800 channel memory
- Internal battery holds memory when power is turned off.
- Scanner option can be added to any FM-28

With or without Scanner option—The Clegg FM-28 is the 2 Meter value of the year.

ORDER DIRECTLY FROM:

Clegg

Communications Corp.
1911 Olde Homestead Lane
Greenfield Industrial Park East
Lancaster, PA 17601
(717) 299-7221

Send check or money order...
$395.00 for FM-28 with scanner option
$295.00 for FM-28 without scanner option
or
Charge to VISA or Master Charge
—Detailed brochure available on request—

Karl Schulte WA2KBZ
3711 N. Firestone Dr.
Hoffman Estates IL 60195

Marine-Band Activity

— a complete guide

Tune in to the world's top traffic.

Between 160 meters and 10 meters, we amateurs generally think in terms of the six HF amateur bands. There are, however, a great many other services operating in those large gaps between our bands. Most hams are aware of some of those other users, such as shortwave broadcasters (Voice of America and Radio Moscow are two examples), if for no other reason than the QRM they cause on the 40 meter phone band at night!

A partial list of the HF band population would include such services as land mobile (U.S. Corps of Engineers, on 5,015 kHz, for example), special industrial, on 4,637.5 kHz (mineral exploration), forestry (in the Pacific Northwest, primarily), and, of course, the military of all nations.

But there is one other major service, one of the oldest, known as the maritime service; that is the subject of this article.

Why is the maritime (or marine) service worth listening to? Because it usually provides the most interesting listening of the communications services (which excludes the broadcast service) and it is the busiest (and therefore easiest to tune in). Also, since it was the first regular user of radio, ship radio has an aura of romance and adventure.

SOS and Mayday — cries for help across the sea — are still heard today, although (thankfully) less frequently than in the past. The famous ship disasters of the last seven decades electrified the public and brought a fleeting fame to the "sparks," as ship operators were known.

Before the SOS was accepted, the most common call for help was CQD, which was made famous in 1909 by Jack Binns, radio officer of the British ship *Republic*. His heroism saved most of the passengers of his doomed ship, which had been rammed by the *S.S. Florida* one day out of New York. Working by candlelight in the January cold, he remained at his key for a continuous 36-hour shift. He delayed his escape from the sinking ship until he knew that help was at hand, risking his life to save the lives of many others.

From the first radio call for help from the British *Goodwin Sands* lightship in March, 1899, through the famous *Titanic* tragedy and the *Morro Castle*, whose smoldering hulk became a tourist attraction when it beached near Asbury Park, New Jersey, boardwalk in the mid 1930s, to the *Andrea Dorea* and the oil tanker sinkings of today's TV news, the tradition of the radio operator's staying at the key until the last possible minute (sometimes losing his life as a result) has remained constant.

I remember following the terrible events of the Texas tower which sank off New Jersey in the early 1960s, from the first Mayday signal to the last announcement that the tower had disappeared with all hands in the horrified sight of the rescue ship. There was a violent gale and there was no way of effecting a rescue. The frequencies used were 2,182 kHz and 500 kHz for phone and CW, both easily heard on an old Navy receiver. That was my introduction to marine radio.

Of course, these tragic

Frequency	Emission		Service
500.0 kHz	A1, A2	(CW)	marine/air
2,182.0	A3, A3A, A3H, A3J	(voice)	marine/air
4,134.3 (ship T) / 4,428.7 (ship R)	A3J	(voice)	marine (U.S.C.G.)
6,200.0 (ship T) / 6,506.4 (ship R)	A3J	(voice)	marine (U.S.C.G.)
8,241.5 (ship T) / 8,765.4 (ship R)	A3J	(voice)	marine (U.S.C.G.)
156.8 MHz	F3	(voice)	VHF marine (ch. 16)
121.5 MHz	A3, A2	(voice/tone)	air/marine*
243.0 MHz	A3, A2	(voice/tone)	air/marine*

*Table 1. Emergency frequencies. *E.P.I.R.B. uses these frequencies — an automatic floating SOS beacon.*

Voice signal	Morse equivalent	Meaning
Mayday	SOS (3 times) (sent as one letter, not S O S)	*Distress*—when there is immediate danger to life or property. Has priority over all other signals. Preceded by "auto-alarm" when time permits.
Pan	XXX (3 times)	*Urgency*—when safety of life or vessel is threatened or if a less immediate danger exists (sickness, out of fuel in open water and no immediate danger, "man overboard," etc.).
Securité	TTT (3 times) (sent 3 letters not as an "O")	*Safety*—when a danger to navigation (hulk in channel, buoy missing, severe weather) exists.
(Voice) Auto-alarm (two alternating audio tones, 1 min. max.)	Auto-alarm (4 sec. on, one sec. off, dashes, one min.)	Sent before Mayday or SOS when time permits, to attract listeners.

Table 2. Priority signals for voice and Morse.

Channel	Frequency*	Channel	Frequency*
4A	4136.3 kHz	22A	22,094.5 kHz
4B	4139.5 kHz	22B	22,098.0 kHz
4C	4434.9 kHz	22C	22,101.5 kHz
6A	6210.4 kHz	22D	22,105.0 kHz
6B	6213.5 kHz	22E	22,108.5 kHz
6C	6518.6 kHz		
			2-MHz frequencies
8A	8281.2 kHz		2,182 kHz
8B	8284.4 kHz		2,638 kHz
12A	12,421.0 kHz		2,670 kHz
12B	12,424.5 kHz		(U.S.C.G.)
12C	12,428.0 kHz		2,738 kHz
16A	16,565.0 kHz		
16B	16,568.6 kHz		
16C	16,572.0 kHz		

*Table 3. HF ship-ship (plus limited coast) simplex channels. *Carrier frequencies are listed; listen on USB. The above 2-MHz frequencies are not, strictly speaking, in the same category, but are often used for similar purposes.*

events are luckily less common today, due to the availability of search planes and fast boats and the fine job done by the Coast Guard. Yet there are about two or three Mayday calls on 2,182 kHz in a week in the Gulf of Mexico alone. Most are promptly solved by the U.S. Coast Guard or nearby ships with no loss of life.

The bulk of traffic is more mundane by comparison, but still very interesting. Some typical SSB traffic, heard on almost any day, would include oil well drilling operational information, fishing fleet chatter, river tugboats, tankers and freighters talking to their home ports or arranging for supplies at their next port, and international radio telephone (phone patch) conversations. I often receive Germany and English marine operators at my Chicago home. If you wish to copy CW, telegrams, ship supply orders, news, weather, and ship arrival times can be heard if one knows where to listen.

Now that I have (hopefully) aroused your interest and curiosity, you are probably wondering where to listen, so here is a fairly complete guide to the marine bands. The information is as accurate and up to date as possible, being derived from a combination of sources, one of which is the rule book of the International Telecommunications Union – a source of many FCC regulations. To this is added my own experience in working with marine radio as HF-SSB consultant for a large Chicago-based company and as an SWL.

The maritime service is divided into several operational categories, four major frequency bands, and two

City	Primary coast transmit	Primary coast receive	Secondary coast transmit	Secondary coast receive
Boston	2506 kHz	2406 kHz	2450 kHz	2366 kHz
New York	2590 kHz	2198 kHz	2522 kHz	2126 kHz
Miami	2514 kHz	2118 kHz	2490 kHz	2031.5 kHz
New Orleans	2598 kHz	2206 kHz	2482 kHz	2382 kHz
Galveston	2530 kHz	2134 kHz	2450 kHz	2366 kHz
San Francisco	2506 kHz	2406 kHz	2450 kHz	2003 kHz
San Pedro (L.A.)	2566 kHz	2009 kHz	2466 kHz	2382 kHz
Seattle	2522 kHz	2126 kHz	2482 kHz	2430 kHz
Hawaii	2530 kHz	2134 kHz	—	—
Great Lakes	2514 kHz	2118 kHz	2550 kHz	2158 kHz
Mississippi (simplex)	2782 kHz	2782 kHz		

Table 4. 2-MHz marine operators.

VIBROPLEX®

Vibroplex® has built for those who use electronic keyers, the finest keying mechanism available.

the Vibro-Keyer "deluxe" $65.00

- Adjustable jeweled bearings.
- Tension and contact spacing fully adjustable.
- Large, solid, coin silver contact points.
- 2½ lb. chrome plated steel base rests on non-skid feet.
- Top parts designed from our world famous Vibroplex® "Original."
- Lifetime guarantee against manufacturing defects.
- Registered serial number.
- Vibroplex® quality through-out.

"THE OLDEST NAME IN AMATEUR RADIO"

"Standard" model with wrinkle finished cast iron base available for $49.50.

Available at your dealers or through the factory. Send check, money order, or use your VISA or Master Charge. We pay all shipping charges except on orders outside the continental U.S.

See your dealer or write for literature on all our world famous line to:

The Vibroplex Company, Inc. V24

P.O. Box 7230 476 Fore St. Portland, Maine 04112

Or call: (207) 775-7710

Station	Code U.S. channels	Ship transmit frequency	Ship receive frequency
KMI—Oakland	401	4063.0	4357.4
	416	4109.5	4403.9
	417	4112.6	4407.0
	804	8204.3	8728.2
	809	8219.8	8743.7
	822	8260.1	8784.0
	1201	12330.0	13100.8
	1202	12333.1	13103.9
	1602	16463.1	17236.0
	2214	22040.3	22636.3
WLO—Mobile	WLO-4	4118.8	4413.2
	WLO-8	8284.9	8808.8
	WLO-13	12407.5	13178.3
	WLO-17	16584.0	17356.9
WOM—Ft. Lauderdale	403	4069.2	4363.6
	412	4097.1	4391.5
	417	4112.6	4407.0
	423	4131.2	4425.6
	802	8198.1	8722.0
	805	8207.4	8731.3
	810	8222.9	8746.8
	825	8269.4	8793.3
	831	8288.0	8811.9
	1206	12345.5	13116.3
	1208	12351.7	13122.5
	1209	12354.8	13125.6
	1215	12373.4	13144.2
	1223	12398.2	13169.0
	1601	16460.0	17232.9
	1609	16484.8	17257.7
	1610	16487.9	17260.8
	1611	16491.0	17263.9
	2215	22043.4	22639.4
	2216	22046.5	22642.5
	2222	22065.1	22661.1
WOO—New York	410	4090.9	4385.3
	416	4109.5	4403.9
	422	4128.1	4422.5
	811	8226.0	8749.9
	826	8272.5	8796.4
	1203	12336.2	13107.0
	1210	12357.9	13128.7
	1605	16472.4	17245.3
	1626	16537.5	17310.4

European channels	Channel #	U.S. Co-user
GCN—Portishead, England	410	(see WOO)
	826	(see WOO)
	1202	(see KMI)
	1611	(see WOM)
PCH—Shevenigen, Holland	802	(see WOM)
	1215	(see WOM)
	1626	(see WOO)
ROME RADIO—Rome, Italy	826	(WOO)
	1209	(WOM)
	1603	(KMI)
		(also Cyprus)
SVA—Athinai, Greece	802	(WOM)
	1232	(none)
	1609	(WOM)
	WLO-17	(WLO)
Atlantic channels		
VRT—Bermuda	410	(WOO)
Caribbean channels		
PLC—Curacao, Antilles	408	(WUQ)
	1607	(WLO-17)
8PO—Barbados	4098.0 (?)	4396.6 (?)
(in process of change)	8210.8	8744.8
Pacific channels		
KQM—Honolulu, Hawaii	418	(none)
	808	(WOO)
	1222	(none)
	1601	(WOM)
KUQ—Pago Pago, Samoa	806	(none)
	1232	(none)
UIS—Sydney, Australia	419	(WLO)
(or other Australian station)	802	(WOM)
	1203	(KMI)
	1610	(WOM)
VQJ—Honiara, Solomon Islands (in change)	8204.4 (?)	8738.4 (?)
ZLW—Wellington, New Zealand	408	(KUQ)
	813	(none)
	1209	(WOM)
P29—Papua, N.G.	805	(WOM)
9VG—Singapore	4078.8	4377.4
	824	(WLO-8)
	1641	(WLO-17)
Tokyo (JMC-?)	810	(WOM)
	1605	(WOO)

Table 5. Selected high seas marine radiotelephone stations (frequencies are shared).

fundamental station types – fixed (coast) and mobile (ship) stations.

Of primary interest to the amateur or SWL are the frequencies, of course, but a summary of the other information will prove useful, enabling the listener to find the type of station he would like to hear.

The basic operational division is that of radiotelegraph (CW) and radiotelephone (phone) operations. These two divisions are interspersed in alternating subbands throughout the 2-26 MHz portion of the spectrum, plus the VLF bands below 500 kHz (exclusively CW except for some weather broadcasts and foreign broadcasting) and the VHF-FM main band which is exclusively phone. RTTY and special data are used a great deal, but are difficult for most SWLs to decode.

An important fact to keep in mind, with regard to ship and shore stations, is that most of their frequency assignments are duplex (actually half-duplex, or two-frequency simplex, at the ship station), with the two stations transmitting and receiving on different frequencies. This is true of many marine channels, from VLF to VHF. An example, WOO 8-26 (WOO is "Ocean Gate Radio" in New York), is given below under "Reading the Tables." The reason for this duplex operation is that the shore stations usually

Station location	Station callsigns	Typical frequency***
Azores	CUG	6,393.5 kHz
Cuba	CLQ	6,435.0 kHz
Dominican Republic	HIA	8,642.0 kHz
England* (Portishead)	GKI**	12,858.0 kHz
Halifax	CFH	12,726, 8,697 kHz
Greece	SVA	12,689, 12,858 kHz
Italy	IAR	8,670.0 kHz
Japan	JOS	8,706.0 kHz
Philippines	DZR	8,568.0 kHz
U.S.A.—East	WSL, WSC**	6-, 8-, 12-MHz bands
U.S.A.—West	KFS**, WNU	6-, 8-, 12-MHz bands, 4,310 kHz
Honolulu—CG	NMO	9,050, 13,655 kHz

*Table 6. Selected CW shore stations. *Sister station of GCN (phone). **Also listen 420-500 kHz. ***Operate many frequencies. See Table 8 for band limits.*

Channel Designator	Ship Rx	Ship Tx
401	4357.4	4063.0
402	4360.5	4066.1
403	4363.6	4069.2
404	4366.7	4072.3
405	4369.8	4075.4
406	4372.9	4078.5
407	4376.0	4081.6
408	4379.1	4084.7
409	4382.2	4087.8
410	4385.3	4090.9
411	4388.4	4094.0
412	4391.5	4097.1
413	4394.6	4100.2
414	4397.7	4103.3
415	4400.8	4106.4
416	4403.9	4109.5
417	4407.0	4112.6
418	4410.1	4116.7
419	4413.2	4118.8
420	4416.3	4121.9
421	4419.4 (4C)	4125.0 (4A)
	Ship simplex	
422	4422.5	4128.1
423	4425.6	4131.2
424	4428.7	4134.3
425	4431.8	4137.4
426	4434.9	4140.5
427	Ship simplex	4143.6 (4B)
601	6506.4	6200.0
602	6509.5	6203.1
603	6512.6	6206.2
604	6515.7	6209.3
605	6518.8	6212.4
606	6521.9 (6C)	6215.5
607	Ship simplex	6218.6 (6A)
608	Ship simplex	6221.6 (6B)
801	8718.9	8195.0
802	8722.0	8198.1
803	8725.1	8201.2
804	8728.2	8204.3
805	8731.3	8207.4
806	8734.4	8210.5
807	8737.5	8213.6
808	8740.6	8216.7
809	8743.7	8219.8
810	8746.8	8222.9
811	8749.9	8226.0
812	8753.0	8229.1
813	8756.1	8232.2
814	8759.2	8235.3
815	8762.3	8238.4
816	8765.4	8241.5
817	8768.5	8244.6
818	8771.6	8247.7
819	8774.7	8250.8
820	8777.8	8253.9
821	8780.9	8257.0
822	8784.0	8260.1
823	8787.1	8263.2
824	8790.2	8266.3
825	8793.3	8269.4
826	8796.4	8272.5
827	8799.5	8275.6
828	8802.6	8278.7
829	8805.7	8281.8
830	8808.8	8284.9
831	8811.9	8288.0
832	Ship simplex	8291.1 (8A)
833	Ship simplex	8294.2 (8B)
1201	13100.8	12330.0
1202	13103.9	12333.1
1203	13107.0	12336.2
1204	13110.1	12339.3
1205	13113.2	12342.4
1206	13116.3	12345.5
1207	13119.4	12348.6
1208	13122.5	12351.7
1209	13125.6	12354.8
1210	13128.7	12357.9
1211	13131.8	12361.0
1212	13134.9	12364.1
1213	13138.0	12367.2
1215	13144.2	12373.4
1216	13147.3	12376.5
1217	13150.4	12379.6
1218	13153.5	12382.7
1219	13156.6	12385.8
1220	13159.7	12388.9
1221	13162.8	12392.0
1222	13165.9	12395.1
1223	13169.0	12398.2
1224	13172.1	12401.3
1225	13175.2	12404.4
1226	13178.3	12407.5
1227	13181.4	12410.6
1228	13184.5	12413.7
1229	13187.6	12416.8
1230	13190.7	12419.9
1231	13193.8	12423.0
1232	13196.9	12426.1
1233	Ship simplex	12429.2 (12A)
1234	Ship simplex	12432.3 (12B)
1235	Ship simplex	12435.4 (12C)
1601	17232.9	16460.0
1602	17236.0	16463.1
1603	17239.1	16466.2
1604	17242.2	16469.3
1605	17245.3	16472.4
1606	17248.4	16475.5
1607	17251.5	16478.6
1608	17254.6	16481.7
1609	17257.7	16484.8
1610	17260.8	16487.9
1611	17263.9	16491.0
1612	17267.0	16494.1
1613	17270.1	16497.2
1614	17273.2	16500.3
1615	17276.3	16503.4
1616	17279.4	16506.5
1617	17282.5	16509.6
1618	17285.6	16512.7
1619	17288.7	16515.8
1620	17291.8	16518.9
1621	17294.9	16522.0
1622	17298.0	16525.1
1623	17301.1	16528.2
1624	17304.2	16531.3
1625	17307.3	16534.4
1626	17310.4	16537.5
1627	17313.5	16540.6
1628	17316.6	16543.7
1629	17319.7	16546.8
1630	17322.8	16549.9
1631	17325.9	16553.0
1632	17329.0	16556.1
1633	17332.1	16559.2
1634	17335.2	16562.3
1635	17338.3	16565.4
1636	17341.4	16568.5
1637	17344.5	16571.6
1638	17347.6	16574.7
1639	17350.7	16577.8
1640	17353.8	16580.9
1641	17356.9	16584.0
1642	Ship simplex	16587.1 (16A)
1643	Ship simplex	16590.2 (16B)
1644	Ship simplex	16593.3 (16C)
2201	22596.0	22000.0
2202	22599.1	22003.1
2203	22602.2	22006.2
2204	22605.3	22009.3
2205	22608.4	22012.4
2206	22611.5	22015.5
2207	22614.6	22018.6
2208	22617.7	22021.7
2209	22620.8	22024.8
2210	22623.9	22027.9
2211	22627.0	22031.0
2212	22630.1	22034.1
2213	22633.2	22037.2
2214	22636.3	22040.3
2215	22639.4	22043.4
2216	22642.5	22046.5
2217	22645.6	22049.6
2218	22648.7	22052.7
2219	22651.8	22055.8
2220	22654.9	22058.9
2221	22658.0	22062.0
2222	22661.1	22065.1
2223	22664.2	22068.2
2224	22667.3	22071.3
2225	22670.4	22074.4
2226	22673.5	22077.5
2227	22676.6	22080.6
2228	22679.7	22083.7
2229	22682.8	22086.8
2230	22685.9	22089.9
2231	22689.0	22093.0
2232	22692.1	22096.1
2233	22695.2	22099.2
2234	22698.3	22102.3
2235	22701.4	22105.4
2236	22704.5	22108.5
2237	22707.6	22111.6
2238	22710.7	22114.7
2239	22713.8	22117.8
2240	22716.9	22120.9
2241	Ship simplex	22124.0 (22A)
2242	Ship simplex	22127.1 (22B)
2243	Ship simplex	22130.2 (22C)
2244	Ship simplex	22133.3 (22D)
2245	Ship simplex	22136.4 (22E)

Table 7. ITU channels for marine HF use.

have separate receive and transmit sites to reduce interaction between on-the-air transmitters and receivers monitoring other channels, thus providing for a more efficient system. It also helps to compensate for the often inefficient ship, yacht, or boat antenna.

There are also a number of simplex channels, such as 2,182 kHz for calling and Mayday use, and 4,125 kHz for ship-to-ship or limited coast station usage.

These frequencies are spread throughout the range of 2-27 MHz, but the most useful for the average listener are between 4 and 17 MHz, providing high activity both day and night and allowing both sides of the conversation to be heard with one receiver, even far inland. Table 3 lists these simplex channels by number and frequency, while Table 4 lists the most interesting duplex channels by band, station, and frequency.

Morse operation is found on the frequencies listed in Tables 6 and 8.

Although not the main purpose of this article, in the interest of completeness I have included several tables listing all the marine bands from VLF to VHF. One last

Limits (kHz)	Assignable working frequencies for high-traffic ships b)	Limits	Calling frequencies d)	Limits (kHz)
4,172.25	4,172.5 -- 4,177.5 11 frequencies spaced 0.5	4,178	4,178.5--- 4,186.5 17 frequencies spaced 0.5	4,187
6,258.25	6,258.75-- 6,266.25 11 frequencies spaced 0.75	6,267	6,267.75- -6,279.75 17 frequencies spaced 0.75	6,280.5
8,341.75	8,342-- 8,345 -- 8,355 14 frequencies spaced 1	8,356	8,357--c)-- 8, 373 17 frequencies spaced 1	8,374
12,503.25	12,504--12,513--12,517.5 --12,532.5 20 frequencies spaced 1.5	12,534	12,535.5 ---12,559.5 17 frequencies spaced 1.5	12,561
16,660.5	16,662--16,672--16,684--16,690 --16,710 25 frequencies spaced 2	16,712	16, 714 ---16,746 17 frequencies spaced 2	16,748
22,184.5	22,187----------22,221 18 frequencies spaced 2	22,222.5	22,225 ---22,265 17 frequencies spaced 2.5	22,267.5

Assignable working frequencies for low-traffic ships		Limits
Group A	Group B	
4,187.5 -- 4,208 84 frequencies spaced 0.5	4,208.5 -- 4,229	4,231
6,281.25-- 6,312 84 frequencies spaced 0.75	6,312.75-- 6,343.5	6,345.5
8,375 -- 8,416 84 frequencies spaced 1	8,417 -- 8,458	8,459.5
12,562.5 --12,624 84 frequencies spaced 1.5	12,625.5 --12,687	12,689
16,750 --16,832 84 frequencies spaced 2	16,834 --16,916	16,917.5
22,270 --22,320 41 frequencies spaced 2.5	22,322.5 --22,370	22,374

Limit	Calling frequencies	Limit
25,070	25,073.5 ---------- 25,081 6 frequencies spaced 1.5	25,082.5

Limit	Working frequencies	Limit
25,082.5	25,084 ---------- 25,106.5 16 frequencies spaced 1.5	25,110

(RTTY and data)

Ship stations, wide-band telegraphy, facsimile, transmission systems:

4,142.5 - 4,162.5 kHz
6,216.5 - 6,244.5 kHz
8,288 - 8,328 kHz
12,431.5 - 12,479.5 kHz
16,576 - 16,636.5 kHz
22,112 - 22,160.5 kHz

Ship stations, oceanographic data transmission:

4,162.5 - 4,166 kHz
6,244.5 - 6,248 kHz
8,328 - 8,331.5 kHz
12,479.5 - 12,483 kHz
16,636.5 - 16,640 kHz
22,160.5 - 22,164 kHz

Ship stations, narrow-band direct-printing telegraph data transmission systems:

4,166 - 4,172.25 kHz
6,248 - 6,258.25 kHz
8,331.5 - 8,341.75 kHz
12,483 - 12,503.25 kHz
16,640 - 16,660.5 kHz
22,164 - 22,184.5 kHz

Coast stations, wide-band and manual telegraphy, facsimile, special and data transmission systems and direct-printing telegraph system:

4,231 - 4,361 kHz
6,345.5 - 6,514 kHz
8,459.5 - 8,728.5 kHz*
12,689 - 13,107.5 kHz
16,917.5 - 17,255 kHz
22,374 - 22,624.5 kHz
*plus 8078.1—U.S. Navy, Va.

Table 8. Frequencies assignable to ship radiotelegraph stations using the maritime mobile service bands between 4 and 27.5 MHz.

note on the calls you will hear is that the callsigns follow the same general assignments as amateur calls and a three-letter call is that of a shore station, while a four-letter or letter/number combination is usually that of a ship. Finally, in order to help you read the tables, the following section explains the channel designation numbering system and summarizes what information can be found in the various tables.

Reading The Tables

Many of the frequencies listed have channel designations after the frequency. These refer to the band and number of channels on a particular band. Therefore, a channel labeled "410" tells us that it is a 4-MHz channel, and refers to a particular frequency. Stating the channel as WOM 410, however, tells us that this is a 4-MHz channel of the Fort Lauderdale, Florida, high seas station and is registered as being 4090.9 kHz (ship transmit)/4385.3 kHz (ship receive). These are always half-duplex frequencies.

International

Channel designators		Ship stations	Coast stations
c)	60	156.025	160.625
01		156.050	160.650
	61	156.075	160.675
02		156.100	160.700
	62	156.125	160.725
03		156.150	160.750
	63	156.175	160.775
04		156.200	160.800
	64	156.225	160.825
05		156.250	160.850
	65	156.275	160.875
06 e)		156.300	
	66	156.325	160.925
07		156.350	160.950
	67	156.375	156.375
08		156.400	
	68	156.425	156.425
09		156.450	156.450
	69	156.475	156.475
10		156.500	156.500
	70	156.525	
11		156.550	156.550
	71	156.575	156.575
12		156.600	156.600
	72	156.625	
13		156.650	156.650
	73	156.675	156.675
14		156.700	156.700
	74	156.725	156.725
15 d)		156.750	156.750
16		156.800	156.800
17 d)		156.850	156.850
	77	156.875	
18		156.900	161.500
	78	156.925	161.525
19		156.950	161.550
	79	156.975	161.575
20		157.000	161.600
	80	157.025	161.625
21		157.050	161.650
	81	157.075	161.675
22		157.100	161.700
	82	157.125	161.725
23		157.150	161.750
	83	157.175	161.775
24		157.200	161.800
	84	157.225	161.825
25		157.250	161.850
	85	157.275	161.875
26		157.300	161.900
	86	157.325	161.925
27		157.350	161.950
	87	157.375	161.975
28		157.400	162.000
c)	88	157.425	162.025

U.S. channels

Channel	Frequency (MHz) Ship	Coast	Function Intership	Ship-to-shore
	Distress, safety and calling (worldwide)			
16	156.800	156.800	YES	YES
	Intership safety (worldwide)			
6	156.300	156.300	YES	NO
	Liaison U.S. Coast Guard			
22	157.100	157.100	YES	YES
	Navigational (worldwide)			
13	156.650	156.650	YES	YES
	State control			
17	156.850	156.850	NO	YES
	Commercial			
7	156.350	156.350	YES	YES
8	156.400	NONE	YES	NO
9	156.450	156.450	YES	YES
10	156.500	156.500	YES	YES
11	156.550	156.550	YES	YES
18	156.900	156.900	YES	YES
19	156.950	156.950	YES	YES
67	156.375	NONE	YES	NO
77	156.875	NONE	YES	NO
79	156.975	156.975	YES	YES
80	157.025	157.025	YES	YES
88	157.425	NONE	YES	NO
	Noncommercial			
9	156.450	156.450	YES	YES
68	156.425	156.425	YES	YES
69	156.475	156.475	NO	YES
70	156.525	NONE	YES	NO
71	156.575	156.575	NO	YES
72	156.625	NONE	YES	NO
78	156.925	156.925		YES
	Public correspondence (note: 4.6 MHz T/R)			
24	157.200	161.800	NO	YES
25	157.250	161.850	NO	YES
26	157.300	161.900	NO	YES
27	157.350	161.950	NO	YES
28	157.400	162.000	NO	YES
84	157.225	161.825	NO	YES
85	157.275	161.875	NO	YES
86	157.325	161.925	NO	YES
87	157.375	161.975	NO	YES
	Port operations			
12	156.600	156.600	YES	YES
14	156.700	156.700	YES	YES
20	157.000	161.600	YES	YES
65	156.275	156.275	YES	YES
66	156.325	156.325	YES	YES
73	156.675	156.675	YES	YES
74	156.725	156.725	YES	YES

Weather

Channel	Frequency	Usage
WX1	162.550	NOAA primary weather channel
WX2	162.400	NOAA secondary weather channel
WX3	161.650	Canadian weather channel (ITU channel 21)

Table 9. VHF.

Band (kHz)	Comments
14-160	VLF, Morse, shared with radio navigation and direction finding
255-285	VLF, Morse, shared with radio navigation and direction finding
410 ±5	Reserved for direction finding
415-525	MF-low, Morse—most common ship frequency band in early days—still used for medium range today
500	"SOS" and calling
1605-2850	Morse and voice—primarily old "ship-to-shore" band in "AM" days; mostly being replaced for short range by VHF
3155-3400	Voice, Morse—less common in U.S.
3400-3800	In some parts of world, shared with amateur service
4060-4440	CW, Morse, RTTY—propagation like 75m
6200-6524	Mostly CW with a few ship-to-ship and duplex SSB channels. Propagation like 40m
8194-8815	Voice, CW, many high seas overseas stations at night—propagation like 40m
12330-13200	Voice, CW, many high seas overseas stations during day—propagation like 20m
16460-17360	Voice, CW, many high seas overseas stations during day—propagation like 20m
22000-22720	Voice, CW, RTTY—propagation like 15m
25060-25110	Mostly CW—very long daytime range
156.0-162.6 MHz	VHF-FM, voice, weather. 156.8 MHz for emergency calling—40-mile range

Table 10. Summary of marine bands.

NMO—Honolulu	All use AMVERS
NMC—Pt. Reyes CA	frequencies plus
NMN—Portsmouth VA	following: 4955,
NAM—Portsmouth VA	8150, 8682, 13380,
NGR—Athens, Greece	16445, 12730 for CW
NPN—Guam	
NDT, NPO—Slave stations (for weather)	

Table 11. High seas Navy and Coast Guard stations.

For another example, WOO 811 is one of the 8-MHz channels for New York's (actually located in New Jersey, near Atlantic City) Ocean Gate Radio (8226.0T/8749.9R). Table 4 provides a listing of many of the major world high seas stations and their frequencies. There are two other types of channel numbers: for HF ship-to-ship (a number and letter combination), and for VHF-FM (a simple channel number). These are to be found in Tables 3 and 9, respectively.

In order to find the emergency frequencies quickly, they are listed separately in Table 1, followed by the types of emergency or priority signals heard on them in Table 2.

For those who have transceivers or receivers with spare bands, the various bands, channel breakdown schemes, and voice as well as Morse operation are to be found in the remaining tables.

That's it. Pick out where and what you want to hear, tune it in, and enjoy the excitement and fascination of the marine bands. ■

BASSETT HELIUM TRAP ANTENNAS **BASSETT HELIUM MOBILE ANTENNAS**

The result of nearly two years of continuous development and nearly fifty years of amateur and commercial antenna design and manufacture Bassett helium filled antennas are for the amateur who demands the very best in American made automatic bandchange systems and mobile antennas that are compatible with all transceivers including the new "no tune"units. Trap systems are fundamental dipoles on each band and do not require antenna tuners.

- Helium filled traps impervious to all weather
- Maintains precise resonance and efficiency
- Systems easily handle legal amateur power
- Multiband amateur and MARS with one coax
- Fully compatible with"no tune" transceivers
- Short enough to fit on a small 50'by 100' lot
- Rugged white traps only 1"diameter, 5" long
- Uses your RG-8 or RG-58 coax in any length
- Center"isolator" equipped to accept a PL-259
- Solid Copperweld, stainless, nylon end lines

MULTIBAND TRAP SYSTEMS

VAC-40/75--$54.50
VAC-20/40--$54.50
VAC-15/20--$54.50
VAC-20/40/75--$74.50
VAC-15/20/40--$74.50
VAC-10/15/20--$74.50
VAC-10/15/20/40-----$104.50
VAC-15/20/40/75-----$104.50
VAC-10/15/20/40/75--$134.50

- Helium filled for a lifetime of high efficiency
- Completely adjustable to precise resonance
- Power handling capability to 750 watts PEP
- Beautiful white 32" Fiberglass lower section
- Stainless 38" 17-7 tapered top whip section
- Very low weight. VAC-20 weighs 6.5 ounces
- Low wind drag. Holds vertical at high speed
- All chrome plated polished brass hardware
- Models for all bands with a 2 meter collinear
- Mates with any standard 3/8-24 mobil mount

SINGLE BAND MOBILES

VAC-2 collinear for 2 meter mobile---$29.50
VAC-6, VAC-10, VAC-15, VAC-20---$29.50
VAC-40, VAC-75 (40 and 75 meters)--$34.50

Postpaid UPS delivery in 48 States. Florida residents add 4% Florida sales tax to above prices. Special models are available for any use, commercial, security, utility, military, or marine.

master charge your BANKAMERICARD welcome

REX BASSETT ELECTRONICS, INC.
BOX 4163 FORT LAUDERDALE, FLORIDA 33304
TEL: 305-561-1400

B52

Reader Service—see page 211

DSI COMMUNICATIONS SERIES

1.3GHz — 1GHz — 700MHz

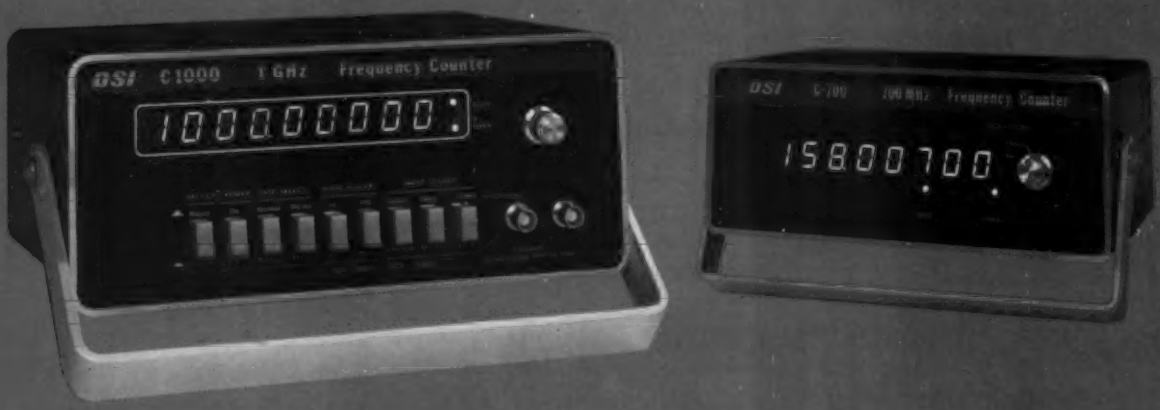

MODEL C1000 10Hz to 1GHz

$499.95

- INCLUDES BATTERY PACK
- AUTO ZERO BLANKING
- AUTO DECIMAL POINT
- 10MHz TIME BASE

Accuracy . . . that's the operational key to this rugged advanced design Model C1000 1GHz frequency counter . . . a significant achievement from DSI. That's because you get . . . .1 PPM 0° to 40°C proportional oven time base . . . Built in 25DB preamplifier with a 60DB adjustable attenuator . . . x10 & x100 audio scaler which yields .01 Hz resolution from 10Hz to 10KHz equivalent to 10 sec. & 100 sec.Gate Time . . . Selecrable .1 & 1 sec. time base and 50 ohms or 1 meg ohm input impedance . . . Built-in battery charging circuit with a Rapid or Trickle Charge Selector . . . Color keyed high quality push button operation . . . All combined in a rugged black anodized (.125" thick) aluminum cabinet. The model C-1000 reflects DSI's on going dedication to excellence in instrumentation for the professional service technician, engineer, or the communication industry.

MODEL C700 50Hz to 700MHz

$369.95

- INCLUDES BATTERY PACK
- AUTO ZERO BLANKING
- AUTO DECIMAL POINT
- 10MHz TIME BASE

ALL NEW! All UNPARALLELED DSI QUALITY! The model C 700 700 MHz frequency counter features . . . .2 PPM 0° to 40° C proportional oven time base . . . 25db preamplifier with a 60db adjustable attenuator. Built in battery charger with a rapid or trickle charge selector . . . Combined in a rugged (.125" thick) aluminum cabinet makes the C700 ideal for the communication industry and professional service technician.

3600A OWNERS: Up date your 3600A frequency counter to a C 700 includes, new back board, .2PPM proportional oven, 25db preamplifier, rugged .125" thick aluminum cabinet, order 3600A-700. Unit must be returned to DSI factory for modification.

DSI — GUARANTEED SPECIFICATIONS — FACTORY ASSEMBLED — MADE IN USA

Model	Frequency Range	Proportional Oven Accuracy Over Temperature	50Hz To 75MHz	75MHz To 500MHz	500MHz To 1GHz	Number Of Digits	Size Of Digits	Power Requirements	Size
C700	50Hz to 700MHz	.2PPM 0° to 40°C	50MV	10MV	NA	8	.5 Inch	115 VAC-BATT 8 to 15VDC	3"H x 8"W x 6"D
C1000	10Hz to 1GHz	.1PPM 0° to 40°C	20MV	1MV	>50MV	9	.5 Inch	115VAC-BATT 8 to 15VDC	4"H x 10"W x 7½"D

— All Units Are Factory Assembled, Tested And Carry A Full 5 Year Limited Warranty —

Model C 700	$369.95
3600A-700 Factory Update (3600A only) Includes Labor & Re-Calibration	$199.95
Model C 1000	$499.95
Opt. 01 1.3 GHz (C1000 only)	$ 99.95
Opt. 02 .05 PPM 10MHz Double Oven 0° to 50° C Time Base (C1000 only)	$129.95
Ant. 210 Telescopic Ant./BNC Adapter	$11.95

FOR MORE INFORMATION

Call Toll Free (800) 854-2049 *DSI Instruments Inc.*
California Exchanges Call Collect (714) 565-8402
7914 Ronson Road, San Diego, CA 92111

Atlanta (800) 242-4545
Georgia Exchanges Call Collect (404) 977-2226
53 Old Stone Mill Road, Atlanta, GA 30067

SWAN and G.I.S.M.O.

PSU–5 100MX Mobile Transceiver ST–3

You can't beat the combination!

Impressive. State-of-the-art styling and design make Swan's 100 MX Mobile Transceiver one of the most desirable units available today! This solid state, made in America transceiver operates from 11 to 15 VDC source negative ground. Boasts USB, LSB, CW. Semi-CW break in. Built-in noise blanker. Preselector for transmit and receive. Call us now for your free instant quote on this or any other Swan product!

ALLIANCE and G.I.S.M.O.

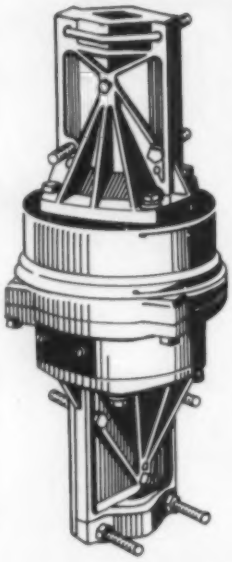

Selection and savings and quality!

For antennas up to 10.7 sq. ft. of wind load area. Mast support bracket design permits easy centering and offers a position drive no-slip option. Automatic brake action cushions stops to reduce inertia stress. Unique control unit features DUAL-SPEED rotation with one five-position switch. SOME SPECS: Max wind load bending movement––10,000 lbs. (side-thrust overturning) * Starting torque––400 lbs. * Hardened steel drive gears. * Bearings––100 3/8" diameter (hardened) * Meter––D'Arsonval, taut band (back lighted).

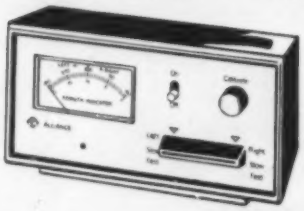

HD-73 HEAVY-DUTY ROTATOR
with exclusive Dual-Speed Control!

Mail's too slow-- call NOW for an instant, TOLL FREE quote!

G.I.S.M.O. 1-800-845-6183

In S.C. call 1-366-7157
2305 Cherry Road, Rock Hill, S.C.
29730 (Exit 66-B off I-77)

G22

Reader Service—see page 211

If you ever worked a repeater... Chances are. it was one of these!

Self contained, all solid state repeaters. Conservatively rated, high quality components, assure excellent reliability. Careful consideration has been given to both interfacing and control flexibility.

RPT 50B, RPT 144B or RPT 220B Kit.....599.95
RPT 432B Kit.....649.95
RPT 50B, RPT 144B or RPT 220B factory wired and tested.....899.95
RPT 432B factory wired and tested.....949.95

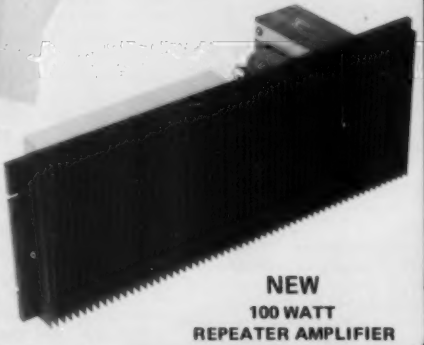

NEW
100 WATT
REPEATER AMPLIFIER

AVAILABLE AT THESE DEALERS:

CALIFORNIA
C & A Electronic Enterprises, Carson, CA 90745, Ph. 213-834-5868
Tele-Com Electronics, San Jose, CA 95121, Ph. 408-274-4479
Zackit Corporation, Vallejo, CA 94590, 707-644-6676

COLORADO
A.E.S. Communications, Wes-Com, Colorado Springs, CO 80909, Ph. 303-475-7050

FLORIDA
Amateur Electronic Supply, Orlando, FL 32803, Ph. 305-894-3238
N & G Distributing, Miami, FL 33126, Ph. 305-592-9685
VHF/JAX, Orange Park, FL 32073, Ph. 904-264-7176

GEORGIA
Creative Electronics, Marietta, GA 30065, Ph. 404-971-2122

ILLINOIS
Klaus Radio, Peoria, IL 61614, Ph. 309-691-4840
Spectronics, Oak Park, IL 60304, Ph. 312-848-6777

IOWA
Bob Smith Electronics, Fort Dodge, IA 50501, Ph. 515-576-3886

MASSACHUSETTS
Tufts Radio Electronics, Medford, MA 02155, Ph. 617-395-8280

MICHIGAN
Adams Distributing, Detroit, MI 48228, Ph. 313-584-4640
The Ham Shack, Kentwood, MI 49508, Ph. 616-531-1976

MINNESOTA
PAL Electronics, Minneapolis, MN 55412, Ph. 612-521-4662

MISSOURI
Alpha Electronic Labs, Columbia, MO 65201, Ph. 314-449-1362

NEBRASKA
Communications Center, Lincoln, NE 68504, Ph. 402-466-3733

NEVADA
Communications Center West, Las Vegas, NV 89106, Ph. 702-647-3114

NEW YORK
Barry Electronics, New York, NY 10012, Ph. 212-925-7000
Delmar Electronics, W. Babylon, LI, NY 11704, Ph. 516-420-1234
VHF Communications, Jamestown, NY 14701, Ph. 716-664-6345

OHIO
Universal Amateur Radio, Reynoldsburg, OH 43068, Ph. 614-866-4267

OKLAHOMA
Derrick Electronics, Broken Arrow, OK 74012, Ph. 918-251-9923

PENNSYLVANIA
LaRue Electronics, Scranton, PA 18509, Ph. 717-343-2124

SOUTH DAKOTA
Burghardt Amateur Center, Watertown, SD 57201, Ph. 605-886-7314

TEXAS
AGL Electronics, Dallas, TX 75234, Ph. 214-241-6414
Madison Electronics Supply, Houston, TX 77002, Ph. 713-658-0268

VIRGINIA
Radio Communications, Roanoke, VA 24016, Ph. 703-342-8513

WASHINGTON
A-B-C Communications, Seattle, WA 98155, Ph. 206-364-8300

WISCONSIN
Amateur Electronic Supply, Milwaukee, WI 53216, Ph. 414-442-4200

CANADA
Bytown Marine Ltd., Ottawa, Ontario, Can. K2H 7V1, Ph. 613-820-6910
Traeger Distributors, Richmond, BC, Can. V6X 2A7, Ph. 604-278-1541

Vhf engineering V5

DIVISION OF BROWNIAN ELECTRONICS CORP.

320 WATER STREET / BINGHAMTON, NEW YORK 13901 / PHONE 607-723-9574

Prices and specifications subject to change without notice. / Export prices slightly higher.

Reader Service—see page 211

W2NSD/1
NEVER SAY DIE
editorial by Wayne Green

from page 6

the blame, so I can understand the need to try to revise the one lone vote against the project into an even split. It was an ambitious project which might have managed to die on its own accord without the jugular being cut by Tenney . . . but that we'll not know for sure, and so, should amateur radio lose frequencies at WARC this fall, we certainly know where to point the finger. My own evaluation is that the project to interest African countries in the benefits of amateur radio to their people would have worked, just as it did in Jordan, and could have made a decisive difference at Geneva . . . perhaps getting some backing for the US proposal for even more amateur bands.

Future historians interested in getting facts on these ARMA meetings should contact me for copies of the tapes. It's all there for anyone with the constitution to listen through.

FM STARTED IT

The Japanese had no serious foothold in the US with ham gear until the advent of FM and repeaters. I would like to point out that when I started pushing FM in *73 Magazine* back in 1969, I made sure that every US manufacturer of ham equipment knew what I was doing and the impact that I expected it to have. They ignored my predictions, feeling that FM never would be a significant factor in the ham market.

This reminded me of my similar failure to interest the major firms in getting into sideband back in 1955 when I saw that one coming. I talked with Hallicrafters, Hammarlund, National, etc., about it and none of them had any interest at the time. It took Central Electronics to get things moving and the big firms came along when there was no other choice.

By leaving the FM field open to imports, the US industry made it possible for them to set up importing and marketing in this country on a large scale . . . laying the foundation for the 70% penetration we see today. If US manufacturers will be adventurous and try to lead the market instead of follow it, they can sell everything they can make.

CANADIAN HIJINKS

Having received some sanctimonious letters from Canada in response to my criticisms of the ARRL pulling what appears to be a con job on the Canadians, I had someone look into the state of affairs of the supposed incorporation of a Canadian League . . . and nothing could be found filed with the Canadian government. This would lead a naive person like me to suspect that all those promises of untying the apron strings are the usual baloney.

In looking over the list of officers for Canada, I see W2HD listed as their vice president. I dunno why Canadians put so much stock in carpetbaggers and prefer to be run from the US instead of from Canada. Perhaps they are still too weak to stand on their own? Yet, which way is the money flowing? Is it going to Canada or from it . . . and I'm kidding there, because I know as well as you which way the money goes . . . into the bottomless pit down in Connecticut.

MEMBERSHIP DISASTER

The League officials were wearing very worried looks at Dayton. It was difficult to even get them to come forth with a wan smile. It seems that the $18 fee has brought renewals almost to a halt. Now hams are taking a gimlet-eyed look at what they are buying. They see a magazine with few interesting articles . . . they see a lot of back-patting news which is stale before they even get the magazine . . . and ads.

The directors have been trying to get the magazine beefed up, but as the editor complained at Dayton, hardly anyone will write for *QST* anymore. They just don't have the articles—except those from the few staffers who have not yet left the magazine.

SUNSPOT MADNESS

It has not been with a little smugness that we've been watching the sunspot cycle to see how well it would correspond with the model predicted by our resident expert, John Nelson . . . particularly as compared with the predictions for this cycle by the many other experts in the field.

Probably one of the real sleepers in the radio publishing field has been John's book, *The Propagation Wizard's Handbook* ($6.95 from Radio Bookshop, Peterborough NH 03458). John was virtually the only "expert" in the field to have accurately predicted this cycle as it has evolved—and his prediction was way out in left field. He predicted a very low sunspot number for this cycle, with the appearance of a very few large spots instead of the myriad of small spots which have made up the past cycles . . . and he has been absolutely right!

The Nelson book is now being ordered in larger numbers by the scientists at NASA and at Boulder, where the National Bureau of Standards runs a propagation laboratory. Nelson's predictions have been right on the nose, while the government predictions have been noticeably short on accuracy.

There is nothing really new about the Nelson system. He's been using it for about 30 years and has described it in many articles down through the years. When I first ran into his concept of the planets having an influence on sunspots, some 25 years ago, it made a lot of sense to me. I met John when he was giving a talk on his system at a Long Island ham club. I was impressed by his cautious approach and penchant for rigorous attention to details. I noted that only his predictions seemed to stand up, while those of the Bureau of Standards and George Jacobs (VOA) would be frequently in serious error. When John said conditions were going to stink, that was the time to take a vacation. When he said they would be hot, you made sure your antenna was working right.

Oh, what value are these long-range predictions? John wrote an article for *73* quite some time ago telling us what we could expect from the eleven meter CB frequencies during this cycle . . . and his predictions have been most accurate. Since this cycle is unlike any other in history and was predicted by John this way, the effects on both the CB frequencies and the ham bands have been remarkably different from past cycles. Knowing about this ahead of time is valuable in making rules and planning activities. Is it worthwhile to put a lot of development time and money into ten meter repeaters? That depends on propagation.

TURKEY CLUB

One club and one club only refused to cooperate with the ham clubs in the greater St. Louis area on their recent ARCH MARCH hamfest. Their excuse was that as an ARRL club they refused to support any amateur activity where Wayne Green was going to talk.

When I heard about this, I wrote to the club and offered to come to St. Louis a day early and go to a special club meeting where the members could have an opportunity to face me with their beefs and have an opportunity to find out the truth of things they believed on trust from the ARRL. The club flatly refused to face me. Failing in that, I tried to get a meeting with the head of the club and this was agreed upon.

Came the time for the meeting, the only time this chap could make it, at 10:00 pm the night before the hamfest, and the chap didn't show up. I sat and waited for almost an hour, but no message and no club president. I was worn out after a full day of television appearances, meeting the mayor of St. Louis, and other meetings. When the chap didn't show, I went to bed to get rested up for the busy hamfest on the day to come. I had to be up very early to set up our booth, get set for my two major talks that day, etc.

Suddenly, the phone rang . . . our friend had finally gotten to the hotel. He got angry when I said I wouldn't get dressed again and come down to argue with him for an hour or so. I had gone to a lot of trouble to make the time available for him—which was wasted—and I was not about to stay up a good part of the night and thus make my talks the next day less entertaining just because he was unable to keep an appointment.

Phooey.

MARCH WINNER

"The NCX-Match" was a close winner over K6IQL's "The 10-GHz Cookbook" in our March Reader Service card balloting, so Rick Ferranti WA6NCX/1 (Newton Centre MA) will be receiving our $100 bonus check for being the author of that issue's most popular article.

Ham Help

I would appreciate it if anyone could help me connect a Heathkit HG-10B vfo to my Swan 500CX to be used as an outboard vfo.

Ancel W. Norris WB4AUB
4357 Mountaindale Road
Birmingham AL 35213

CALL A.R.S.O.N. NOW!
615 868·4956
for the Best DEALS

Amateur Radio Supply of Nashville, Inc.

615 South Gallatin Road, Madison, Tennessee 37115

A40

best prices · best service · best trades

YAESU FT 901 DM

Call for yours today!

THE NEW FT101ZD
!! IN STOCK !!

Digital 160M-10M • Deluxe Features
Check the others . . . then get our price!

NEW!
YAESU FT207R

Synthesized Handi-Talkie. 3 Watts. In Stock! Write or Call for Price.

NEW!

DENTRON GLA 1000

1 KW DC Input! • 1200 W. PEP!!
Clipperton L • MLA 2500 B • DTR 2000L

We have the New Dentron AF-1A Audio Processor. Dentron Antenna Tuners, Antennas and SWR Meters.
CHECK OUR PRICES

J. W. Miller - Daiwa **NEW!**

Call or write for Super Low Prices.

Fast UPS delivery. Place your order then standback!!! We ship your order the same day we get it. Best prices and quick handling of your order.

Used Equipment? Our stock turns fast - write or call your specific needs.

CLOSEOUT SPECIALS!

Send S.A.S.E. for our pink sheet specials.

STORE HOURS

Mon. - Fri. 9 AM - 5 PM

NEW!
KENWOOD TS180S

All Solid State with Digital Frequency Control. 200W P.E.P. Best Prices!

NEW!
KENWOOD'S
NEW TS 120S

ALL SOLID STATE HF TRANSCEIVER
PLUS A FULL LINE OF ACCESSORIES
Before You Buy, Get Our Prices!

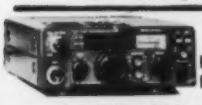

NEW!
KENWOOD TR7600
KENWOOD TR7625

10 or 25 Watt FM 2 meter xcvr synthesized with memory. **Get our best price!**

IN STOCK!! Also ask about the RM 76 MICRO processor for the 7600/7625

WE STOCK THE FULL KENWOOD LINE AND PROVIDE WARRANTY AND AFTER-WARRANTY SERVICE. BUY WITH CONFIDENCE!

SSTV — ROBOT

PUT YOURSELF IN THE PICTURE!!
Get in on the latest in Ham Radio.

IN STOCK
Call or write for prices.

ICOM 701, 211, 215, 280, 30A -
ALL IN STOCK!!

Compare Our Prices!!!

CDE ROTOR SPECIALS

The NEW HAM IV Rotor

NEW!

Shipping included
HAM IV Rotor $147.00
HAM IV Rotor with 100 ft. rotor cable $162.00
HAM IV Rotor plus 100 ft each - rotor cable and first grade RG8A $185.00
Send cashiers check or M.O. please.

2M HANDI TALKIES??
WILSON, YAESU, TEMPO

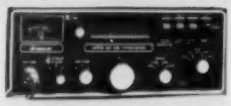

SWAN ASTRO 150

HF SSB Transceiver featuring "VRS" Fully Synthesized 235 Watts PEP & CW. See the Swan ads and Call us or write for Best Prices anywhere!!

MIRAGE

B108 2M AMP • MP1 HF SWR MTR
MP2 VHF SWR MTR

We've got 'em in stock! Call or write for prices.

DATONG

We have in stock the amazing Datong FL-1 active audio filter. Also now have the ASP, Automatic speech processor . . . plus the Code tutor . . . Fantastic additions to your station. Call or write for information and prices.

Get On Frequency!

DSI Counter Semi-kit

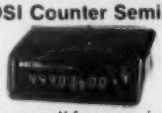

Write or call for special price.

Rotor Special
ALLIANCE HD-73

SPECIAL OFFER!!
$105.00 including Shipping in U.S.A.
HD-73 with 100 feet rotor cable $120.00
HD73 with 100 feet rotor cable and 100 feet RG8X $150.00
Cashiers check or M.O. please.

Sure, we take trades on new equipment! Call or write. We're Burning to Make "Hot" Deals!!

Reader Service—see page 211

RTTY Loop

Program 1 (continued).

```
01060 009B 5C            FCB   $5C,$CC,$DD  \=BS
01070 009E 5D            FCB   $5D,$24,$24  ]=))
01080 00A1 5E            FCB   $5E,$F0,$B4  ↑=UP
01090 00A4 5F            FCB   $5F,$F0,$A4  ←=UL
01100 00A7 0000    TEMPO1 FDB   0000
01110 00A9 00      SHIFT  FCB   0
01120 00AA 00      CHRCNT FCB   0
01130 00AB 0D      CRLFST FCB   $D,$A,$15,0,0,4
01140                     * ABOVE PROGRAM STARTS HERE
01150                     *
01160 0100                ORG   $0100
01170 0100 8E AC70 START  LDS   #$AC70
01180 0103 4F             CLR A
01190 0104 B7 801D        STA A PIACA
01200 0107 4A             DEC A
01210 0108 B7 801C        STA A PIADA
01220 010B 86 04          LDA A #$4
01230 010D B7 801D        STA A PIACA
01240 0110 86 01          LDA A #$01
01250 0112 B7 801C        STA A PIADA
01260 0115 BD E1AC INCHR  JSR   INEEE
01270 0118 B7 011F        STA A INDEX+1
01280 011B CE 0020        LDX   #TABLE
01290 011E A6 00   INDEX  LDA A X
01300 0120 81 FF          CMP A #$FF
01310 0122 27 3C          BEQ   SPLCHR
01320 0124 4D             TST A
01330 0125 27 EE          BEQ   INCHR
01340 0127 81 90          CMP A #$90
01350 0129 26 08          BNE   AROUND
01360 012B C6 3C          LDA B #60
01370 012D D1 AA          CMP B CHRCNT
01380 012F 2D 02          BLT   AROUND
01390 0131 20 5A          BRA   CRLFOT
01400 0133 8D 05   AROUND BSR   OUTPUT
01410 0135 7C 00AA        INC   CHRCNT
01420 0138 20 DB          BRA   INCHR
01430 013A 48      OUTPUT ASL A
01440 013B 25 11          BCS   CALTRS
01450 013D 7D 00A9 CAFIGS TST   SHIFT
01460 0140 27 1B          BEQ   OUTCHR
01470 0142 36             PSH A
01480 0143 86 1B          LDA A #$1B
01490 0145 BD 01AD        JSR   OUTBDT
01500 0148 32             PUL A
01510 0149 7F 00A9        CLR   SHIFT
01520 014C 20 0F          BRA   OUTCHR
01530 014E 7D 00A9 CALTRS TST   SHIFT
01540 0151 26 0A          BNE   OUTCHR
01550 0153 36             PSH A
01560 0154 86 FF          LDA A #$FF
01570 0156 BD 01AD        JSR   OUTBDT
01580 0159 32             PUL A
01590 015A 7C 00A9        INC   SHIFT
01600 015D 8D 4E   OUTCHR BSR   OUTBDT
01610 015F 39             RTS
01620 0160 B6 011F SPLCHR LDA A INDEX+1
01630 0163 81 0D          CMP A #$0D
01640 0165 27 26          BEQ   CRLFOT
01650 0167 CE 0080        LDX   #SPTABL
01660 016A A1 00   SPLOOP CMP A X
01670 016C 27 05          BEQ   FOUND
01680 016E 08             INX
01690 016F 08             INX
01700 0170 08             INX
01710 0171 20 F7          BRA   SPLOOP
01720 0173 08      FOUND  INX
01730 0174 A6 1C          LDA A #$1C
01740 0176 8D C2          BSR   OUTPUT
01750 0178 A6 00          LDA A X
01760 017A 8D BE          BSR   OUTPUT
01770 017C 08             INX
01780 017D A6 00          LDA A X
01790 017F 8D B9          BSR   OUTPUT
01800 0181 86 1C          LDA A #$1C
01810 0183 8D B5          BSR   OUTPUT
01820 0185 C6 04          LDA B #$4
01830 0187 DB AA          ADD B CHRCNT
01840 0189 D7 AA          STA B CHRCNT
01850 018B 20 88          BRA   INCHR
01860 018D CE 00AB CRLFOT LDX   #CRLFST
01870 0190 BD E07E        JSR   PDATA
01880 0193 86 88          LDA A #$88
01890 0195 8D A3          BSR   OUTPUT
01900 0197 86 88          LDA A #$88
01910 0199 8D 9F          BSR   OUTPUT
01920 019B 86 A0          LDA A #$A0
01930 019D 8D 9B          BSR   OUTPUT
01940 019F 86 FF          LDA A #$FF
01950 01A1 8D 97          BSR   OUTPUT
01960 01A3 86 FF          LDA A #$FF
01970 01A5 8D 93          BSR   OUTPUT
01980 01A7 7F 00AA        CLR   CHRCNT
01990 01AA 7E 0115        JMP   INCHR
02000                     *
02010 01AD C6 05   OUTBDT LDA B #$05
02020 01AF 8D 16          BSR   SNDSPC
02030 01B1 48      SFTLFT ASL A
02040 01B2 25 04          BCS   ARROUT
02050 01B4 8D 11          BSR   SNDSPC
02060 01B6 20 0E          BRA   NXTBLE
02070 01B8 8D 08   ARROUT BSR   SNDMRK
02080 01BA 5A      NXTBLE DEC B
02090 01BB 26 F4          BNE   SFTLFT
02100 01BD 8D 03   SNDSTP BSR   SNDMRK
02110 01BF 8D 01          BSR   SNDMRK
02120 01C1 39             RTS
02130                     *
02140 01C2 36      SNDMRK PSH A
02150 01C3 86 01          LDA A #$01
02160 01C5 20 03          BRA   OUTDAT
02170 01C7 36      SNDSPC PSH A
02180 01C8 86 00          LDA A #$00
02190 01CA B7 A7   OUTDAT STX   TEMPO1
02200 01CC B7 801C        STA A PIADA
02210 01CF 8D 04          BSR   MSEC20
02220 01D1 32             PUL A
02230 01D2 DE A7          LDX   TEMPO1
02240 01D4 39             RTS
02250                     *
02260 01D5 8D 01   MSEC20 BSR   MSEC10
02270 01D7 01             NOP
02280 01D8 CE 0480 MSEC10 LDX   #$480
02290 01DB 09      MSLOOP DEX
02300 01DC 26 FD          BNE   MSLOOP
02310 01DE 39             RTS
02320                     *
02330 A048                ORG   PGCTR
02340 A048 0100           FDB   START
02350                     *
02360                     END
```

from page 14

Certain characters, not represented in Baudot, have an $FF stored at their location. This directs the program to use the special table (SPLTBL), located from $80 to $A6. The table is organized as a three-byte, fixed-format table. The first byte is the ASCII character, and the next two are the Baudot codes for the two-letter symbol for each ASCII code.

The main program starts at $0100 by setting up the stack and initializing the PIA, addressed to port 7, as an output. A character is input through the monitor's input routine and used as the index for the table. If the retrieved character is $FF, the ASCII code needs a special character representation, and a branch to SPLCHR is executed. A retrieved null, $00, initiates a branch back to input, with no output produced. One more test and we're ready to fly. If the retrieved character is a space ($90 in Baudot), a check is made on the running total characters in the line. If it is greater than sixty, forget the space and send a carriage-return, line-feed sequence. If it is not a space, hooray—we put it out.

First things first, the MSB is shifted into the carry bit, where it can be used to set or reset the software flip-flop used to monitor case. This was well diagrammed last month and will not be detailed here. Each of the five data bits is then shifted out and sent sequentially, after a character START bit is sent, and a STOP bit, 33 milliseconds of pure MARK, is plastered on at the end.

Now things are going to get a bit tacky. Each data bit must be sent for exactly 22 ms. The timing is set in a software delay loop, called MSEC10, set for approximately an eleven ms delay. Since this delay is produced by loading a number into the index register and decrementing it, the speed of the computer's clock can make a significant difference in the delay.

For the "original" SWTPC 6800, with the MP-A CPU board, the clock speed is roughly 902.255 kHz, and a delay constant of $0480 is used. If you have the MP-A2 CPU board, your clock speed may be anything from about 900 kHz to 1.5 MHz. To find the constant that is right for your system, enter Program 2 into your computer and type "G". Time, exactly, the interval, in seconds, between the "B" and "E". Use the formula shown in Fig. 1 to calculate your delay constant. Remember, this is hexadecimal arithmetic. Work through the example to be sure you've got it right.

One more thing to do before we can use the program on the

Program 2.

```
00010                     NAM   CHKSPEED
00020                     OPT   O

00040                     *
00050                     * PROGRAM TO DETERMINE
00060                     * DELAY CONSTANT BY
00070                     * ESTIMATING CLOCK
00080                     * SPEED OF THE SWTPC
00090                     * 6800 COMPUTER
00100                     *
00110                     * MARC I. LEAVEY, M.D.
00120                     *
00130                     ***************************
00140                     * EXTERNAL REFERENCES
00150                     *
00160          E1D1       OUTEE  EQU   $E1D1
00170          E0E3       SWTBUG EQU   $E0E3
00180          A048       PGCTR  EQU   $A048
00190 0100                ORG   $0100
00200 0100 86 42   START   LDA A #'B      PUT OUT A "B"
00210 0102 BD E1D1        JSR   OUTEE     IN THE BEGINNING
00220 0105 8D 10          BSR   ONEMIN    ;   N O W
00230 0107 8D 0E          BSR   ONEMIN    ;   W A I T
00240 0109 8D 0C          BSR   ONEMIN    ;   F O R
00250 010B 8D 0A          BSR   ONEMIN    ;   F I V E
00260 010D 8D 08          BSR   ONEMIN    ; M I N U T E S
00270 010F 86 45          LDA A #'E       PUT OUT AN "E"
00280 0111 BD E1D1        JSR   OUTEE     AT THE END
00290 0114 7E E0E3        JMP   SWTBUG    AND GO TO MONITOR
00300                     *
00310 0117 86 C7   ONEMIN LDA A #$07      RING THE BELL
00320 0119 BD E1D1        JSR   OUTEE     EACH MINUTE
00330 011C C6 3B          LDA B #$3B      ;
00340 011E CE FB00 LOOP1  LDX   #$FB00    ; THIS LOOP
00350 0121 09      LOOP2  DEX             ; IS TIMED
00360 0122 09             DEX             ; TO RUN
00370 0123 08             INX             ; ONE MINUTE
00380 0124 26 FB          BNE   LOOP2     ; WITH A
00390 0126 5A             DEC B           ; CLOCK OF
00400 0127 26 F5          BNE   LOOP1     ; ONE MHZ
00410 0129 39             RTS             ;
00420                     *
00430 A048                ORG   PGCTR     SET UP PROGRAM COUNTER
00440 A048 0100           FDB   START     WITH STARTING ADDRESS
00450                     *
00460                     END
```

The Scanning Memorizers

FT-127RA
(220 MHz)

FT-227RB
(144 MHz)

FT-627RA
(50 MHz)

The FT-127RA, FT-227RB and FT-627RA, FM transceivers, allow scanning and expanded memory coverage for the demanding VHF FM operator. All feature up/down scanning capability with control from the microphone; the scanner will also search for a busy or clear channel. Four memory channels are available — two for simplex, three for repeater channels,one for a split of up to 4 MHz. Other performance features are similar to those of the renowned FT-227R.

OPTIONAL EQUIPMENT

Keyboard Microphone: YM-22 for FT-127RA and FT-627RA; YM-23 for FT-227RB (YM-22 standard feature with FT-227RB) • Squelch Unit • FP-4 AC Power Supply

CPU-2500R/K 2M FM Transceiver
with Central Processing Unit

The age of computers has entered the amateur scene with the announcement of the CPU-2500R/K 2-meter FM transceiver. Controlled by a 4-bit central processing unit (CPU), the CPU-2500R/K contains a scanner, 4 memory channels, manual or automatic tone burst, an optional sub-audible tone squelch, and 25 watts output.

The keyboard microphone allows two-tone input for autopatch or control purposes, as well as remote programming of dial or memory frequencies.

Automatic ±600 kHz repeater split, or program a split up to 4 MHz using the memory. Keyboard microphone allows remote programming of odd splits.

CPU scanner will search for a busy or clear channel, upon your command.

Four memory channels for simplex or repeater use, plus another memory channel for a split of up to 4 MHz.

C&A Electronic Enterprises
Distributors of Commercial and Amateur Radio Equipment
22010 S. Wilmington Ave., Suite 105
Carson, CA 90745

Available from C & A Electronics
Call for best price.
800-421-2258
(TOLL FREE — OUT OF CALIFORNIA)
213-834-5868
(CALIFORNIA)

Reader Service—see page 211

air: Interface it. The data is coming out of bit 0 (the LSB) of the A side of a PIA interface on port 7. This TTL level signal represents MARK with a high and SPACE with a low. If you have an ST-6 or equivalent, interfacing may be accomplished easily, adding only one diode, as described several months ago for the test generator. Other interfacing schemes could include an opto-isolator or reed relay. Remember, though, *don't* allow the loop voltages access to the computer or you will have a smoking pile of expensive "junque."

If all goes well, when you load the program, adjust the delay constant, and accomplish interfacing, any character struck on the keyboard should come out in Baudot on the other end.

General Formula:
"Constant Delay" × "Constant Time" =
"New Delay" × "New Time"

Constants for MP-A System:
Constant Delay = $480 (1152 Decimal)
Constant Time = 332 Seconds

Practical Formula:
$\frac{1152 \times 332}{\text{New Time}}$ = New Delay

An Example:
MP-A2 System Time = 234 Seconds
$\frac{1152 \times 332}{234}$ = 1634 = $666 New Delay

Fig. 1.

Now, one last hooker: If you are using an MP-C "control interface" (the one that was supplied with the computer if it had an MP-A CPU board) and you type in a character while one is sending, you will get garbage. This is an unfortunate result of the software UART written into the MIKBUG™ or SWTBUG™ monitor to handle serial data through a PIA interface on port 1. Yes, I know we are doing essentially the same thing on port 7, but that is the problem. While the system will support one delay loop, it will not support two running at the same time. The solution is to take one of the I/O structures out of a *software* UART and into a *hardware* UART, or ACIA. The easiest way to do that is to use a serial MP-S interface for control on port 1. Now, characters input during an output are simply ignored. Not an ideal solution, but adequate for this simple program.

Next month, we'll . . . no, I'm not going to tell you! There are few surprises in life; let one of them be next month's RTTY Loop.

Contests

from page 19

Phone—3920, 7260, 14300, 21360, 28600, 50.3, 145.1.

Use of FM simplex is encouraged but no repeater contacts are allowed.

AWARDS:

A plaque to the top RI and non-RI scorer, plus certificates will be awarded to the top scoring station in each RI county, state, province, DX country, the top scoring Novice and Technician station in each RI county and state, and the ARC in each state, province, and DX country that submits the highest aggregate score with a minimum of 3 logs per club.

ENTRIES:

Logs must show date/time in GMT, call, exchange, band, and mode. On a separate sheet show name, call, mailing address, club affiliation if any, total QSO points, multiplier claimed, and final score. Entries must be postmarked no later than August 31. Send logs and summary to: East Bay Amateur Wireless Association, PO Box 392, Warren RI 02885. Include an SASE for results.

NEW JERSEY QSO PARTY

Contest Periods:
2000 GMT Saturday, July 28 to 0700 GMT Sunday, July 29
1300 GMT Sunday, July 29 to 0200 GMT Monday, July 30

Sponsored by the Englewood Amateur Radio Association, the contest is open to all amateurs worldwide for the 20th year. Phone and CW are considered the same contest. A station may be contacted once on each band. Phone and CW are considered separate bands, but CW contacts may not be made in the phone segments. NJ stations may work other NJ stations. General call is "CQ NJ." NJ stations are requested to identify themselves by signing "DE NJ."

EXCHANGE:

QSO number, RS(T), and QTH (ARRL section or country/NJ county).

FREQUENCIES:

1810, 3535, 3900, 7035, 7135, 7235, 14035, 14280, 21100, 21355, 28100, 28600, 50-50.5, and 144-146.

Suggest phone activity on the even hours, 15 meters on the odd hours 1500 to 2100 GMT, 160 meters at 0500 GMT.

SCORING:

Out-of-state stations multiply number of complete contacts with NJ stations times the number of NJ counties worked (21 maximum). NJ stations score 1 point per W-K-VE-VO QSOs, 3 points per DX QSO. Multiply total number of points times the number of ARRL sections (including NNJ and SNJ—75 max.). KP4, KH6, KL7, KZ5, etc., count as 3-point DX contacts and as section multipliers.

AWARDS:

Certificates will be awarded to the first-place station in each NJ county, ARRL section, and country. In addition, a second-place certificate will be awarded when four or more logs are received. Novice and Technician certificates will also be awarded.

ENTRIES:

Logs must show GMT date/time, band, and emission, and be received not later than August 25. The contact for each claimed multiplier must be indicated and numbered and a checklist of contacts and multipliers should be included. Multi-operator stations should be noted and calls of participating operators listed. Logs and comments should be sent to: Englewood Amateur Radio Assoc., PO Box 528, Englewood NJ 07631.

A size #10 SASE should be included for results. Stations planning active participation in NJ are requested to advise the EARA by July 7 of your intentions so that they can plan for full coverage from all counties. Portable and mobile operation is encouraged.

ENDEAVOUR AWARD

The Royal Naval Amateur Radio Society already sponsors two awards, the Mercury Award for contacting members of the Society, and the Hampshire County Award for contacting amateurs in the English county of Hampshire. The Society now has great pleasure in announcing a third award, called the Endeavour Award, for contacting Society members residing in Australia. The title of the award links the Royal Navy with Australia and the award is open to all radio amateurs.

Applicants must establish two-way amateur communications with RNARS members residing in Australia. Points will be awarded on the basis of one point per VK RNARS member worked per band, after the commencement date of January 1, 1979. To qualify, the following is required: for amateurs residing inside Australia—15 points; for amateurs residing inside Oceania—10 points; for amateurs residing outside Oceania—5 points.

In addition, for amateurs residing outside Oceania, contacts with VK RNARS members on the 3.5 MHz band will count double points. For the purposes of this award, any RNARS maritime-mobile member when located inside Australian waters may be counted as a VK member.

The award will be endorsed only on the request of the applicant and the following endorsements are available: all CW, all SSB, all 3.5 MHz, all 28 MHz, all Novice, and five-by-five, the last endorsement being for gaining at least five points on each of the five high frequency bands.

To claim the award, no QSLs are required. However, full log details showing the VK member (or /MM + QTH) worked, their RNARS number, date, time, frequency, mode, plus an application fee of $1.50 Aust or 7 IRCs are to be sent to the Endeavour Award Custodian: R. Baty VK5MD, 43, HMAS Australia Road, Henley Beach South, SA 5022 Australia. Please ensure all checks are in Australian currency and made payable to "R. Baty." Clearly state what endorsements are claimed. Certificates to successful applicants will be forwarded by airmail as soon as possible after the claim has been checked.

TESLA COMMEMORATIVE AWARD

A very attractive award is being offered by YU2EAB, the Gospic Amateur Radio Club, to commemorate the birth of Nikola Tesla. To obtain this award you must work the special station YU0NT for 5 points plus any other Gospic station for one point. Six points are needed for the award. No band or mode restrictions exist. YU0NT will operate from July 7 through July 17 from the house where Nikola Tesla was born. Some of the other stations to look for in Gospic include YU2CET, YU2CGE, YU2CGG, YU2CPJ, YU2CTK, YU2CUD, YU2EAB, YU2RWI, YU2RWY, and YU2VE.

No QSLs are necessary to obtain the award; send only the usual log data along with 5 IRCs or $2.00 to: YU2EAB, Box 55, 48000 Gospic, Yugoslavia.

'79 ARRL NATIONAL CONVENTION

Baton Rouge, Louisiana

Louisiana Council of Amateur Radio Clubs

INVITES YOU

July 20, 21, 22, 1979

TO

Grandeur on the Mississippi

Riverside Centroplex
"The amateurs unique ability to enhance international Goodwill."
Fais do-do, Jambalaya and Crawfish Pie,
Louisiana QSL contest. Show 15 Louisiana '79 Convention QSL cards and attend fine tuning free. (Cards must be dated after Dec. '78)

SHOPPING, GREAT FOOD, PLUS ALL THESE CONVENTION EXTRAS!!!

SPECIAL LADIES PROGRAMS
LAS VEGAS NITE
OUTSTANDING SPEAKERS
HOSPITALITY ROOMS
SATURDAY NITE WOUFF HONG
CHILDRENS ACTIVITIES AND TOURS
MANY CONTESTS AND AWARDS

LOTS OF PRIZES

QCWA BREAKFAST
ARRL FORUMS
SUNDAY LUNCHEON
COCKTAIL PARTIES
SCENIC TOURS AVAILABLE
SUNDAY SERVICES
SUNDAY BRUNCH

LARGE EXHIBIT AREA WITH MANY NEW PRODUCTS
ARRL HEADQUARTERS AND FIELD PERSONNEL WILL BE HERE
ALL TOPPED OFF WITH A SUPER, SUPER SATURDAY BANQUET BASH
YOU'LL COME . . . Programs start Friday afternoon; Saturday, all day; Sunday, all day. NO OTHER CONVENTION HAS EVER SURPASSED OUR TREMENDOUS PROGRAMS!

A registration is required for admission to all activities (inc. ladies)

INFORMATION: '79 ARRL National Convention
P.O. Box 891
Baton Rouge, LA 70821

Looking West

from page 12

more fitting than this contact. Fate had been very kind indeed.

The station operates under the callsign W6RO—W6 "Rolling Ocean"—as a tribute to one of the founding members of the club sponsoring the overall *Queen Mary* wireless operation. Amateurs wishing to operate from the *Queen Mary* can do so in one of two ways. Those living in the area and wishing to serve as scheduled volunteer operators can contact the Associated Radio Amateurs of Long Beach and make their intentions and availability known. However, if you are planning a trip to Los Angeles and would like to operate the station, you can take the *Queen Mary* tour and, when it gets to the wireless room, locate the operator in charge and explain your desires. You will have to present your original amateur license and some additional identification before you will be permitted to operate. Guest operating periods will be approximately 15 minutes in duration.

Currently, two motion pictures are in production which in part are being done aboard the *Queen*. One is the epic film "Titanic," scheduled for release late next year. The other hits much closer to home. In early September or thereabouts, the ARRL will be releasing its new film, "The World of Amateur Radio," produced by Emmy-award-winning filmmaker Dave Bell W6AQ. Thanks to Nate and his organization, Dave was able to film the narration sequences (which feature NBC News correspondent Roy Neal W6DUE) aboard the *Queen Mary*.

Dave has made one request of the amateur community now that the news of the new film has been made public. It will be several months before the film is ready for distribution. Please do not call either Dave or the ARRL requesting the film until its availability has been announced. The initial prints are destined for showing at the World Administrative Radio Conference in Geneva in order to underline the attributes of the worldwide amateur service. Eventually, there will be enough prints for all of us to see, so it is suggested that you monitor *QST*, *HR Report*, The Westlink Amateur Radio News, and this column to find out the availability date. Your cooperation in this regard is deeply appreciated.

Joe Rudi WA6PVA, baseball player with the California Angels, makes the first official QSO from W6RO. Looking on is Nate Brightman K6OSC, of the Associated Radio Amateurs of Long Beach, the club which installed the gear. (Photo by W6VGQ)

THE "THEY-WON'T-LET-220-DIE" DEPARTMENT

The 220-SMA of southern California has gone on record as being willing to take any action necessary to ensure that the 220-to-225-MHz amateur band never falls into the hands of maritime interests. To show that they really mean business, what is called a "WARC Action Committee" was formed at their April 22 meeting, with Ray Von Neumann K6PUW as its chairman.

At present, a number of directions are being considered, although two tend to offer the most promise of at least marginal success. The 220-SMA may well have hired a Washington-based attorney by the time this reaches print. His job will be to go into federal court and either file a direct appeal on the matter or request an injunction barring the use by our WARC delegation of the portion of the US WARC proposal dealing with the 216-to-225-MHz spectrum. It is the 220-SMA's contention that both the FCC and the maritime services may have violated the Federal Administrative Procedures Act in regard to the preparation of that portion of the document. One lawyer explained to me that if the 220-SMA were successful in obtaining such an order, then our delegation would be barred from discussing or voting on issues brought before WARC dealing with that spectrum. This could place the US in a rather awkward position at the conference later this year, but the same legal expert did say that he did not feel the 220-SMA could obtain such an order. I thus suspect that any legal action will come in the form of an appeal. Only time will tell where the 220-SMA will go if they choose this route at all.

Another direct offensive action they are considering—one I expect to see initiated quickly—is filing a formal Petition for Rulemaking with the FCC requesting the immediate transfer of currently unused maritime VHF spectrum to the amateur service. The feeling is that the

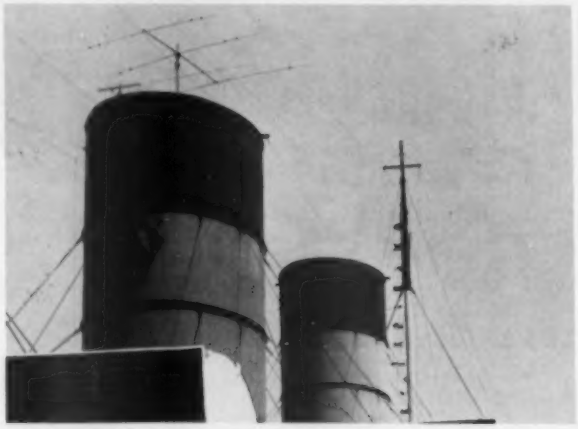

A new triband addition to the Queen Mary. *(Photo by KH6IAF)*

TV actor/comedian Stu Gilliam WD6FBU operates W6RO, the new amateur station aboard the Queen Mary. *(Photo by W6VGQ)*

New MFJ 3 & 1.5 KW Versa Tuners

Run up to 3 KW or 1.5 KW PEP and match everything from 1.8 thru 30 MHz: coax, balanced line, random wire. Built-in balun.

3 KW VERSA TUNER IV's

1.5 KW VERSA TUNER III's

NEW MFJ KW VERSA TUNERS HAVE THESE FEATURES IN COMMON

These 6 new MFJ KW Versa Tuners let you run up to 3 KW or 1.5 KW PEP (depending on the model) and match any feedline continuously from 1.8 to 30 MHz: coax, balanced line or random wire. Gives maximum power transfer. Harmonic attenuation reduces TVI, out of band emissions.

All metal, low profile cabinet gives RFI protection, rigid construction, sleek styling. Black. Rich anodized aluminum front panel. 5x14x14 inches. Flip down stand tilts tuner for easy viewing.

Efficient, encapsulated 4:1 ferrite balun. 250 pf, 6000 volt capacitors. 18 position dual inductor, 17 amp, 3000 V ceramic rotary switch (3 KW version). 12 position inductor, ceramic rotary switch (1.5 KW version). 2% meters. SO-239 coax connectors, ceramic feedthru for random wire and balanced line. One year limited warranty. Made in U.S.A.

3 KW VERSA TUNER IV's

[1] MFJ-984 3 KW VERSA TUNER IV

$299.95 ***EXCLUSIVE RF AMMETER insures maximum power to antenna at minimum SWR. Built-in dummy load.***

This is MFJ's best 3 KW Versa Tuner IV. The MFJ-984 Deluxe 3 KW Versa Tuner IV gives you a combination of quality, performance, and features that others can't touch at this price.

An exclusive 10 amp RF ammeter insures maximum power to antenna at minimum SWR. A separate meter gives SWR, forward, reflected power in 2 ranges (2000 and 200 watts).

Versatile antenna switch lets you select 2 coax lines thru tuner and 1 thru or direct, or random wire, balanced line or dummy load.

A 200 watt 50 ohm dummy load lets you tune your exciter off air for peak performance. Efficient, encapsulated 4:1 ferrite balun.

[2] MFJ-981 3 KW VERSA TUNER IV

$199.95 ***Accurate meter gives SWR, forward and reflected power in 2 ranges: 2000 and 200 watts. 4:1 ferrite balun.***

The MFJ-981 3 KW Versa Tuner IV is one of MFJ's most popular Versa Tuners. An accurate meter gives you SWR, forward and reflected power in 2 ranges: 2000 and 200 watts. Encapsulated 4:1 ferrite balun.

[3] MFJ-982 3 KW VERSA TUNER IV

$199.95 ***Antenna switch lets you select 1 coax thru tuner and 2 coax thru tuner or direct, or random wire and balanced line.***

The MFJ-982 3 KW Versa Tuner IV gives you a versatile 7 position antenna switch that lets you select 1 coax thru tuner and 2 coax thru tuner or direct, or random wire and balanced line. Encapsulated 4:1 balun.

If you already have a SWR/wattmeter, the MFJ-982 is for you.

[4] MFJ-980 3 KW VERSA TUNER IV

$169.95 ***Heavy duty encapsulated 4:1 ferrite balun for balanced lines.***

The MFJ-980 is MFJ's lowest priced 3 KW Versa Tuner IV but has the same matching capabilities as the other 3 KW Versa Tuner IV's.

Features an efficient, encapsulated 4:1 ferrite balun for balanced lines.

1.5 KW VERSA TUNER III's

[5] MFJ-962 1.5 KW VERSA TUNER III

$169.95 ***SWR, dual range forward and reflected power meter, 6 position antenna switch, encapsulated 4:1 ferrite balun.***

The MFJ-962 1.5 KW Versa Tuner III is an exceptional value.

An accurate meter gives SWR, forward and reflected power in 2 ranges (2000 and 200 watts).

A versatile six position antenna switch lets you select 2 coax lines thru tuner or direct, or random wire and balanced line. Encapsulated 4:1 balun.

Black front panel has reverse lettering.

[6] MFJ-961 1.5 KW Versa Tuner III

$149.95 ***6 position antenna switch lets you select 2 coax lines thru tuner or direct, or random wire and balanced line.***

The MFJ-961 1.5 KW Versa Tuner III gives you a versatile six position antenna switch. It lets you select 2 coax lines thru tuner or direct, or random wire and balanced line. Encapsulated 4:1 ferrite balun.

If you already have a SWR/wattmeter, the MFJ-961 is for you.

Black front panel has reverse lettering.

FOR YOUR NEAREST DEALER OR FOR ORDERS

CALL TOLL-FREE 800-647-1800

Why not visit your dealer today? Compare these 3 KW and 1.5 KW Versa Tuners to other tuners. You'll be convinced that its value, quality and features make it a truly outstanding value. If no dealer is available, order direct from MFJ and try it. If not delighted, return it within 30 days for a prompt refund (less shipping). Charge VISA, MC. Or mail check, money order plus $10 shipping/handling.

For technical information, order/repair status, in Mississippi, outside continental USA, call 601-323-5869.

Order By Mail or Call TOLL FREE 800-647-1800 and Charge It On VISA MasterCard

MFJ ENTERPRISES, INC. P. O. BOX 494 ✓M52 MISSISSIPPI STATE, MISSISSIPPI 39762

✓ Reader Service—see page 211

need for this can be easily documented by showing the overall inactivity in current VHF maritime operations and the current growth patterns in VHF amateur activity. Basically, the 220-SMA feels that it is time to stop being on the defensive and become outward and aggressive in fighting to save our spectrum. They hope to rally support not only from 220-MHz spectrum users, but also from the overall amateur community.

Already, some words of support have been voiced, such as the following statement issued by the Jet Propulsion Laboratory's Amateur Radio Club: "The Jet Propulsion Laboratory's Amateur Radio Club supports the 220-SMA of southern California in its efforts to keep the 220-to-225-MHz band an amateur one. To this end we have pledged our support." The JPL ARC did more than just add a bit of encouragement. They also provided the facilities and hosted the meeting.

THE "NAVY-TO-THE-RESCUE—MAYBE" DEPARTMENT

The 220-SMA sent copies of its since-denied Petition for Reconsideration to several government agencies in addition to the FCC. Among those who received copies were the nation's military branches. Just prior to the April 22 meeting at JPL, the 220-SMA dropped what might best be described as a bombshell. It had been contacted by the Chief of Naval Operations and had been told that neither the Chief's office nor the Naval Telecommunications Frequency Management Group had ever been informed of any proposed reallocation of the 216-to-225-MHz spectrum. As it turns out, the Navy has a rather vested interest in this spectrum. It operates what is known as the Space Surveillance Systems Group, a nationwide communications network that keeps track of all space debris resulting from US space operations. In fact, the Space Surveillance Systems Group utilizes frequencies from 216 through 233 MHz, according to an SMA-220 spokesman, and is what is termed a "long-term, high-monetary-investment naval operation."

Needless to say, the Navy is more than just a bit upset over finding out that it may be evicted along with the amateur service from spectrum in which it has a definite interest. Apparently, it is upset enough to have ordered the Telecommunications Frequency Management Group to start a detailed investigation of the matter and report their findings back to the Chief's office. What seems to have irritated them the most were the official statements contained in the WARC position paper itself, rhetoric that said this proposed transition had been cleared with the military prior to its inclusion. If this is true, then I wonder whose military the FCC and maritime services cleared it with. According to the Navy, it wasn't ours.

THE "I-NEED-A-FOREIGN-CORRESPONDENT" DEPARTMENT

Is there an amateur in Geneva, Switzerland, who happens to read Looking West? If so, I need your help. I need a volunteer to act as a Looking West correspondent during the World Administrative Radio Conference later this year. His or her job would be to sniff out any news of what's happening at the conference in relation to VHF/UHF spectrum matters, write same into a monthly synopsis, and forward it to me for inclusion in this column. If you have both the time and interest, drop me a line at the address given at the column's top and we can go from there.

THE "BIG-CHANGE-AT-WESTLINK" DEPARTMENT

Actually, there has been more than one change, but the one that affects most Westlink service users is the discontinuance of their "Cassette Exchange Program." Effective immediately, the cassette program has been replaced by an automated telephone system that permits those wishing to obtain the weekly newscasts to simply dial a telephone number in order to obtain the information.

There were two reasons for Network Director Jim Hendershot to make this decision. First, the Westlink News Service has grown far larger than he ever expected. This is a free, nonprofit service, but he found himself spending virtually every free moment duplicating tapes. He could have gone to a high-speed duplication house to have this work done, but it would have meant going away from the free aspect of the operation and possibly charging upwards of $100 or more annually for the service. This he did not want to do.

Second, there have been ongoing postal problems. Not a week had gone by when a subscriber didn't call to complain that his tape had not arrived or that it had arrived too late to air that week. Consequently, Jim has dropped the cassette exchange system.

There has been a second big change at Westlink. Alan Kaul W6RCL, Bill Orenstein KH6IAF/6, and I recently produced a 20-minute documentary entitled "The Peril to 220" which covered the many aspects of the current situation in that spectrum. The response to that special was so positive that Jim asked us to continue producing such programs on a monthly basis. We have accepted the assignment. In fact, currently in production are programs dealing with the OSCAR satellites, DXing from DX lists, and handling malicious interference.

To accomplish this, a second Westlink studio is being assembled at Bill's office in Hollywood; by midsummer, we should be in full production. Distribution will also be via a dial-in telephone number. We will also be setting up another telephone number so that amateurs can leave input for either the weekly newscast or the monthly "magazine of the air." Those interested in obtaining either or both of these services should contact Jim at the Westlink Radio Network, 8331 Joan Lane, Canoga Park CA 91402. Jim no longer must limit the service to repeaters and bulletin stations, so the service is available to just about anyone.

DX

from page 27

The following information has been provided by OK3BG on OK3TAB/D2A. OK3TAB is Laci Toth who arrived in Angola in March. He went to Luanda on a long business trip and was able to get on the air almost immediately. Laci is using a home-brew transceiver running 200 Watts to a triband quad. Look for him after 1700Z around 21360 kHz or 14250 kHz. He seldom strays far from these frequencies. QSLs have already been printed and you can QSL via OK3ALE or through the OK bureau.

Alex Kasevich W1CDC passes along the word that he is planning an extended stay on Montserrat beginning in August when he will be signing VP2MM. Look for him on CW only in the lower 25 kHz listening up 5. QSL to his home call with an SASE, of course.

The 1978 annual report of the Hong Kong Amateur Radio Transmitting Society lists 56 full members, 31 associate members, and six overseas members. With VS6FE as president, the group has an active 2-meter repeater and conducts the nightly Cantonese Net on 14130 kHz. VS6GW runs the QSL bureau at Box 541, Hong Kong.

The Gilbert Islands become independent on July 10 with the present KH1/VR1 prefixes being replaced by one new prefix. Prefix hunters must be going crazy these days trying to keep up.

14240 kHz and 14275/280 kHz are good areas to monitor for various list-type operations, generally after 2300Z.

Joe Ely 7P8BI reports that anyone needing a card for his 3D6BL operation from September, 1977, to August, 1978, or his present stint in Lesotho can QSL to his new manager, Gary Yarus WB0MSZ, 921 N. Clay Avenue, St. Louis MO 63122.

The Mad River Radio Club managed over 4,000 contacts during the ARRL CW DX Contest from FG7AR/FS7 for a score of some 3.4 million points. All contacts from March 14 to March 20 should be QSLed to K8OCR. Neither FG7AR nor his managers have records for contacts during this period.

The Sorel-Tracy Amateur Radio Club, VE2CBS—Province of Quebec, will sponsor a DXpedition to Zone 2 this month to aid those needing this rare zone to fill out their WAZ Award.

The operation will take place the week of July 21—July 28. They plan to operate all amateur frequencies using both CW and SSB.

As club Public Relations Director Marcel Lapolice VE2EML, would say, "Au plaisir de vous recontrer sur les ondes durant cette semaine de DX-pedition dans le nord de la province de Quebec." Right on, Marcel.

That station on during the WPX contest signing HD1A was a multi-multi operation by K7CA, WA4UAZ, K4ERO, and KA6CNS. HD1 is a special Ecuador prefix and you can obtain a QSL by dropping an SASE to WA4QMQ.

That about covers it for this month. We hope some of the preceding information will help you pick up a few new ones. In the meantime, we are always looking for DX information and photos. Photos can be either black and white or color. We in particular need information pertaining to CW, SSTV, OSCAR, VHF/UHF, and 160 meters. Thanks as usual to the *West Coast DX Bulletin*, LIDXA *DX Bulletin*, and *Worldradio News* for much of the preceding information.

Mt. Sopris, Colorado — In ETO's "back yard" Photo by Douglas J. Martin

ALPHA POWER... Rugged, Cool & Quiet

When you buy an ALPHA linear amplifier you make a long term investment in dependable power and operating pleasure.

You can take your ALPHA for granted — it will go on delivering that big, clean, maximum-legal-power signal no matter how tough the contest or how long the SSTV or RTTY QSO's.

We strive constantly to make every ALPHA even better. If we can't improve it, we don't change it.

DURABILITY? You get TWO YEARS of factory warranty protection with your new ALPHA . . . other manufacturers give you 90 days.

CONVENIENCE? Every ALPHA is self-contained, compact, and smooth-tuning. All 76A - 374A - 78 models can be shipped via economical, door-to-door UPS.

VERSATILITY? The new ALPHA 374A delivers full legal power (in any mode) on all amateur HF bands WITHOUT TUNE-UP and with excellent efficiency. (On 160M you peak the output manually; new FCC rules permit easy owner modification to restore full 10M capability, too.)

The ALPHA 78 combines the best of everything: full instant CW break-in (QSK) and NO-TUNE-UP bandchange! And of course all ALPHAs substantially exceed every applicable FCC requirement.

For detailed literature and fast delivery of your new ALPHA, contact your dealer or ETO direct. While you're at it, ask for a free copy of our brief guide, *"Everything You Always Wanted to Know About (Comparing) Linears . . . But Didn't Know Whom to Ask."*

ALPHA — Sure you can buy a cheaper linear . . . But is that <u>really</u> what you want?

ETO Ehrhorn Technological Operations, Inc.
P.O. Box 708 · Cañon City, Colorado 81212 · (303) 275-1613

New Products

Micronta 12-volt 8-Amp power supply from Radio Shack.

from page 24

Radio Shack stores and dealers. *Radio Shack, 1300 One Tandy Center, Fort Worth TX 76102; phone (817)-390-3272.*

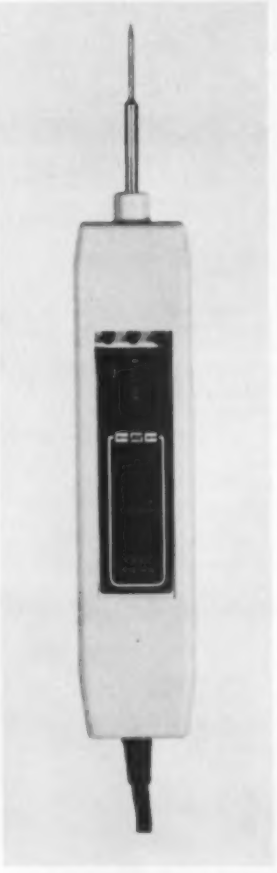

LPK logic probe from CSC.

CSC LOGIC PROBE KIT OFFERS KIT-BUILDERS MULTIPLE BENEFITS

For Continental Specialties Corporation, already well known as a manufacturer of professional digital troubleshooting instruments, their first kit-style test instrument logically emulates their line of logic probes. Both as a kit and as a probe, the CSC Model LPK Logic Probe Kit represents an excellent value.

The kit instructions are exceptionally well-written, offering step-by-step assembly procedures. Solder, wire, and all miscellaneous hardware are included in the kit—along with the printed circuit board, case, and all components, of course—leaving no extras to buy. Even beginning-level kit-builders can assemble the LPK quickly.

Once assembled, the LPK offers respectable performance as a logic probe. It is circuit powered through attached clip leads. HI, PULSE, and LO LEDs display logic states and transitions. The high logic state is defined as 70% or more of the supply voltage, the low state as 30% or less, making the probe compatible with most digital logic technologies or families. With its high (300,000-Ohm) input impedance, circuit loading is minimized.

With the LPK, even very narrow pulses can be detected. Internal circuitry stretches pulses as short as 300 nanoseconds into 1/10 second flashes of the PULSE LED; pulse trains at repetition rates up to 1.5 MHz keep the PULSE LED flashing.

The LPK includes self-protecting circuitry which permits the power leads to be connected in reverse or to as much as 25 V dc without permanent damage; the probe tip, similarly, can contact ±50 V continuously or 110 V ac for up to 15 seconds without permanent damage to the probe.

As a troubleshooting tool, the LPK holds its own against any logic probe in all but very high speed applications. As an educational venture for the kit-builder, it should be noted that the LPK, while a digital tool, is based on analog circuitry, offering a unique opportunity to see how the two disciplines merge.

The LPK Logic Probe Kit is available through selected local distributors both in the US and around the world.

For more information, or for the name of your nearest CSC stocking distributor, call *Continental Specialties Corporation, 70 Fulton Terrace, New Haven CT 06509; phone (203)-624-3103, TWX (710)-465-1227.* Reader Service number C9.

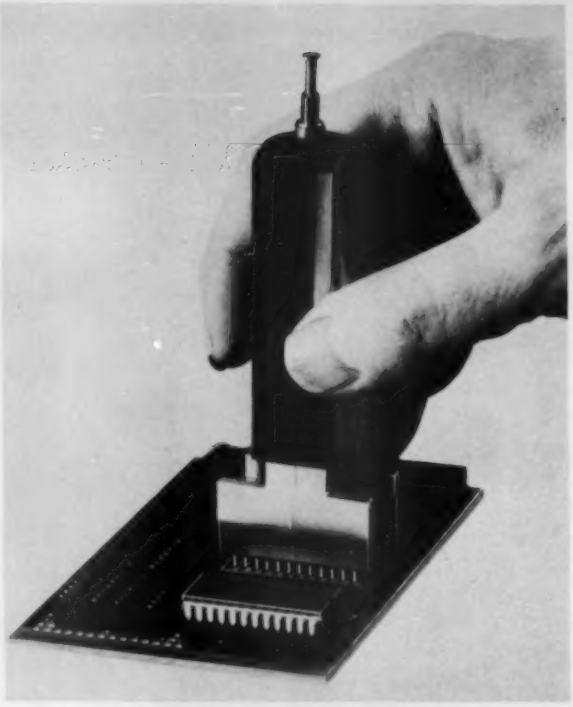

IC Insertion Tool from OK Machine and Tool.

IC INSERTION TOOL

The new Model MOS-2428 DIP Inserter handles all MOS, CMOS, and regular 24- and 28-pin ICs. This unique new insertion tool also aligns bent-out pins. Simply rock the IC on the straightening saddle to align the pins. Press the tool over the IC to pick it up, then simply place the tool onto the socket and depress the plunger for instant and accurate insertion. The tool features heavy chrome plating throughout for reliable static dissipation. It includes a terminal lug for attachment of a ground strap. The MOS-2428 IC Insertion Tool is available from your local electronics distributor or directly from *OK Machine and Tool Corporation, 3455 Conner Street, Bronx NY 10475.* Reader Service number O5.

FREQUENCY COUNTER PREAMP

This general-purpose counter preamp has up to 25 dB gain from 10 MHz to 1 GHz. Designed to front-end a frequency counter's 50-Ohm VHF/UHF input, the AP-8015 preamplifier can be used with an antenna or pickup loop as well as be direct-coupled to allow low-level signal sources to be counted. The AP-8015 includes a 115 V wall plug transformer for ac operation as well as a dual 9-volt battery harness for portable operation. The preamp is enclosed in a heavy-duty anodized aluminum case. Size: 4-1/8" L x 2-1/4" W x 1-1/4" D. Weight: 6 ounces. For orders or information, contact *Optoelectronics, Inc., 5821 N.E. 14th Avenue, Ft. Lauderdale FL 33334; phone (305)-771-2050/1.* Reader Service number O3.

FSK-1000 DEMODULATOR FROM IRL

"This is not a sedan or a truck. This is a sports car."

That's how the engineers at iRL describe their new FSK-1000 demodulator.

The FSK-1000 is a new, sophisticated, two-tone limiterless demodulator which offers selectivity as narrow as 55 Hz in each of its matched, selectable-bandwidth, active-filter tone channels. Although it includes such "extras" as continuously adjustable shift, dual-mode autostart, and a keyboard-activated switch, the designers insist, "We don't want a family sedan dressed up with mud flaps and raccoon tails. We want to give the serious HF or VHF operator a TU with the best raw performance available anywhere."

The FSK-1000 has both high-voltage current loop and low-voltage (RS-232 compatible) outputs to interface readily with mechanical teleprinters, computers, or both.

Receiver tuning requires a careful touch with the narrow filters switched in, but this gives the serious operator the selectivity he needs when the QRM gets really bad.

The FSK-1000 circuitry utilizes 48 operational amplifiers (twenty FET types) and a host of other devices. Complete details are available from iRL dealers or by writing *iRL, 700 Taylor Road, Columbus OH 43230.* Reader Service number 127.

NEW RTTY TERMINAL FROM HAL

HAL Communications is proud to announce a new compact and low-cost RTTY terminal—the DS2000 KSR. The new terminal features operation with Baudot, ASCII, and Morse codes (Morse receive optional) and incorporates many of the features of more expensive terminals. A new 72-character line by 24-line display format, two 32-character programmable "Here Is" messages, and CW identification at the touch of a key simplify operation. A terminal-status line keeps the operator aware of data rate, data code, and other terminal conditions. Text is transmitted one word at a time and editing is possible anywhere in the line being composed. All terminal functions are controlled by a combination of a control key and a key from the top row of the keyboard. Other deluxe features such as unshift-on-space, synchronous idle, keyboard-operated switch, and both QBF and RY test messages are available at the stroke of a key. Connect the DS2000 KSR to a standard 18-120 mA, 200 V dc (maximum) current loop for Baudot and ASCII operation. Morse output is accomplished via a transistor switch to ground for keying either "grid-block" or "cathode" circuits. An optional Morse receive board (MR2000) is available for reception of Morse code at rates from 1-175 wpm and is customer installable allowing purchase at any time. An optional 9-inch diagonal measure video monitor is also available. The terminal weighs 6 lbs. (2.75 kg) net (10 lbs/4.55 kg shipping) and comes in an attractive blue and beige cabinet. Contact *HAL Communications Corp., PO Box 365, Urbana IL 61801,* for further information.

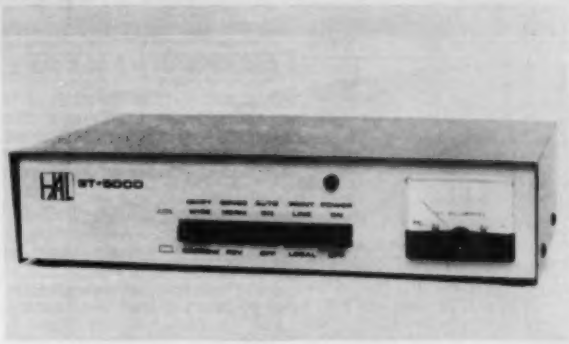

DS2000 RTTY terminal from HAL.

ROHN NO. 25 FOLD-OVER TOWER

When an amateur thinks of towers, chances are that he thinks of Rohn. And for good reason. Rohn has been building towers for a long time, providing amateurs with a variety of top-quality models at a reasonable price.

Recently, when I needed a new tower, my thoughts turned naturally enough to Rohn. Getting out their catalog, I thumbed through it to see just what they had to meet my particular requirements. After a few minutes of browsing, I decided that the 48-foot No. 25 Fold-Over was just what I was looking for.

Among the considerations I had in mind while choosing a new tower was that it get my beams clear of adjacent buildings and trees but not be so tall as to stand out prominently from its surroundings. As a result, I concluded that it should be approximately 50 feet high. And, since I prefer to keep my feet firmly on the ground, it should fold over so that work on the beams and rotor could be done from the ground or, at most, while standing on a short stepladder.

I also felt it highly desirable that the tower be easily assembled and disassembled by two people. And the likelihood that I would want to relocate it within the foreseeable future meant that it should be readily transportable, preferably in a small pickup or van. In addition, it should be rugged, durable, and easy and inexpensive to maintain. And, of course, it should be affordable.

The more I studied the Rohn catalog, the more I became convinced that the No. 25 Fold-Over was the answer. While I had never owned a Rohn tower, I was quite familiar with those used by friends and had been very favorably impressed by what I had seen. I liked the way they stood up to everything from hurricane winds in my native Florida to severe New England ice storms.

No. 25 towers utilize heavy-duty 1¼-inch-diameter #16-gauge steel tubing for side rails in a 12½-inch equilateral triangular design with solid-steel zig-zag cross pieces, entirely electrically-welded and fabricated by precision machines. There are 8 zig-zag steps per 10-foot tower section. Design and construction enables No. 25 towers to be installed at guyed heights up to 200 feet.

The tower's hot-dipped zinc galvanizing provides protection from rust and corrosion. A minimum molten zinc coating of 2 ounces for every square foot of surface fuses permanently to the metal, becoming an actual part of the steel so that it cannot be separated. Also, the tubular steel used in the towers is coated both inside and out to provide protection against deterioration from condensation and moisture. If a galvanized surface becomes scratched or chipped, the surrounding zinc actually "heals the wound" and continues to seal out corrosive elements.

Double-bolted joints are used to join tower sections for sturdiness and dependability. The No. 25's strength allows it to be self-supporting, provided a house bracket is used; it can go 35 feet above the bracket under normal conditions. A 200-foot No. 25 tower will withstand a 30-lb.-per-square-foot wind load—equivalent to 86.6 mph true wind velocity—when guyed and installed according to the manufacturer's specifications. This includes an antenna with an area of 6 square feet as well as 2 transmission lines. Those figures made me confident that a 48-footer with the sort of antennas I planned to use should be almost indestructible under typical New England weather conditions.

One of the things I like best about the No. 25 Fold-Over is the variety of mounting options that are available, covering virtually any situation you're ever likely to face. In addition to the more or less standard short base section for concrete, there is a hinged version for mounting in concrete, hinged and non-hinged base plates for use with concrete, plus mounts for flat and peaked roofs. And, also available and especially handy for Field Day are a single drive-in base and a base plate for use with drive rods. If you can't guy, or you simply prefer not to, there are several sizes and types of house- and eave-brackets available. In my own case, I decided to install the tower at the rear of the barn using a house bracket for support.

In choosing a location for the tower, care should be taken to ensure that it will be well clear of trees, wires, buildings, and other objects, to permit a free swing of the hinged portion of the tower and antenna. If guys are to be used, the location should be suitable for placing four guy anchors at the appropriate distances.

The work begins with the digging of a hole 30 inches square by approximately 36 inches deep. After spreading a couple of inches of gravel in the bottom of the hole, attach the base section to the first 10-foot section and set the assembly on the gravel. Then spread another 3 inches of gravel around the legs of the base. This allows the tower base legs to extend the required amount below the base of the concrete, thus allowing for drainage of moisture into the gravel.

Before pouring the concrete, coat the base section over an area about 3 inches above and 3 inches below the space where the top of the concrete base will be, using a water-proof asphalt-type material. If the tower is situated near a building, be sure that the base is set so that two of the tower legs lie in a plane perpendicular to the wall of the building. This will cause the hinge axis to also be at right angles to the wall, and the tower will fold clear of the building. With the base set, pour the concrete around it and check its plumb with a carpenter's level on one or more of the legs of the tower. The top of the concrete should be slightly crowned to

prevent water accumulation.

It's a good idea to allow at least three days for the concrete to harden before continuing to erect the tower. An erection fixture or gin pole will make the process easier and faster, especially if you decide to add one or two additional 10-foot sections, bringing the total height to 58 or 68 feet.

If you're doing a 48-footer like mine, you place the hinged section atop the second 10-foot section, making sure the shipping-tab bolt is closed and that the hinge is positioned on the correct side of the tower. Guy wires (if used) are then installed on the guying tabs near the hinge point. The next step is to align and bolt together the two pieces of the boom (lever) section. The boom is then attached to the hinged section. Be sure the hinge bolts are loosened before you attempt to fold the tower over. If practical, a house- or eave-bracket may be used at the hinge point in place of guy wires. The bracket must be placed within 2 feet of the hinge point.

The remaining sections are lifted into place and installed in the usual manner. Next, the winch and cable mechanism is bolted to the leg of the lower tower section, just below the clevis on the boom. If an additional 10-foot tower section has been placed below the hinge section, an extra pulley must be installed just below the clevis on the boom. Finally, the cable must be secured with clamps and a wire rope thimble to the boom clevis and to the winch.

That's all there is to putting up a Rohn No. 25 Fold-Over tower. The installation instructions are quite simple and straightforward. Follow them and you'll get your tower up quickly, easily, and, most important of all, safely!

Once the hole is dug and the base assembly is installed, two people can complete the job in a morning or afternoon, including mounting a rotor and beam. Then you can sit back and enjoy operating, secure in the knowledge that if you pull routine preventative maintenance a couple of times a year and take prompt care of anything that crops up between times, you'll have a setup that should provide many years of reliable service.

While the 48-foot No. 25 Fold-Over tower proved just right for me, it may not be what you need. In that case, you should check out the other versions of the No. 25, as well as the many other models available from Rohn. For more information, write *Unarco-Rohn, a Division of Unarco Industries, Inc., 6718 West Plank Road, PO Box 2000, Peoria IL 61656.* Reader Service number U2.

Morgan W. Godwin W4WFL
Brattleboro VT

LETTERS

from page 10

windows at the higher elevations to Midland, El Paso, and Carlsbad. For the NBVM QSOs, we are carrying a GE Microcassette recorder.

All radio systems will be powered directly, without the use of a battery, from a 72-cell solar array which weighs four pounds. Limited night operations from dark to bedtime will be powered by a palm-sized nicad battery. Antennas will be half-wave slopers or quarter-wave radiators against quarter-wave counterpoises, as most of that area offers a very poor rf ground.

On-the-air operations will occur according to the following schedule, beginning as early as midday Sunday; listen for CQ NBVM from K5SBU on NBVM, SSB, and CW.

0600 CDT/1100 UT	14,235 kHz
0700 CDT/1200 UT	7,195 kHz
0900 CDT/1400 UT	14,235 kHz
1000 CDT/1500 UT	28,85 kHz
1100 CDT/1600 UT	21,385 kHz
1230 CDT/1730 UT	7,195 kHz
1500 CDT/2000 UT	21,385 kHz
1700 CDT/2200 UT	14,260 kHz
1900 CDT/0000 UT	14,385 kHz
2000 CDT/0100 UT	21,385 kHz
2100 CDT/0200 UT	14,260 kHz

The first Texas NBVM station, Bob W5GEL (W5BT), will be on frequency to coordinate, as his time allows. We would be pleased to QSO with any mode and will listen carefully for other QRP stations and DX stations. All NBVM stations should be prepared to tape-record QSOs; send the tape with your QSL. If we can find our tape of the QSO, it will be recorded on the blank side of your tape and returned.

The signal from K5SBU will be very weak, so tune slowly. Ten minutes after the schedule time, if we do not have a QSO, we may QSY to the QRP CW calling frequency for that band (60 kHz up from the bottom of each band). QSL to address below.

C. Richard Hoffman K5SBU
Box 1600
Corpus Christi TX 78403

WAYNE GREEN'S LAIR

I found this editorial, *Wayne Green's Lair* (*VHFER*, Vol. 1, No. 5, September, 1963, Comaire Electronics, Ellsworth MI), written some time ago by Doug DeMaw (Senior Technical Editor, ARRL) and thought you might be interested.

Wayne Green's Lair

The trip would not be complete without a visit to "73 Acres" in Peterborough, N.H. Never before have we been greeted with such hospitality and friendliness. No one should sojourn through N.H. without meeting this dedicated man, his wife, and his staff, who have completely thrown themselves into the cause for improved amateur radio conditions. We enjoyed our overnight stay at W2NSD. A personally prepared waffle breakfast, by the "Ed." himself, with New Hampshire pure maple syrup and all the trimmings and garnished with a vigorous discussion related to the controversial matters of the day (which are destined to affect all ham radio operators) was very invigorating.

For many months I have tried to understand this man Green's motives and his attacks on other publishers and organizations, but until I met this guy face to face, I could not properly evaluate his thoughts. I am convinced through seeing the results of his publishing house efforts, listening to his explanation of his convictions, and hearing him relate his hopes for the ham fraternity and its future, that he is neither vindictive nor radical. He believes in what he is doing, and is willing to fight for those who share his beliefs.

Wayne's empire includes a mountaintop location a few miles distant from his main facility, which is composed of numerous sky wires, a farm house and a magnificent 125' tower supporting 96 elements on 2 meters. Along with all this, a mountain of radio gear reposes in the "shack" and is presently being assembled into operating positions of one kW denomination for all bands.

All in all, we were mighty glad to meet Wayne, his charming XYL, and staff. They are truly a wonderful group. Don't miss stopping at Peterborough when you are in that area.

I have been reading your magazine since its beginning, and I even went on the *73* trip to Europe. I still think you are one of the good guys.

Wm. Edwards K8DNV
Bellaire MI

GUATEMALA '76

One of my favorite pastimes is handling traffic from the nets as fast as I am able. Although the messages that are handled are of the health and welfare type, there is a certain amount of satisfaction which one gains in being able to deliver the message in the least amount of time. Until recently, the practice did not appear too important, but after several proddings by my fellow hams on various nets, I agreed to jot down the details of the contact that took place during the Guatemala earthquake in 1976.

Without any doubt, a major part of the credit for saving lives and organizing the rescue effort during the disaster is due to that very fine group of amateurs that carried the greatest load in and around Guatemala City. Our efforts at the time were devoted to assisting wherever we could and fitting into any circumstance where help was needed. For a time, the traffic was picked up from the Interstate Net on seventy-five in the evening and relayed to the Guatemala City stations the first thing the following morning. Many nets were utilized to ensure the most expeditious handling of the traffic.

During this time, not very many minutes passed when there was a lack of traffic. On February 14, 1976, an amateur station in Peru, OA4CYC, called. It seems that Maria OA4CYC had tried for several days to secure information on two sisters in Guatemala City and had probably monitored the traffic being passed on to the Guatemala City station, TG9DF, which she was unable to hear. After gaining our attention and the verification of callsigns, Maria asked for our help.

After trying for the previous three days by telephone and wire services, Maria wanted to know if it would be possible to secure health and welfare information on the two sisters who were in Guatemala City. On securing the details from Maria in Peru, the information was relayed immediately to Don TG9DF. He recognized the location where the two sisters were, or would be, in the city and indicated that he would try to reach that point via the local telephone system. In less than five minutes, Don had the answer for Maria: "The two sisters were not injured, were feeling fine, and were working hard."

That message was relayed to Dayton OH and then to OA4CYC in Peru within eleven minutes of the moment the message was

received. This was amateur radio in action, and a small example of the real-life drama that can occur.

This short experience of mine would not even have been in print had it not been for my friends and fellow amateurs who pointed out that the benefits afforded by amateur radio would be far greater if the story was put in print.

Paul Weigert, Jr. W8TH
Centerville OH

NEEDED LESSON?

I had no complaints about Bill Pasternak's Looking West column until now, but since he went over to the Int'l HFers Headquarters and was baptized, it seems to me that he may be needed more in their Fox Tango Newsletter than in *73*. These people haven't changed a bit—they still espouse and promote illegal, scofflaw bootlegging outside of the CB band. But I guess even Pasternak is no exception—California is a veritable hotbed of illegal activity—must go along with the kook philosophies prevalent out there in the Land of the Cults.

CB neighbors of mine are in receipt of several letters from various printing callbooks (phoney calls and first names only, of course) and operating QSL card bureaus out of PO boxes. For anywhere from two to ten dollars, you can get a 2 Echo, 19 Whiskey, TCN66, or whatever happens to be in vogue at the moment, plus your QSL cards forwarded to your QTH monthly! Neat.

What I can't understand is how some of them can "guarantee" that the FCC will leave them alone "if they use their Echo call and only operate on certain frequencies." Another club claims that they have "advance notice" when the FCC is going to appear in a given area! Is the FCC really cooperating with these bandits?

Another thing I fail to understand is why the FCC can't seem to find these people, even though the same ones are on the air every day, day in and day out, and talk for hours! Even an idiot could drive up to their door with a simple receiver with no S-meter!

At least (so far) most of the nitwits have had the good sense (or are afraid) to stay out of the 10-meter ham band. But I'd like to see the FCC legalize 27.4 to 28.0—*then* "superior" ones would surely move into ten. There is a certain type of CBer who just *has* to operate illegally, even if there's no reason to. This type will eventually take over and ruin what's left of ham radio.

Frankly, I'm hoping that WARC '79 will give all our ham bands to the minority countries. It might teach the whole damned bunch of us a much-needed lesson!

William L. Harris KN9FOV
Lafayette IN

ASHAMED

This isn't really a letter to the editor, but I thought you should know that Stan Jopek K2JQT passed away on April 13, 1979. Stan was 40 years old and in excellent health, but he had a sudden fatal heart attack. He leaves his wife, Joan, and four teenage children. Stan was very active on six meters in the past, and was more active recently on 2 FM as the owner/operator of the .07/.67 repeater in Fredonia NY.

As tragic as Stan's sudden death was, subsequent events were repulsive, and they were the reason for this letter. One day after his death, while the family and friends were at the funeral home, someone broke into the .07/.67 repeater site and stole the entire machine and backup systems. The total value of the loss was over $3800.

What I find most repulsive in this is that the theft had to have been done by hams. The .07/.67 repeater was located in a remote area, and very few people even in amateur circles knew its exact location. It was located in a building along with several other commercial repeaters and transmitters which were much more valuable, less traceable, and much more portable. These units were not touched. The thieves were thorough. They even searched out the manuals for the 2-meter gear and took them also; they pig-tailed off the power leads, took the input tags for identification, and even taped up the leads to the stand-by batteries.

A four-wheel-drive vehicle was used, and at least two people carried the 6' high 19" rack over the muddy ground to the vehicle. The theft is being investigated by the Chautauqua County Sheriff's Department, and any information should be forwarded to them at (716)-672-5151. The Spectrum 1000 serial number is 0219.

I feel confident that a theft of this magnitude and perfidy will be solved. I only hope that the persons responsible are apprehended by the authorities rather than members of the repeater club. This is the first time I've ever really been ashamed of being a ham.

Ron Warren WA2LPB
Fredonia NY

JUST GETTING ON THE AIR?
See Adirondack for

☐ New Equipment
☐ Used Gear
☐ Friendly Advice

ADIRONDACK Radio Supply
185-191 West Main Street • P.O. Box 88
Amsterdam, N.Y. 12010 Tel. (518) 842-8350
Just 5 minutes from N.Y. Thruway—Exit 27

FLESHER CORP.
RTTY made easy !

TR-128
NEW FROM FLESHER

*RTTY REGENERATIVE BAUD RATE CONVERTER
TTL compatible connections for direct hook-up to the TU-170, also adaptable to other units.

- Five standard baud rates
- Stable crystal-controlled oscillator
- 128 Character storage capacity with storage status meter to show buffer fill
- Continuously variable character rate

Wired $239.95 Kit $169.95

TU-170
TERMINAL UNIT

Connect to your receiver speaker, transmitter microphone jack, and teletype machine and you're on the air. Ideal for HF and VHF auto start operation.

- Autostat with threshold control and solid state relay
- Stable audio frequency shift oscillator produces phase coherent sine wave tones
- TTL compatible inputs and outputs for auxilliary equipment
- High level output for scope tuning

WIRED $234.95 KIT $159.95

Flesher products . . . the critics choice!
FLESHER CORP.
P.O. Box 976 Topeka, Ks. 66601 913/234-0198
Add $3.00 for postage and handling.

The LEADER In the Northwest!

ATLAS • ICOM • KENWOOD • YAESU

Come to **ABC Communications** today for the best solution to your particular communication requirements, whether they be Amateur, Two-way Business Band, VHF Marine or Police Scanner.

Kenwood 7625
2m FM Transceiver

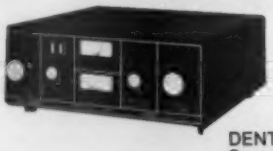

DENTRON MT-3000A
Deluxe Tuner

DENTRON 160-10 AT (not shown)
Super Tuner

TS 180S

TS 120S

Kenwood 7600
2m FM Transceiver

NATIONWIDE NUMBER

Call 206-364-8300 to place your order.

We will pay for call when order is shipped.

ICOM Transceiver 2M FM
SSB IC 211

ICOM—IC280

YAESU 901 DM

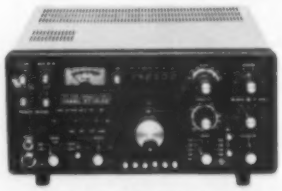

Yaesu FT101ZD

ABC COMMUNICATIONS

17550 15TH AVE. N.E. • SEATTLE, WASH. 98155 • (206) 364-8300

A46

We also handle Wilson, Cushcraft, Hy-Gain, Antenna Specialists, KLM, etc.

Attention Washington residents: Come on in for excellent service in our complete Communications Repair Shop.

Write or call for SPECIAL tower, rotor, antenna package! Tri-Ex, Rohn, Wilson Towers. Shipping info: F.O.B. Seattle via UPS, truck, or parcel post.

Washington residents add sales tax.

Other locations: (Walk-in customers only) • Bellevue — 12001 N. E. 12th • Everett — 4610 Evergreen Way • Open Mon. thru Sat.

RESETTABLE TO EXACT FREQ.--BASE TUNED WITH LOG

STAINLESS STEEL WHIP--FIBERGLASS LOADING COIL--PATENT APPLIED

ANTECK, INC.

A80

BOX 415
RT. 1
HANSEN, IDAHO 83334
(208) 423-4100

master charge

VISA

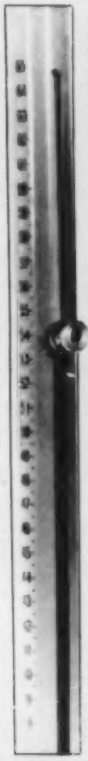

NO COILS TO CHANGE--NO TUNERS REQUIRED--POSITIVE TUNING LOCK

The model MT-1 Mobile Antenna tunes 3.5 to 30 MHz inclusive. 750 WATTS for HAM BANDS, MILITARY, MARS, MARINE, and C.B. Center Loaded for high efficiency. EXACT RESONANCE. FULL OUTPUT from Finals. Base tuned with logging scale and correlation chart from logging scale to Freq. Max. length—116 inches at 3.5 MHz Min. length—92.5 inches at 30 MHz. 3/8 x 24 Std. Mt.
SEE AT YOUR LOCAL DEALER OR ORDER DIRECT
$119.95 EA.

DEALERS—(Inquiries invited)

Clegg Communications **Lancaster, Pennsylvania**	**Conley Radio** **Billings, Montana**
Quement Electronics **San Jose, California**	**Radio World** **Oriskany, New York**
Ross Distributing **Preston, Idaho**	**C-Comm** **Seattle, Washington**
Omar Electronics **Durand, Michigan**	**Colville Amateur Supply** **Colville, Washington**
Burghardt Amateur Center **Watertown, So. Dakota**	**Cohoon Amateur Supply** **Santa Maria, California**

LESS THAN 1.5 VSWR (ENTIRE TUNING RANGE)

CoaxProbe*

Coaxial RF Probe for Frequency Counters and Oscilloscopes That Lets You Monitor Your Transmitted Signal Directly From the Coax Line.

Only **$9.95**
plus 1.00 postage

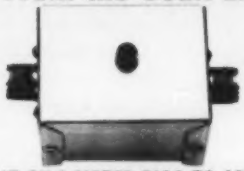

FINALLY! A RF PROBE that lets you connect into your coax cable for frequency measurements and modulation waveform checks directly from the transmitter.

JUST CONNECT THE CoaxProbe* into your transmission line and plug the output into the frequency counter or oscilloscope. Insertion loss is less than .2db so you can leave it in while you operate.

A NECESSITY IN ANY WELL-ORGANIZED HAM SHACK, the CoaxProbe* eliminates "jerry-rigging" and hassles when tapping into the coax line is desired.

A SPECIAL METHOD OF SAMPLING keeps output relatively constant with a wide variation of power. Power output of 8 watts gives .31v out, while 800 watts will give 1.8v out. (rms 3-30 mhz.) 2000 watts PEP rating too!

*Trademark of Eagle Electronics.

USE IT ON 2 METER RIGS TO ADJUST FREQUENCY. The CoaxProbe* has a range of 1.8 to 150 mhz.

MONITOR YOUR MODULATION WAVEFORM. With an oscilloscope of proper bandwidth, you can check your modulation for flat-topping, etc. Ideal for adjusting the speech processor.

NOW YOU CAN MONITOR SIGNALS when connected to the dummy load, eliminating unnecessary on-the-air radiation.

AVAILABLE FOR THE FIRST TIME TO AMATEURS. Try it for 10 days. If not satisfied, send it back for refund (minus shipping charges).

Order today from:

Eagle Electronics

Box 426 D, Portage, MI 49081
Michigan Res. Add 4% Sales Tax

SECOND ANNUAL LITTLE ROCK HAM-A-RAMA
Aug. 4 & 5, 1979
9:00 a.m. to 6:00 p.m. Saturday
9:00 a.m. to 2:00 p.m. Sunday
(Dealers may set up Friday evening)

ARKANSAS STATE FAIRGROUNDS
LITTLE ROCK, ARKANSAS

- ★ Dealer displays in air-conditioned building
- ★ ARRL-approved hamfest with ARRL booth in display building
- ★ ARRL forum and MARS meeting
- ★ Giant flea market, $2 per parking space
- ★ Party Saturday night
- ★ Covered flea market area in case of rain
- ★ No commercial dealers in flea market area
- ★ RV hookups on fairgrounds and two KOA campgrounds within 20 miles
- ★ Hamfest located 2 miles west of I-30 on Roosevelt Road
- ★ Talk-in on 146.34/.94
- ★ Hourly door prizes plus 2 major prizes
- ★ For further information contact:

Morris Middleton AD5M
19 Elmherst Drive Dept. B
Little Rock, Ark. 72209
Phone (501)-568-0938

Key Electronics

GRI

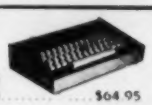

Full ASCII Professional Keyboard Kit, Model 756

Model 756 Keyboard Kit		$64.95
Model 701 Plastic Enclosure		$14.95
Model 702 Steel Enclosure		$29.95
INTEGRATED CIRCUITS:		
SN76477N Complex Sound Gen	$2.95	2/$5.50
CA3140 Op Amp		.60
CA3240 Dual Op Amp		$1.10
uA555 Timer		.45
SOCKETS:		
8 pin Low profile	15	8/$1.00
14 pin Low profile	19	6/$1.00
16 pin Low profile	22	5/$1.00
Transistor Socket	12	10/$1.00

FREE: CA3140 with orders of $5.00 or more
Please include $1.00 for postage and handling
N.Y.S. Residents Add 4% Sales Tax
Send to: Key Electronics
P.O. Box 3506
Schenectady, NY 12303

K14

Ham Help

If anyone has a Heathkit HW-20 Pawnee (2m AM tunable xcvr) that is physically complete but not necessarily operating, I am interested in purchasing it. Please state whether or not the manual would be included. I will be happy to pay shipping via UPS.

Wm. C. Aycock WB5YEE
257 Belair Dr.
Pearl MI 39208

Our radio club has been given an old US Coast Guard receiver, model R-649/UR, made by Hallicrafters. Can anyone help me find a schematic for it? Thanks.

Thomas Dick WA9QDZ
2851 Wayside Dr.
Evansville IN 47711

I desperately need the schematic for a Hy-Gain UHF 4-channel pocket scanner. Any help would be most appreciated.

Dennis Lemonds WB4QCD
PO Box 194
Estill Springs TN 37330

I have a 0-500-MHz frequency counter made by Northeastern Engineering, Inc., Model 14-20C. The counter is a large unit, about 75 lbs. and two feet square with tube-type design using nixie tubes for the frequency readout. I've been trying to find a manual for this gear with no success thus far. Fair Radio Sales can offer a schematic but no manual. Can anyone out there help me? Any effort would be greatly appreciated. Thank you.

R. W. Bowyer KA4DTP
7335 Sunnybrook Dr.
Roanoke VA 24019

I bought a Kenwood TS-520S and have never felt like I have the tune adjustment right for best resonance of the final 6146Bs. The book furnished isn't too clear. Could anyone help me by explaining the proper procedure for adjusting this rig?

A. E. Farrell KA5DFV
4324 S.E. 16
Del City OK 73115

I would like to know what the boom length and element spacings are on a TA-33 Jr. Mosley triband: The moving company lost my boom.

Hubert J. Harlow KA5COS
1812 Arnold Palmer
El Paso TX 79935

I need a relay coil for a Central Electronics 20-A SSB exciter. Please give price.

Odell Gatlin W4MEM
R#1, Box 279
Killen AL 35645

I need the schematic for an old Hallicrafters receiver, model number SX77A or S-77A. Can anyone help?

P. B. Bjorklund
1075 Los Altos Ave.
Los Altos CA 94022

I need a Tempo One external vfo.

Keith H. Gilbertson WB0LXM
Rt. #4, Box 29A
Detroit Lakes MN 56501

I would like to arrange a CW 15 meter QSO with a Vermont ham in order to complete my WAS.

Bob Cent WB7UNM
US PHS
Rocky Mtn. Lab
Hamilton MT 59840

ONE FEEDLINE—MULTIPLE ANTENNAS—NO WIRES WITH INLINE "wireless" coaxial relays you can expand your antenna system, adding nothing but antennas.

INLINE'S exclusive coaxial coupler at the radio energizes a weatherproof relay/s mounted on the tower, pole, tree, or wherever the antennas are via any length coaxial cable. Using more than one antenna lets you reach out further because you can instantly compensate for changes in propagation or signal path conditions. You can also change bands, or polarization, or phase arrays. You can eliminate a rat's nest of wires. Ideal for apartment dwellers.
INLINE relays are in constant use worldwide, in more than 100 countries, in any conceivable climate, by Amateurs, International News Services, Embassies, Cable TV, Government Agencies, Airlines, Etc. where reliable communications is a must.

Two position relays

Type 101*	DC to 550 MHz	2000 W PEP	$31.45
Type 103	20 to 550 MHz	1000 W PEP	43.45
Type 105	1.5 to 180 MHz	2000 W PEP	53.45

Three position relays

Type 1013*	DC to 550 MHz	2000 W PEP	48.45
Type 1033	20 to 550 MHz	1000 W PEP	60.45
Type 1053	1.5 to 180 MHz	2000 W PEP	70.45

*(not "wireless" controlled — use 1 wire + Gnd.)

Literature and application data on request.

If not in stock at your dealer order direct.
Prepaid orders shipped free via UPS only in USA

INLINE INSTRUMENTS, INC. ✓139
Box 473, Hooksett, N.H. 03106 Tel. (603) 622-0240

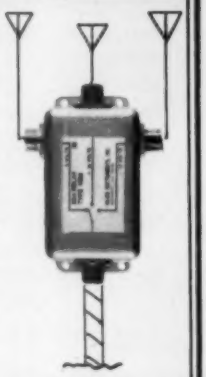

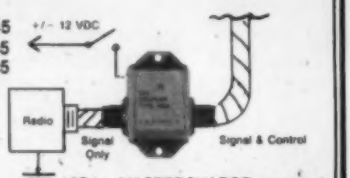

VISA - MASTERCHARGE accepted

RT-524M TRANSCEIVER

Covers 136.00 to 149.95 Mhz in 50 Khz crystal-controlled steps; 15 watts output. Has volume and squelch controls; requires 27 VDC 6 amps. With tubes 8156, 2/8102, 6/6CW4, and 2/7587. O/A size: 6-3/8x3-1/2x14; 10 lbs. sh. Used, no covers **$54.95**

R-390A/URR RECEIVER: 2 to 32 Mhz AM in 1 Khz steps; mechanical filters. Used reparable **$295** Checked ..... **$450** Manual **$12.00**

VACUUM VARIABLE CAPACITOR: 50-2000 pf, 3 KV. Right-angle manual tune drive with 1/4"-3/8" dia. shaft. On 5-3/4"x3-1/4"x3-3/4" mount bracket. O/A 10-3/4x3-1/4x5, 9 lbs. sh. #C818/WRT. Used **$75.00**

7.5 KV VARIABLE CAPACITOR: 55-420 pf single section; 0.22" air gap. 13-1/2x3-1/2x6-1/2" plus 2-1/4x3/8" dia. shaft #7765118 ..... **$23.00**

EIMAC SK610/JOHNSON 124-110 socket & Chimney for 4X150/4CX250, used **$9.00**

Use your Visa or Mastercharge cards.
All Prices F.O.B. Lima, Ohio. Please Allow for Shipping.
Send for FREE Copy of NEW Catalog '79!
Address Dept. 73 • Phone 419/227-6573

FAIR RADIO SALES ✓F1
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

NOW! NOW! NOW! NOW! NOW!

The ultimate answer for eliminating the damaging effects of antenna weight on your rotor .... it's the

"UDM THRUSTOR"

- Fits any taper tower or can be used with flat top.
- Accepts 1¼" mast pipe
- All steel construction.
- Utilizing precision ground & hardened ball-type thrust bearing.
- Comes ready to install.
- Eliminates the damaging effect on your rotor.
- Shipped prepaid UPS (U.S.A.)
- Check, cash, money order, Visa, MasterCharge. $49.95 complete.
- Also available for 2" mast pipe for $59.95

UDM ENTERPRISES ✓U10
P.O. Box 2037, Sandusky, Ohio 44870

THE CRITIC'S CHOICE

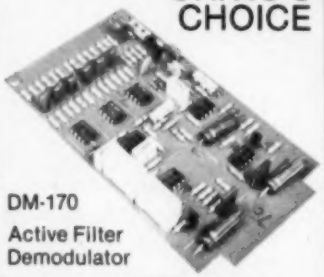

DM-170
Active Filter
Demodulator

Critical buyers are choosing the DM-170 RTTY demodulator to give them more features at lower cost. Write for information and compare. Discover what the critics have **$44.95 Kit $66.95 Wired**

FLESHER CORP.
P.O. Box 976
Topeka, Kansas 66601
(913) 234-0198 ✓F5

VISA
master charge

✓ Reader Service—see page 211

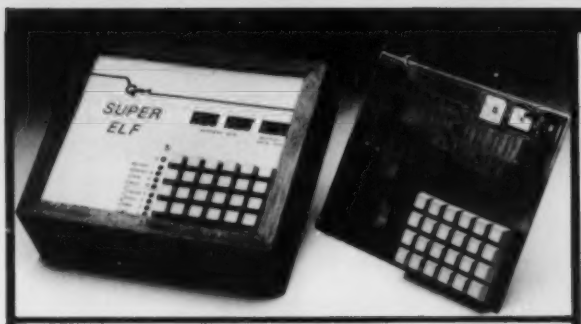

RCA Cosmac Super Elf Computer $106.95

Compare features before you decide to buy any other computer. There is no other computer on the market today that has all the desirable benefits of the **Super Elf** for so little money. The Super Elf is a small single board computer that does many **big** things. It is an excellent computer for training and for learning programming with its machine language and yet it is easily **expanded** with **additional memory, Tiny Basic, ASCII Keyboards, video character generation, etc.**

The **Super Elf** includes a **ROM** monitor for program loading, editing and execution with **SINGLE STEP for program debugging** which is not included in others at the same price. With **SINGLE STEP** you can see the microprocessor chip operating with the **unique Quest** address and data bus displays **before, during** and **after** executing instructions. Also, CPU mode and instruction cycle are decoded and displayed on eight LED indicator lamps.

An RCA 1861 **video graphics** chip allows you to connect to your own TV with an inexpensive video modulator to do graphics and games. There is a **speaker system** included for writing your own music or using many music programs already written. The speaker amplifier may also be used to drive relays for control purposes.

A 24 key **HEX keyboard** includes 16 HEX keys plus **load, reset, run, wait, input, memory protect, monitor select** and **single step**. Large, on board displays provide output and optional **high and low address**. There is a 44 pin standard connector for PC cards and a 50 pin connector for the **Quest Super Expansion Board**. Power supply and sockets for **all** IC's are included in the price plus a detailed 127 pg. instruction manual which now includes over 40 pgs. of software info. including a series of lessons to help get you started and a music program and graphics target game.

Remember, other computers only offer Super Elf features at additional cost or not at all. **Compare before you buy. Super Elf Kit $106.95. High address option $8.95, Low address option $9.95. Custom Cabinet** with drilled and labelled plexiglass front panel **$24.95. NiCad Battery Memory Saver Kit $6.95.** All kits and options also come completely assembled and tested.

Quesidata, a 12 page monthly software publication for 1802 computer users is available by subscription for $12.00 per year.

Attention Elf Owners

New products in hardware and software coming soon.

Tiny Basic cassette $10.00, on ROM $38.00, original Elf kit board $14.95.

Super Expansion Board with Cassette Interface $89.95

This is truly an astounding value! This board has been designed to allow **you** to decide how you want it optioned. **The Super Expansion Board comes with 4K of low power RAM** fully addressable anywhere in 64K with built-in memory protect and a **cassette interface**. Provisions have been made for all other options on the same board and it fits neatly into the hardwood cabinet alongside the **Super Elf**. The board includes slots for up to 6K of **EPROM** (2708, 2758, 2716 or TI 2716) and is **fully socketed.** EPROM can be used for the monitor and Tiny Basic or other purposes.

A 1K Super ROM Monitor $19.95 is available as an on board option in 2708 EPROM which has been preprogrammed with a program loader/editor and error checking multi file cassette read/write software, (relocatible cassette file) another exclusive from Quest. It includes register save and readout, block move capability and video graphics driver with blinking cursor. Break points can be used with the register save feature to isolate program bugs quickly, then follow with single step. The Super Monitor is written with subroutines allowing users to take advantage of monitor functions simply by calling them up. Improvements and revisions are easily done with the monitor. If you have the **Super Expansion Board** and **Super Monitor** the monitor is up and running at the push of a button.

Other on board options include **Parallel Input and Output Ports** with **full handshake**. They allow easy connection of an ASCII keyboard to the input port. **RS 232 and 20 ma Current Loop** for teletype or other device are on board and if you need more memory there are two **S-100** slots for static RAM or video boards. A Godbout 8K RAM board is available for $135.00. Also a 1K Super Monitor version 2 with video driver for full capability display with Tiny Basic and a video interface board. **Parallel I/O Ports $9.85, RS 232 $4.50, TTY 20 ma I/F $1.95, S-100 $4.50. A 50 pin connector set** with ribbon cable is available at $12.50 for easy connection between the **Super Elf** and the **Super Expansion Board.**

The **Power Supply Kit** for the Super Expansion Board is a 5 amp supply with multiple positive and negative voltages $29.95. Add $4.00 for shipping. Prepunched frame $5.00. Case $10.00. Add $1.50 for shipping.

Auto Clock Kit $15.95
DC clock with 4-.50" displays. Uses National MA-1012 module with alarm option. Includes light dimmer, crystal timebase PC boards. Fully regulated, comp. instructs. Add $3.95 for beautiful dark gray case. Best value anywhere.

RCA Cosmac VIP Kit $229.00
Video computer with games and graphics. Fully assem. and test. **$249.00**

Not a Cheap Clock Kit $14.95
Includes everything except case. 2-PC boards. 6-.50" LED Displays. 5314 clock chip, transformer, all components and full instructions. Orange displays also avail. **Same kit w/.80" displays.** Red only. **$21.95** Case **$11.75**

60 Hz Crystal Time Base Kit $4.40
Converts digital clocks from AC line frequency to crystal time base. Outstanding accuracy. Kit includes: PC board, IC, crystal, resistors, capacitors and trimmer.

Digital Temperature Meter Kit
Indoor and outdoor. Switches back and forth. Beautiful, .50" LED readouts. Nothing like it available. Needs no additional parts for complete, full operation. Will measure −100° to +200°F, tenths of a degree, air or liquid. Very accurate. **$39.95**
Beautiful woodgrain case w/bezel **$11.75**

NiCad Battery Fixer/Charger Kit
Opens shorted cells that won't hold a charge and then charges them up, all in one kit w/full parts and instructions. **$7.25**

PROM Eraser Will erase 25 PROMs in 15 minutes. Ultraviolet, assembled **$34.50**

Rockwell AIM 65 Computer
6502 based single board with full ASCII keyboard and 20 column thermal printer. 20 char. alphanumeric display, ROM monitor, fully expandable. $375.00. 4K version $450.00. 4K Assembler $85.00. 8K Basic Interpreter $100.00. Power supply assembled in case $60.00.

Multi-volt Computer Power Supply
8v 5 amp, ±18v .5 amp, 5v 1.5 amp, −5v .5 amp, 12v .5 amp, −12 option, ±5v, ±12v are regulated. Kit $29.95. Kit with punched frame $34.95. Woodgrain case $10.00.

Video Modulator Kit $8.95
Convert your TV set into a high quality monitor without affecting normal usage. Complete kit with full instructions.

2.5 MHz Frequency Counter Kit
Complete kit less case **$37.50**
30 MHz Frequency Counter Kit
Complete kit less case **$47.75**
Prescaler kit to 350 MHz **$19.95**

79 IC Update Master Manual $35.00
Complete IC data selector, 2500 pg. master reference guide. Over 50,000 cross references. Free update service through 1979. Domestic postage $3.50. Foreign $5.00. 1978 IC Master closeout $19.50.

Stopwatch Kit $26.95
Full six digit battery operated, 2-5 volts. 3.2768 MHz crystal accuracy. Times to 59 min., 59 sec., 99 1/100 sec. Times std., split and Taylor. 7205 chip, all components minus case. Full instructions.

Hickok 3½ Digit LCD Multimeter
Batt/AC oper. 0.1mv−1000v. 5 ranges. 0.5% accur. Resistance 6 low power ranges 0.1 ohm−20M ohm. DC curr. .01 to 100ma. Hand held, ½" LCD displays, auto zero, polarity, overrange. $74.95.

S-100 Computer Boards

8K Static RAM Kit Godbout	$135.00
16K Static RAM Kit	265.00
24K Static RAM Kit	423.00
32K Dynamic RAM Kit	310.00
64K Dynamic RAM Kit	470.00
8K/16K Eprom Kit (less PROMS)	**$89.00**
Video Interface Kit	**$139.00**
Motherboard **$39.** Extender Board	**$8.99**

TERMS: $5.00 min. order U.S. Funds. Calif residents add 6% tax.
BankAmericard and Master Charge accepted.
Shipping charges will be added on charge cards.

FREE: Send for your copy of our NEW 1979 QUEST CATALOG. Include 28¢ stamp.

Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

P.O. Box 4430M Santa Clara, CA 95054
For will call only: (408) 988-1640
2322 Walsh Ave.

Quest ELECTRONICS ✓Q3

INTEGRATED CIRCUITS

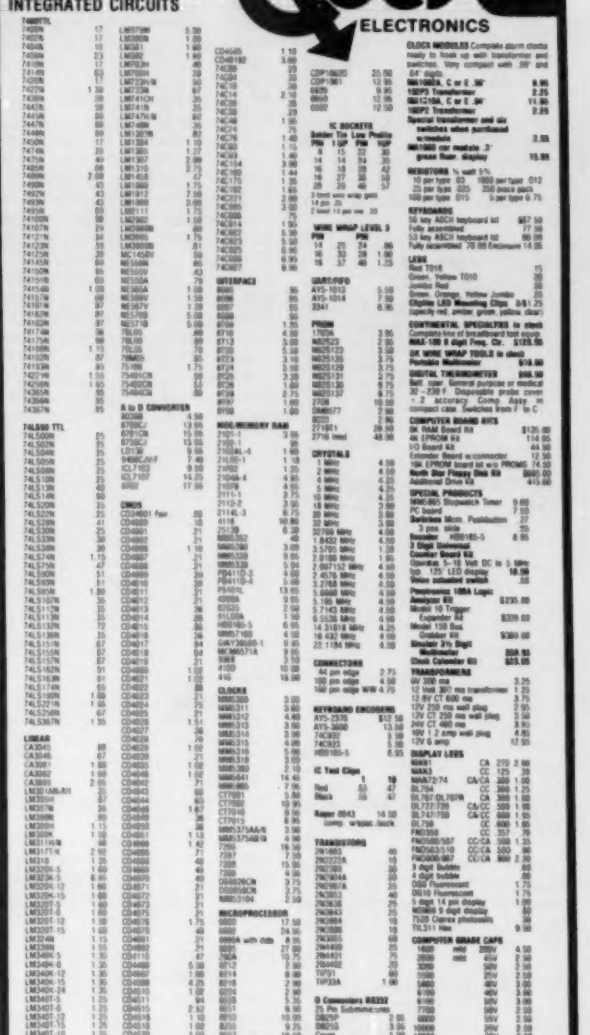

Social Events

from page 130

hope to arrange special licenses for visiting hams who may wish to operate from XE1-land during their stay. There will be a flea market and demonstrations at the convention hall. For more information, contact the Radio Club Leon, PO Box 12A, Leon, Guanajuato, Mexico.

ESSEX MT
JUL 21-22

The International Glacier-Waterton Hamfest will be held on July 21-22, 1979, at the Three Forks Campground, ten miles east of Essex, Montana, on US Highway 2. Registration is at 9:00 am. Talk-in on .52 and .34/.94. For more information, write Glacier-Waterton Hamfest, PO Box 2225, Missoula MT 59806.

EUGENE OR
JUL 21-22

The 4th annual Lane County Ham Fair will be held on July 21-22, 1979, at the Oregon National Guard Armory, 2515 Centennial Blvd., Eugene, Oregon. Registration is $3.00, and an extra drawing ticket is given with advance registration. There will be displays, lectures, contests, swapshop, transmitter hunt, and entertainment. The facilities provide plenty of free parking for motor homes and trailers.

For information and advance reservations, phone or write Wanda or Earl Hemenway, 2366 Madison, Eugene OR 97405 at (503)-485-5575.

PITTSFIELD MA
JUL 21-22

The NoBARC Hamfest will be held on July 21-22, 1979, at Cummington Fairgrounds, Pittsfield, Massachusetts. There will be tech talks, demonstrations, and dealers. Flea market admission is $1.00. Advance registration is $3.00 single and $5.00 with spouse, and $4.00/$6.00 at the gate. Gates open at 5:00 pm on Friday for free camping. Talk-in on 146.31/.91. For reservations, contact Tom Hamilton WA1VPX, 206 California Ave., Pittsfield MA 01201.

GOLDEN CO
JUL 22

The Rocky Mountain Radio League, Inc., will hold its Field Demonstration Day and Swapfest on July 22, 1979, at the home of Karl Ramstetter WA0HJZ, which is located on Highway 93, Golden Gate Canyon Road. This is accessible by going one mile north of the city limits of Golden, turning westward off Highway 93 onto Golden Gate Canyon Road, proceeding for approximately 7½ miles, and making a right turn across the cattle guards. Signs will be posted for further directions. There will be demonstrations, including slow-scan TV and computers, door prizes, and a potluck lunch, with soft drinks and ice supplied by the League. It would be appreciated if everyone would make his contribution to the potluck lunch by bringing his favorite dish and helping out the League with any spare blankets and chairs. There will be camping facilities available for campers, trailers, mobile homes, etc., on Saturday afternoon before the Fest. No dogs, guns, or motorbikes, please.

MARSHALL MO
JUL 22

The Indian Foothills Amateur Radio Club will hold its 4th annual hamfest on July 22, 1979, at the Saline County Fairgrounds, Marshall, Missouri. Tickets are $2.00 each or 3 for $5.00 in advance; $2.50 at the door. Registration is at 8:00 am, with lunch at 11:30 pm (all you can eat) and the drawing at 2:30 pm. Prizes include a Tempo S1, a DenTron Jr. Monitor™ tuner, and many more. There will be flea markets for the OM and XYL. There is no charge for flea market tables this year, but reservations are requested. There will also be old and new equipment displays, a 10-X booth, and other activities for the XYLs. Talk-in on .52, .28/.88, and 147.84/.24. For information and tickets, write Norman Gibbins WB0SZI, 692 North Ted, Marshall MO 65340.

SHEBOYGAN WI
JUL 22

The annual Lakeshore Swapfest and Bratwurst Fry will be held on Sunday, July 22, 1979. Events include prizes, a flea market, an auction, and manufacturers' displays. Admission is $1.00. Talk-in on .66/.06. For further information, contact WB9NRM at (414)-457-3203.

BELVIDERE IL
JUL 22

The Big Thunder Amateur Club will hold its annual hamfest on Sunday, July 22, 1979, at the Boone County Fairgrounds. The fairgrounds are located one mile north of Belvidere on IL-76. Talk-in on .52 simplex. Donations are $2.00 at the door. Advance tickets are $1.50. For information and tickets, contact Michael Santucci WD9JGH, 862 Ivy Oaks Rd., Caledonia IL 61011.

MACKS INN ID
JUL 27-29

WIMU (Wyoming, Idaho, Montana, and Utah) will hold its 47th annual hamfest on July 27-29, 1979, at Macks Inn, Idaho. Festivities include 2-meter hunts, OSCAR demonstrations, ladies' crafts, and a repeater display. The pre-registration prize will be a Wilson Mark II handie-talkie complete with touchtone™, battery pack, and charger. The grand prize is your choice of an Icom IC-211 or a Kenwood TS-520. Saturday night special events include kids' movies and an adult dance. For further information, contact Dave Hunting WB7FGV, Box 662, Kemmerer WY 83101, or call (307)-877-9440.

MOOSE JAW SASKATCHEWAN CAN
JUL 27-29

The Moose Jaw Amateur Radio Club will hold its 1979 Hamfest (Particifest 79) on July 27-29, 1979, at the Saskatchewan Technical Institute, 600 Saskatchewan St. W., Moose Jaw, Saskatchewan, Canada. Registration will be held on Friday evening with a full day of activities on Saturday culminating in a banquet and dance. Most of the meetings and workshops will be held on Sunday. There will also be a busy schedule for the XYLs.

OKLAHOMA CITY OK
JUL 27-29

The Central Oklahoma Radio Amateurs will sponsor the Oklahoma State ARRL Convention and "Ham Holiday" on July 27-29, 1979, at Lincoln Plaza, 4445 Lincoln Blvd., Oklahoma City, Oklahoma. The program will include an ARRL forum and technical talks on 1-GHz techniques, fast-scan TV for radio amateurs, NBVM, and other subjects of current interest. In addition, a full program is scheduled for the ladies. Pre-registration will be $4.00 if received before July 20. After that date, it will be $5.00. A synthesized 800-channel VHF transceiver will be awarded to encourage pre-registration. The main award will be a TS-120V with power supply. Adequate rooms are available for commercial exhibitors and swappers. Mail your registration to CORA, PO Box 14424, Oklahoma City OK 73113.

Unlimited parking space is also available.

OLIVER BC CAN
JUL 28-29

The Okanagan International Hamfest will be held on July 28-29, 1979, at Gallagher Lake KOA Kampsite, 8 miles north of Oliver, B.C., Canada. Registration starts at 9:00 am Saturday. Activities start at 1:00 pm Saturday and continue until 2:00 pm Sunday. Ladies may bring their hobbies and items for a white-elephant sale. Featured will be prizes, a flea market, bunny hunts, entertainment, a home-brew contest, and more. A potluck lunch will be served Sunday at noon. Call-in on 3800, .34/.94, and .76 simplex. For information, write John Juul-Andersen VE7DTX, 8802 Lakeview Dr., Vernon, B.C., Canada V1B 1W3, or Lota Harvey VE7DKL, 584 Heather Rd., Penticton, B.C., Canada V2A 1W8.

BOWLING GREEN OH
JUL 29

The Wood County Amateur Radio Club will hold its 15th annual Wood County Ham-a-Rama on July 29, 1979, at the Bowling Green Fairgrounds, Bowling Green, Ohio. Gates will open at 10:00 am, with free admission and parking. Dealer tables and space are available. Trunk sale space and food will also be available. Tickets are $1.50 in advance and $2.00 at the door. Prizes will be awarded. Talk-in on .52 K8TIH. For information, write Wood County ARC, c/o Eric Willman, 14118 Bishop Road, Bowling Green OH 43402.

NASHVILLE TN
JUL 29

The Radio Amateur Transmitting Society (R.A.T.S.) of Nashville, Tennessee, will sponsor the Nashville Hamfest on Sunday, July 29, 1979, at the National Guard Armory on Sidco Drive, in Nashville, Tennessee. Tables, bargains, and refreshments are available, as well as prizes. Admission is $3.00. Talk-in on .90/.30. For more information, contact Richard Wagner K4MZE, 1015 Haber Drive, Brentwood TN 37027, or phone (615)-794-5356.

BALTIMORE MD
JUL 29

The Baltimore Radio Amateur Television Society (BRATS) will be holding the annual BRATS Maryland Hamfest on Sunday, July 29, 1979, at the Howard County Fairgrounds, Rtes. 32 and I-70, 15 miles west of Baltimore, Maryland. The event, beginning at 8:00 am rain or shine, includes a giant flea market, indoor and outdoor exhibit areas, top prizes, and plenty of good food and refreshments. Tickets are $2.00, tailgating is $2.00, and tables are $4.00 in advance, $5.00 at the

Continued on page 204

QUESTION: Who has Advanced Electronics, Alpha, AMECO, Amphenol, Antenna Specialists, Astatic, Atlas, Bencher, Bird, Bomar, B&W, CDE, CES, CSC, Cushcraft, Daiwa, Datong, DGM, Drake, ETO, F9FT, Finco, Ham Key, Henry Hustler, Hygain, JMR, KLM, Kenwood, Larsen, MFJ, Microwave Filter, Morgain, Mosley, Newtronics, NPC, Nye Viking, Regency, Robot, Rohn, Sharp, SST, TPL, YAESU, more? ANSWER: TUFTS RADIO ELECTRONICS. Send for our fabulous radio catalog today.

PALOMAR ENGINEERS

R-X NOISE BRIDGE $49.95

- Learn the truth about your antenna.
- Find its resonant frequency.
- Find R and X off-resonance.
- Broadband 1-100 MHz.
- Simple to use. — Self contained.

VLF CONVERTER $55.00

- New device opens up the world of VLF radio.
- Converts VLF to 80 meters. For use with any shortwave receiver covering 3.5 - 4 MHz.
- Advanced design for simple operation, high performance.
- Gives reception of the 1750 meter band.
- Also covers navigation radiobeacons, WWVB, ship-to-shore, and LF broadcast band.

LOOP ANTENNA
Loop Amplifier $67.50
Plug-in loops $47.50 ea.

- Plug-in loops available for: 1600-3000 KHz (160/80 meter amateur bands) 950-1600 KHz (Broadcast Band) 150-550 KHz (VLF, 1750 meter band) 40-150 KHz (WWVB, Loran) 10-40 KHz (Omega)
- Nulls out interference

ALL BANDS PREAMPLIFIER $89.50

- Tunes 1.8 to 54 MHz. Covers ALL amateur bands 160 to 6 meters. ALL shortwave broadcast bands.
- For receivers AND transceivers.
- Up to 20 db gain.
- Pegs up that tired receiver.
- Reduces image and spurious response.

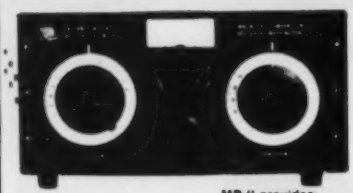

Nye Viking

Model MB II $295 (with Balun) $325

MB II provides:
*Constant SWR monitoring. *Precision tuning of final amp. *Harmonic suppression. *Receiver input impedance-matching. *Maximum power transfer to antenna. *Continuous frequency coverage 1.8 to 30 MHz. *Precision tuning of any wire ½ wavelength or longer, with SWR of 1:1.

MB II features:
*Finest quality, made-in-USA components. *Large, precision, easy-to-read dials with 360° readout. *Optional 3000 watt Balun for twin lead antennas.

BIRD Electronic Corporation

$94 VHF model 4362 (140-180 MHz)
$94 HF model 4360 (18- 30 MHz)

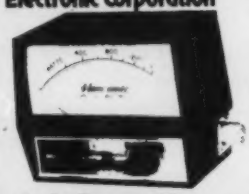

The 4360, 4362 HAM-MATE Directional Wattmeters are insertion type instruments for measuring forward or reflected power in 50-ohm coaxial transmission lines. They are direct descendants of the model 43 THRULINE® Wattmeter — the professional standard of the industry — and will accurately measure RF power flow under any load condition. Each wattmeter is made up of a precisely machined section of 50-ohm line, a rotatable sensing element and meter calibrated in watts, all mounted in a high impact plastic housing. It is this type of solid construction and the directional THRULINE coupling circuit, without toroids, that account for the superiority of the HAM-MATE Wattmeters.

the indispensable BIRD 43 THRULINE WATTMETER

Power Range	Frequency Bands (MHz)				
	2	25	100	250	1000
	30	60	250	500	1000
5 watts		5A	5C	5D	5E
10 watts		10A	10C	10D	10E
25 watts		25A	25C	25D	25E
50 watts	50H	50A	50C	50D	50E
100 watts	100H	100A	100C	100D	100E
250 watts	250H	250A	250C	250D	250E
500 watts	500H	500A	500C	500D	500E
1000 watts	1000H	1000A	1000C	1000D	1000E
2500 watts	2500H				
5000 watts	5000H				

MODEL 43	$125.00
Elements (Table 1) 2-30 MHz	45.00
Elements (Table 1) 25-1000 MHz	38.00
Carrying case for Model 43 & 6 elements	27.50
Carrying case for 12 elements	17.00

READ RF WATTS DIRECTLY! (Specify Type N or SO239 connectors) 0.45 – 2300 MHz, 1-10,000 Watts ±5%, low insertion VSWR – 1.05. Unequalled economy and flexibility. Buy only the element(s) covering your present frequency and power needs, add extra ranges later if your requirements expand.

B&W Barker & Williamson

5 –BAND TRAP DIPOLE (80 thru 10 Meters)

Power rated 2k WPEP, approx. 110 ft. span

Complete with: wire, traps, end insulators, 50 ft. RG-8/U, PL-259 connector, heavy-duty cast aluminum and steatite center connector. 4-Band (40 thru 10M) 55 ft.

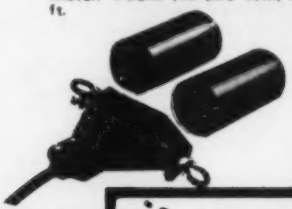

Pre-assembled: Model 370-11 – $59.95

Kit (illustrated): Model 370-12 – $49.95

BOMAR Crystal Company

TWO METERS CRYSTALS IN STOCK

Motorola HT 220 Crystals In Stock!

Standard ● Icom ● Heathkit ● Ken ● Clegg ● Regency ● Wilson ● VHF Eng ● Drake ● And Others! Lifetime Guarantee! Now only $9/pair.

Hy-Gain REEL TAPE PORTABLE DIPOLE for 10 thru 80 Meters Model 18TD

The most portable high performance dipole ever...

The Model 18TD is unquestionably the most foolproof high performance portable doublet antenna system ever developed. It has proven invaluable in providing reliable communications in vital military and commercial applications throughout the world. Two stainless steel tapes, calibrated in meters, extend from either side of the main housing up to a total distance of 132 feet for 3.5 mc operation. 25 ft. lengths of polypropylene rope attached to each tape permits installation to poles, trees, buildings... whatever is available for forming a doublet antenna system. Integrated in the high impact housing is a frequency to length conversion chart calibrated to meter measurements on the tapes... makes installation foolproof. Feeds with 52 ohm coax. Delivers outstanding performance as a portable or permanent installation. Measures 10x5½x2 inches retracted. Wt., 4.1 lbs.
Order No. 228 Price: $94.95

hy-gain

BANDPASS-REJECT DUPLEXER DPLA-144 FOR 144-174 MHz

Also available for 54, 220, 450 MHz.

$409.95

Name _____ Call _____
Address _____
City _____ State _____ Zip _____
Order: _____

Prices FOB Medford, MA. MA residents add 5% sales tax.
Minimum $3.00 for shipping and handling on ALL ORDERS.

☐ Check Enclosed ☐ Visa ☐ Master Charge ☐ Send for Free Catalog
PRICES SUBJECT TO CHANGE WITHOUT NOTICE
Card no. _____ Card exp. date _____
Signature _____

TUFTS

Radio Electronics T3
OPEN DAILY 9-9
SATURDAY 9-6

206 Mystic Avenue, Medford, Mass. 02155, 1-800-225-4428, (Mass. residents: 1-617-395-8280)

Reader Service—see page 211

NEW! NEW! NEW!

KDK

FM2016A

All Solid State-CMOS PL digital synthesized - No Crystals to Buy! 5KHz steps - 144-149 MHz-HUGE ⅜" LED digital readout PLUS MARS-CAP and MULTIPLE OFFSET BUILT IN. ● 5 MHz Band Coverage - 1000 Channels (instead of the usual 2 MHz to 4 MHz-400 to 800 Channels) ● 4 CHANNEL RAM IC MEMORY WITH SCANNING AND AUTO TRANSMIT ● MULTIPLE FREQUENCY OFFSETS ● ELECTRONIC AUTO TUNING - TRANSMIT AND RECEIVE ● INTERNAL MULTIPURPOSE TONE OSCILLATOR ● RIT ● RF ATT ● DISCRIMINATOR METER - 16 Watts Output-Superior Receiver Sensitivity and Selectivity - 15 POLE FILTER, MONOLITHIC CRYSTAL FILTER AND AUTOMATIC TUNED RECEIVER FRONT END, COMPARE! ● Superb Engineering and Superior Commercial Avionics Grade Quality and Construction Second to None at ANY PRICE.

INTRODUCTORY PRICE

$369.00

ALSO - **NEW** FM 6016A FOR 6 METERS

Regulated AC/PS
Model FMPS-4R . . . $39.95

SHOWN WITH OPTIONAL μP-800 MICRO-PROGRAMMER* $99.00

FMMC-1* Microphone with Built-in Touch Tone Pad.

WHY BUY LESS? THE FMMC-1 HAS IT *ALL!*

- New! Auto key up
- Snap-Action Keyboard
- Adj. level and tone balance
- Use with any transceiver
- Only 3¼" x 2" *$39.95

- **FREQUENCY RANGE**: Receive and Transmit: 144.00 to 148.995 MHz, 5 Khz steps (1000 channels) + MARS-CAP and MULTIPLE OFFSET BUILT IN.
- **HUGE ⅜" LED DIGITAL READOUT.**
- **4 CHANNEL RAM SCANNER WITH IC MEMORY AND AUTO TRANSMIT**: Program any 4 frequencies and reprogram at any time using the front panel controls—search for occupied (closed) channel or vacant (open) channels. Internal Ni-Cad included to retain memory (no diode matrix to wire or change).
- **MULTIPLE FREQUENCY OFFSETS. NO CRYSTALS TO BUY - EVER** - Any offset any split! "Odd Ball" splits accomplished by digital programming. Never any need for crystals!
- **INTERNAL MULTIPURPOSE TONE OSCILLATOR BUILT IN**: Sine Wave 1750 Hz tone burst for "whistle on operation" and subaudible tone operation. Internal 2 position switch for automatic and manual operation, tone burst or sub audible tone. PL - adjustable 60-203 Hz (100 Hz Pre-Set).
- **AIRCRAFT TYPE FREQUENCY SELECTOR**: Large and small coaxially mounted knobs select 100KHz and 10KHz steps respectively. Switches click-stopped with a home position facilitate frequency changing without need to view LED's while driving and provides the sightless amateur with full Frequency Selection as standard equipment.
- **FULL AUTOMATIC TUNING OF RECEIVER FRONT END AND TRANSMITTER CIRCUITS**: DC output of PLL fed to varactor diodes in all front end RF tuned circuits provides full sensitivity and optimum intermodulation rejection over the entire band. APC (AUTO POWER CONTROL) - Keeps RF output constant from band edge to band edge. NO OTHER AMATEUR UNIT AT ANY PRICE has these features which are found in only the most sophisticated the expensive aircraft and commercial transceivers.
- **TRUE FM**: Not phase modulation - for superb emphasized hi-fi audio quality second to none.
- **RIT CONTROL**: Used to improve clarity when contacting stations with off frequency carrier.
- **MONITOR LAMPS**: 2 LED's on front panel indicate (1) incoming signal-channel busy, and (2) Transmit.
- **FULLY REGULATED INTEGRAL POWER SUPPLY**: Operating voltage for all 9v circuits independently regulated. Massive Commercial Hash Filter.
- **MODULAR COMMERCIAL GRADE CONSTRUCTION**: 3 Unitized modules eliminate stray coupling and facilitate ease of maintenance.
- **ACCESSORY SOCKET**: Fully wired for touch tone, phone patch, and other accessories. Internal switch connects receiver output to internal speaker when connector is not in use.
- **MULTI-PURPOSE METER**: Triple Function Meter Provides Discriminator Meter, "S" Reading on receive and Power Out on Transmit.
- **RECEIVE**: Better than .25uv sensitivity, 15 POLE FILTER as well as monolithic crystal filter and AUTOMATIC TUNED LC circuits provide superior skirt selectivity - COMPARE!
- **HIGH/LOW POWER OUTPUT**: 16 watts and 1 watt, switch selected. Low power may be adjusted anywhere between 1 and 16 watts. Fully protected - short or open SWR.
- **RF ATT**: Live right next to King Kong Repeater and can't operate? With the 2016A You Can - Just flick the RF ATT switch. Only the 2016A has this feature.
- **OTHER FEATURES**: Dynamic Microphone, built in speaker, mobile mounting bracket, external 5 pin accessory jack, speaker jack, and much, much more. Size 2½ x 7 x 7½. All cords, plugs, fuses, microphone hanger, etc. included. Weight 5 lbs.

Manufactured by one of the world's most distinguished Avionics manufacturers, Kyokuto Denshi Kaisha, Ltd. First in the world with an all solid state 2 meter FM transceiver.

master charge

VISA*

AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129th Terrace, Miami, Florida 33176
Telephone (305) 233-3631 ● Telex: 80-3356
U.S. DISTRIBUTOR DEALER INQUIRIES INVITED

ORDER NOW TOLL-FREE
Credit card holders may use our toll-free ordering number
Ask for operator 701
(800) 824-7888
In California (800) 852-7777
Alaska and Hawaii (800) 824-7919

A21

Regional Sales & Service Centers:

East: Sanford Communications, Inc. Colonia, N.J. (201) 574-3003
Northeast: Buzzards Bay Electronics Buzzards Bay, Mass. (617) 759-3376
West: The Radio Place Sacramento, Cal. (916) 441-7388
Northwest: Action Supply, Inc. Boise, Idaho (208) 344-5084
Midwest: Universal Service Columbus, Ohio (614) 866-4267
South: Electronic Communications Highland Springs, Virginia (804) 737-5100

COMPARE AT ANY PRICE!

µP-800 MICRO-PROGRAMMER

FOR KDK 2016A AND 2015R

- 800 CHANNEL PROGRAMMABLE MEMORY WITH SCAN. RETAINS MEMORY WHEN OFF ... AND ...
- FULL BAND RANDOM SCAN - UP OR DOWN
- SINGLE STEP SCAN FEATURE IN ANY MODE.
- MEMORY SLOW SCAN
- HOLD AND TRANSMIT AT ANY TIME.
- AUTOMATIC RESUME
- EASY INSTALLATION

$99.00

ACCESSORIES FOR KDK: FM2016A AND FM2015R

- µP 800 - Micro Programmer 99.00
- FMPS-4R Regulated AC Power Supply ... 39.95
- FMMC-1 Touch Tone Microphone 39.95
- FMAT-1 ¼ Wave Portable Antenna For Motel, Hotel, or Apt. 7.95
- Extra DC Power Cord & Plug 4.00
- Extra Mounting Bracket 6.00

NEW CDE HAM IV ROTATORS

Reg. $189.95

Our Price $149.00

SUPERB! NEW ICOM IC-701S H.F. XCEIVER

Please Call or Write for Special Package Price

NEW! TRISTAO'S 40 foot Self-Supporting Crank-up Mast

Regular **$399**

COMPLETE With Hinged Mounting Plate And House Bracket

Our Price $359

$19 Shipping Anywhere USA

NEW!

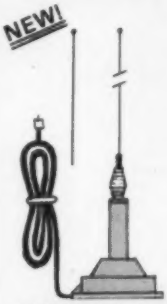

KDK MAX II

TWIN ANTENNA

- SUPER 80 LB. 100 M.P.H. BLACK MAGNETIC MOUNT
- ½ WAVE FOR MAX II SIGNAL AND
- ¼ WAVE FOR CLOSE-IN AND RESTRICTED HEIGHT AREAS
- INSTANT CHANGE-OVER
- SUPERIOR PERFORMANCE
- STAINLESS STEEL SPRING AND WHIP, CHROME ON BRASS BASE - COMPARE!
- COMPLETE WITH 17' COAX AND CONNECTOR

$29.95

COMPARE!! Nothing Else Does!

SIGMA RF-2000 SWR & POWER METER

Cal PWR Scales 200W-2000W Freq. Range 3.5-150 MHz. Please do not confuse the RF2000 with similar appearing lower priced units. RF2000 is an individually calibrated professional quality instrument. Unequaled at many times the price. Size 7" (w) x 2-1/3" (d).

Shipping Anywhere in USA $1.00 **$35**

AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129 Terr.
Miami, Fla. 33176
Tel: (305) 233-3631

ORDER NOW TOLL-FREE
Credit card holders may use our toll-free ordering number
Ask for operator 701
(800) 824-7888
In California (800) 852-7777
Alaska and Hawaii (800) 824-7919

2 Larsen Kūlrod® Antennas which need no ground plane!

OMNI MODELS

For easy mounting on fiberglass or where mounting material thickness prohibits usual mounts. Mounting flange and base loading coil housing is a single, sealed, waterproof unit. Handles a full 150 watts. Models available for High Band and UHF.

OM-150-K
Base loaded 1/2 wave antenna. Delivers unity gain **without** a ground plane. Delivers 2 to 2.5 db gain over 1/4 wave whip with ground plane of 1/2 wave or more radius. For 144-148 MHz.

OM-440-K
Collinear antenna with phasing coil. Delivers 2 db gain **without** a ground plane. Delivers 4 db gain over 1/4 wave whip with ground plane of 24" or more radius. For 440-450 MHz.

You can HEAR the difference with Kūlrod! For details on OMNI models and other Larsen Kūlrod Mobile Antennas write:

Larsen Antennas L23

IN USA P.O. BOX 1686
VANCOUVER, WA 98663
PHONE: (206) 573-2722
IN CANADA Unit 101, 283 E. 11th Avenue
VANCOUVER, B.C. V5T 2C4
PHONE: (604) 872-8517

® Kūlrod is a Registered Trademark of Larsen Elec., Inc.

MURATA CERAMIC FILTERS
Model SFD-455D
455 kHz $3.00
Model SFB-455D
455 kHz $2.00

TYCO
10.7 MHz Monolithic
Crystal Filter
$5.95

BEACON TRANSMITTER
Microwave Associates Model MA-86C16
An all solid state high power fixed tuned C-band RF Generator. This unit is crystal controlled, and provides frequency stability in extreme environments. Designed for use in high performance aircraft and ground based beacon applications, this device can also be used as an up-converter pump for microwave communications relay.

Frequency Range	6.0 to 6.3 GHZ
Power Output	1 Watt Min. 3 Watts Max.
Frequency Stability	+/– 1 x 10-6
Spurious Harmonics	–30dB
Input Voltage	24 to 32 Volts DC

ONLY $69.95

TEKTRONIX
Model 519 Oscilloscope DC to 1GHz
$699.00

HEWLETT PACKARD
Model 140A Oscilloscope
W/1402A, 1400A $495.00
(also available 1415A $300)

TEKTRONIX
IL30 Spectrum Analyzer plug-in
925MHz-10.25GHz $899.00

HEWLETT PACKARD UHF, VHF, AND MICROWAVE SIGNAL GENERATORS AND SWEEPERS, AND OTHER EQUIPMENT

MODEL 434A
Calorimetric power meter
$450.00

MODEL 416A
Ratio meter
$125.00

MODEL 413AR
DC null voltmeter
$112.50

MODEL 400DR
Vacuum tube voltmeter
$79.95

MODEL 618B
3.8 to 7.6 GHz
only $499.99

WISPER FANS
This fan is super quiet, efficient cooling where low acoustical disturbance is a must. Size 4.68" x 4.68" x 1.50", Impedance protected, 50/60 Hz 120 volts AC

ONLY $9.95 or 2/$18.00

TRW BROADBAND AMPLIFIER MODEL CA615B
Frequency response 40 to 300 MHZ

Gain	300 MHZ 16dB MIN.
	17.5dB MAX.
	50 MHZ 0 to – 1dB from 300 MHZ
Voltage	24 volts DC at 220ma MAX

ONLY $14.95

Slow scan CRTs
Used but good
Some may have small burn spots
JAN-3CAP7A
$24.95

2C39A, 2C42, 2C43, 2C46
All JAN tubes
Used but guaranteed
$9.95/each

MARCONI Model TF791C Carrier Deviation Meter
4.0 MHz to 270 Mhz
$299.95

INTEGRATED CIRCUITS

MC1303L	$ 2.00	MC1460R	$ 5.40
MC1461R	6.90	MC1463R	5.15
MC1469G	2.05	MC1469R	3.55
MC1550G	1.50	MC1560G	10.20
MC1560R	12.40	MC1563R	10.00
MC1568G	5.31	MC1568L	5.00
MC1569R	8.15	MC1590G	6.50
MC4024P	3.82	MC6800P	9.95
MC6820P	6.95	MC68B21P	12.00
2513	6.95	4116-200NS	10.37
8080A	3.95	TMS4060	6.95
2708TI	8.95	TMS4024	13.90
2716TI	29.95	1702A	4.95

ALL CRYSTALS $4.95

37.35kc	2.222125MC	2.7735MC	3.255MC	6.537MC	13.3045MC
49.710	2.22325	2.776625	3.256125	6.567	13.3145
70	2.22675	2.78	3.258625	6.582	13.3245
81.9	2.22875	2.814	3.261	6.612	13.3345
96	2.23725	2.817	3.261125	6.6645	13.3445
225	2.2395	2.8225	3.268625	6.673	13.3545
250	2.24075	2.835	3.271125	6.693	14.315
285.714	2.241	2.85	3.273625	6.723	15.016
576	2.246	2.854	3.276125	6.7305	15.036
720	2.2475	2.854285	3.3	6.738	16.80417
1.2288MC	2.2925	2.865	3.3345	6.75125	17.2800
1.3047	2.2975	2.868	3.4045	6.753	17.8710
1.4	2.3	2.8725	3.4115	6.7562	17.9065
1.455	2.320	2.876875	3.4325	6.7605	17.9165
1.5	2.325	2.887	3.4535	6.7712	17.9265
1.689600	2.32625	2.889	3.4675	6.77625	17.9365
1.7	2.32885	2.894	3.4815	6.880000	17.9465
1.76375	2.3525	2.910	3.5	6.910	17.9665
1.77125	2.35256	2.920	3.579545	6.940	17.975
1.773125	2.368	2.925450	3.64	7.15	17.9735
1.78675	2.374	2.92545	3.75	7.26	19.100
1.80224	2.375	2.931	3.7735	7.35	19.55416
1.81875	2.38725	2.94375	3.80	7.390	20.1
1.8275	2.395	2.945	3.805	7.423	21.99965
1.845125	2.396875	2.94675	3.803	7.443	22.
1.84375	2.42	2.952	3.901	7.473	23.25
1.845625	2.4375	2.966	3.908	7.5	23.575
1.84575	2.44275	2.973	3.9168	7.81	25.47667
1.846	2.4496	2.980	4.0000	8.00764	25.9
1.8425	2.45	2.981	4.011	8.00824	25.99961
1.84975	2.4585	2.98325	4.126666	8.075	26.66667
1.8575	2.46125	2.987	4.26	8.12	26.8965
1.908125	2.482	2.9989	4.3	8.15571	26.9
1.925	2.486	3.001	4.6895	8.364	26.958
1.927	2.5	3.0235	4.6965	8.64	27.77778
1.932	2.51375	3.045	4.7	8.820	27.9
1.982	2.56	3.049	4.7175	8.8285	28.728
1.985	2.581	3.053	4.7245	8.837	28.88889
1.9942	2.604	3.062	4.7315	8.8455	28.9
1.995975	2.6245	3.067	4.765	8.854	28.93888
1.984750	2.618	3.074	4.89	8.8625	29.
2.0000	2.62825	3.1125	5.0000	8.871	29.896
2.0285	2.633125	3.126	5.13125	8.879500	29.9
2.05975	2.639	3.137	5.139585	8.888	30.0000
2.126175	2.63575	3.13975	5.147917	8.905	30.9
2.12795	2.64325	3.1435	5.164583	8.9305	31.0000
2.1315	2.646	3.144	5.348400	8.939	31.11111
2.133275	2.647	3.145	5.426636	8.956	31.66667
2.13505	2.650750	3.151	5.436636	9.0265	31.9
2.136825	2.6545	3.1545	5.456	9.65	32.0000
2.1425	2.65825	3.158	5.4675	9.65	32.22222
2.144625	2.660	3.1585	5.4990	9.7	32.9
2.14675	2.662	3.1615	5.5065	9.75	33.0000
2.148875	2.66575	3.1625	5.515	9.8	33.33333
2.151	2.6695	3.166	5.5215	9.85	33.9
2.153125	2.677	3.16975	5.544	9.9	34.0000
2.15375	2.68075	3.177	5.5515	9.95	34.4
2.155	2.681	3.181	5.559	9.999	34.4444
2.15525	2.6845	3.1825	5.5665	10.0000	34.44444
2.157375	2.68825	3.18475	5.574	10.021	35.0000
2.1595	2.69575	3.1885	5.5815	10.20833	35.25000
2.16375	2.7	3.2	5.589	10.80375	35.55555
2.165875	2.702	3.2035	5.604	11.	36.0000
2.170125	2.704	3.20725	5.619	11.1805	36.21750
2.17225	2.71075	3.2105	5.6115	11.228	36.6666
2.174375	2.715	3.2165	5.6265	11.2375	36.66666
2.1765	2.716	3.2175	5.6415	11.2995	36.66667
2.17925	2.723	3.2315	5.6715	11.3565	37.00000
2.18475	2.730	3.23275	5.675	11.535	37.2175
2.18575	2.7315	3.2365	5.680	11.69626	37.385
2.194125	2.73225	3.23775	5.695	12.29	37.460
2.207063	2.732625	3.23775	5.7	12.39	37.77777
2.208313	2.733	3.2385	5.7105	12.49	38.00000
2.209563	2.737	3.238875	5.733333	12.69	38.33333
2.210812	2.73975	3.23925	6.110	12.79	38.77777
2.210813	2.742125	3.24	6.210	12.89	38.77778
2.212063	2.7425	3.24025	6.321458	12.99	38.88888
2.214562	2.744	3.2405	6.424583	13.09	38.88889
2.214563	2.7445	3.241	5.425	13.102	39.00000
2.215625	2.74475	3.2425	6.427083	13.2155	39.160
2.217938	2.746875	3.244	6.45	13.2455	40.00000
2.21975	2.751	3.248875	6.47	13.2745	41.11111
	2.754	3.24975	6.4711	13.2845	43.33333
	2.75525	3.4975	6.510	13.2945	47.48
	2.762375	3.2515			48.97222

CRYSTALS (Con't)

49.84166 MC
49.95
50.14166
53.45
54.95MC
55.45
57.45
58.45
59.45
60.45
61.95
63.80833
66.66667
72.855
75.185
76.66667
82.75
83.
84.
85.833330
90.833
93.1346
93.535
93.9353
94.3
95.
95.35
106.850
123.5
146.64
147.09
165.5

Alfred Model 632D
Sweep signal generator
2-4 GHz $399.00

Polorad Model 1206
1.95 to 4.20 GHz
signal source
$400.00
Model 1107 3.8 to 8.20
GHz signal generator
$550.00

FETs
3N128 1.00
40673 1.39
MPF102 .45
MPF121 1.00
MPF131 1.00

TUNNEL DIODES

TYPE	PRICE
TD281A	$10.00
TD266A	10.00
1N2930	7.85
1N2939	7.85
1N4395	5.40

RF TRANSISTORS

TYPE	PRICE
2N1561	$15.00
2N1562	15.00
2N1692	15.00
2N1693	15.00
2N2857JAN	2.45
2N2876	12.35
2N2880	25.00
2N2927	7.00
2N2947	17.25
2N2948	15.50
2N2949	3.90
2N2950	5.00
2N3267	4.30
2N3294	1.15
2N3302	1.05
2N3307	10.50
2N3309	3.90
2N3375/MM3375	7.00
2N3553	1.45
2N3818	6.00
2N3866	1.09
2N3866JAN	2.70
2N3866JANTX	4.43
2N3924	3.20
2N3925	6.00
2N3927	11.50
2N3950	26.25
2N3961	6.80
2N4072	1.70
2N4135	2.00
2N4427	1.09
2N4430	20.00
2N4440	8.80
2N4957	3.50
2N4958	2.80
2N4959	2.12
2N4976	19.00
2N5090	6.90
2N5108	3.90
2N5109	1.55
2N5160	3.34
2N5177	20.00
2N5179	.49
2N5184	2.00
2N5216	47.50
2N5583	4.43
2N5589	4.60
2N5590	6.30
2N5591	10.35
2N5637	20.70
2N5641	4.90
2N5643	14.38
2N5645	11.00
2N5764	27.00

TYPE	PRICE
2N5842	$ 8.85
2N5862	50.00
2N5913	3.25
2N5922	10.00
2N5942	46.00
2N5943	1.75
2N5944	7.50
2N5945	10.90
2N5946	13.20
2N6080	5.45
2N6081	8.60
2N6082	9.90
2N6083	11.80
2N6084	13.20
2N6094	5.75
2N6095	10.35
2N6096	19.35
2N6097	28.00
2N6136	18.70
2N6166	36.80
2N6439	43.45
MM1500	32.20
MM1550	10.00
MM1552	50.00
MM1553	56.50
MM1601	5.50
MM1602/2N5842	7.50
MM1607	8.85
MM1661	15.00
MM1669	17.50
MM1943	3.00
MM2605	3.00
MM2608	5.00
MM8002	2.05
MM8006	2.15
MRF304	43.45
MRF502	.49
MRF504	6.95
MRF509	4.90
MRF511	8.60
MRF901	3.00
MRF5177	20.70
MRF8004	1.44
HEP78/S3014	4.95
HEPS3002	11.30
HEPS3003	29.88
HEPS3005	9.95
HEPS3006	19.90
HEPS3007	24.95
HEPS3010	11.34
HEPS5026	2.56
MMCM918	1.00
MMT72	.61
MMT74	.94
MMT2857	1.43

TYPE	PRICE
MMT3960A	$ 6.25
PT3539B	3.00
PT4186B	3.00
PT4571A	1.50
PT4612	5.00
PT4626	5.00
PT4640	5.00
PT8659	10.72
PT9784	24.30
PT9790	41.70
PT9847	26.40
SD1043	5.00
SD1116	3.00
SD1118	5.00
SD1119	3.00
40281	10.90
40282	11.90
40290	2.48
TA7994	50.00

MHZ ELECTRONIC KITS:

kit #1
Motorola MC14410CP CMOS Tone Generator
CMOS Tone Generator uses 1MHZ crystal to produce standard dual frequency dialing signal. Directly compatible with 12 key Chomeric Touch Tone Pads. Kit includes the following:
1 Motorola MC14410CP Chip
1 PC Board
And all other parts for assembly. **NOW ONLY $15.70**

Kit #2
Fairchild 95H90DC Prescaler 350MHZ.
95H90DC Prescaler divides by 10 to 350 MHZ. This kit will take any 35MHZ Counter to 350 MHZ. Kit includes the following:
1 Fairchild 95H90DC Chip
1 2N5179 Transistor
2 UG-88/U BNC Connectors
1 PC Board
And all other parts for assembly. **NOW ONLY $19.95**

FAIRCHILD VHF AND UHF PRESCALER CHIPS

95H90DC	350MHZ Prescaler Divide by 10/11	$ 8.95
95H91DC	350MHZ Prescaler Divide by 5/6	8.95
11C90DC	650MHZ Prescaler Divide by 10/11	15.95
11C91DC	650MHZ Prescaler Divide by 5/6	15.95
11C83DC	1GHZ Divide by 248/256 Prescaler	29.90
11C70DC	600MHZ Flip/Flop with reset	12.30
11C58DC	ECL VCM	4.53
11C44DC	Phase Frequency Detector (MC4044P/L)	3.82
11C24DC	Dual TTL VCM (MC4024P/L)	3.82
11C06DC	UHF Prescaler 750MHZ D Type Flip/Flop	12.30
11C05DC	1GHZ Counter Divide by 4	74.35
11C01FC	High Speed Dual 5-4 Input NO/NOR Gate	15.40

CRYSTAL FILTERS: Tyco 001-10880 same as 2194F
10.7MHZ Narrow Band Crystal Filter
3 db bandwidth 15khz minimum 20 db bandwidth 60khz minimum 40 db bandwidth 150khz minimum. Ultimate 50 db: Insertion loss 1.0db Max. Ripple 1.0db Max. Ct. 0 + – 5pf. Rt. 3600 Ohms.
NOW ONLY $5.95

TUBES

2E26	$5.00	4CX350A	$32.25
3-500Z	90.00	4CX100A	289.00
3-1000Z	225.00	4CX1500B	285.00
3B28	5.00	572B	33.60
4-65A	54.50	811A	12.95
4-125A	68.75	5894	39.00
4-250A	80.00	6146A	5.25
4-400A	81.50	6146B	6.25
4-1000A	255.00	6360	7.95
4CX250B	38.50	6907	35.00
4CX250F	53.50	6939	9.95
4CX250G	53.50	7360	10.80
4CX250K	72.00	8072	45.00
4CX250R	48.00	8295A/PL172	150.00
		8950	5.95

SONALERT Model SL628P
6-28 volts DC
3-14 ma
$5.95

1 MHz TCXO Crystal Oscillator
TTL output
3.3 volts DC
$19.95

Prices Subject to Change

TERMS
All CHECKS and MONEY ORDERS ARE IN US FUNDS!
ALL ORDERS SENT FIRST CLASS OR UPS.
Please include $1.50 Minimum for postage.
ALL PRICES ARE IN US DOLLARS.
ALL PARTS PRIME/GUARANTEED

BANK AMERICARD/VISA/MASTERCHARGE
Your Number
(or equivalent)
_____
Exp. Date
_____
Your Signature:
_____

MHz electronics ✓MB

(602) 242-3037
2111 W. Camelback
Phoenix, Arizona 85015

FREQUENCY COUNTER KIT

Outstanding Performance

Incredible Price $89.95

CT-50

The CT-50 is a versatile and precision frequency counter which will measure frequencies to 60 mHz and up to 600 mHz with the CT-600 option. Large Scale Integration, CMOS circuitry and solid state display technology have enabled this counter to match performance found in units selling for over three times as much. Low power consumption (typically 300-400 ma) makes the CT-50 ideal for portable battery operation. Features of the CT-50 include: large 8 digit LED display, RF shielded all metal case, easy pushbutton operation, automatic decimal point, fully socketed IC chips and input protection to 50 volts to insure against accidental burnout or overload. And, the best feature of all is the easy assembly. Clear, step by step instructions guide you to a finished unit you can rely on. **Order your today!**

SPECIFICATIONS

Frequency range: 6 Hz to 65 mHz, 600 mHz with CT-600
Resolution: 10 Hz @ 0.1 sec gate, 1 Hz @ 1 sec gate
Readout: 8 digit, 0.4" high LED, direct readout in mHz
Accuracy: adjustable to 0.5 ppm
Stability: 2.0 ppm over 10° to 40° C. temperature compensated
Input: BNC, 1 megohm, 20 pf direct, 50 ohm with CT-600
Overload: 50VAC maximum, all modes
Sensitivity: less than 25 mv to 65 mHz, 50-150 mv to 600 mHz
Power: 110 VAC, 5 Watts or 12 VDC @ 400 ma
Size: 6" x 4" x 2", high quality aluminum case, 2 lbs
ICs: 13 units, all socketed

CT-50, 60 mHz counter kit	$89.95
CT-50WT, 60 mHz counter, wired and tested	159.95
CT-600, 600 mHz scaler option, add	29.95
CB-1, Color TV calibrator-stabilizer	$14.95
DP-1, DC probe, general purpose probe	12.95
HP-1, high impedance probe, non-loading	15.95

CAR CLOCK

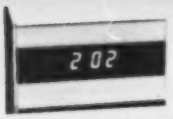

The UN-KIT, only 5 solder connections

Here's a super looking, rugged and accurate auto clock which is a snap to build and install. Clock movement is completely assembled—you only solder 3 wires and 2 switches, takes about 15 minutes! Display is bright green with automatic brightness control photocell—assures you of a highly readable display, day or night. Comes in a satin finish anodized aluminum case which can be attached 5 different ways using 2 sided tape. Choice of silver, black or gold case (specify).

DC-3 kit, 12 hour format	$22.95
DC-3 wired and tested	$29.95
110V AC adapter	$5.95

Under dash car clock

12/24 hour clock in a beautiful plastic case features: 6 jumbo RED LEDS, high accuracy (1 min./mo.), easy 3 wire hookup, display blanks with ignition, and super instructions. Optional dimmer automatically adjusts display to ambient light level.

DC-11 clock with mtg. bracket	$27.95
DM-1 dimmer adapter	2.50

PRESCALER

Extend the range of your counter to 600 mHz. Works with any counter. Includes 2 transistor pre-amp to give super sens., typically 20 mv at 150 mHz. Specify ÷ 10 or ÷ 100 ratio.

PS-1B, 600 mHz prescaler	$59.95
PS-1BK, 600 mHz prescaler kit	49.95

OP-AMP SPECIAL

741 mini dip	12/$2.00
B1-FET mini dip, 741 type	10/$2.00

VIDEO TERMINAL

A completely self-contained, stand alone video terminal card. Requires only an ASCII keyboard and TV set to become a complete terminal unit. Two units available, common features are: single 5V supply, XTAL controlled sync and baud rates (to 9600), complete computer and keyboard control of cursor. Parity error control and display. Accepts and generates serial ASCII plus parallel keyboard input. The 3216 is 32 char. by 16 lines, 2 pages with memory dump feature. The 6416 is 64 char. by 16 lines, with scrolling, upper and lower case (optional) and has RS-232 and 20ma loop interfaces on board. Kits include sockets and complete documentation.

RE 3216, terminal card	$149.95
RE 6416, terminal card	189.95
Lower Case option, 6416 only	13.95
Power Supply Kit	14.95
Video/RF Modulator, VD-1	6.95
Assembled, tested units, add	60.00

CALENDAR ALARM CLOCK

The clock that's got it all: 6-.5" LEDs, 12/24 hour, snooze, 24 hour alarm, 4 year calendar, battery backup, and lots more. The super 7001 chip is used. Size: 5x4x2 inches.
Complete kit, less case (not available)

DC-9	$34.95

30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain. 1 W in for 8 out, 2 in for 15 out, 4 W in for 30 out. Max. output of 35 W, incredible value, complete with all parts, less case and T-R relay.

PA-1, 30 W pwr amp kit	$22.95
TR-1, RF sensed T-R relay kit	6.95

FM MINI MIKE KIT

A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case, mike, on-off switch, antenna, battery and super instructions. This is the finest unit available.

FM-3 kit	$12.95
FM-3 wired and tested	16.95

CLOCK KITS

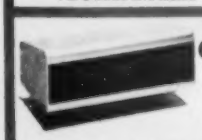

our Best Seller
your Best Deal

Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six .4" LED digits provide a highly readable display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, bronze, black, blue (specify).

Clock kit, 12/24 hour, DC-5	$22.95
Clock with 10 min. ID timer, 12/24 hour, DC-10	27.95
Alarm clock, 12 hour only, DC-8	24.95
12V DC car clock, DC-7	27.95

For wired and tested clocks add $10.00 to kit price.

Hard to find PARTS

LINEAR ICs		REGULATORS	
301	$ .35	78MG	$1.25
324	1.50	723	.50
380	1.25	3095	.85
380-8	.75	7805	.85
555	.45	78L05	.25
556	.85	7905	1.25
566	1.15	7812	.85
567	1.25	7912	1.25
1458	.50	7815	.65
3900	.50	**TTL ICs**	
CMOS ICs		74S00	.35
4011	.20	7447	.65
4013	.35	7475	.50
4046	1.85	7490	.50
4049	.40	74196TI	1.35
4518	1.25	**SPECIAL ICs**	
5369	1.75 ea	11C90	13.50
TRANSISTORS		10116	1.25
2N3904 type	10/1.00	4511	2.00
2N3906 type	10/1.00	5314	2.95
NPN 30W Pwr	3/1.00	5375AB	2.95
PNP 30W Pwr	3/1.60	7001	6.50
2N3055	.60	4059 - N	9.00
UJT 2N2646 type	3/2.00	7208	17.95
FET MPS102 type	3/2.00	**LEDs**	
UHF 2N5179 type	3/2.00	Jumbo red	8/1.00
MRF-238 RF	11.95	Jumbo green	6/1.00
SOCKETS		Jumbo yellow	6/1.00
8 pin	10/2.00	Mini red	8/1.00
14 pin	10/2.00	Micro red	8/1.00
16 pin	10/2.00	Bi-Polar	.75
24 pin	4/2.00	**FERRITE BEADS**	
28 pin	4/2.00	with info specs	15/1.00
40 pin	3/2.00	8 hole balun	5/1.00

Ramsey's famous MINI-KITS

FM WIRELESS MIKE KIT

Transmits up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type RM-2 has added sensitive mike preamp stage.

FM-1 kit $2.95 FM-2 kit $4.95

COLOR ORGAN/MUSIC LIGHTS

See music come alive! 3 different lights flicker with music. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300W. Great for parties, band music, nite clubs and more.

Complete kit, ML-1 $7.95

LED BLINKY KIT

A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volts.

Complete kit, BL-1 $2.95

VIDEO MODULATOR KIT

Converts any TV to video monitor. Super stable, tunable over ch. 4-6. Runs on 5-15V, accepts std. video signal. Best unit on the market!

Complete kit, VD-1 $6.95

TONE DECODER

A complete tone decoder on a single PC board. Features: 400-5000 Hz adjustable range via 20 turn pot, voltage regulation, 567 IC. Useful for touch-tone decoding, tone burst detection, FSK, etc. Can also be used as a stable tone encoder. Runs on 5 to 12 volts.

Complete kit, TD-1 $5.95

WHISPER LIGHT KIT

An interesting kit, small mike picks up sounds and converts them to light. The louder the sound, the brighter the light. Completely self-contained, includes mike, runs on 110VAC, controls up to 300 watts.

Complete kit, WL-1 $6.95

SUPER SLEUTH

A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2 W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker.

Complete kit, BN-9 $5.95

POWER SUPPLY KIT

Complete triple regulated power supply provides: variable +5 to 18 volts at 200 ma and +5V at 1 Amp. Excellent load regulation, good filtering and small size. Less transformers, requires 6.3V @ 1 A and 24 VCT.

Complete kit, PS-3LT $6.95

SIREN KIT

Produces upward and downward wail characteristic of a police siren. 5 W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker.

Complete kit, SM-3 $2.95

ramsey electronics

BOX 4072, ROCHESTER, N.Y. 14610

PHONE ORDERS CALL
(716) 271-6487

TERMS: Satisfaction guaranteed or money refunded. COD: add $1.50. Minimum order $5.00. Orders under $10.00: add $.25. Add 5% for postage, insurance, handling. Overseas: add 15%. NY residents: add 7% tax.

RS

These Low Cost SSB TRANSMITTING CONVERTERS

Let you use inexpensive recycled 10 or 11 meter SSB exciters on VHF!

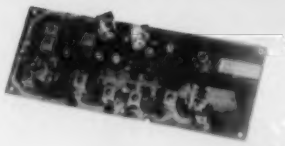

- Linear Converter for SSB, CW, FM, etc.
- A fraction of the price of other units
- 2W p.e.p. output with 1 mW drive
- Use low power tap on exciter or attenuator pad
- Easy to align with built-in test points
- Link with VHF RX converter for transceive

KIT ONLY $69.95

MODEL	INPUT (MHz)	OUTPUT (MHz)
XV2-1	28-30	50-52
XV2-2	28-30	220-222
XV2-3	28-30 (26-28)	222-224 (220-222)
XV2-4	28-30	144-146
XV2-5	28-30	145-147
XV2-6	26-28	144-146
XV2-7	144-146	50-52
XV2-8	144-146	220-222

FAMOUS HAMTRONICS PREAMPS

Let you hear the weak ones too!

Great for OSCAR. SSB. FM. ATV. Over 14,000 in use throughout the world on all types of receivers.

P9 Kit $12.95
P14 Wired $24.95
Specify band when ordering

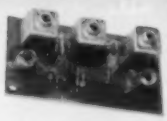

● Deluxe vhf model for applications where space permits ● 1⅛" x 3" ● Models available to cover any 4 MHz band in the 26 to 230 MHz range ● 12 Vdc ● 2 stages ● Ideal for OSCAR ● 20 dB gain

P8 Kit $10.95
Specify band when ordering

● Miniature vhf model for tight spaces – size only ½ x 2 ⅜ ● Models available to cover any 4 MHz band in the range 20 to 230 MHz ● 20 db gain ● 12 Vdc

P15 Kit $18.95
P35 Wired $34.95

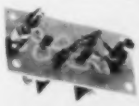

● Covers any 6 MHz band in UHF range of 380 to 520 MHz ● 20 dB gain ● 2 stages ● 12 Vdc

Easy to Build FET RECEIVING CONVERTERS

Let you receive OSCAR and other exciting VHF and UHF signals on your present HF or 2M receiver

VHF KIT STILL ONLY $34.95

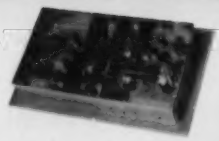

MODEL	RF RANGE	OUTPUT RANGE
C28	28-32 MHz	144-148
C50	50-52	28-30
C50-2	50-52	144-146
C144	144-146	28-30
C145	145-147	28-30
C146	146-148	28-30
C146	144-146	26-28
C220	220-222	28-30
C220-2	220-222	144-146
C110	Any 2 MHz of Aircraft Band	26-28 or 28-30
C110-ELT	121.5 (121.6)	CB Chan 9 (17)

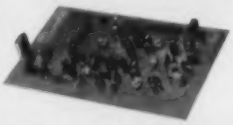

UHF KIT ONLY $34.95

MODEL	RF RANGE	OUTPUT RANGE
C432-2	432-434	28-30
C432-5	435-437	28-30
C432-4	432-436	144-148
C432-7	427.25	61.25
C432-9	439.25	61.25

Professional Quality VHF/UHF FM/CW EXCITERS

- Fully shielded designs
- Double tuned circuits for spurious suppression
- Easy to align with built-in test aids

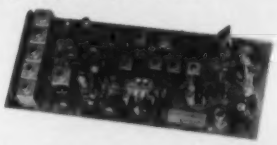

T50-50	6-chan, 6M, 2W Kit	$49.95
T50-150	6-chan, 2M, 2W Kit	$49.95
T50-220	6-chan, 220 MHz, 1½W Kit	$49.95
T40/T20	11-chan, 450 MHz, 200mW Kit	$49.95

See our Complete Line of VHF & UHF Linear PA's

- Use as linear or class C PA
- For use with SSB Xmtg Converters, FM Exciters, etc.

LPA 2-15 VHF PA, 2W in/15-20W out. Solid-state t/r switching. Kit only $59.95

LPA 2-45 VHF PA, 2W in/40-45W out. Can also be used with 8-10W drive. Kit price $109.95

LPA 4-10 UHF PA, 200-500mW in/6-10W out. Kit price only $79.95

New R75 One Channel VHF FM RECEIVER

Offers Unprecedented Range of Selectivity Options!

- New generation
- More sensitive
- More selective
- Uses crystal filters
- Smaller
- Easy to align

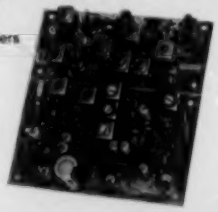

R75A Kit for monitor or weather satellite service. -60dB at ± 30 KHz. $69.95

R75B Kit for normal nbfm service. -60dB at ±17KHz, -80dB at ± 25 KHz. $74.95

R75C Kit for repeater service. -60dB at ± 14 KHz, -80dB at ± 22 KHz. $84.95

R75D Kit for split channel operation. Uses 8 pole crystal filter! -60dB at ± 9 KHz, -100dB at± 15 KHz... $99.95

Specify band: 10M, 6M, 2M, or 220 MHz. May also be used on adjacent commercial bands. Use 2M version for 137MHz WX satellite.

HAMTRONICS SIX CHANNEL VHF & UHF FM RECEIVERS

In use by the hundreds throughout the world. Unlimited applications.

- Commercial grade design
- Easy to build & align
- 70 or 100dB selectivity options
- Low system cost
- Compartmentized shielding

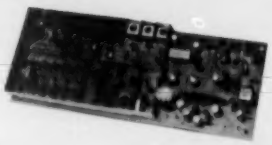

R70 VHF Receiver kit for 10M, 6M, 2M, 220 MHz or adjacent commercial bands $74.95
Optional xtal filter for 100dB adjacent channel... $10.00

R90 UHF Receiver kit for any 2MHz segment of 380 to 520 MHz band $89.95

IT'S EASY TO ORDER!

- Write or phone 716-392-9430 (Electronic answering service evenings & weekends)
- Use Credit Card. UPS COD. Check. Money Order
- Add $2.00 shipping & handling per order

Call or Write to Get FREE 1979 CATALOG With Complete Details

(Send 4 IRC's for overseas mailing)

hamtronics, inc.

65A MOUL RD · HILTON, NY 14468

DEALER INQUIRIES INVITED

NATIONAL SEMICONDUCTOR *NEW!*

CAR CLOCK MODULE - #MA6008

$6.99 each

SPECIAL OFFER: Two for $13

Originally used by HYGAIN to indicate time and channel on an expensive C.B. Mini size, self contained module. Not a Kit. Four digits plus flashing indicator for seconds. Includes MM5369 and 3.58 MHZ crystal for super accurate time base. With hookup data.

INCLUDES CRYSTAL TIMEBASE!
WORKS ON 12 VDC!

MFGR's CLOSEOUT
LIMITED QTY.

NATIONAL SEMICONDUCTOR — MILITARY TIME FORMAT!

JUMBO CLOCK MODULE

MA1008D BRAND NEW!

ASSEMBLED, NOT A KIT!

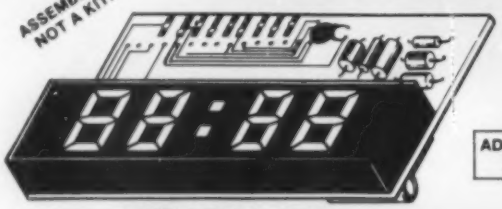

$4.95

REG. $9.95

ADD $1.95 FOR AC XFMR

FEATURES:
- FOUR JUMBO ½ INCH LED DISPLAYS
- 24 HR REAL TIME FORMAT
- 24 HR ALARM SIGNAL OUTPUT
- 50 OR 60 Hz OPERATION
- LED BRIGHTNESS CONTROL
- POWER FAILURE INDICATOR
- SLEEP & SNOOZE TIMERS
- DIRECT LED DRIVE (LOW RFI)
- COMES WITH FULL DATA

ZULU

50% OFF SALE!

PERFECT FOR USE WITH A TIMEBASE.

COMPARE AT UP TO TWICE OUR PRICE!

MANUFACTURER'S CLOSEOUT!

NATIONAL SEMICONDUCTOR

SIX DIGIT ALARM CLOCK CHIP

National's second generation clock chip.
24 Pin Dip. Super easy to use.

FEATURES:
12 HOUR DISPLAY ★ 24 HOUR ALARM
4 OR 6 DIGITS ★ ALARM TONE OUTPUT
SNOOZE ALARM ★ EASY LED INTERFACE
POWER FAIL IND. ★ BRIGHTNESS CONTROL
AM/PM INDICATION ★ SINGLE POWER SUPPLY
FAST AND SLOW SET ★ LOW POWER
HOUSE #
WE SUPPLY FULL DATA, SPECS.
MM5375AA

$2.49 each

3 FOR $5.95

HUGE SPECIAL PURCHASE!

NATIONAL SEMICONDUCTOR

JUMBO CLOCK MODULE

$6.95

3 FOR $13

(AC XFMR $1.95)

FEATURES:
- FOUR JUMBO ½ INCH LED DISPLAYS
- 12 HR REAL TIME FORMAT
- 24 HR ALARM SIGNAL OUTPUT
- 50 OR 60 Hz OPERATION
- LED BRIGHTNESS CONTROL
- POWER FAILURE INDICATOR
- SLEEP & SNOOZE TIMERS
- DIRECT LED DRIVE (LOW RFI)
- COMES WITH FULL DATA

ASSEMBLED! NOT A KIT!

MANUFACTURER'S CLOSEOUT!

PERFECT FOR USE WITH A TIMEBASE.

COMPARE AT UP TO TWICE OUR PRICE!

MICRO-MINI TOGGLE SWITCH

SPDT. By RAYTHEON.
MADE IN USA! WITH HDWR.

99¢ EACH

6 FOR $5

---

60 Hz CRYSTAL TIME BASE
$4.95 (Complete Kit)
Uses MM5369 CMOS divider IC with high accuracy 3.579545 MHZ Crystal. Use with all MOS Clock Chips or Modules. Draws only 1.5 MA. All parts, data and PC Board included.

FET SALE
2N4304. Brand New N Channel, Junction Fet. BVGD0-30V IDSS-15 MA Typ. 1500 uMHOS. TO-18 Plastic Case. Mfg. by Teledyne.
6 FOR $1

FAIRCHILD PNP "SUPER TRANSISTOR"
2N4402. TO-92 Plastic. Silicon PNP Driver. High Current. VCEO-40 HFE-50 to 150 at 150 MA. FT-150 MHZ. A super "BEEFED-UP" Version of the 2N3906.
8 FOR $1

JUMBO IC ASSORTMENT
All new not rejects. BIG computer mfg. Surplus. Some standard marked, many house numbered. TTL, DTL, LINEAR. All prime. 1st line.
50 for $1.59 500 for $12.95

MORE CLOCK CHIPS!

MM5316 - 4 Digit W/Alarm. An old reliable, work horse chip — **$1.99**

MK50380 - 4 Digit - Direct Drive on Readouts. Like FCM 7010 — **$1.99**

MK50250 - 6 Digits with Alarm. For multiplexed Led R.O. — **$2.95**

Digital Research Corporation

(OF TEXAS) ✓D20

P.O. BOX 401247 • GARLAND, TEXAS • (214)271-2461

TERMS: Add 30¢ postage, we pay balance. Orders under $15 add 75¢ handling. No C.O.D. We accept Visa, MasterCharge and American Express cards. Tex. Res. add 5% Tax. Foreign orders (except Canada) add 20% P&H. 90 Day Money Back Guarantee on all items.

16K EPROM CARD-S 100 BUSS

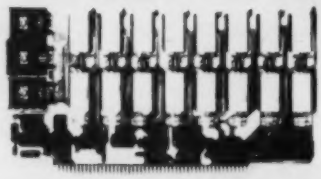

$59.95 KIT

OUR BEST SELLING KIT!

USES 2708's!

Thousands of personal and business systems around the world use this board with complete satisfaction. Puts 16K of software on line at **ALL TIMES!** Kit features a top quality soldermasked and silk-screened PC board and first run parts and sockets. All parts (except 2708's) are included. Any number of EPROM locations may be disabled to avoid any memory conflicts. Fully buffered and has WAIT STATE capabilities.

OUR 450NS 2708'S ARE $8.95 EA. WITH PURCHASE OF KIT

ASSEMBLED AND FULLY TESTED ADD $25

8K LOW POWER RAM KIT-S 100 BUSS
250 NS SALE!

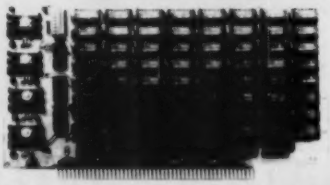

ADD $5 FOR 250NS!

$129 KIT

(450 NS RAMS!)

Thousands of computer systems rely on this rugged, work horse, RAM board. Designed for error-free, NO HASSLE, systems use.

KIT FEATURES:

1. Doubled sided PC Board with solder mask and silk screen layout.Gold plated contact fingers.
2. All sockets included.
3. Fully buffered on all address and data lines.
4. Phantom is jumper selectable to pin 67.
5. FOUR 7805 regulators are provided on card.

Blank PC Board w/Documentation **$29.95**
Low Profile Socket Set...**13.50**
Support IC's (TTL & Regulators) **$9.75**
Bypass CAP's (Disc & Tantalums) **$4.50**

ASSEMBLED AND FULLY BURNED IN ADD $30

16K STATIC RAM KIT-S 100 BUSS

$295 KIT

FULLY STATIC, AT DYNAMIC PRICES

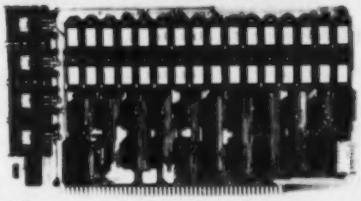

WHY THE 2114 RAM CHIP?

We feel the 2114 will be the next industry standard RAM chip (like the 2102 was). This means price, availability, and quality will all be good! Next, the 2114 is FULLY STATIC! We feel this is the **ONLY** way to go on the S-100 Buss! We've all heard the HORROR stories about some Dynamic Ram Boards having trouble with DMA and FLOPPY DISC DRIVES. Who needs these kinds of problems? And finally, even among other 4K Static RAM's the 2114 stands out! Not all 4K static Rams are created equal! Some of the other 4K's have **clocked** chip enable lines and various timing windows **just as critical** as Dynamic RAM's. Some of our competitor's 16K boards use these "tricky" devices. But not us! The 2114 is the ONLY logical choice for a trouble-free, straightforward design.

KIT FEATURES

1. Addressable as four separate 4K Blocks.
2. ON BOARD BANK SELECT circuitry. (Cromemco Standard!). Allows up to 512K on line!
3. Uses 2114 (450NS) 4K Static Rams.
4. ON BOARD SELECTABLE WAIT STATES.
5. Double sided PC Board, with solder mask and silk screened layout. Gold plated contact fingers.
6. All address and data lines fully buffered.
7. Kit includes ALL parts and sockets.
8. PHANTOM is jumpered to PIN 67.
9. LOW POWER: under 2 amps TYPICAL from the +8 Volt Buss.
10. Blank PC Board can be populated as any multiple of 4K.

BLANK PC BOARD W/DATA—**$33**
LOW PROFILE SOCKET SET—**$12**
SUPPORT IC'S & CAPS—**$19.95**
ASSEMBLED & TESTED—**ADD $30**
2114 RAM'S—**8 FOR $69.95**

COMPLEMENTARY POWER TRANSISTORS

SILICON NPN AND PNP. TO-220 CASE.
VCEO - 40V PD - 30 WATTS
FOR AUDIO POWER AMPS, ETC.

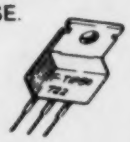

TIP29 - NPN
TIP30 - PNP

YOUR CHOICE
3 FOR $1

16K DYNAMIC RAM CHIP

16K X 1 Bits. 16 Pin Package. Same as Mostek 4116-4. 250 NS access. 410 NS cycle time. Our best price yet for this state of the art RAM. 32K and 64K RAM boards using this chip are readily available. These are new, fully guaranteed devices by a major mfg.

VERY LIMITED STOCK!

8 FOR $89.95

NOT ASSOCIATED WITH DIGITAL RESEARCH OF CALIFORNIA, THE SUPPLIERS OF CPM SOFTWARE.

450 NS!

2708 EPROMS

Now full speed! Prime new units from a major U.S. Mfg. 450 N.S. Access time. 1K x 8. Equiv. to 4-1702 A's in one package.

~~$15.75 ea.~~ **$9.95** ~~4 FOR $50.00~~

PRICE CUT

NATIONAL SEMICONDUCTOR ***NEW!***

CAR CLOCK MODULE - #MA6008

$6.99 each

Originally used by HYGAIN to indicate time and channel on an expensive C.B. Mini size, self contained module. Not a Kit. Four digits plus flashing indicator for seconds. Includes MM5369 and 3.58 MHZ crystal for super accurate time base. With hookup data.

INCLUDES CRYSTAL TIMEBASE! WORKS ON 12 VDC!

MFGR's CLOSEOUT LIMITED QTY.

EXPERIMENTER'S HEATING PLATE

Large Manufacturers Surplus. 5½x10½ in. Made of 3/8 in. tempered glass with heating element laminated on back. Works off 120 VAC. Protected by thermostat and two thermal fuses. Rated 120 Watts. Use for any heating applications. Perfect for heating ferric chloride to increase PC Board etching efficiency. Units are brand new, non-submersible.

WHILE THEY LAST—$2.99 each

MALLORY COMPUTER GRADE CAPACITOR

30,000 MFD 15 WVDC
Small: 3 x 2 Inches
$1.99 ea. 3 For $4.99

New! REAL TIME Computer Clock Chip

N.S. MM5313. Features BOTH 7 segment and BCD outputs. 28 Pin DIP. **$4.95 with Data**

Z-80 PROGRAMMING MANUAL

By MOSTEK, or ZILOG. The most detailed explanation ever on the working of the Z-80 CPU CHIPS. At least one full page on each of the 158 Z-80 instructions. A MUST reference manual for any user of the Z-80. 300 pages. Just off the press.

$12.95

GENERAL INSTRUMENT
FULL WAVE BRIDGE
4 AMP 600 PIV
3/4 IN. SQUARE - WITH LUGS

LOOK!

75¢ ea. 3 FOR $2 KLM-1

"THE COLOSSUS"
FAIRCHILD SUPER JUMBO LED READOUT

A full .80 inch character. The biggest readout we have ever sold! Super efficient. Compare at up to $2.95 each from others!

YOUR CHOICE
FND 843 Common Anode
FND 850 Common Cathode **$1.49 ea (8 for $6.95)**

Digital Research Corporation
(OF TEXAS)

P.O. BOX 401247 GARLAND, TEXAS 75040 • (214) 271-2461

TERMS: Add 30¢ postage, we pay balance. Orders under $15 add 75¢ handling. No C.O.D. We accept Visa, MasterCharge, and American Express cards. Tex. Res. add 5% Tax. Foreign orders (except Canada) add 20% P & H. 90 Day Money Back Guarantee on all items.

85 TON SURPLUS DEAL!!!

170,000 pounds of new surplus electronics was too much for either Digital Research Corporation or Bullet Electronics to handle ALONE! So we pooled our resources and rolled a convoy of four eighteen wheelers into our new Texas warehouse. You may order any of the **below** items from **either** company along with any other items from our respective ads elsewhere in 73. However, please DO NOT order Bullet Kits from Digital Research, or vice-versa.

TEMPERATURE CONTROLLED HEATING PLATE

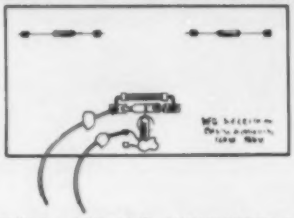

$2.99

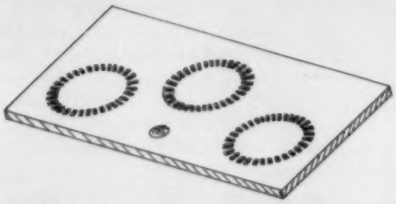

5⅜ x 10⅜ In. 120 VAC, 120 WATTS. Made of 1/4 In. tempered plate glass with Ni-Chrome heating element laminated to back. Element size is 4¼ x 9¼ Inches. Double protected by TI KLIXON Thermostat and two thermal fuses. Each also has neon ready light.

Besides the obvious use as a bun warmer, food warmer, coffee warmer, glue warmer, etc., our tests show this plate to be an excellent warmer for ferric chloride solution used in etching PC Boards by hobbyists. Typically increases etching efficiency by 300% over room temperature. Non-Submersible.

CMOS PARTS BONANZA

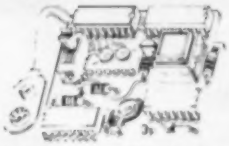

99¢ EACH

Complete Module: 2 x 1¾ In.

Contains: MC14553 3 DIGIT BCD COUNTER, MC14511 BCD to 7 segment decoder latch, CD4060 OSCILLATOR and RIPPLE COUNTER, CD4011 Nand gate. Also was square N.O. push button, 9V battery clip, SPDT Sub-Mini slide switch. Plus misc. resistor, caps, transistor. All parts easily removed. Reg. Dist. List on MC14553 alone is over $4 each!

FIBER POINT PENS

Writes on almost anything. Water Soluble ink. Designed to write on plastic etc. Black. Fine Tip. 49¢ Value.

SPECIAL: 6/$1 100/$14

PUSH BUTTON SWITCH

N.O. SPst. P.C. Mount. Same as used on CMOS Parts Bonanza at left.

5 FOR $1

4 BIT MICROPROCESSOR MODULE

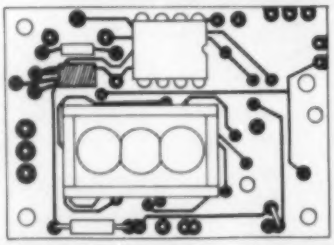

75¢ (MODULE ONLY) **3 FOR $2**

Originally custom designed for a large US Consumer Mfg. These were used as part of a weight loss program. Unit counts up to 25 bites with 24 flashes between bites to indicate chewing rate. Has 2 Digit LED readouts, adjustable on board oscillator, 4 Bit Microprocessor with PROM. Our experimentation shows this module has many applications for timing, pacing, etc. Also there are on board signals that can produce various beeping, warble and exotic tones. Some application data included. Complete units in case, as above: **$2.49 each.**

74C903 CMOS:

National Semiconductor. New CMOS Part. Hex Inverting Buffer. Use for interface from PMOS to TTL or CMOS. Can Drive LED'S. **6/$1**

ORDER FROM EITHER COMPANY: SEE TERMS OF SALE ON OUR RESPECTIVE ADS

Digital Research Corpration
(OF TEXAS)
P.O. BOX 401247 • GARLAND, TEXAS 75040 • (214)271-2461

BULLET ELECTRONICS
P.O. BOX 401244E • GARLAND, TEXAS 75040
(214)278-3553

BULLET ELECTRONICS

P.O. BOX 401244E
GARLAND, TX 75040
(214) 278-3553

* Phone orders accepted on credit card orders

WE APOLOGIZE!

JUST WHEN IT LOOKED LIKE ALL THE HOOPLA ABOUT OUR LOW COST HIGH CURRENT REGULATED **PS-14 POWER SUPPLY KIT** WAS FADING AWAY AND OUR **COMPETITORS** COULD BREATHE A LITTLE EASIER, WE GO AND DO SOMETHING LIKE THIS!

PS-15 POWER SUPPLY KIT
12V 30 AMPS

SPECS:

CONTINUOUS CURRENT	30 AMPS
REGULATION	200 MV LOAD AND LINE
RIPPLE	LESS THAN 300MV @ 30A
CURRENT LIMIT	ADJUSTABLE FOLDBACK TYPE
VOLTAGE OUTPUT	ADJUSTABLE 11.5 TO 14 VDC
SAFETY FEATURES	SHORT CIRCUIT PROTECTION; THERMAL SHUTDOWN; RF BY-PASSED

YOU GET:

- HUGE 40 AMP TRANSFORMER
- 3 LARGE HEATSINKS
- DRILLED & PLATED PC BOARD
- LARGE COMPUTER GRADE CAP
- ALL ELECTRONIC PARTS
- FUSES, FUSEHOLDERS, LINE CORD WIRE, MICA INSULATORS
- COMPLETE STEP-BY-STEP INSTRUCTIONS
- COMPLETE WARRANTY AND REPAIR SERVICE
- **WE PAY SHIPPING!***

PRICE DOES NOT INCLUDE CHASSIS, METERS OR JACKS

59.95

*Canadian Orders add $10.00 for Shipping and Insurance.

PS-14 Power Supply Kit.
Same features as above but 20 AMP max current. SHIPPING PAID. **45.00**

Regulator Card & Components: 14.95

OVP-2 OVERVOLTAGE PROTECTOR
Protect your expensive gear from overvoltage from transients or power supply malfunctions. Use with any fused power supply. Compatable with PS-14 or PS-15. Adjustable 10-20 VDC

MATCHED METER SET
A quality pair of American Made 3½" rectangular panel meters. 5% Accuracy. Modern styling.
SET 0-15VDC, 0-30ADC **12.95 set**

SPECIAL PACKAGE:
PS-15; OVP-2 AND METERS
SHIPPING PAID
75.00

SE-01 SOUND EFFECTS KIT

- ALL PARTS
- COMPLETE INSTRUCTIONS
- QUALITY PLATED & DRILLED BOARD
- IC SPECS INCLUDED
- RUNS ON ONE 9-VOLT BATTERY
- SMALL 3½" x 5"
- **$16.95** LESS SPEAKER & BATTERY
- 76477 CHIP IS INCLUDED. EXTRA CHIPS $2.95 EACH

OTHERS WILL SELL YOU THE CHIP, BUT ONLY **BULLET** CAN FURNISH YOU A COMPLETE KIT OF ALL THE PARTS YOU NEED TO PUT THE **T.I. 76477 SOUND CHIP** THROUGH ITS PACES! WE INCLUDE SPECS AND PROGRAMMING CHARTS. YOU WILL BE AMAZED AT THE THOUSANDS OF **SOUND EFFECTS** YOU CAN PRODUCE WITH OUR KIT! MAKE **PHASOR GUN, STEAM TRAIN, GUNSHOT** AND OTHER SOUNDS. BOARD HAS AUXILLARY PULSE GENERATOR, COMPARATOR AND MULTIPLEX OSC FOR EVEN MORE VERSATILITY.

7 WATT AUDIO AMP KIT
SMALL, SINGLE HYBRID IC AND COMPONENTS FIT ON A 2" x 3" PC BOARD (INCLUDED). RUNS ON 12 VDC. GREAT FOR ANY PROJECT THAT NEEDS AN INEXPENSIVE AMP. LESS THAN 3% THD @ 5 WATTS. COMPATIBLE WITH SE-01 SOUND KIT. **$5.95**

6 DIGIT AUTO/VAN CLOCK
NEW!
- LARGE ½" CHARACTERS (LED)
- QUARTZ XTAL TIMEBASE
- ALARM & SNOOZE OPTIONS
- NOISE FILTERING
- EASY TO ASSEMBLE
- 4⅝" x 3" x 1½"
- DRILLED & PLATED PC BOARDS

COMPLETE KIT 12 VDC **$16.95**

ULTRASONIC RELAY KIT
INVISIBLE BEAM WORKS LIKE A PHOTO ELECTRIC EYE. USE UP TO 25 FT. APART. COMPLETE KIT. ALL PARTS & PC BOARDS. **$21.50**

PARTS

301 OP AMP 8 LEAD CAN	3/1.00
723 VOLT REG. 10 LEAD CAN	.50
*13741 FET INPUT 741 MINI DIP	3/1.10
30,000 @ 15V COMPUTER GRADE	2.10
2N4400 NPN GEN. PURPOSE	8/1.00
2N4402 PNP COMPLIMENT	8/1.00
2N6028 P.U.T. W/SPECS	.50
LM380 2W AUDIO IC W/SPECS	1.00
LM377 DUAL LM380 W/SPECS	2.50
*7815 VOLT REG. 1A 15V	.89
*725 LOW NOISE OP AMP	.99
IL-1 OPTO ISOLATOR MINI DIP	.80
*MEM 631 DUAL GATE MOSFET, DIODE PROTECTED. SIMILAR TO 40673	.50
MV1624 VARICAP DIODE 10 PFD	.49
1N4003 1A 200V DIODE	15/1.00
TIP30 TAB PNP POWER	3/1.00
*MC1351P FM IF. DISC IC	.50

*INDICATES ITEM IS "HOUSE NUMBERED"

LED'S

JUMBO GREEN	4/.89
JUMBO RED	5/.89
MEDIUM RED (⅛")	.15
MEDIUM GRN OR YELLOW	.16

- NO COD'S
- SEND CHECK, M.O., M.C. OR VISA
- ADD 5% FOR SHIPPING
- CATALOG FREE UPON REQUEST
- ORDERS UNDER $10 ADD 75¢
- TEX. RESIDENTS ADD 5% SALES TAX
- FOREIGN ADD 10%

Reader Service—see page 211

RF POWER transistors ...

2NRF-1 2 GHz RF power transistor. Pd. max. (@ 25 degrees C) 3.5W, Pout min. @ 2 GHz 1.0W, Pin 310 mW, efficiency @ 2 GHz 30%, round shape, similar to RCA 2N5470. **$4.95**

2NRF-2 2 GHz RF power transistor. Pd. 8.7W, Pout 2.5W, Pin 300 mW, efficiency 33%, cross shape, similar to RCA TA8407. **$5.95**

2NRF-3 2 GHz RF power transistor. Pd. 21W, Pout 5.5W, Pin 1.25W, efficiency 33%, cross shape. Similar to RCA 2N6269. **$6.95**

2NRF-4 2 GHz RF power transistor. Pd. 29W, Pout 7.5W, Pin 1.5W, efficiency 33%, cross shape. Factory selected, prime 2N6269. **$7.95**

★★★★★★★★★★★★★★★★

★★MEMORY★★
★★★★CHIP★★★★
SPECIAL !!

It has never been less expensive to play with memory ... you can now buy 10 2102-L1 memory ICs for only $9.90. These are low power units, suitable for use with any 2 MHz computer system; they are fully static, and are new, prime, high quality parts.

MA1003 CLOCK/CASE COMBINATION $19.95

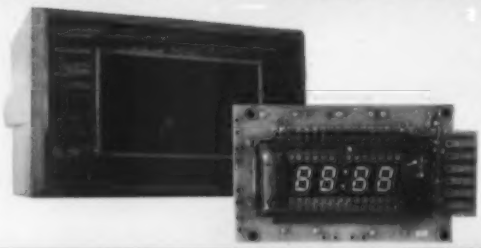

Easy to build — just add 12V DC and time setting switches. Since the MA1003 is car battery compatible and includes a built-in, precision crystal timebase, it's the easiest clock we've seen to get up and running in mobile applications. Unlike LED displays, the 4 blue/green fluorescent digits won't wash out in sunlight ... and for something like a van clock, they look really beautiful. The matching case includes an optical filter that brings out the best of the readouts, as well as mounting hardware. Why pay the high prices of built-in car or van clocks? Do it yourself, and save lots of bucks.

The MA1003 clock module is available separately for $16.50, while the case is available separately for $5.95 ... but we recommend the $19.95 combination price for maximum savings.

NEW FROM MULLEN COMPUTER PRODUCTS: H8 EXTENDER BOARD KIT

Mullen Computer Products has come up with another winner to go along with their **S-100 Extender Board Kit** (which is also available from us, and also costs $39). The **H8 Extender Board Kit** really takes the trouble out of testing or repairing H8 boards; it includes, among other things, jumper links in the power supply lines for insertion of fuses, Ammeters, current limiters, and the like, and a heavy-duty board that stands up to constant usage.

$39

12V, 8A POWER SUPPLY KIT $44.50

This is our longest-running kit, and the specs tell you why. Handles 8 Amps continuous, or 12A with a 50% duty cycle. Includes foldback current limiting, crowbar overvoltage protection, RF suppression, adjustable output 11-14V, more. Ideal for powering mobile transceivers, tape equipment, or TVs at home; also powers disc drives and makes a great lab bench supply. Easy to assemble — except for transformer, diodes, and filter caps, all parts mount on heavy-duty circuit board. Does not include case.

REGULATOR ICs

+ 5V, 1A, TO-220 (340/ 5T)	$1.25
+ 6V, 1A, TO-220 (340/ 6T)	$1.25
+ 8V, 1A, TO-220 (340/ 8T)	$1.25
+12V, 1A, TO-220 (340/12T)	$1.25
+15V, 1A, TO-220 (340/15T)	$1.25
+18V, 1A, TO-220 (340/18T)	$1.25
+24V, 1A, TO-220 (340/24T)	$1.25
− 5V, 1A, TO-220 (320/ 5T)	$1.35
− 6V, 1A, TO-220 (320/ 6T)	$1.35
− 8V, 1A, TO-220 (320/ 8T)	$1.35
−12V, 1A, TO-220 (320/12T)	$1.35
−15V, 1A, TO-220 (320/15T)	$1.35
−18V, 1A, TO-220 (320/18T)	$1.35
−24V, 1A, TO-220 (320/24T)	$1.35

16K MEMORY EXPANSION CHIP SET

$109 (3/$320)

For **Radio Shack-80, Exidy Sorcerer,** and **Apple** machines. Compare our features with similar chip sets: 250 ns access time, low power parts used exclusively, DIP shunts included, 1 year limited warranty, and easy-to-follow instructions that make memory expansion a snap — even for beginners!

BIPOLAR, REGULATED, VIRTUALLY BLOW-OUT PROOF, ¼ AMP PER SIDE POWER SUPPLY KIT: ONLY $15!

These power supplies are great for fixed voltage applications. Available in ±5V, ±6V, ±8V, ±9V, ±12V, and ±15V — specify project #13-XX, where the XX stands for the desired output voltage. Compact, simple assembly; does not include case.

TERMS: Add $1 handling to orders under $15. Allow up to 5% shipping, more for power supplies (excess refunded). Give street address for UPS delivery. Prices good through cover month of magazine. VISA® /Mastercharge® call our 24 hour order desk at **(415) 562-0636.** CODs OK with street address. Cal. res. add sales tax. **Thanks for your business!**

GODBOUT

BILL GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

G4

FREE FLYER: Our new catalogue is something you need if you're into electronics. Parts, kits, computers, electronic music, specials ... it's really packed, and it's free. Just send us your name and address, we'll take care of the rest. If you want 1st class delivery, please enclose 41¢ in stamps.

7400 TTL

SN7400N	16	SN7470N	29	SN74160N	80
		SN7472N	29		
SN7401N	18	SN7473N	35	SN74161N	80
SN7402N	18	SN7474N	35	SN74162N	80
SN7403N	18	SN7475N	49	SN74163N	1.95
SN7404N	18	SN7476N	35	SN74164N	80
SN7405N	20	SN7480N	50	SN74165N	80
SN7406N	29	SN7482N	99	SN74166N	1.25
SN7407N	29	SN7483N	59	SN74167N	1.95
SN7408N	20	SN7485N	79	SN74170N	1.50
SN7409N	20	SN7486N	35	SN74172N	6.00
SN7410N	18	SN7489N	1.75	SN74173N	1.25
SN7411N	25	SN7490N	65	SN74174N	80
SN7412N	25	SN7491N	59	SN74175N	80
SN7413N	40	SN7492N	43	SN74178N	79
SN7414N	70	SN7493N	43	SN74177N	79
SN7416N	25	SN7494N	65	SN74179N	1.95
SN7417N	25	SN7495N	65	SN74180N	79
SN7420N	20	SN7496N	65	SN74181N	1.95
SN7421N	29	SN7497N	3.00	SN74182N	79
SN7422N	39	SN74100N	89	SN74184N	1.95
SN7423N	25	SN74107N	39	SN74185N	1.95
SN7425N	29	SN74109N	59	SN74186N	9.95
SN7426N	29	SN74116N	1.95	SN74189N	3.95
SN7427N	25	SN74121N	35	SN74190N	1.25
SN7428N	39	SN74122N	39	SN74191N	1.25
SN7430N	20	SN74123N	49	SN74192N	79
SN7432N	25	SN74125N	49	SN74193N	79
SN7437N	25	SN74126N	49	SN74194N	80
SN7438N	25	SN74132N	79	SN74195N	80
SN7439N	25	SN74136N	75	SN74196N	80
SN7440N	20	SN74141N	79	SN74197N	89
SN7441N	89	SN74142N	2.95	SN74198N	1.49
SN7442N	49	SN74143N	2.95	SN74199N	1.49
SN7443N	75	SN74144N	2.95	SN74S200	4.95
SN7444N	75	SN74145N	79	SN74251N	1.79
SN7445N	75	SN74147N	1.95	SN74279N	79
SN7446N	69	SN74148N	1.29	SN74283N	2.25
SN7447N	59	SN74150N	89	SN74294N	3.95
SN7448N	79	SN74151N	59	SN74295N	3.95
SN7450N	20	SN74152N	59	SN74365N	69
SN7451N	20	SN74153N	59	SN74366N	69
SN7453N	20	SN74154N	99	SN74367N	69
SN7454N	20	SN74155N	79	SN74368N	69
SN7458A	25	SN74156N	79	SN74390N	1.95
SN7460N	20	SN74157N	65	SN74393N	1.95

C/MOS

CD4000	23	CD4028	89	CD4070	55
CD4001	23	CD4029	1.19	CD4071	23
CD4002	23	CD4030	49	CD4072	49
CD4006	1.19	CD4031	99	CD4076	1.39
CD4007	25	CD4033	49	CD4081	23
CD4008	49	CD4035	99	CD4082	23
CD4010	49	CD4040	1.19	CD4093	99
CD4011	23	CD4041	1.25	CD4098	2.49
CD4012	25	CD4042	99	MC14409	14.95
CD4013	39	CD4043	89	MC14410	14.95
CD4014	1.39	CD4044	89	MC14411	14.95
CD4015	1.19	CD4046	1.79	MC14419	4.95
CD4016	49	CD4047	2.50	MC14433	19.95
CD4017	1.19	CD4048	1.35	MC14506	75
CD4018	99	CD4049	49	MC14507	99
CD4019	49	CD4050	49	MC14562	14.50
CD4020	1.19	CD4051	1.19	MC14583	3.50
CD4021	1.19	CD4052	1.19	CD4508	2.95
CD4022	1.19	CD4056	2.95	CD4510	1.39
CD4023	23	CD4059	9.95	CD4511	1.29
CD4024	79	CD4060	1.49	CD4515	2.95
CD4025	23	CD4066	79	CD4518	1.79
CD4026	2.25	CD4068	39	CD4520	1.79
CD4027	69	CD4069	45	CD4566	2.75

74C00

74C00	39	74C85	2.49	74C163	2.49
74C02	39	74C86	1.95	74C164	2.49
74C04	39	74C90	2.49	74C173	2.60
74C08	.49	74C93	1.95	74C192	2.49
74C10	39	74C95	1.95	74C193	2.49
74C14	1.95	74C95	1.95	74C195	2.49
74C20	39	74C107	1.25	74C822	5.95
74C30	39	74C151	2.90	74C823	6.25
74C42	1.95	74C154	3.00	74C925	9.95
74C48	2.49	74C157	2.15	74C926	9.95
74C73	89	74C160	2.49	80C95	1.50
74C74	89	74C161	2.49	80C97	1.50

LINEAR

.1MEG	1.75	LM308N	89	LM710N	79
LM106H	99	LM309H	89	LM711N	39
LM300H	80	LM340K-18	1.35	LM723H,N	55
LM301CN,H	35	LM340K-24	1.35	LM733N	1.00
LM302H	75	LM340T-5	1.25	LM739N	1.19
LM304H	1.00	LM340T-6	1.25	LM741CN,H	35
LM305H	60	LM340T-8	1.25	LM741-14N	39
LM307CN,H	35	LM340T-12	1.25	LM747N,H	79
LM308CN,H	1.00	LM340T-15	1.25	LM748N,H	39
LM309H	1.10	LM340T-18	1.25	LM1310N	2.95
LM309K	1.25	LM340T-24	1.25	LM1458CN,H	59
LM310CN	1.15	LM358N	1.00	MC1488N	1.30
LM311N,H	.90	LM370N	1.95	MC1489N	1.39
LM312H	1.95	LM373N	3.25	LM1496N	89
LM317K	6.50	LM377N	4.00	LM1556V	1.75
LM318CN,H	1.50	LM380N	1.25	MC1741SCP	3.00
LM319N	1.35	LM390CN	.99	LM2111N	1.95
LM320K-5	1.35	LM392N	1.79	LM2901N	2.95
LM320K-5.2	1.35	LM382N	1.79	LM3053N	1.50
LM320K-12	1.35	NE5911N	0.00	LM3086N	1.49
LM320K-15	1.35	NE510N	6.00	LM3900N,34011	.49
LM320K-18	1.35	NE529N	4.95	LM3905N	1.25
LM320K-24	1.35	NE531H/V	3.95	LM3089N	1.25
LM320T-5	1.25	NE536T	6.00	MC3556N	59
LM320T-5.2	1.25	NE540L	6.00	80J65	4.95
LM320T-8	1.25	NE544N	4.95	LM7345ON	49
LM320T-12	1.25	NE550N	1.30	75451CN	39
LM320T-15	1.25	NE555V	.39	75452CN	.39
LM320T-18	1.25	NE559N	.99	75453CN	.39
LM320T-24	1.25	NE560B	5.00	75454CN	.39
LM323K-5	5.95	NE561B	5.00	75491CN	.79
LM324N	1.00	NE562B	5.00	75492CN	.89
LM339N	.99	NE565A,H	1.75	75493N	.69
LM340K-5	1.35	NE566CN	1.75	75494CN	.89
LM340K-6	1.35	NE567V,H	.99	RC4136	1.25
LM340K-8	1.35	NE570N	4.95	RC4151	2.85
LM340K-12	1.35	LM703CN,H	.69	RC4196	5.95
LM340K-15	1.35	LM709N,H	.29	RC4195	4.49

74LS00TTL

74LS00	29	74LS47	89	74LS138	89
74LS01	29	74LS48	89	74LS139	89
74LS02	29	74LS51	29	74LS151	89
74LS03	29	74LS53	29	74LS153	89
74LS04	35	74LS54	29	74LS157	89
74LS05	39	74LS55	29	74LS158	1.15
74LS08	29	74LS73	49	74LS161	1.15
74LS09	35	74LS74	49	74LS162	1.15
74LS10	29	74LS75	59	74LS163	1.15
74LS11	75	74LS76	45	74LS164	1.25
74LS13	59	74LS78	49	74LS175	99
74LS14	1.25	74LS83	89	74LS181	2.49
74LS15	35	74LS85	1.25	74LS190	1.15
74LS20	29	74LS86	45	74LS191	1.15
74LS21	35	74LS90	59	74LS192	1.15
74LS22	35	74LS92	75	74LS193	1.15
74LS26	35	74LS93	75	74LS194	1.15
74LS27	35	74LS95	99	74LS195	1.15
74LS28	35	74LS96	1.15	74LS253	99
74LS30	29	74LS107	45	74LS257	89
74LS32	35	74LS109	45	74LS258	1.15
74LS37	45	74LS112	45	74LS260	69
74LS40	35	74LS123	1.35	74LS279	75
74LS42	89	74LS125	89	74LS367	75
		74LS132	99	74LS368	75
		74LS136	49	74LS670	2.49

EXCITING NEW KITS

JE600 HEXADECIMAL ENCODER KIT

NEW!

FEATURES:
- Full 8 bit latched output for microprocessor use
- 3 User Definer keys with one being bi-stable operation
- Debounce circuit provided for all 19 keys
- LED readout to verify entries
- Easy interfacing with standard 16 pin IC connector
- Only +5VDC required for operations

FULL 8 BIT LATCHED OUTPUT—19 KEYBOARD

The JE600 Encoder Keyboard provides two separate hexadecimal digits produced from sequential key entries to allow direct programming for 8 bit microprocessor or 8 bit memory circuits. Three (3) additional keys are provided for user operations with one having a bistable output available. The outputs are latched and monitored with LED readouts. Also included is a key entry strobe.

JE600 ..... $59.95

Digital Thermometer Kit

NEW!

- Dual sensors—switching control for indoor/outdoor or dual monitoring
- Continuous LED .8" ht. display
- Range -40°F to 199°F / -40°C to 100°C
- Accuracy ±1° nominal
- Set for Fahrenheit or Celsius reading
- Slim, walnut case - AC wall adapter incl.
- Size: 3-1/4"Hx6-5/8"Wx1-3/8"D

JE300 ..... $39.95

DISCRETE LEDS

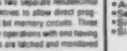

	.250" dia.				.125" dia.		
XC556R	red	5/$1		XC208R	red	5/$1	
XC556G	green	4/$1		XC209G	green	4/$1	
XC556Y	yellow	4/$1		XC209Y	yellow	4/$1	
XC556C	clear	4/$1		XC209Y	clear	4/$1	
	.200" dia.				.100" dia.		
XC22R	red	5/$1		XC526R	red	5/$1	
XC22G	green	4/$1		XC526G	green	4/$1	
XC22Y	yellow	4/$1		XC526Y	yellow	4/$1	
	.170" dia.			XC526C	clear	4/$1	
MV10R	red	4/$1			.196" dia.		
	.085" dia.			XC111R	red	5/$1	
MV50	red	6/$1		XC111G	green	4/$1	
	INFRA-RED LED			XC111Y	yellow	4/$1	
	1/4"x1/4"x1/16" flat			XC111C	clear	4/$1	
	.5/$1						

TIMEX T1001
LIQUID CRYSTAL DISPLAY CLASS II
FIELD EFFECT

4 DIGIT - .5" CHARACTERS
THREE ENUNCIATORS
2.00" X 1.20" PACKAGE
INCLUDES CONNECTOR

T1001-Transmissive $7.95
T1001A-Reflective 8.25

DISPLAY LEDS

TYPE	POLARITY	HT	PRICE	TYPE	POLARITY	HT	PRICE
MAN 1	Common Anode-red	270	2.95	MAN 6730	Common Anode-red ± 1	560	99
MAN 2	5 x 7 Dot Matrix-red	300	4.95	MAN 6740	Common Cathode-red-D.D.	560	99
MAN 3	Common Cathode-red	125	.25	MAN 6750	Common Cathode-red ± 1	560	99
MAN 4	Common Cathode-red	167	1.95	MAN 6760	Common Anode-red	560	99
MAN 7G	Common Anode-green	300	1.25	MAN 6780	Common Cathode-red	560	99
MAN 7Y	Common Anode-yellow	300	99	DL701	Common Anode-red ± 1	560	99
MAN 72	Common Anode-red	300	99	DL704	Common Cathode-red	300	99
MAN 74	Common Cathode-red	380	1.25	DL707	Common Anode-red	300	99
MAN 82	Common Anode-yellow	300	99	DL726	Common Cathode-red	500	1.49
MAN 84	Common Cathode-yellow	300	99	DL741	Common Anode-red	630	1.25
MAN 3620	Common Anode-orange	300	99	DL746	Common Anode-red ± 1	630	1.49
MAN 3630	Common Anode-orange ± 1	300	99	DL747	Common Anode-red	880	1.49
MAN 3640	Common Cathode-orange	300	99	DL749	Common Cathode-red ± 1	630	1.49
MAN 3650	Common Anode-orange	300	99	DL750	Common Cathode-red	880	1.49
MAN 4640	Common Cathode-orange	400	99	DL338	Common Cathode-red	110	.35
MAN 4710	Common Anode-red	400	99	FND70	Common Cathode	250	69
MAN 4730	Common Anode-red ± 1	400	99	FND358	Common Cathode ± 1	357	99
MAN 4740	Common Cathode-red	400	99	FND358	Common Cathode	357	75
MAN 4810	Common Anode-yellow	400	99	FND503	Common Cathode(FND500)	500	99
MAN 4840	Common Cathode-yellow	400	99	FND507	Common Anode (FND510)	500	99
MAN 6610	Common Anode-orange-D.D.	560	99	5082-7730	Common Anode-red	300	1.30
MAN 6630	Common Anode-orange ± 1	560	99	HDSP-3400	Common Anode-red	600	2.10
MAN 6640	Common Cathode-orange D.D.	560	99	HDSP-3403	Common Cathode-red	600	2.10
MAN 6650	Common Cathode-orange ± 1	560	99	5082-7300	4 x 7 sgl. Digit-RHDP	600	19.95
MAN 6660	Common Anode-red	560	99	5082-7302	4 x 7 Sgl. Digit-LHDP	600	19.95
MAN 6680	Common Cathode-orange	560	99	5082-7304	Overrange character (±1)	600	15.00
MAN 6710	Common Anode-red D.D	560	99	5082-7340	4 x 7 Sgl. Digit Hexadecimal	600	22.50

RCA LINEAR

CA3013T	2.15	CA3082N	2.00
CA3023T	2.56	CA3083N	1.60
CA3035T	2.49	CA3086N	.85
CA3039T	1.35	CA3089N	3.75
CA3046N	1.30	CA3130T	1.35
CA3059N	3.25	CA3140T	1.25
CA3060N	3.25	CA3160T	1.25
CA3080T	.85	CA3401N	.49
CA3081N	2.00	CA3600N	3.90

CALCULATOR CHIPS/DRIVERS

MM5725	$2.95
MM5738	2.95
DM8654	2.00
DM8655	1.00
DM8867	.75
DM8869	.75
8374 7 seg	
C.A. LED driver	1.50

CLOCK CHIPS

MM5309	$4.95
MM5311	4.95
M-m5312	4.95
MM5314	4.95
MM5316	6.95
MM5318	9.95
MM5369	2.95
MM5387/1988A	4.95
MM5841	9.95

MOTOROLA

MC14OL7	$4.95
MC14OL8	5.75
MC1436L	2.95
MC3302P	1.00
MC3051P	3.50
MC4015(74410)	7.50
MC4024P	3.95
MC4040P	6.95
MC4044P	4.50

IC SOLDERTAIL — LOW PROFILE (TIN) SOCKETS

	1-24	25-49	50-100
8 pin LP	$17	16	15
14 pin LP	20	19	18
16 pin LP	22	21	20
18 pin LP	29	28	27
20 pin LP	34	32	30
14 pin ST	$ 27	25	24
16 pin ST	30	27	25
18 pin ST	35	32	30
24 pin ST	49	45	42

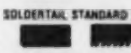

SOLDERTAIL STANDARD (TIN)

	1-24	25-49	50-100
8 pin LP	$ .37	35	35
14 pin LP	38	37	36
16 pin LP	45	44	43
18 pin LP	60	59	58
20 pin LP	63	62	61
28 pin ST	$ .99	90	81
36 pin ST	1.39	1.26	1.15
40 pin ST	1.59	1.45	1.30

SOLDERTAIL STANDARD (GOLD)

8 pin SG	$ .70	63	57
14 pin SG	1.10	1.00	90
16 pin SG	1.65	1.48	1.35
18 pin SG	1.75	1.58	1.45
24 pin SG	2.70	2.43	2.20
28 pin SG	3.50	3.15	2.85
36 pin SG	4.65	4.18	3.80
40 pin SG	5.25	4.73	4.30

WIRE WRAP SOCKETS (GOLD) LEVEL #3

8 pin WW	$ .35	35	31
14 pin WW	.45	41	37
16 pin WW	.50	46	37
18 pin WW	.63	42	41
20 pin WW	.73	68	62
22 pin WW	$ .95	85	75
24 pin WW	1.05	95	85
28 pin WW	1.25	1.20	1.10
36 pin WW	1.59	1.45	1.30
40 pin WW	1.75	1.55	1.40

1/4 WATT RESISTOR ASSORTMENTS – 5%

ASST. 1	5 ea	10 OHM - 1 MEG	50 PCS	$1.75
ASST. 2	5 ea	10 OHM - 1 MEG	100 PCS	1.75
ASST. 3	5 ea	10 OHM - 1 MEG	150 PCS	1.75
ASST. 4	5 ea	10 OHM - 1 MEG	200 PCS	1.75
ASST. 5	5 ea	10 OHM - 1 MEG	250 PCS	1.75
ASST. 6	5 ea	10 OHM - 1 MEG	300 PCS	1.75
ASST. 7	5 ea	10 OHM - 1 MEG	350 PCS	1.75
ASST. 8R	Includes Resistor Assortments 1-7 (350 PCS.)			$9.95 ea.

$10.00 MINIMUM ORDER — U.S. Funds Only Spec Sheets – 25¢
California Residents — Add 6% Sales Tax 1979 Catalog Available—Send 41¢ stamp

FREE A 1979 CATALOG

Jameco ELECTRONICS

J1 PHONE ORDERS WELCOME (415) 592-8097

MAIL ORDER ELECTRONICS – WORLDWIDE
1021 HOWARD AVENUE, SAN CARLOS, CA 94070
ADVERTISED PRICES GOOD THRU JULY

TELEPHONE/KEYBOARD CHIPS

AY-5-9100	Push Button Telephone Dialler	$14.95
AY-5-9200	Repertory Dialler	14.95
AY-5-9500	CMOS Clock Generator	4.95
AY-5-2376	Keyboard Encoder (58 keys)	14.95
HD0165	Keyboard Encoder (16 keys)	7.95
74C922	Keyboard Encoder (16 keys)	5.95

ICM CHIPS

ICM7045	CMOS Precision Timer	24.95
ICM7205	CMOS LED Stopwatch/Timer	19.95
ICM7207	Oscillator Controller	7.50
ICM7208	Seven Decade Counter	19.95
ICM7209	Clock Generator	6.95

NMOS READ ONLY MEMORIES

MCM6571	128 X 9 X 7 ASCII Shifted with Greek	13.50
MCM6574	128 X 9 X 7 Math Symbol & Pictures	13.50
MCM6575	128 X 9 X 7 Alphanumeric Control Character Generator	13.50

MISCELLANEOUS

TL074CN	Quad Low Noise bi-fet Op Amp	2.49
TL494CN	Switching Regulator	4.49
TL496CP	Single Switching Regulator	1.75
11C90	Divide 10/11 Prescaler	19.95
95H90	Hi Speed Divide 10/11 Prescaler	11.95
4N33	Photo-Darlington Opto-Isolator	3.95
MM50240	Top Octave Freq. Generator	17.50
DS0026CH	5MHz 2-phase MOS clock driver	3.75
TIL308	.27" red num. display w/integ. logic chip	10.50
MM5320	TV Camera Sync. Generator	14.95
MM5330	4½ Digit LOPIC Logic Book (Special)	3.95
LD110/111	3½ Digit A/D Converter Set	25.00/set

LITRONIX ISO-LIT 1
Photo Transistor Opto-Isolator (Same as MCT 2 or 4N25)
2/99¢

SN 76477
SOUND GENERATOR
- Generates Complex Sounds
- Low Power - Programmable

3.95 each

TV GAME CHIP AND CRYSTAL
AY-3 8500-1 and 2.01 MHZ Crystal (Chip & Crystal includes score display, 6 games and select angles, etc.) **7.95/set**

XR205	$8.40			XR2242CP	1.50
XR210	4.40	**EXAR**		XR2284	4.25
XR215	4.40			XR2556	3.20
XR320	1.50	JE2206KA	14.95	XR2567	2.99
XR-L565	1.50	JE2206KD	19.95	XR3403	1.25
XR555	.59	XR1800	3.20	XR4136	1.25
XR566	.99	XR2206	4.40	XR4151	2.85
XR567CP	.99	XR2207	3.85	XR4194	4.50
XR567CT	1.25	XR2208	5.20	XR4200	3.60
XR2310P	1.30	XR2209	1.75	XR4212	2.85
XR1488CN	3.85	XR2211	5.25	XR4558	.75
XR1488	1.39	XR2212	4.35	XR4739	1.15
XR1489	1.39	XR2240	3.45	XR4741	1.47

DIODES

TYPE	VOLTS	W	PRICE	TYPE	VOLTS	W	PRICE
				1N4002	100 PIV	1 AMP	12/1.00
				1N4003	200 PIV	1 AMP	12/1.00
1N746	3.3	400m	4/1.00	1N4004	400 PIV	1 AMP	12/1.00
1N751	5.1	400m	4/1.00	1N4005	600 PIV	1 AMP	10/1.00
1N752	5.6	400m	4/1.00	1N4006	800 PIV	1 AMP	10/1.00
1N753	6.2	400m	4/1.00	1N4007	1000 PIV	1 AMP	10/1.00
1N754	6.8	400m	4/1.00	1N3880	50	200m	6/1.00
1N757	9.0	400m	4/1.00	1N4148	75	10m	15/1.00
1N759	12.0	400m	4/1.00	1N4154	35	10m	12/1.00
1N960	6.2	400m	4/1.00	1N4448	75	10m	15/1.00
1N965	15	400m	4/1.00	1N4734	5.6	1w	28
1N5232	5.6	500m	28	1N4735	6.2	1w	28
1N5234	6.2	500m	28	1N4736	6.8	1w	28
1N5235	6.8	500m	28	1N4738	8.2	1w	28
1N5236	7.5	500m	28	1N4742	12	1w	28
1N5242	12	500m	28	1N4744	15	1w	28
1N5245	15	500m	28	1N1183	50 PIV	35 AMP	1.60
1N4148	25	40m	6/1.00	1N1184	100 PIV	35 AMP	1.70
1N458	150	7m	5/1.00	1N1185	150 PIV	35 AMP	1.70
1N485A	180	10m	5/1.00	1N1186	200 PIV	35 AMP	1.80
1N4001	50 PIV	1 AMP	12/1.00	1N1188	400 PIV	35 AMP	3.00

SCR AND FW BRIDGE RECTIFIERS

C3ED	15A ea 400V	SCR(2N1840)	$1.95
C3BM	35A ea 600V	SCR	1.95
2N2328	1.6A ea 300V	SCR	.50
MDA 980-1	12A ea 50V	FW BRIDGE REC	1.95
MDA 980-3	12A ea 200V	FW BRIDGE REC	1.95

TRANSISTORS

C10881	50	2N3055	89	2N3904	4/1.00
MPSA05	20	2N3055	89	2N3905	4/1.00
MPSA06	5/1.00	MJE3055	1.00	2N3906	4/1.00
TIS97	6/1.00	2N3390	5/1.00	2N3903	4/1.00
TIS98	6/1.00	2N3398	5/1.00	2N4123	6/1.00
40405	1.75	PN2907	3/1.00	PN4249	4/1.00
40410	1.75	PN3569	4/1.00	PN4250	4/1.00
40673	1.75	PN3569	4/1.00	PN4400	4/1.00
2N918	4/1.00	MPS3638A	5/1.00	2N4401	4/1.00
2N2219A	2/1.00	MPS3702	5/1.00	2N4402	4/1.00
2N2222A	4/1.00	2N3704	5/1.00	2N4403	4/1.00
2N2222A	5/1.00	MPS3704	5/1.00	2N4400	5/1.00
PN2222 Plastic	7/1.00	2N3705	5/1.00	2N5086	4/1.00
2N2369	5/1.00	MPS3705	5/1.00	2N5087	4/1.00
2N2369A	4/1.00	2N3708	5/1.00	2N5088	4/1.00
MPS2369	5/1.00	MPS3708	5/1.00	2N5089	4/1.00
2N2484	4/1.00	2N3707	5/1.00	2N5129	5/1.00
2N2905	4/1.00	2N3711	5/1.00	PN5134	5/1.00
2N2907	4/1.00	2N3724A	85	PN5138	5/1.00
PN2907 Plastic	7/1.00	2N3725A	1.00	PN5139	5/1.00
2N2925	5/1.00	2N3772	2.25	2N5210	5/1.00
MJE2955	1.25	2N3823	1.00	2N5449	3/1.00
2N3053	2/1.00	2N3903	5/1.00	2N5961	3/1.00

CAPACITOR CORNER

50 VOLT CERAMIC DISC CAPACITORS

	1-9	10-99	100+
10 pf	05	04	03
22 pf	05	04	03
47 pf	05	04	03
100 pf	05	04	03
220 pf	05	04	03
470 pf	05	04	03
.001mf	05	04	03
.002	05	04	03
.0047mf	05	04	03
.01mf	12	10	07
.02	12	10	07
.047mf	12	10	07
.1mf	12	10	07
.22mf	12	10	07

	1-9	10-99	100+
1.0mf	25	22	17
1.5mf	30	28	21
2.2mf	31	27	22
3.3mf	31	27	22
4.7mf	32	28	23
6.8mf	36	31	25
10mf	40	35	29
15mf	53	46	40

+20% TIPPED TANTALUMS (SOLID) CAPACITORS

	1-9	10-99	100+
1.0mf	30	28	21
2.2mf	31	27	22
3.3mf	31	27	22
4.7mf	32	28	23
6.8mf	36	31	25
10mf	40	35	29
15mf	53	46	40

MINIATURE ALUMINUM ELECTROLYTIC CAPACITORS

	Axial Lead			Radial Lead		
47/6V	15	13	10	47/25V	15	13	10
1.0/50V	16	14	11	47/50V	16	14	11
3.3/50V	17	14	12	68/16V	15	13	10
4.7/25V	15	13	10	1.0/25V	16	14	11
10/25V	15	13	10	1.0/50V	16	14	11
10/50V	16	14	12	2.7/16V	15	13	10
22/25V	17	15	12	4.7/25V	15	13	10
22/50V	24	20	16	4.7/50V	16	14	11
47/25V	19	17	15	10/16V	14	12	09
47/50V	25	21	19	10/25V	15	13	10
100/25V	24	20	18	10/50V	16	14	12
100/50V	35	30	26	47/50V	24	21	19
220/25V	30	26	25	100/16V	19	16	14
220/50V	45	41	38	100/25V	24	20	18
470/25V	33	29	27	100/50V	35	30	26
1000/16V	55	50	45	220/16V	23	17	16
2200/16V	70	62	55	470/25V	31	28	25

ASSOCIATED RADIO

913-381-5900
8012 CONSER BOX 4327
OVERLAND PARK, KANSAS 66204

CALL US WITH YOUR REQUIREMENTS

AMERICA'S NO. 1 Real Amateur Radio Store

Associated Wants to TRADE - BUY - SELL
GOT YOUR BEST DEAL? THEN CALL US AT
913-381-5900 - NO TRADE? ASK FOR EXT. 12

NOTE: SEND $1.00 FOR OUR CURRENT CATALOG OF NEW AND RECONDITIONED EQUIPMENT.

*ALSO WE PERIODICALLY PUBLISH A LIST OF UNSERVICED EQUIPMENT AT GREAT SAVINGS. A BONANZA FOR THE EXPERIENCED OPERATOR. TO OBTAIN THE NEXT UNSERVICED BARGAIN LIST, SEND A SELF ADDRESSED STAMPED ENVELOPE.

CUSTOMERS THE WORLD OVER ARE CLAMORING FOR OUR GIANT "ONE CENTERS"

SALE

A PENNY MORE GETS YOU TWO

Spectrol

"SKINNY-TRIMS" POTENTIOMETERS

SINGLE TURN FLAT Type-63 Cat. No. 92CU3806

10	1K	25K
20	2K	50K
50	2.5K	100K
100	5K	200K
200	10K	500K
500	20K	1 Meg

3/8" square! Single turn style. Screwdriver adjust. 20% tolerance. 0.5 Watt ratings, cermet construction. PC leads.

2 FOR $1.29

4 FOR $1.30

ORDER BY CAT. NO. AND VALUE

25 AMP BRIDGE RECTIFIERS

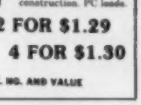

	PIV	SALE	2 FOR
☐	25	1.25	1.30
☐	50	1.95	1.99
☐	100	2.25	2.30
☐	200	2.95	2.99
☐	400	3.50	3.51
☐	600	4.25	4.30
☐	800	4.95	4.99

sorry, no choosing

Order No. 2373 & voltage

"CRIMP-ON" COAX PLUG PL-259

2 for $1.29

Quick, Easy plier crimping. No Soldering! Strip insulation squeeze. Mates to RG-239. For RG58/U. 50 U. Cat. No. 92CU5890

4 for $1.30

"THE FAT" MALLORY AA MERCURY BATTERY

$1.49

2 for $1.50

Cat. No. 92CU5679

1N4000 Epoxy Rectifiers

Cat. No.	Type	Volts	Sale	1¢ SALE!
2377	1N4001	50	10 for $.75	20 for $.76
2378	1N4002	100	10 for .85	20 for .86
2379	1N4003	200	10 for .95	20 for .96
2380	1N4004	400	10 for 1.19	20 for 1.20
2381	1N4005	600	10 for 1.39	20 for 1.40
2382	1N4006	800	10 for 1.49	20 for 1.50
2383	1N4007	1000	10 for 1.59	20 for 1.60

LEDS!

YOUR CHOICE 6 for $1.29 12 for $1.30

Order by Cat. No.

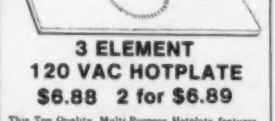

☐	1780	MICRO TOPHAT RED
☐	1942	MED YELLOW STUBBY
☐	1962	MICRO SINGLE PIN RED
☐	2130	JUMBO RED
☐	2150	JUMBO GREEN
☐	2160	MICRO RED
☐	2700	JUMBO RED CLEAR

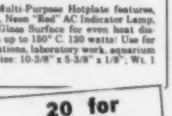

3 ELEMENT 120 VAC HOTPLATE

$6.88 2 for $6.89

This Top Quality, Multi-Purpose Hotplate features, Built-In Thermostat, Neon "Red" AC Indicator Lamp, and 1/8" Textured Glass Surface for even heat distribution. Generates up to 150° C. 120 watts: Use for photographic applications, laboratory work, aquarium heater, plants, etc. Size: 10-3/8" x 5-3/8" x 1/8". Wt. 1 lb. 2 oz.

Cat. No. 92CU5723

1 AMP 1000 VOLT MINI RECTIFIERS

20 for $2.49

40 for $3.50

Famous 1N4007 epoxy rectifiers, marked (color coded). 100% Prime, with axial leads. 1000's of hobby uses.

Cat. No. 92CU2363

■	6-OPTO-COUPLER, 1500V isolation, hobby material, u test(#2629A)	1.29	12 for 1.30
■	6-2N915 UHF TO-18 TRANSISTORS(#1423)	1.29	12 for 1.30
■	73-MOLEX SOCKETS, Type M1938-4, makes 14 to 40 pin sockets(#1609)	1.29	150 for 1.30
■	6-CALCULATOR AC ADAPTOR JACK, standard threads 3 terminals(#2318)	1.29	12 for 1.30
■	50-TUBE SOCKETS, 4,5,6,7 pin tubes, asst(#3839)	1.29	100 for 1.30
■	40 CTS RESISTOR NETWORK, asst styles and values, singles and dips,(#3699)	1.29	80 for 1.30
■	10-BULLETT RECTIFIERS, 7.5 amp, 200V, axial(#84)	1.29	20 for 1.30
■	6-READOUTS, MAN-3, common cath, LED, the claw, RED(#3338)	1.29	12 for 1.30
■	8-LEDS, asst sizes and shapes, red, green, yellow, amber(#3869)	1.29	16 for 1.30
■	PHOTO FLASH ELECTRO. CAP, 600 MF @ 360V(#3897)	1.29	2 for 1.30
■	4 MICRO SWITCH, plunger style. N.O. contacts, SPDT, solder tabs,(#5785)	1.29	8 for 1.30
■	10 TRANSISTOR/LED SOCKETS, 1/4" high, 3-pc leads, plastic base,(#5745)	1.29	20for 1.30
■	5-SLIDE VOLUME CONTROLS, asst of popular values, for HiFi(#2318)	1.29	10 for 1.30
■	10-D33021 TRANSISTORS, low power, silicon, hfe-60, TO-92(#5627)	1.29	20 for 1.30
■	50 1/4 WATTERS, asst value carbon resistors, some 5%ers,(#5797)	1.29	100 for 1.30
■	60-CERAMIC CAPS, Incl. NPO's, neg. coef. N750's asst values(#590)	1.29	120 for 1.30
■	10-TV/FM SPLICERS, for 300 ohm shielded twin lead. Bakelite.(#3547)	1.29	20 for 1.30
■	30'#30 WIRE-WRAP WIRE, fits all tools and machines, continuous length,(#3803)	1.29	60 for 1.30
■	10-G.E. POWER TAB TRANSISTORS, D40N1,N2, some NS, TO-220(#5629)	1.29	20 for 1.30
■	2-¼" BLOCK TRIM POTS, 200K, 15-TURN PC-leads.(#2535)	1.29	4 for 1.30
■	1-12VDC SMIL REED RELAY, spst, N.O. 2200 ohms, 7/8" x 5/16" x 5/16"(#5515)	1.29	2 for 1.30
■	50-TEMP. COEFFICIENT VOLTAGE REF. DIODES, asst volt, +50%(#5647)	1.29	100 for 1.30
■	6 -SLIDING TRIM POTS, PRECISION, 50% yield(#3309)	1.29	12 for 1.30
■	60-pc-PRECUT, PRETINNED WIRE, various lengths and colors(#1971)	1.29	120 for 1.30
■	5 DUAL DIGIT READOUTS, H.P. 5082 Type, Bubble Magnifier,(#5748)	1.29	10 for 1.30
■	4 CALCULATOR KEYBOARDS, 17 keys and up, multi-function,(#5777)	1.29	8 for 1.30
■	10-5K POTS, audio taper, plastic snap-in mounting(#5124)	1.29	20 for 1.30
■	10-1&2 MEG DUAL POTS, audio taper, snap-in mounting(#5125)	1.29	20 for 1.30
■	50-1 AMP ZENERS, wide asst of values, untested(#1964)	1.29	100 for 1.30
■	12-SCR'S & TRIACS, 10 AMP, asst values, untested(#2087)	1.29	24 for 1.30
■	3-QUADRACS, 10 AMP, 100% prime, 50-100-200V, TO-220(#3048)	1.29	6 for 1.30
■	20-MINI RECTIFIERS, 1½ AMPS, 25V, epoxy, axial(#5374)	1.29	40 for 1.30
■	10-2N3704 TRANSISTORS, silicon, TO-92 case, hfe-300 100%(#5625)	1.29	20 for 1.30
■	50-IF TRANSFORMERS, asst sizes(#35A9)	1.29	100 for 1.30
■	10-TV CHEATER CORD JACKS(#5519)	1.29	20 for 1.30
■	10-2N3765 TRANSISTORS, silicon, TO-92 case, hfe-150 100%(#5626)	1.29	20 for 1.30
■	4-1.5V SILVER OXIDE WATCH BATTERIES, specify; RW-15,18(#5063)	1.29	8 for 1.30
■	3-LCD WATCH READOUTS, 3½" digits, 7 seg, dim 1½ x 1"(#5066)	1.29	6 for 1.30
■	100 RED BLOCK DISC CAPS, asst values, 50% material(#1690)	1.29	200 for 1.30
■	10-INSTRUMENT KNOBS, asst styles and colors, ¼" shaft(#5121)	1.29	20 for 1.30
■	4-MIKE HOLDERS, for CB's and other mobile rigs(#5634)	1.29	8 for 1.30
■	50-1N4688 RECTIFIERS, asst to 800V, u test(#2594)	1.29	100 for 1.30
■	20-UPRIGHT ELECTROS, asst'd values & capacitance.(#3226A)	1.29	40 for 1.30
■	1-UHF TUNER, solid state, standard type(#2927)	1.29	2 for 1.30
■	6-IT'S A SNAP, 9 VDC BAT-clip, red n black lead(#2852)	1.29	12 for 1.30
■	8-1400 VOLT "RED BALL" RECTIFIERS, axial 1 AMP(#2590)	1.29	16 for 1.30
■	20-1N4148 SWITCHING DIODES, 4 nsec. axial(#3000)	1.29	40 for 1.30
■	6-AMP QUADRACS, w/trigger diode up 600V(#3620)	1.29	12 for 1.30
■	1-8' LINE CORD, 2-cond., 18 gauge, moulded plastic plug, black, new.(#3803)	1.29	2 for 1.30
■	40-SQUARE DISC STYLE CHOKES, color coded(#3203)	1.29	80 for 1.30
■	30-TRANSISTORS TO92 2N4400 series, u test(#3291)	1.29	60 for 1.30
■	6-TRANSISTORS TRANSFORMERS, audio, inter, etc mini(#3295)	1.29	12 for 1.30
■	15-PRINTED CKT TRIMMER POTS, asst values, etc(#3346)	1.29	30 for 1.30
■	7-2N3055 HOBBY NPN TRANSISTORS, TO-3(#3771)	1.29	14 for 1.30

***Buy any item on this page and get 2nd item of the same cat. no. for only one penny!**

■	25-DTL FAIRCHILD IC's, gates and flip flops, Dip, 100%(#3709)	1.29	50 for 1.30
■	1-24 VOLT 50 MIL. TRANSFORMER, 115V input, open frame, 1x1x3/4"(#5631)	1.29	2 for 1.30
■	5-SPST PUSHBUTTON MOMENTARIES, rt. angle, pc mt, on-on'(#5635)	1.29	10 for 1.30
■	1 3" x 4" DOUBLE SIDED PC BOARD, hi-quality, copper plated,(#5694)	1.29	2 for 1.30
■	30-RADIO AND TV KNOBS, asst styles, sizes(#217)	1.29	60 for 1.30
■	60-TUBULAR CAPACITORS, asst. volts and sizes(#219)	1.29	120 for 1.30
■	4-ROCKER SWITCHES, DPDT, solder tab leads,(#3382)	1.29	8 for 1.30
■	50-POWER RESISTORS, 3,5,7 w. axial, pop sizes(#228)	1.29	100 for 1.30
■	$25 SURPRISE, all kinds of parts in a pak(#294)	1.29	2 for 1.30
■	12-PANEL SWITCHES, rotary, slide, toggle etc(#295)	1.29	24 for 1.30
■	60 COILS AND CHOKES,rf, parasitic, if, etc(#297)	1.29	120 for 1.30
■	60-TERMINAL STRIPS, up to 4 solder lugs(#334)	1.29	120 for 1.30
■	25-PLASTIC TRANSISTORS, untested and hobby, TO-92, TO-18,(#2604A)	1.29	50 for 1.30
■	50-MICA CAPACITORS, asst values(#373)	1.29	100 for 1.30
■	10-SETS RCA PLUGS AND JACKS, phono(#402)	1.29	20 for 1.30
■	60 DISC CAPACITORS, asst values long leads(#437)	1.29	120 for 1.30
■	20-TRANSISTOR ELECTRO'S, asst up and ax(#453)	1.29	40 for 1.30
■	75-HALF WATTERS, resistors, color coded, asst(#454)	1.29	150 for 1.30
■	35-SILVER MICAS, red backs, axial, asst(#455)	1.29	70 for 1.30
■	4-PUSH BUTTON, SPST, PANEL, N.C. 125V, @ 1A(#5289)	1.29	8 for 1.30
■	100-GERMANIUM DIODES, axial leads, u test(#642)	1.29	200 for 1.30
■	100-STABISTORS, Regulator, sensing and computer. Axial, ex. yield(#3148)	1.29	200 for 1.30
■	100-PRINTED CIRCUIT ½ WATT RESISTORS, asst(#1060)	1.29	200 for 1.30
■	12-TRANSISTOR SOCKETS, asst npn and pnp types(#651)	1.29	24 for 1.30
■	50-3 AMP SILICON RECTIFIERS, axial, asst V(#665)	1.29	100 for 1.30
■	50-POLYSTYRENE CAPS, plastic coated, prec.(#1052)	1.29	100 for 1.30
■	30-4" CABLE TIES, non-clip white plastic(#5217)	1.29	60 for 1.30
■	30-pc-HEAT SHRINK, asst sizes, 50% shrinkage(#3248)	1.29	60 for 1.30
■	2-5.1V, 5%, 10W, STUD ZENER, DO-4 case(#5287)	1.29	4 for 1.30
■	10-RCA PHONO JACKS, chasis mount, teflon base(#5119)	1.29	20 for 1.30
■	15-THERMISTORS, asst types, styles & values(#2048)	1.29	30 for 1.30
■	4-5-DIGIT 7-SEGMENT READOUTS, in flat pak case(#5616)	1.29	8 for 1.30
■	25-METAL CAN TRANS., asst, prime, hobby, TO-1, TO-5, TO-18,(#2603A)	1.29	50 for 1.30
■	1-"FOTO-FET" N CHANNEL, Crystalonics, J-Sealed Fiber Transistors(#1169)	1.29	2 for 1.30
■	1-VOLTAGE REGULATOR, TO202 case, 12V 600MA(#1900)	1.29	2 for 1.30
■	2-3 DIGITS ON A DIP, LED, red, DL-33(#1887)	1.29	4 for 1.30
■	3-MM5262 2K DYNAMIC RAM, specify type(#3459)	1.29	6 for 1.30
■	10-2N711 HIGH SPEED SWITCHING TRANSISTORS, TO18, npn(#3374)	1.29	20 for 1.30
■	2-15W HI POWER TRANSISTORS, 220V, npn, TO66(#2797)	1.29	4 for 1.30
■	1-HEAVY DUTY LINE CORD, 8 ft., 2 cond. #18 guage, black,(#5803)	1.29	2 for 1.30
■	1-MM5312 DIGITAL CLOCK CHIP, 100%(#1525)	1.29	2 for 1.30
■	2-MM5725 4 FUNCTION CALCULATOR CHIP, 100%(#2836)	1.29	4 for 1.30
■	25 PLASTIC TRANSISTORS, untested, TO-92,(#5731)	1.29	50 for 1.30
■	3-10 AMP 25V BRIDGE RECT, comb style(#2447)	1.29	6 for 1.30
■	1-ALLEN BRADLEY POT, 10K, 2-14 watts, type-I, 2x¼" shaft(#1748)	1.29	2 for 1.30
■	6-LINEAR SWITCHING TRANSISTORS, 2N2905, pnp, TO5(#3375)	1.29	12 for 1.30
■	50-2 AMP CYLINDRICAL RECT., up to 1K, u test(#4006)	1.29	100 for 1.30
■	1-HEAVY DUTY LINE CORD, 2 cond. 6 ft. #18 guage, white,(#5804)	1.29	2 for 1.30
■	10-2N2222 (or equiv.), TO-18 metal case(#1992)	1.29	20 for 1.30
■	10-DATA ENTRY SWITCHES, SPST, 1 amp, norm open 125V(#5321)	1.29	20 for 1.30
■	8-TRANSISTOR RADIO EARPHONES, 8 ohms imped(#2944)	1.29	16 for 1.30
■	15-FLUORESCENT OVERFLOW READOUT TUBES, w/leads(#3288)	1.29	30 for 1.30
■	2-ALUMINUM HEAT SINKS, for TO-220(#5338)	1.29	4 for 1.30
■	1-2N5001 80V TRANSISTORS STUD(#2800)	1.29	2 for 1.30

"ONE PENNY MORE GETS YOU TWO" MINI LECTROS Plastic

MFD.	VOLTS	SALE	LEADS	2 FOR
25	15	.14	Axial	.15
25	25	.17	Axial	.18
25	50	.24	P.C.	.25
50	15	.17	Axial	.18
50	25	.19	Axial	.20
50	100	.21	Axial	.22
100	15	.23	Axial	.24
100	25	.25	P.C.	.26
100	50	.35	Axial	.36
100	100	.39	Axial	.40
180	15	.23	Axial	.24
200	15	.24	P.C.	.25
220	25	.32	P.C.	.33
250	15	.29	Axial	.30
250	25	.32	Axial	.33
250	50	.45	Axial	.46
300	15	.31	Axial	.32
300	25	.33	P.C.	.34
500	15	.33	P.C.	.34
800	25	.36	P.C.	.37
900	50	.39	Axial	.40
1000	15	.35	P.C.	.36

Order by Cat. No. 92CU5715 and Value

40 CHANNEL CB BOARD

$9.99

2 for $10

Poly Paks buys up factory close-out from Hy gain on you gain!" Boards have Featured 9 Watt Amp Chip, RF and Mod. Transistors, and National Semi MM series PLL. May be used for 10 meter conversion (see 6 month series "CB to 10" in 73 Mag.) The parts alone make it an offer you can't refuse.

Cat. No. 92CU5680

MOTOROLA STYLE "SANDY DISC" 10 AMP RECTIFIERS

	PIV	SALE	2 FOR
☐	50	.35	.35
☐	100	.39	.39
☐	200	.43	.44
☐	400	.54	.55
☐	600	.61	.62
☐	800	.70	.71
☐	1000	1.19	1.20

• Heavy Sand Type Hermet Construction

Cat. No. 92CU5677 (Specify voltage)

"BEEM 'O' LIGHT" LASER DIODES

Rated @ 5-9 Watts Wavelength 904 nm.

$5.99

2 for $6

Cat. No. 92CU4998

LED WATCH GUTS

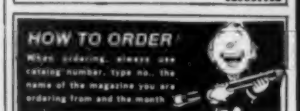

$1.49

2 for $1.50

(Ladies') Cat. No. 92CU5115C

(Men's) Cat. No. 92CU5116B

HOW TO ORDER

When ordering, always use catalog number, type no., the name of the magazine you are ordering from and the month

POLY PAKS®

COD's MAY BE PHONED!

P.O. BOX 942-A7
SO. LYNNFIELD, MA 01940

Terms: Add Postage **Rated:** Net 30
Phone: (617) 245-3828.
Retail: 16-18 Del Carmine St.
MINIMUM ORDER: $8 Wakefield, MA

7294 N.W. 54 STREET
MIAMI, FLORIDA 33166

SURPLUS ELECTRONICS CORP.

PHONE: (305) 887-8228
TWX: 810-848-6085

WHOLESALE - RETAIL

PL259's/SO 239's
Quality American Made
10/$5.00 100/$35.00
50/$20.00 1000/$300.00

E. F. Johnson NICAD
12.0 V. 1.2 AH @ 10 hr rate
4 1/2" x 1 7/8" x 1 3/4" $1495ea.

E F Johnson External Battery Charger Model 239-0206-001 Output
14.5 V dc @ 50 mA. $3.50 ea.

E. F. Johnson S Meter
Edge Meter 250 UA. Fits in 5/8" x 1-3/8" hole. MTG holes on each end 1-1/4" behind panel. Black scale 0-5 bottom 1-20 top
$1.25 ea. 5/$5.00

Edge meter same as above with silver scale and reads SWR 1-10
$1.25ea 5/$5.00

E. F. Johnson Signal Strength Meter 200 UA 2½" x 2½" Sq. mounts in 1¾" hole 1" behind panel. Scale: 1-30 db top 0-5 bottom.
$4.95ea 5/$20.00

E. F. Johnson Desk Top Microphone
Ceramic Element/High Imp
was ~~$26.00~~ now $15.00
While They Last

NEW E.F. Johnson Power Mic/Less Cord
Desk Top Style $19.95 ea

ASTATIC T-UG8-D104
PREAMP Desktop microphone w/crystal element 3 Pin Plug $35 ea.

CB SPECIAL
Brand new printed circuit board assembly. Used in all HyGain 40 channel CB transceivers. Fits many other manufacturers' units also. Squelch pot/volume control/ channel selector switch not included.
1- 9—7.50 ea.
10-49—6.50 ea.
50-99—6.00 ea.
100-up—5.50 ea
Board Dimensions 6" x 6½"

NEW Hy-Gain Remote 40ch CB Less Case, Speaker & Control Mic (as is) $14.95 ea

New 40 CH CB Boards w/40 ch SW
1-9 $10.50 ea 50-99 $9.00 ea
10-49 $9.50 ea 100-up $8.50 ea

Serviceman Special
New Hy-Gain 40ch CB Less Case, Speaker & Knobs (as is) $14.95 ea

IC SOCKETS
Cambion
Gold Plated Wire Wrap
14 pin .35 ea 10/$3.00
16 pin .38 ea 10/$3.30

MODEM CABLE
50' cable contains 13 # 22 ga. wire DB-25p with DB-51226-1 cover on one end
$6.50 ea 10/$50.00

EFJ CRYSTAL OVENS
6V/12V 75°
$5.00 ea.

MOTOROLA SRF 574
house marked
9W 175 MHz Amp.
$5.00 ea.

PANEL METERS
$4.00 ea ·2 for $7.00
10-0-10 dc Amps / 25-0-25 dc Volts } 2¼" x 3"
0-25 dc Volts / 0-50 ac Volts } 2¼" x 2¼"
·Shunt Required·

MINI TOGGLE SW C&H
SPDT
$1.00 ea 6/$5.00

E. F. Johnson
40ch Selector Switch
$3.50ea

2 SIDED .062 Copper Clad Board
9¼" x 10¼"
$2.00ea 3/$5.00

Sony RK64A
2 conductor mini phono plug w/patch cord 3'6" long $2.00ea

POLYFOAM COAX—50 OHM
Equal to RG174
$4.95/100'
Low Loss
Polyfoam
Coax Cable

MUFFIN FANS
3 Blades, 110 Vac, 4¾" sq.
Removed from equipment—
Excellent condition—$4.95

RECEIVER FRONT ENDS
Made by EFJ
132-174 MHz
$12.00 ea.

CMOS
RCA CD 4012 AE
Dual 4 In Nand Gate
6/$1.00 100/$10.00
50/$6.00 1000/$80.00

12 Vdc RELAY
SPST Open Frame
5 Amp Contacts
Mfg-Magnecraft
$1.50 ea 4/$5.00

12 Vdc RELAY
SPST 35 Amp Contacts
Open Frame
Rugged, great for mobile use
$4.50 ea 5/$20.00

TRIMMER CAPS
Small enough to fit in your watch—
3.5 to 20 pF
5 to 30 pF
$.75 ea., 2 for $1.25
5 for $3.00

D Cell Nicad
mfg. by G. E. 2.50 ea
1.2 volts 3.5 amp hrs.
cat No. 41B004 AD08G5

Computer Grades
34,000 uf @50 Vdc 3.00 ea
3" diam x 6½" high Mallory

Coax Connectors
UG-273/U BNC-F/UHF-M 2.50
UG-255/U BNC-M/UHF-F 3.00
UG-146A/U N-M/UHF-F 4.50
UG-83B/U N-F/UHF-M 4.50
UG-175 RG-58 Adapt. .20
UG-176 RG-59 Adapt. .20

CRYSTAL FILTERS
10.7 3/Lead
Can Type
$3.00 ea.

CERAMIC IF FILTERS
EFC L455K
$3.50 ea.

CAPS
2200 UF @ 16V
Radial Leads
.25 ea. 10/$2.00

White Porcelain Egg Insulator
1½" x 1" 50¢ ea.
3 for $1.25

GOLD PLATED CARD EDGE CONNECTORS

Double Row/Wire Wrap .100

25 pins	$3.49 ea	10/$30.00
30 pins	$3.96 ea	10/$32.00
50 pins	$5.43 ea	10/$45.00

Double Row/Solder Eyelet .156

6 pins	$1.10 ea	10/$9.00
15 pins	$1.55 ea	10/$12.50
22 pins	$2.08 ea	10/$17.00
43 pins	$3.66 ea	10/$30.00

22 pins/Double Row/Dipped Solder
.156 $2.08 ea 10/$17.00

22 pins/Double Row/Wire Wrap
.156 $2.44 ea 10/$19.00

TERMS: *All material guaranteed ● If for any reason you are not satisfied, our products may be returned within 10 days for a full refund (less shipping). Please add $3 for shipping and handling on all orders. Additional 5% charge for shipping any item over 5 lbs. COD's accepted for orders totaling $50.00 or more. All orders shipped UPS unless otherwise specified. Florida residents please add 4% sales tax. Minimum order $15.00.*

EQUIPMENT / COMPONENTS / WIRE & CABLE / ACCESSORIES

SEMICONDUCTORS SURPLUS

S63

2822 North 32nd Street/Unit -1 Phoenix, Arizona 85008 (602) 956-9423

We accept checks, MasterCharge, and Visa

Prices subject to change without notice

R.F. CONNECTORS

UG-1095A/U	$3.99
UG-58/U	3.29
UG-30C/U	3.00
UG-27C/U	3.50
PL-259	.50
SO-239	.43
UG-175	.36
PL-258	2.99
UG-106	.69
UG-177	.69
UG-274/U	3.27
UG-447/U	1.50
UG-492	3.69
UG-306/U	3.00
UG-646/U	3.29
UG-260B/U	1.59
UG-1094/U	.90
UG-701/U	3.00
UG-212C/U	3.00

TUBES

3-500Z	$90.00
572B/T160L	34.00
6146	5.09
6146A	5.99
6146W	7.95
811A	12.95
811	9.95
4CX250B	29.95
4CX250R	32.95
6KD6	4.99
6LF6	4.99
6LQ6/6JE6	6.25
8950	6.65
2E26	6.00
3B28	5.00
4X150A	15.00
6360/A	7.95
6939	5.95
7289/2C39	4.95
8072	45.00

FERRITE BEADS

12/$.89 or
100/$4.00

TORIDAL CORES

T-37-6	6/1.00
25/4.00,	50/6.00
100/10.00	

1N914/1N4148

30/$1.00 or
120/$3.00

R.F. TRANSISTORS

2N2857	$1.80
2N2857JAN	2.45
2N2947	17.00
2N3375	7.00
2N3553	1.80
2N3818	6.00
2N3866	1.09
2N3866JAN	2.70
2N2866JANTX	4.43
2N3925	6.00
2N3948	2.00
2N3950	26.25
2N3960	4.70
2N4072	1.70
2N4427	1.09
2N4877	2.57
2N4957	3.50
2N5108	3.90
2N5109	1.55
2N5179	.59
2N5589	4.60
2N5583	5.00
2N5590	6.30
2N5591	10.35
2N6080	5.45
2N6081	8.80
2N6082	10.75
2N6083	12.00
2N6084	13.20
2N6095	10.35
2N6097	19.35
MRF502	.69
MRF8004	.75
SS2548	.75
40280	3.50
40281	10.90
40282	11.90

TRIMMERS 5-80pf

45¢ each or 10/3.50
or 100/25.00

CHOKE (U252) 2.5mh

150ma 30MHz
2/$1.00

TRIMMER CAPS

small enough to
fit in your watch
3.5-11pf 75¢ each
or 10/$6.00

PISTON CAPS 1.2-10pf

75¢ each or 10/$5.50

F.E.T.'s

MPF4391	$ .75 or 10/ 6.50
MPF112	.69 or 10/ 5.50
MPF102	.43 or 10/ 3.50
40673	1.39 or 10/10.00
3N128	1.35 or 10/10.00
2N5248	.60 or 10/ 4.50
MPF131	.60 or 10/ 5.00
2N4303	.45 or 10/ 3.50
2N3958	2.95 each
MFE2000	.90 or 10/ 8.00
MFE2001	.99 or 10/ 8.00
MFE2008	4.20 or 10/36.00
MFE2009	4.80 or 10/39.00
MFE3002	3.35 each
MMF-5	5.00 each
MFE120	1.00 or 10/ 8.50
2N3436	2.25 each
2N4416	1.00 each
MFE131	1.05 each

MICROWAVE DIODES

1N21D	$ 1.40
1N21C	1.05
1N21WE	2.00
1N23B	1.05
1N23C	1.05
1N23CR	2.00
1N23E	2.00
1N23F	4.10
1N23WE	2.10
1N25	3.03
1N121WE	4.00
1N286	5.00
1N416E	5.00
1N446	8.00
1N3655A	4.00
1N5153	15.00
1N5711	1.20

ADDITIONAL R.F. TRANSISTORS

40894	$ 2.50
MRF454/568BLYCF	17.10

LM566V VCO/FUNCTION GENERATOR

$.99 each

LM340T-5 & LM340T-12

75¢ each

SEMTECH MINISTIC

high voltage rectifiers SFMS
20K 20,000PIV
20ma $1.99 each

1500PIV 1.5 AMPS RECTIFIERS

10/$1.50

MC4024P & MC4044P

$3.25 each

HEP 170 2.5 Amps

1000PIV 10/$2.00 or 100/$14.50

POTTER & BRUMFIELD 12VDC RELAYS

4PDT	3 Amps	$2.95
SPDT	25 Amps	$5.95
2PDT	3 Amps	$1.99
4PDT	25 Amps	$6.99

BRIDGES 24 AMPS 500PIV

$2.99 each

4CX250B/R SOCKETS AND CHIMNEYS NEW

$14.95 per set (1 socket, 1 chimney)

B&W COILS

1206T	$3.99
2006T	$7.99

FAIRCHILD REGULATOR 78H05KC

$6.99 each

TUBES

6146B	$6.50

MINIMUM ORDER $5.00

Minimum Shipping $1. Insurance 35¢ per $100. COD charges 85¢ to street address only! We prefer street address as we ship UPS and P.O. Box #'s take up to 50% longer to deliver. We accept VISA or Mastercharge. Please list complete card number and expiration date. Allow 10% extra for shipping of heavy items. *We reserve the right to change prices without notice.* All items listed are subject to prior sale. Some items listed are in small quantities.

ALDELCO ELECTRONIC CENTER

OVERVOLT 12

Crow Bar circuit protects Transceivers & Tape Decks from runaway power supply voltage that can zap expensive components. OV 12 causes fuse in Power Supply to blow if voltage exceeds preset level (approx. 16 to 18 volts). Rated at 25 Amperes. $ 7.95
Model OV5. Protects 5 Volt circuits. Triggers at 7.5 Volts $8.95
Other units available at 3.3 to 100 Trigger Voltages $10.95 ea

Aldelco can supply 3 PC boards. Silk screened front panel and complete instructions for only $12.50 & shipping.

SOME PARTS USED IN COUNTER

11C90 Prescaler	14.50
74C925 Multiplex	9.95
F9368 Driver (2)	7.90
1 MHz XTAL	7.95
10.60 pF trim cap	.80
Register kit	1.75
Capacitor kit	5.50

See six page construction article in Dec. 1978 73 Magazine

BUILD A 6 DIGIT 500 MHz FREQUENCY COUNTER

COMPLETE LUNCH COUNTER KIT $79.95
Includes a reprint of six page construction article from Dec. 1978 73 Magazine

For reprint only send 50 cents for handling

RF TRANSISTORS

SD1018-4	40W	4.5db	450MHz	380-4LFL	15.25
SD1074	50W	11db	30MHz	500-6LFL	21.15
SD1076	75W	13	50	500-6LFL	24.00
SD1088	25W	6	450	500-6LFL	23.25
SD1089	40W	5	450	500-6LFL	27.15
SD1143	10W	10	200	MT72	10.95
SD1158	12W	5.3	200	TO117	12.30
SD1272	30W	6	220	MT72	9.60
SD1278	50W	10	50	MT72	16.30
SD1416	70W	6.7	175	500-6LFL	26.80
SD1428	45W	6.5	175	500-6LFL	22.65
SD1433	8W	7.5	450	MT90	9.50
SD1434	50W	5	450	500-6LFL	34.00
SD1451	80	14	50	500-6LFL	18.10
SD1477	100W	6	175	500-6LFL	52.85
2N5945	4W	8	450	MT90	10.75
2N5946	10W	6	450	MT90	13.00

RF DEVICES

2N2876	1W	200 MHz T060	$12.35
2N3375	3.0W	400 MHz TO60	5.60
2N3553	2.5W	175 MHz TO39	1.40
2N3866	1.0W	400 MHz TO39	1.25
2N3926	7.0W	175 MHz TO60	6.30
2N4427	1.0W	175 MHz TO39	1.35
2N5589	3.0W	175 MHz MT71	4.75
2N5590	10W	175 MHz MT72	7.80
2N5591	25W	175 MHz MT72	10.25
2N5913	1.75W	175 MHz TO39	1.70
2N6080	4.0W	175 MHz MT72	5.40
2N6081	15W	175 MHz MT72	8.45
2N6082	25W	175 MHz MT72	10.95
2N6083	30W	175 MHz MT72	12.30
2N6084	40W	175 MHz MT72	16.30
2N6094	4.0W	175 MHz X106 PNP	6.60
2N6095	15W	175 MHz X106 PNP	8.50
2N6096	30W	175 MHz X106 PNP	10.35
2N6097	40W	175 MHz X106 PNP	20.00

ALDELCO KITS

DUAL DIGITAL 12/24 HOUR CLOCK KIT NOW WITH A NEW WALNUT GRAIN WOOD CABINET

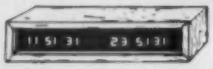

Features:
12 or 24 Hour Operation on either clock
Each Clock separately controlled
Freeze feature for time set
Easy assembly for clock and cabinet

BIG 0.5 LEDS

MODEL ALD 5-W **ONLY $49.95**

NEW! NEW! NEW

KDK

FM2016A

144 to 149 MHz 1000 CHANNELS

All the features of the 2015R and now with adjustable sine wave PL 60 Hz to 203 Hz. Adjustable low power position 1 Watt to 16 Watts.

Buy your KDK 2016A from Aldelco and we'll pay shipping and insurance in the 48 states.

Out of staters save:
New Yorkers must pay sales tax

Sorry no charge cards accepted on 2016A

Low, Low Price

$369

Regulated AC/PS
Model FMPS-4R . . . $39.95

SHOWN WITH OPTIONAL μP-800 MICRO PROGRAMMER

FMMC 1

Dynamic Touch Tone Mic
$39.95

ALARM CLOCK KIT

6 Big 0.5 LED Displays * On Board AC Transformer * 12 Hour Format with 24 Hour Alarm * Snooze Feature * Elapsed Timer. Timer feature makes this Popular in Broadcast Stations. It's a natural for cars, boats and campers when used with optional crystal time base. Fits our standard cabinet. $21.95
Crystal time base when purchased with clock. $3.95

12 or 24 HOUR DIGITAL CLOCK KIT

Uses 0.5 Display LED. 5314 Clock Chip. Freeze feature for accurate set, fits our standard cabinet. ONLY $19.95

CLOCK CABINETS

ea. $4.95

Woodgrain or black leather

CRYSTAL TIME BASE KIT

Includes PC Board, Crystal, all parts and instructions. $4.95

CLOCK FILTERS

Blue, Red, Green, Amber or Smoke $.60

Blinky Flasher Kit

$2.95

PC board, 555 & all parts works on 9 volts. Mouse button—$1.00

THE VERY POPULAR TOPE ACCUKEYER KIT

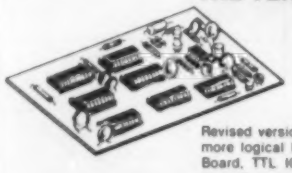

- Self Completing Dots & Dashes
- Iambic Operation
- Single Dot & Dash Memories
- Provision for Attachment of Memory for DX or Contest Work

Revised version of the Accukeyer featured in the ARRL Handbook. Has more logical IC Layout and ON Board sidetone Oscillator. Includes PC Board, TTL ICs, 555 Timer, IC Sockets, Switch, Speaker, Transistors, capacitors and resistors. Requires 5 VDC. ONLY $19.95

NEW 1056 BIT EXPANDABLE MEMORY KIT

ACCUKEYER MEMORY KIT

- Supplied with one 2102 Memory Chip
- Room on the board for three more
- Four chips will total 4224 BITS
- LED indicator for Programming
- Adaptable to other keyers
- Additional 2102s $1.25 each

INCLUDES PC BOARD AND PARTS STILL ONLY $19.95
requires 5 volts DC

CRYSTAL SOCKETS

HOLDS 8 HC25U . . . . $ .59
Single HC25U 29

NATIONAL A1188A

9 digit calculator readout .89

NEW!

Tunable 420 MHz Fast Scan TV Converter

Receive Fast Scan Amateur TV in the 420 to 450 MHz Band with any TV set. Low noise, high gain rf Amp with Varactor tuned input and outputs. Built in AC supply. Comes in two tone walnut & beige cabinet measuring 1 7/8" × 4 1/4" × 41/8". Factory wired with 2 year guarantee. $59.95

ADJUSTABLE POWER SUPPLY KITS

5-15 Volts 500 MA	$6.95
12-28 Volts 500 MA	8.95

ALDELCO A2

2789A MILBURN AVE, BALDWIN, N.Y. 11510
516 378-4555

Add 6% shipping. Add $1.00 for orders under $10.00. Out of U.S.A. add 15% shipping and certified check or money order in U.S. funds.

DIODES/ZENERS

QTY.				
	1N914	100v	10mA	.05
	1N4005	600v	1A	.08
	1N4007	1000v	1A	.15
	1N4148	75v	10mA	.05
	1N4733	5.1v	1 W Zenner	.25
	1N4749	24v	1W	.25
	1N753A	6.2v	500 mW Zener	.25
	1N758A	10v	"	.25
	1N759A	12v	"	.25
	1N5243	13v	"	.25
	1N5244B	14v	"	.25
	1N5245B	15v	"	.25
	1N5349	12v	3W	.25

SOCKETS/BRIDGES

QTY.					
	8-pin	pcb	.16	ww	.35
	14-pin	pcb	.20	ww	.40
	16-pin	pcb	.25	ww	.45
	18-pin	pcb	.30	ww	.95
	20-pin	pcb	.35	ww	1.05
	22-pin	pcb	.40	ww	1.15
	24-pin	pcb	.45	ww	1.25
	28-pin	pcb	.50	ww	1.35
	40-pin	pcb	.55	ww	1.45
	Molex pins .01		To-3 Sockets		.35
	2 Amp Bridge		100-prv		.95
	25 Amp Bridge		200-prv		1.50

TRANSISTORS, LEDS, etc.

QTY.			
	2N2222M	(2N2222 Plastic .10)	.15
	2N2222A		.19
	2N2907A	PNP	.19
	2N3906	PNP (Plastic)	.19
	2N3904	NPN (Plastic)	.19
	2N3054	NPN	.55
	2N3055	NPN 15A 60v	.60
	T1P125	PNP Darlington	1.95
	LED Green,	Red, Clear, Yellow	.19
	D.L.747	7 seg 5/8" High com-anode	1.95
	MAN72	7 seg com-anode (Red)	1.26
	MAN3610	7 seg com-anode (Orange)	1.25
	MAN82A	7 seg com-anode (Yellow)	1.25
	MAN74	7 seg com-cathode (Red)	1.50
	FND359	7 seg com-cathode (Red)	1.25

9000 SERIES

QTY.		QTY.	
9301	.85	9322	.65
9309	.50	9601	.30
		9602	.45

MICRO's, RAMS, CPU's, E-PROMS

QTY.	
8T13	2.50
8T23	2.50
8T24	3.00
8T97	1.75
74S188	3.00
1488	1.25
1489	1.25
1702A	4.50
AM 9050	4.00
ICM 7207	6.95
ICM 7208	13.95
MPS 6520	10.00
MM 5314	4.00
MM 5316	4.50
MM 5387	3.50
MM 5369	2.95
TR 1602B	3.95
UPD 414	4.95
Z 80 A	22.50
Z 80	17.50
Z 80 P10	10.50
2102	1.45
2102L	1.75
2107B-4	4.95
2114	9.50
2513	6.25
2708	11.50
2716 D.S.	34.00
2716 (5v)	69.00
2758 (5v)	26.95
3242	10.50
4116	11.50
6800	13.95
6850	7.95
8080	7.50
8085	22.50
8212	2.75
8214	4.95
8216	3.50
8224	4.25
8228	6.00
8251	7.50
8253	18.50
8255	8.50
TMS 4044	9.95

C MOS

QTY.		QTY.		QTY.		QTY.	
4000	.15	4017	.75	4034	2.45	4069/74C04	.45
4001	.20	4018	.75	4035	.75	4071	.25
4002	.25	4019	.35	4037	1.80	4081	.30
4004	3.95	4020	.85	4040	.75	4082	.30
4006	.95	4021	.75	4041	.69	4507	.95
4007	.25	4022	.75	4042	.65	4511	.95
4008	.75	4023	.25	4043	.50	4512	1.50
4009	.35	4024	.75	4044	.65	4515	2.95
4010	.35	4025	.25	4046	1.25	4519	.85
4011	.30	4026	1.95	4047	2.50	4522	1.10
4012	.25	4027	.35	4048	1.25	4526	.95
4013	.40	4028	.75	4049	.65	4528	1.10
4014	.75	4029	1.15	4050	.45	4529	.95
4015	.75	4030	.30	4052	.75	MC14409	14.50
4016	.35	4033	1.50	4053	.95	MC14419	4.85
				4066	.75	74C151	2.50

– T T L –

4-1-79

QTY.		QTY.		QTY.		QTY.	
7400	.20	7492	.45	74H20	.25	74LS76	.70
7401	.20	7493	.35	74H21	.25	74LS86	.95
7402	.20	7494	.75	74H22	.40	74LS90	.85
7403	.20	7495	.60	74H30	.30	74LS93	.85
7404	.20	7496	.80	74H40	.35	74LS96	2.00
7405	.35	74100	1.15	74H50	.30	74LS107	.90
7406	.25	74107	.35	74H51	.30	74LS109	1.50
7407	.55	74121	.35	74H52	.20	74LS123	1.95
7408	.20	74122	.55	74H53	.25	74LS138	2.00
7409	.25	74123	.55	74H55	.25	74LS151	.95
7410	.20	74125	.45	74H72	.35	74LS153	1.15
7411	.25	74126	.45	74H74	.35	74LS157	1.15
7412	.25	74132	.75	74H101	.95	74LS160	1.15
7413	.45	74141	.90	74H103	.55	74LS164	2.90
7414	.75	74150	.85	74H106	1.15	74LS193	2.00
7416	.25	74151	.95	74L00	.30	74LS195	1.15
7417	.40	74153	.95	74L02	.30	74LS244	2.90
7420	.25	74154	1.15	74L03	.35	74LS259	1.50
7426	.25	74156	.70	74L04	.40	74LS298	1.50
7427	.25	74157	.65	74L10	.30	74LS367	1.95
7430	.20	74161/9316	.75	74L20	.45	74LS368	1.25
7432	.30	74163	.85	74L30	.55	74LS373	2.50
7437	.20	74164	.75	74L47	1.95	74S00	.45
7438	.30	74165	1.10	74L51	.65	74S02	.45
7440	.20	74166	1.75	74L55	.85	74S03	.35
7441	1.15	74175	.90	74L72	.65	74S04	.35
7442	.55	74176	.95	74L73	.70	74S05	.45
7443	.45	74177	1.10	74L74	.75	74S08	.45
7444	.45	74180	.95	74L75	1.05	74S10	.45
7445	.75	74181	2.25	74L85	2.00	74S11	.45
7446	.70	74182	.75	74L93	.75	74S20	.35
7447	.70	74190	1.25	74L123	1.95	74S22	.55
7448	.50	74191	1.25	74LS00	.40	74S40	.30
7450	.25	74192	.75	74LS01	.40	74S50	.30
7451	.25	74193	.85	74LS02	.45	74S51	.35
7453	.20	74194	.95	74LS03	.45	74S64	.15
7454	.25	74195	.95	74LS04	.45	74S74	.70
7460	.40	74196	.95	74LS05	.45	74S112	.80
7470	.45	74197	.95	74LS08	.45	74S114	.85
7472	.40	74198	1.45	74LS09	.45	74S133	.85
7473	.25	74221	1.50	74LS10	.45	74S140	.75
7474	.30	74298	1.50	74LS11	.45	74S151	.95
7475	.35	74367	1.35	74LS20	.45	74S153	.95
7476	.40	75491	.65	74LS21	.45	74S157	.98
7480	.75	75492	.65	74LS22	.45	74S158	.80
7481	.85	74H00	.20	74LS32	.50	74S194	1.50
7482	.95	74H01	.30	74LS37	.45	74S196	2.00
7483	.95	74H04	.30	74LS38	.85	74S257 (8123)	2.50
7485	.75	74H05	.25	74LS40	.70	8131	2.75
7486	.55	74H08	.35	74LS42	.95		
7489	1.05	74H10	.35	74LS51	.75		
7490	.55	74H11	.25	74LS74	.95		
7491	.70	74H15	.45	74LS75	1.20		

I^2L, LINEARS, REGULATORS, ETC.

QTY.		QTY.		QTY.	
MCT2	.95	LM320K24	1.65	LM373	3.95
8038	3.95	LM320T5	1.65	LM377	3.95
LM201	.75	LM320T12	1.65	78L05	.75
LM301	.45	LM320T15	1.65	78L12	.75
LM308	.85	LM323K	5.95	78L15	.75
LM309H	.85	LM324	1.25	78M05	.75
LM309 (340K-5)	1.50	LM339	.75	LM380 (8-14 Pin)	1.19
LM310	.85	7805 (340T5)	1.15	LM709 (8-14 Pin)	.45
LM311 (8-14 Pin)	.75	LM340T12	.95	LM711	.45
LM318	1.50	LM340T15	.95	LM723	.40
LM320H6	.79	LM340T18	.95	LM725	2.50
LM320H15	.79	LM340T24	.95	LM739	1.50
LM320H24	.79	LM340K12	1.25	LM741 (8-14)	.45
7905 (LM320K5)	1.65	LM340K15	1.25	LM747	1.10
LM320K12	1.65	LM340K18	1.25	LM1307	1.75
LM320K15	1.65	LM340K24	1.25	LM1458	.65
				LM3900	.95
				LM75451	.65
				NE555	.45
				NE556	.95
				NE565	1.15
				NE566	1.25
				NE567	.95
				TA7205	6.95
				76477	2.95
				95H90	9.95

INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Blvd., San Diego, California 92111
Out of State 1-800-854-2211 Cable Address:ICUSD Telex: 697-827
(714) 278-4394 California Residents 1-800-542-6239

NAME _____

STREET ADDRESS _____

CITY _____ STATE _____ ZIP _____

PHONE _____ CHARGE CARD # AE Visa BA MC _____ EXP. DATE _____

C.O.D. _____ WILL CALL _____ UPS _____ POST _____ NET 10th OF THE MONTH _____ PO # _____

SPECIAL DISCOUNTS

Total Order	Deduct
$35-$99	10%
$100-$300	15%
$301-$1000	20%

ALL ORDERS SHIPPED PREPAID – NO MINIMUM – COD ORDERS ACCEPTED – ALL ORDERS SHIPPED SAME DAY
OPEN ACCOUNTS INVITED – California Residents add 6% Sales Tax. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.
24 Hour Phone Service – We accept American Express / Visa / BankAmericard / Master Charge

VARIABLE POWER SUPPLY KIT $11.95

- Continuously Variable from 2V to over 15V
- Short-Circuit Proof
- Typical Regulation of 0.1%
- Electronic Current Limiting at 300mA
- Very Low Output Ripple
- Fiberglass PC Board Mounts All Components
- Assemble in about One Hour
- Makes a Great Bench or Lab Power Supply
- Includes All Components except Case and Meters

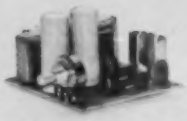

ADD $1.25 FOR POSTAGE/HANDLING

FREE

IC or FET's WITH $5 & $10 ORDERS.† DATA SHEETS WITH MANY ITEMS.

DIODES ZENERS & RECTIFIERS		TRANSISTORS		TRANSISTORS		TRANSISTORS		LINEAR IC's	
1N456 to	6/$1	2N706	$0.24	2N4091	3/$1	2N5638	2/$1	LM340K-5	$1.20
1N4454 to		2N708	.24	2N4092	$0.75	2N5640	2/$1	LM340T-5	1.20
1N4728 to		2N720	.40	2N4121	3/$1	CP643	$0.60	LM340T-6	1.20
1N4759		2N918	3/$1	2N4123	3/$1	CP650*	$5.00	LM340T-12	1.20
1N4763 to	6/$1	2N1613	$0.30	2N4124	3/$1	CP651	$4.50	LM340T-15	1.20
1N5059		2N1711	.29	2N4249	3/$1	E100	5/$1	LM340T-24	1.20
1N746 to	4/$1	2N1893	.50	2N4340	3/$1	E101	3/$1	LM376K*	.95
1N759		2N1953	.30	2N4360	3/$1	E102	3/$1	LM377N	2.50
1N914*	10/$1	2N2218	.24	2N4391	3/$1	E176	3/$1	LM380N	1.25
1N962 to		2N2222	3/$1	2N4392	$0.39	MPF102 to*	3/$1	NE555V*	2/$1
1N974	4/$1	2N2222A	3/$1	2N4393	.29	MPF106		NE566A	$8.50
1N3064	6/$1	2N2369	3/$1	2N4338	$1	MPF112	4/$1	LM709CH	.30
1N3595	5/$1	2N2905 to	$2	2N4360	2/$1	MPS6523	3/$1	LM709CN	.30
1N4001*	13/$1	2N2906		2N4391	$1	E111	4/$1	LM723H	2/$1
1N4002	12/$1	2N2907	$0.24	2N4392	$0.90	E112	4/$1	LM723N	2/$1
1N4003	11/$1	2N2907A	.24	2N4416	2/$1	2N2960	4/$1	LM739N	$1.50
1N4004	13/$1	2N2907*	5/$1	2N4416A	$3.00	SC2002	4/$1	LM741CH	3/$1
1N4005	10/$1	2N3053	$1.00	2N4416 to	$1	SD5001 to	3/$1	LM741CN*	4/$1
1N4006	10/$1	2N3053	5/$1	2N4861		SD5003		LM741C8N	.50
1N4007	10/$1	2N3054	4/$1	2N4867*	2/$1	SD5020	$3.00	LM747CN	.60
1N4148	15/$1	2N3055 to	5/$1	2N4868	2/$1	T073 to	2/$1	748CJ DIP	.35
1N4150*	25/$1	2N3058		2N4891	$2.50	T075		748CJ DIP	1.00
1N4370 to	2/$1	2N3638	5/$1	2N4905	$1	DIGITAL IC's		8402* mDIP	.60
1N4372		2N3638A	5/$1	2N4905	3/$1			LM1304N	1.15
1N4454	15/$1	2N3641	5/$1	2N4907	4/$1	SN7400N	.15	LM1458N*	3/$1
1N4728 to	3/$1	2N3642	5/$1	2N4918	3/$1	SN74H00	.15	LM2111N	$1.40
1N4763		2N3643	5/$1	2N5138 to		SN74121N	.15	XR2556CP	1.95
1N4933 to	4/$1	2N3644	4/$1	2N5139	5/$1	SN74123N	.35	CA3028A	1.50
1N5231 to		2N3645	4/$1	2N5135		SN74H08N	.15	CA3052A	1.75
1N5259		2N3646 to	4/$1	2N5136	5/$1	SN74S51N	.15	CA3046	.65
		2N3650	2/$1	2N5138	4/$1	SN74S74N	.35	LM3876AV	1.65
VARACTORS		2N3691 to	4/$1	2N5139	3/$1	SN74S74N	.35	LM3886*	4.50
1N5139 to	$2	2N3692		2N5210	$0.60	SN74H74N	.15	LM3900N	.52
1N5140		2N3693	$0.60	2N5210	3/$1	SN74H08	.40	RC4194TK*	2.50
1N5496*	$5	2N3822	.70	2N5366	3/$1	LINEAR IC's		RC4195DN*	1.25
FT 4230MP	$2	2N3823	.60	2N5367	$1.50	LM108H	$1.50	RC4195TK*	2.25
MV830 to	$1	2N3906	.70	2N5432	1.00	LM301AN	.27	RC4195TK*	2.25
MV831		2N3903 to*	4/$1	2N5457	3/$1	LM307H	.27	LM4250CN	2.00
MV1830 to	$1	2N3906		2N5458	$0.30	LM308N	.50	RC4558CN	.55
MV1836		2N3919	$5.00	2N5484	3/$1	LM308S	.55	NE592V	.95
MV1860 to	$2	2N3922	5.00	2N5485	3/$1	LM311N	.50	NE592V	.50
MV1872		2N3954	3.25	2N5543	$3.00	LM320K-5	1.25	μA78M05C	1.25
MV2201 to	$1	2N3958	1.15	2N5564	2.50	LM320K-12	1.25	8038 DIP*	3.75
MV2205		2N3970	1.00	2N5591	12.00	LM320K-15	1.25	DM7486*	.50

SPECIALS—THIS MONTH ONLY

1S34A	Germanium Diode 60V 15mA	10/$1	LM380N	Low Bias Current Op Amp Super 709	$0.94
1S270	Germanium Diode 80V 200mA	4/$1	LM309K	5 Volt Regulator TO-3	.94
1N914	Silicon Diode 100V 10mA	25/$1	LM317K	Adjustable Voltage Regulator 2.37V	2.50
1N5393	Hot Carrier Diode (HP2800, etc.)	$1.00	LM380N	2 Watt Audio Power Amplifier DIP	.94
FT	Power Varactor 1–20 Out @ 432MHz (Specs & Circuits included with FT)	$2.00	NE565A	Phase Locked Loop DIP	.94
DIODE GRAB SAC	—Mixed zeners, rectifiers, etc.	50/$1	LM723CN	Precision Voltage Regulator DIP	2/$1
2N706	NPN High Speed Switch 75ns	4/$1	LM747	Dual 741 Compensated Op Amp DIP	2/$1
2N918	UHF Transistor—Osc/Amp up to 1 GHz	4/$1	2102	1024-Bit Static RAM (1024 x 1) DIP	$1.75
2N3058	P-Channel FET Amplifier 250Ω, unbox	$1.00	2740NC	FET Input Op Amp- like RE 536/μA740	1.95
2N3638	MPN Dual Transistor 2mV Match β2/3	2.50	CA3018A	4-Transistor Array/Darlington	.50
2N3904	NPN Amp/Switch β100 40V 200mA	4/$1	CA3028A	RF/IF Amplifier DC to 120MHz	1.40
2N4122	PNP RF Amplifier & Switch	3/$1	CA3075C	FM IF Amp/Limiter/Detector DIP	1.45
2N4858	N-Channel Audio FET Super Low-Noise	2/$1	RC4558	Dual High Gain Op Amp mDIP	3/$1
2N5089	150 Volt PNP Transistor for Keyer	3/$1	MC1550V	Precision Fast Op Amp mDIP	2/$1
E113	N-Channel FET VHF RF Amp	3/$1	NE592V	Dual Hi Gain Op Amp- Comp. mDIP	3/$1
T1674	N-Channel FET High-Speed Switch 40Ω	3/$1	8038	Function Generator/VCO with circuits	$3.75
			LP-10	LOGIC PROBE bit—TTL, CMOS, etc. Workbook size included—5 hr. assembly	$7.95

SEND FOR ADVA'S NEW 1979 CATALOG
NEARLY 1000 SEMICONDUCTORS, KITS, CAPACITORS, ETC.-SEND 25¢ STAMP.

OTHER ADVA KITS:

LOGIC PROBE KIT—Use with CMOS, TTL, DTL, RTL, HTL, NAND, and most MOS IC's. Built in protection against polarity reversal and overvoltage. Draws only a few mA from circuit under test. Dual LED readout. Complete kit includes case and clip leads. ONLY $7.95

FIXED REGULATED POWER SUPPLY KITS—Short-circuit proof, with thermal current limiting. Compact size and typical regulation of 0.5% make these ideal for most electronic projects. Available for 5V @ 500mA, 8V @ 500mA, 9V @ 500mA, 12V @ 400mA, 15V @ 300mA. Specify voltage when ordering. $6.50 ea.

These easy-to-assemble kits include all components, complete detailed instructions and plated fiberglass PC boards. Power supply kits do not include case or meters. Add $1.25 per kit for postage and handling.

†MAIL NOW! FREE DATA SHEETS supplied with many items from this ad. FREE ON REQUEST—741 Op Amp with every order of $5 or more—749 Dual Op Amp or two E100 FET's with every order of $10 or more, postmarked prior to 12/31/79. One free item per order. ORDER TODAY. All items subject to prior sale and prices subject to change without notice. All items are new surplus parts—100% functionally tested.

WRITE FOR FREE CATALOG #79 offering over 700 semiconductors carried in stock. Send 20¢ stamp.

TERMS: Send check or money order (U.S. funds) with order. Add 5% postage for U.S., Canada and Mexico. $1.00 handling charge on orders under $10. Calif. residents add 6% sales tax. Foreign orders add 10% postage. COD orders—add $1.00 service charge.

MORE SPECIALS:

RC4195DN ±15V @ 50mA VOLTAGE REGULATOR IC. Very easy to use. Makes a neat Highly Regulated ±15V Supply for OP AMP's, etc. Requires only unregulated DC (18–30V) and 2 bypass capacitors. With Data Sheet and Schematics. 8-pin mDIP $1.25

RC4136 Quad 741 Low-Noise Op Amp mDIP $0.95

LM1304 FM Multiplex Stereo Demodulator DIP 0.99

LM2111 FM IF Subsystem (IF Amp, Det., Limiter) DIP 0.99

1N6263 Hot Carrier Diode 0.4V @ 1mA 0.1ns DO-35 1.00

ZENERS—Specify Voltage 3.3, 3.9, 4.3, 5.1, 6.8, 9.2 400mW 4/$1.00
9.1, 10, 12, 15, 18, 19, 20, 22, 24, 27, or 33V (±10%) 1 Watt 3/$1.00

- MONEY-BACK GUARANTEE
- ALL TESTED AND GUARANTEED

*SUPER SPECIALS:

1N34	Germanium Diode	10/$1	FSA2501M Diode Array 2/$1
1N914	100V/10mA Diode	20/$1	MPF102 200MHz RF Amp 3/$1
1N4001	50V/1A Rectifier	15/$1	40673 MOSFET RF Amp $1.75
1N4154	30V 1N914	25/$1	LM324 Quad 741 Op Amp .94
BR1	50V 1A Bridge Rec	4/$1	LM376 Pos Volt Reg mDIP .55
2N2222	NPN Transistor	6/$1	NE555 Timer mDIP .39
2N2907	PNP Transistor	6/$1	LM723 2-37V Reg DIP 2/$1
2N3055	Power Xistor 15A	$0.75	LM741 Comp Op Amp mDIP 6/$1
2N3904	NPN Amp/Sw β100	6/$1	LM1458 Dual 741 mDIP 3/$1
2N3906	PNP Amp/Sw β100	6/$1	CA3086 5 Trans Array DIP .62
CP650	Power FET 1/4Amp	$5	RCA29 Pwr Xistor 1A 30W .70

RF391 RF Power Amp Transistor 10-28W @ 3-30MHz TO-3 $6.00
555X Timer 1μs-1hr Different pinout from 555 (w/data) 3/$1
RC4194TK Dual Tracking Regulator ±0.2 to 30V @ 200mA TO-66 $2.50
RC4196TK Dual Tracking Regulator ±16V @ 100mA (TO-66) $2.25
8038 Waveform Generator 1/4TA Wave With Circuits & Data $3.75

NEW SPECIALS

LM318CN	High Speed Op Amp 50V/μs mDIP	$0.94
LM318D	High Speed Op Amp 50V/μs DIP	.90
LM339N	Quad Comparator Single or Dual Supply	.79
LM380N-8	½W Audio Power Amplifier 8-22V	.90
NE567V	Tone Decoder (PLL) 0.01Hz to 500kHz	.99
XR567CP	Tone Decoder (PLL) 0.01Hz to 500 kHz	.99
LM723CN	Precision Voltage Regulator 2-37V DIP	3/$1
LM747CN	Dual 741 Compensated Op Amp	2/$1
SAD1024	Dual 512 Stage (1024) Audio Delay Line "Bucket Brigade" Appl. Data included	$18.95
XR2206CP	Function Generator with applic. data	4.40
XR2242CP	Long-Range Precision Timer μs to days	1.50
1 YEAR TIMER	Kit-2 XR2242's and Applic. Note	3.00
LM2901N	Quad Comparator +5V or 2 to 36VDC	$1.20
CA3018A	4-Transistor Array/Darlington	.99
CA3028A	RF/IF Amplifier DC to 120MHz	1.25
RC4558	Dual High Gain Op Amp mDIP	3/$1
SPACER Kit - 4 ea of 5 assorted size spacers		$1.00
±15 VOLT Regulated Power Supply Kit-Easy assembly, 5mV regulation, 100mA, fully protected. Includes all components and hardware, no PCB or case—Add $1.50 for shipping		$13.95

1N270	Germanium Diode 80V 200mA	4/$1
1N823	Temp Comp Reference 6.2V±5% ± .005%/° C	$0.60
1N914	Silicon Diode 100V 10mA	25/$1
1N3044	100V Zener 1W—Better than an OB3	.75
1N3045	110V Zener 1W—Better than an OB2/OC3	.75
1N3071	200V 100mA Switching Diode 40ns	.30
2N2915	NPN Dual Transistor 3mV Match β100	$1.95
2N3819M	N-Channel RF FET 100MHz Amp	.35
2N4020	PNP Dual Transistor 5mV Match β250	5.00
2N4445	N-Channel FET 5Ω Switch	3.50
2N5394E	Ultra-Low Noise J-FET Audio Amp	$1.25
2N5912	Dual J-FET RF Dif Amp to 800MHz	2.90
2N6028	Programmable Unijunction Transistor	.45
2N6449	300 Volt N-Channel J-FET Amp/Sw	2.00
CP640	Broadband FET RF Amp 140dB Dyn Range	$4.50
E304	N-Channel RF FET 3.8dB NF @ 400MHz	.50
MPSA12	NPN Darlington Transistor β20,000	.75
TIS88	N-Channel FET 400MHz RF Amp	.60
RESISTOR Kit–150 pcs ¼W, 20 most common values, individually packaged, 5 to 20 pcs each.		$4.95
PC BOARD Mounting Kit–8 ea spacer, screw, nut and washer–32 pcs total.		$1.00

SEND FOR ADVA'S NEW 1979 CATALOG
NEARLY 1000 SEMICONDUCTORS, KITS, CAPACITORS, ETC.-SEND 25¢ STAMP.

ADVA ELECTRONICS

A24

BOX 4181 GB
WOODSIDE, CA 94062
Tel.(415) 328-1500

M-M Electronic Sales

A division of united products Corporation

Corp. Hdqts., 2322 1st Ave., Seattle, Wash. 98121 • (206) 682-3025

MOTOROLA 4 MHZ XTAL OSCILLATOR 14 pin dip pkg., 5 VDC in, 4 MHz out. TTL compatible. **$5.95 ea.**

NATIONAL SEMICONDUCTOR - 6 DIGIT CLOCK MODULE A 12-hr. clock featuring alarm and snooze alarm function. Comes complete with everything. All you add is a power cord and switches. Each module utilizes discreet components and is ready for you to mount in your enclosure. Display is 6 each seven segments, .33 inches high, clockchip is MM5375. Can easily be mounted in either of our instrument clock case kits. **$14.95.**

CALCULATOR GUTS
Experimenter's delight. Each keyboard includes a monolithic calculator chip and display. These are rejects. It might be something simple to repair or it could be very nasty. At this price, who cares! 9 volt. **$1.50 ea. 3/$3.00.**

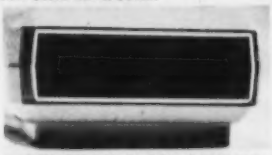

INSTRUMENT CLOCK CASE KIT
A real jewel for those small projects. Hinged top door allows you to hide your control area. O.D. 4½" x 4" x 1¾". **$1.99 each.**

DB-25 FEMALE CONNECTOR
A unique assembly originally adapting the RS232 Type Connector to flat cable. **$1.50 each or 2/$2.50.**

INSTRUMENT/CLOCK CASE KIT
Perfect for your opto projects. Solid aluminum construction with real wainut sides. O.D. 5-3/8" by 5-3/8" by 2". **$6.95 ea.**

EDGE CARD CONNECTOR
Cinch Jones 10/20 Pins. .156 Spacing PC Mount. .85 Burndy 22/44 Pins, .156 spacing PC Mount, **$1.40 each.**

DEFECTIVE CALCULATORS
Well, some are and some are not. We can't afford the time to test them. **$2.50 ea.** Batteries not included. **2/$4.00.**

LINE PRINTER HAMMER DRIVER BOARD Each board contains approx. 130 each #MJE800 (Silicon Darlington NPN hfe 750, 1.5A). About $130.00 worth, over 100 1N4001 diodes, plus support chips. The whole package is yours for only **$14.95.**

HURRY, WE DON'T EXPECT THESE TO LAST VERY LONG!

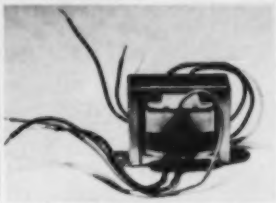

TRANSFORMER Pri. 110 VAC Sec. 11.2 and 5 VCT @ .1 amp. **$.95 ea.**

MINIATURE D.P.D.T. [PUSH BUTTON] momentary, rated 6A/125 VAC, microswitch part #8N2021. **Only $1.54.**

CLOCK DISPLAY
National Semi. 6 Digit Multiplexed Display; .33" Characters (Common Cathode). **A REAL BUY AT JUST $1.00.**

EDGE METER 100-0-100 ua 1/2" by 11/16". Compare with other meters costing $6.00. **Only $2.00 ea.** Why pay more?

DIODE SALE 1N4148
100/$1.95 TAPE/REEL
1000/$14.95

DIODES

TYPE	VOLTS	WATTS	PRICE
1N4001	50	1A	15/$1.00
1N4002	100	1A	15/$1.00
1N4003	200	1A	12/$1.00
1N4004	400	1A	12/$1.00
1N4005	600	1A	10/$1.00
1N4006	800	1A	10/$1.00
1N4007	1000	1A	6/$1.00
1N5400	50	3A	5/$1.00
1N5401	100	3A	5/$1.00
1N5402	200	3A	5/$1.25
1N5403	300	3A	4/$1.25
1N5404	400	3A	4/$1.25
1N5405	500	3A	4/$1.49
1N5406	600	3A	4/$1.49
1N5407	800	3A	3/$1.49
1N5408	1000	3A	2/$ .99
1N4148	75	10M	20/$1.00

SOLID DIPPED TANTALUM CAPACITORS

		1-99	100 PLUS
.1 X 35 VOLT		.23	.19
.15	35	.23	.19
.22	35	.23	.19
.33	35	.23	.19
.47	35	.23	.19
.68	35	.23	.19
1.0	35	.25	.20
1.5	35	.29	.23
2.2	35	.31	.25
3.3	35	.36	.29
4.7	35	.38	.30
6.8	35	.50	.40
10.0	35	.60	.48
15.0	35	.79	.63
22.0	35	1.39	1.12
33.0	35	2.08	1.66
47.0	35	2.65	2.12

VALUES AND QUANT. MAY BE ASSORTED TO ATTAIN QUANT. PRICING

NYLON TIE WRAPS

3"	65000	10/$ .30
4"	65002	10/ .50
5.3"	65003	10/ .59
6.9"	65004	10/ .69
10.8"	65005	10/ 1.59
13.0"	65006	10/ 2.69
14.4"	65055	10/ 2.96
SCREW MOUNT		
13.6"	65054	10/ 4.29
7.4"	65052	10/ .96
5.8"	65051	10/ .89
4.4"	65050	10/ .75

GALLIUM PHOSPHIDE L.E.D.'s
Provide greater light out-put, brighter colors, greater uniformity and less current drain than regular L.E.D.'s

.110 DIAMETER			
P/N 724H	Red Diffused	4/$1.00	
724G	Green Diffused	4/ 1.19	
724Y	Yellow Diffused	4/ 1.49	
7240	Orange Diffused	4/ 1.49	
.220 DIAMETER			
714H	Red Diffused	5/$1.19	
714G	Green Diffused	4/ 1.49	
714Y	Yellow Diffused	4/ 1.59	
7140	Orange Diffused	4/ 1.59	
.220 DIAMETER (low dome)			
704R	Red Diffused	4/$1.59	
704G	Green Diffused	4/ 1.65	
704Y	Yellow Diffused	4/ 1.84	
7040	Orange Diffused	4/ 1.84	
101R-g	Dual (Red and Green)	$2.85	2/5.00
MOUNTING HARDWARE			
.220 Diameter #7aMH			12/$1.44

¼ WATT 5% DEPOSITED CARBON FILM RESISTOR ASSORTMENTS

ASST. A	10 ea 1 OHM 1.5 OHM 2 OHM 2.7 OHM 3 OHM 3.6 OHM 4.7 OHM 5.6 OHM 6.8 OHM 8.2 OHM	100 pcs $2.40
ASST. B	10 ea 10 OHM 12 OHM 15 OHM 18 OHM 22 OHM 27 OHM 33 OHM 39 OHM 47 OHM 56 OHM	100 pcs $2.40
ASST. C	10 ea 68 OHM 82 OHM 100 OHM 120 OHM 150 OHM 180 OHM 220 OHM 270 OHM 330 OHM 390 OHM	100 pcs $2.40
ASST. D	10 ea 470 OHM 560 OHM 680 OHM 820 OHM 1K 1.2K 1.5K 1.8K 2.2K 2.7K	100 pcs $2.40
ASST. E	10 ea 3.3K 3.9K 4.7K 5.6K 6.8K 8.2K 10K 12K 15K 18K	100 pcs $2.40
ASST. F	10 ea 22K 27K 33K 39K 47K 56K 68K 82K 100K 120K	100 pcs $2.40
ASST. G	10 ea 150K 180K 220K 270K 330K 390K 470K 560K 680K 820K	100 pcs $2.40
ASST. H	10 ea 1M 1.2M 1.5M 1.8M 2.2M 2.7M 3.3M 3.9M 4.7M 5.6M	100 pcs $2.40
ASST. A-H	INCLUDES ALL RESISTOR ASSORTMENTS (800 pcs)	$14.95 ea

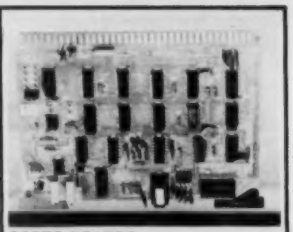

PARTS BOARDS A great way to buy parts on a budget. We guarantee your money's worth. **ONLY $1.00 ea.**

ROTRON WHISPER FAN #WR2H1
3 Blade 4" Diameter 75CFM 115VAC. NET $17.00 **YOUR PRICE $9.95** Wait now, these are not pull-outs or something like that, these are new!

CLAIREX PHOTO CELLS
These have a real USEFUL range to them. Any project involving control from ambient light levels will utilize this photo cell. Light resistance 1K. Fast response. .156 Diameter. **$.75 each or 2/$1.00.**

NOVUS CALCULATOR #824R
Rechargeable NI-Cad calculator WITH MEMORY, EX, CS AND % KEY. **$4.95 ea.** (owners manual and charger are not included)

PLASTIC PARTS BOX A nice little hinged-top box for storing all your small parts. O.d. 6¾" by 3¾" by 2". **$.75 ea. 10/$5.00.**

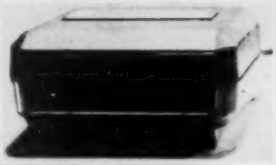

REPEAT OF A SELL-OUT A complete 12 hour digital clock. Some are manufacture line rejects, some are returns, and some are just scratched. Features: hours, minutes, alarm, snooze alarm. Parts value alone would equal $20.00, you pay **only $6.00 ea.**

HOT DEALS

75493N (quad seg. driver)	.55
SN7428N	.25
1000uf 25VDC P-C	.25
2000uf 25VDC AXIAL	.50
18 ga. LINE CORD 6'	.25
2N2222A	4/1.00
2N3054	.75
2N3055 (TO-3)	.99
MEMOREX 1" VIDEO TAPE ½ HOUR (with case)	4.95
SIEMENS MAGNETIC SENSOR	1.99
43/43 GOLD EDGE CONN. .156	4.95
P/B MIN. 12VDC RELAY D.P.D.T.	1.99

FREE BY POPULAR DEMAND
With min. purchase of **$50.00**, you will receive free, a 5 function National Semiconductor L.C.D. mens watch. With min. purchase of **$100.00** you will receive free, our L.C.D. car clock. (watch and clock advertised in Dec. issue of 73 Mag.)

For Master Charge/Visa Orders Use Our TOLL FREE HOT LINE: 1-800-426-0634 for areas outside Washington (incl. Alaska & Hawaii)

O.E.M.'s WELCOME

Terms: All orders shipped promptly. Minimum order $5.00. Telephone orders accepted. All orders shipped UPS or PP. Add 5% extra for shipping & handling. Washington state residents add additional 5.4% sales tax. Master Charge & Visa cards accepted. Money orders & your personal or company check are welcome. Funds made payable in U.S. currency only. No C.O.D. orders. Your satisfaction is guaranteed on all merchandise purchased. All merchandise subject to prior sale. Open account to govt. agencies & publicly funded schools.

Store Hours M-F 9-6 • SAT 9-5

Reader Service—see page 211

Social Events

from page 182

door. Talk-in on .16/.76, .63/.03, .52/.52, and 52.525. For information, contact BRATS, PO Box 5915, Baltimore MD 21208.

IRVING TX
AUG 3-5

Encounter '79, the Texas VHF-FM Society's 1979 Summer Convention, will be held August 3-5, 1979, at the Villa Inn, Irving, Texas. Activities include a transmitter hunt, flea market, FCC exams, manufacturers' exhibits, hospitality room, and several programs and forums. Talk-in on 146.52 and repeaters in the area. Pre-registration is $5.00 until July 1. Registration at the door is $6.00. For information, write Encounter '79, PO Box 3608, Arlington TX 76010.

FLAGSTAFF AZ
AUG 3-5

The Amateur Radio Council of Arizona will hold its annual Ft. Tuthill Hamfest on August 3-5, 1979, at Flagstaff, Arizona. Prizes include TS-520 transceivers, a microwave oven, a Wilson Mark II HT, a Wilson System III triband antenna, and more. Featured will be a western barbecue, tech sessions, and exhibits. Camping facilities are also available. For further details or information, write Ft. Tuthill Hamfest, c/o 8520 E. Edwards Ave., Scottsdale AZ 85253.

LITTLE ROCK AR
AUG 4-5

The Central Arkansas Radio Emergency Net (CAREN) Amateur Radio Club will hold its second annual Ham-a-Rama on Saturday and Sunday, August 4-5, 1979, at the Arkansas State Fairgrounds, Little Rock, Arkansas. There will be two main prizes given, as well as door prizes. Featured will be forums, dealers' exhibits, a Saturday night party, and a large flea market. Talk-in on 146.34/.94. For details, send an SASE to Morris Middleton AD5M, 19 Elmherst Drive, Little Rock AR 72209.

REND LAKE IL
AUG 5

The Shawnee Amateur Radio Association Hamfest will be held on August 5, 1979, at Rend Lake in southern Illinois. Complete camping and recreational facilities will be available, so plan to spend the weekend at the lake and attend the hamfest on Sunday. Family activities are planned. Hourly door prizes will be awarded. There will be no charge to vendors. For information, contact WB9ELP or WB9SWG.

PITTSBURGH PA
AUG 5

The South Hills Brass Pounders and Modulators will hold its 42nd annual Pittsburgh Hamfest on August 5, 1979, from noon until dusk at the Allegheny County Community College south campus on Rte. 885, 2 miles south of the Allegheny County Airport and approximately 15 miles southeast of Pittsburgh, Pennsylvania. Advance registration is $1.50; $2.00 at the door. There will be a large indoor air-conditioned area for vendors and the flea market, and a large paved surface for the outdoor flea market. There will also be prizes and food. Talk-in on 146.13/.73 and .52/.52. For information and preregistration, write Bruce Banister, 5954 Leprechaun Dr., Bethel Park PA 15102.

MT SINAI LI NY
AUG 5

The Radio Central Amateur Radio Club will hold its "Ham-Central" on Sunday, August 5, 1979 (rain date is August 12, 1979), at the Mt. Sinai Elementary School, Rte. 25A, Mt. Sinai, Long Island, New York. Admission for sellers is $3.00 per tailgate space and $1.50 for buyers, with XYL and children under 12 free. Monies are to be used for Radio Central and the St. Charles Hospital Repeater. Doors will open at 7:00 am for sellers and 9:00 for others. They will close at 4:00 pm. Featured will be antenna advice with Art and Madeline Greenberg, a Novice table, great food, a CW contest, an ARRL table, a special event of a fly-in by the Suffolk County Police Dept. helicopter, and a Radio Central Club table. Talk-in on 146.52 WA2UEC and 144.71/145.31 K2VL. For information, call Joan Longtin at (516)-924-8438 or Robin Goodman at (516)-744-6260, or write Radio Central, "Ham-Central," PO Box 680, Miller Place NY 11764.

JACKSONVILLE FL
AUG 4-5

The Jacksonville Hamfest Association is pleased to announce the 1979 Jacksonville Hamfest and ARRL North Florida Section Convention to be held on August 4-5, 1979, at the Jacksonville Beach Municipal Auditorium, Jacksonville, Florida. The location is just one block from the beach, where U.S. 90 meets the sea.

Advanced registrations are available at $3.00 per person from R. J. Cutting W2KGI/4, 303 10th St., Atlantic Beach, Florida 32233. Price at the door will be $3.50.

A large indoor swap area will be featured, with advance table reservations available for $5.00 per table per day from Robbie Roberts KH6FMD/W4, 10557 Atlantic Blvd., #31, Jacksonville, Florida 32211. Information on exhibitors' booths and space are available from the same address.

Other features and programs include statewide organization meetings on such topics as traffic nets and MARS, a microprocessor seminar, a solar power demonstration, a DX "pileup" contest, a hidden transmitter hunt, an OSCAR forum, ARRL forums, emergency preparedness programs, DX and contest presentations, antenna and technical seminars, and much more.

More general information may be obtained from JHA, 911 Rio St. Johns Dr., Jacksonville FL 32211.

SALEM OH
AUG 5

The second annual Salem Area Hamfest will be held on August 5, 1979, from 9:00 am to 3:00 pm at the Kent State Salem campus, Salem, Ohio. Tickets are $1.50 in advance and $2.00 at the door. Inside tables are $5.00 with space for your own table at $2.00. Flea market space is $1.00. There will be air-conditioning, a wheelchair ramp, free parking, refreshments, and prizes, consisting of an Atlas RX-110, TX-110, and a PS-110. Talk-in on 146.52. For details, write Harry Milhoan WA8FBS, 1128 West State, Salem OH 44460.

AMARILLO TX
AUG 10-12

The Panhandle Amateur Radio Club will hold its sixth annual Golden Spread Hamfest and Convention on Friday, Saturday, and Sunday, August 10-12, 1979, at The Inn of Amarillo, 601 Amarillo Blvd. West, Amarillo, Texas. The format consists of two full days of exhibits and trading, six technical sessions, programs for the ladies, valuable door prizes, Army and Navy MARS meetings, ARES meeting, an ARRL forum, and plenty of free parking. Displays may be set up any time after 1:00 pm on Friday, August 10th, at a fee of $20.00 per table. For information, write Hamfest, PO Box 10221, Amarillo TX 79106, or phone Jay Ledbetter WB5UBM at (806)-376-6042 (nights and weekends) or Chuck Passmore WB5BRC at (806)-372-1631.

NOTE to 73 Subscribers

From time to time 73 Magazine makes its subscriber lists available to carefully-screened companies and organizations whose products, services or information may be of interest to you. In every case, we must approve all organizations wishing to mail to our subscribers. In every case they receive a list of names and addresses only—no other information we may have is divulged. Each organization may use the list only once and agrees never to make any personal or telephone solicitations from it.

The overwhelming majority of our subscribers appreciate this controlled use of our mailing lists—it helps them shop conveniently by mail for products and services they need, often at substantial savings. A few people prefer their names not be used. It is to them we address this message.

If you do *not* wish to be a part of this service, please complete the form below . . . your name will not be used in this manner for any reason.

(If you asked us in the past to remove your name from our lists, there is no need to repeat the request.) Please allow about six weeks for your request to take effect.

◇◇◇◇◇◇◇◇◇◇◇◇◇

☐ I wish to have my name removed from the list of subscribers receiving mail other than the regular subscription to 73 Magazine.

◇◇◇◇◇◇◇◇◇◇◇◇◇

Mr.
Mrs.
Ms. _____
Please Print

Address _____

City _____ State _____ Zip _____

Mail this form with your mailing label from the latest issue (or fill out the information as it appears on the label) to:

73 Magazine
Subscription Services Dept.
P.O. Box 931
Farmingdale NY 11737

Radio Bookshop

License Study Guides & Tapes

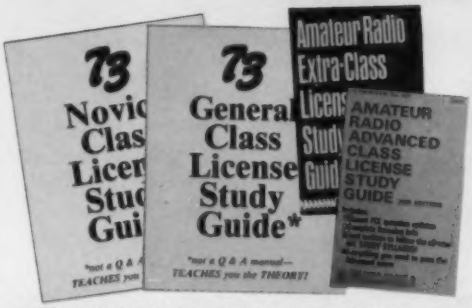

• NOVICE STUDY GUIDE—SG7357—Here is a completely new study guide and reference book for the potential ham. This is not a question/answer memorization course. Electronic and radio fundamentals are presented and explained in an easy-to-understand fashion, preparing the beginner for the Novice exam. Includes the latest FCC amateur regulations, as well as application forms. Easily the best path into the exciting world of ham radio! $4.95.*

• GENERAL CLASS STUDY GUIDE—SG7358—A complete theory course for the prospective General or Technician. This reference explains transistor, amplifier, and general radio theory, while preparing the Novice for the "big" ticket. After getting your ticket, you'll use this guide again and again as an electronic reference source. Not a question/answer guide that becomes dated when the FCC updates the amateur exams. $5.95.*

• ADVANCED CLASS STUDY GUIDE—SG1081—Ready to upgrade your license? To prevent retaking the FCC theory exam, you need the *73* Advanced theory guide. SSB, antenna theory, transmitters, and electronics measuring techniques are covered in detail in this easy-to-follow study guide. Special modes and techniques, such as RTTY, are also treated. An engineering degree is *not* necessary to master Advanced theory—try this book before visiting the examiner's office! $5.95.*

• EXTRA CLASS LICENSE STUDY GUIDE—SG1080—Before going for your 1 × 2 call, it pays to be a master of the Extra class electronic theory. This study guide is the logical extension of the *73* theory course. All the theory necessary to pass the exam is presented. Antennas, transmission lines, swr are discussed, as well as noise, propagation, and specialized communication techniques. This book is not a classroom lecture or memorization guide, but rather a logical presentation of the material that must be *understood* before attempting the Extra exam. Save yourself a return trip to the FCC and try the *73* method first! $5.95.*

NOVICE THEORY TAPES
Startling Learning Breakthrough

• NOVICE THEORY TAPES—CT7300—Startling Learning Breakthrough. You'll be astounded at how really simple the theory is when you hear it explained on these tapes. Three tapes of theory and one of questions and answers from the latest Novice exams give you the edge you need to breeze through your exam. *73* is interested in helping get more amateurs, so we're giving you the complete set of our tapes for the incredibly low price of **ONLY $15.95.***

Scientists have proven that you learn faster by listening than by reading because you can play a cassette tape over and over in your spare time—even while you're driving! You get more and more info each time you hear it.

You can't progress without solid fundamentals. These four hour-long tapes give you all the basics you'll need to pass the Novice exam easily. You'll have an understanding of the basics which will be invaluable to you for the rest of your life! Can you afford to take your Novice exam without first listening to these tapes? Set of 4—$15.95.*

SSTV

• SLOW SCAN TELEVISION TAPE—CT7350—Prize-winning programs from the 73 SSTV contest. Excellent for Demo! $5.95.*

73 CODE SYSTEM TAPES

Any Four Tapes For $15.85! * $4.95 Each! *

"GENESIS"

5 WPM—CT7305—This is the beginning tape for people who do not know the code at all. It takes them through the 26 letters, 10 numbers and necessary punctuation, complete with practice every step of the way using the newest blitz teaching techniques. It is almost miraculous! In one hour many people—including kids of ten—are able to master the code. The ease of learning gives confidence to beginners who might otherwise drop out.

"THE STICKLER"

6+ WPM—CT7306—This is the practice tape for the Novice and Technician licenses. It is made up of one solid hour of code, sent at the official FCC standard (no other tape we've heard uses these standards, so many people flunk the code when they are suddenly—under pressure—faced with characters sent at 13 wpm and spaced for 5 wpm). This tape is not memorizable, unlike the zany 5 wpm tape, since the code groups are entirely random characters sent in groups of five.

"THE CANADIAN"

10+ WPM—CT7310—73 hasn't forgotten the Canadian hams—our 10 WPM tape prepares you to breeze through your country's licensing exams. Like the other code groups, the tape is not memorizable and, once mastered, provides a margin of safety in the actual text situation.

"BACK BREAKER"

13+ WPM—CT7313—Code groups again, at a brisk 13 per so you will be at ease when you sit down in front of the steely-eyed government inspector and he starts sending you plain language at only 13 per. You need this extra margin to overcome the panic which is universal in the test situations. When you've spent your money and time to take the test, you'll thank heavens you had this back-breaking tape.

"COURAGEOUS"

20+ WPM—CT7320—Code is what gets you when you go for the Extra class license. It is so embarrassing to panic out just because you didn't prepare yourself with this tape. Though this is only one word faster, the code groups are so difficult that you'll almost fall asleep copying the FCC stuff by comparison. Users report that they can't believe how easy 20 per really is with this fantastic one hour tape.

"OUTRAGEOUS"

25+ WPM—CT7325—This is the tape for that small group of overachieving hams who wouldn't be content to simply satisfy the code requirements of the Extra Class license. It's the toughest tape we've got and we keep a permanent file of hams who have mastered it. Let us know when you're up to speed and we'll inscribe your name in 73's CW "Hall of Fame."

Use the order card in the back of this magazine or itemize your order on a separate piece of paper and mail to:
73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information.
*Add $1.00 handling charge. Note: Prices subject to change on books not published by 73 Magazine.

FOR CUSTOMER SERVICE CALL (603) 924-7298

Radio Bookshop

73 TECHNICAL LIBRARY

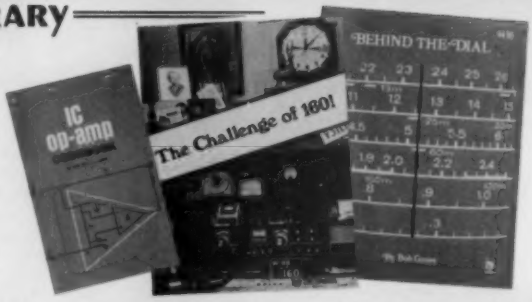

● **BEHIND THE DIAL**—BK7307—By Bob Grove. Get more fun out of shortwave listening with this interesting guide to receivers, antennas, frequencies and interference. $4.95.*

● **THE CHALLENGE OF 160**—BK7309—is the newest book in the *73* technical library, dedicated to 160 meter operating. Si Dunn provides all necessary information to get started on this unique band. The all-important antenna and ground systems are described in detail. The introduction contains interesting photos of Stew Perry's (the King of 160) shack. This reference is a must for new and experienced "Top Band" operators. Price: $4.95.*

● **IC OP-AMP COOKBOOK**—BK1028—by Walter G. Jung. Covers not only the basic theory of the IC op amp in great detail, but also includes over 250 practical circuit applications, liberally illustrated. 592 pages, 5½ × 8½, softbound. $12.95.*

● **THE POWER SUPPLY HANDBOOK**— BK7305—Need a power supply for a gadget you're building? In the **POWER SUPPLY HANDBOOK** there are dozens ready-to-build, plus detailed steps for designing your own. There are circuits and parts lists for all kinds of supplies, ranging from simple DC types to highly stable regulated versions. If you need a circuit to convert a DC voltage to a higher or lower voltage, turn DC into AC, or AC to DC—then this is the book you need. With more than 400 pages, you should be able to find just the circuit you need. Without a doubt one of the best power supply source books available, compiled by the editors of 73. $7.95.*

● **INTRODUCTION TO RTTY**—BK7380—A beginner's guide to radioteletype including teletypewriter fundamentals, signals, distortion and RTTY art. You can be a RTTY artist! A *73* publication. $2.00.*

● **THE NEW RTTY HANDBOOK**—BK7347—is a new edition and the only up-to-date RTTY book available. The state of the art has been changing radically and has made all previous RTTY books obsolete. It has the latest circuits, great for the newcomer and expert alike. $5.95.*

● **PROPAGATION WIZARD'S HANDBOOK**—BK7302—by J. H. Nelson. When sunspots riddled the worldwide communications networks of the 1940's, John Henry Nelson looked to the planets for an answer. The result was a theory of propagation forecasting based upon interplanetary alignment that made the author the most reliable forecaster in America today. The book provides an enlightened look at communications past, present, and future, as well as teaching the art of propagation forecasting. $6.95.*

● **SSB . . . THE MISUNDERSTOOD MODE**—BK7351—by James B. Wilson. Single Sideband Transmission . . . thousands of us use it every day, yet it remains one of the least understood facets of amateur radio. J. B. Wilson presents several methods of sideband generation, amply illustrated with charts and schematics, which will enable the ambitious reader to construct his own sideband generator. A must for the technically-serious ham. $5.50.*

● **SSTV HANDBOOK**—BK7354(hardcover), BK7355(softcover)—This excellent book tells all about it, from its history and basics to the present state-of-the-art techniques. Contains chapters on circuits, monitors, cameras, color SSTV, test equipment and much more. Hardbound $7.00, softbound $5.00.*

● **WEATHER SATELLITE HANDBOOK**—BK7370—Simple equipment and methods for getting good pictures from the weather satellite. Antennas, receivers, monitors, facsimile you can build, tracking, automatic control (you don't even have to be home). Dr. Taggart WB8DQT. $4.95.*

● **73 DIPOLE AND LONG-WIRE ANTENNAS**—BK1016—by Edward M. Noll W3FQJ. This is the first collection of virtually every type of wire antenna used by amateurs. Includes dimensions, configurations, and detailed construction data for 73 different antenna types. Appendices describe the construction of noise bridges, line tuners, and data on measuring resonant frequency, velocity factor, and swr. $5.50.*

ANTENNAS
73 Dipole and Long-Wire Antennas
73 Vertical, Beam, and Triangle Antennas
The GIANT Book of Amateur Radio Antennas

● **THE GIANT BOOK OF AMATEUR RADIO ANTENNAS**—BK7304—With the **GIANT Book of Amateur Radio Antennas** by your side, antennas will become the least of your worries. Over 450 pages of design ideas, theory and reference data make this book live up to its title. The 7 chapters cover everything from basic antenna theory through designs for DIY accessories, as well as dozens of antenna designs. Whether planning to build or buy, design or admire, test or enjoy a ham antenna—this is the book for you. From the editors of 73; published by Tab Books. $12.95 Hardback.*

● **73 VERTICAL, BEAM AND TRIANGLE ANTENNAS**—BK1069—by Edward M. Noll W3FQJ. Describes 73 different antennas for amateurs. Each design is the result of the author's own experiments covering the construction of noise bridges and antenna line tuners, as well as methods for measuring resonant frequency, velocity factor, and standing-wave ratios. 160 pages. $5.50.*

● **VHF ANTENNA HANDBOOK**—BK7368—The NEW VHF Antenna Handbook details the theory, design and construction of hundreds of different VHF and UHF antennas . . . A practical book written for the average amateur who takes joy in building, not full of complex formulas for the design engineer. Packed with fabulous antenna projects you can build. $4.95.*

Use the order card in the back of this magazine or itemize your order on a separate piece of paper and mail to:
73 Radio Bookshop ● Peterborough NH 03458. Be sure to include check or detailed credit card information.
*Add $1.00 handling charge. Note: Prices subject to change on books not published by 73 Magazine.

FOR TOLL FREE ORDERING CALL 1-800-258-5473

Radio Bookshop

TEST EQUIPMENT

● **RF AND DIGITAL TEST EQUIPMENT YOU CAN BUILD**—BK1044—Rf burst, function, square wave generators, variable length pulse generators—100 kHz marker, i-f and rf sweep generators, audio osc, af/rf signal injector, 146 MHz synthesizer, digital readouts for counters, several counters, prescaler, microwave meter, etc. 252 pages. $5.95.*

● **VOL. I COMPONENT TESTERS**—LB7359—. . . how to build transistor testers (8), diode testers (3), IC testers (3), voltmeters and VTVMs (9), ohmmeters (8 different kinds), inductance (3), capacity (9), Q measurement, crystal checking (6), temperature (2), aural meters for the blind (3) and all sorts of miscellaneous data on meters . . . using them, making them more versatile, making standards. Invaluable book. $4.95.*

● **VOL. II AUDIO FREQUENCY TESTERS**—LB7360—. . . jam packed with all kinds of audio frequency test equipment. If you're into SSB, RTTY, SSTV, etc., this book is a must for you . . . a good book for hi-fi addicts and experimenters, too! $4.95.*

● **VOL. III RADIO FREQUENCY TESTERS**—LB7361—Radio frequency waves, the common denominator of Amateur Radio. Such items as SWR, antenna impedance, line impedance, rf output and field strength; detailed instructions on testing these items includes sections on signal generators, crystal calibrators, grid dip oscillators, noise generators, dummy loads and much more. $4.95.*

● **VOL. IV IC TEST EQUIPMENT**—LB7362—Become a troubleshooting wizard! In this fourth volume of the 73 TEST EQUIPMENT LIBRARY are 42 home construction projects for building test equipment to work with your ham station and in servicing digital equipment. Plus a cumulative index for all four volumes of the 73 TEST EQUIPMENT LIBRARY. $4.95.*

THE well-equipped HAM SHACK

● ***73 MAGAZINE* BINDERS**—Preserve and protect your collection for your lifetime! There's no excuse for lost issues when you have these handsome red binders with gold lettering. Order 1—BN1001—for $6.50*; 2 or more—BN1002—for $6.00 each.* (specify 1978 or 1979 binders)

● **QSL CARDS**—*73* turns out a fantastic series of QSL cards at about half the cost of having them done elsewhere because they are run as a fill-in between printing books and other items in the 73 Print Shop. 250 Style W—QW0250—for $8.95*; 500 Style W—QW0500—for $13.95*; 250 Style X—QX0250—for $8.95*; 500 Style X—QX0500—for $13.95*; 250 Style Y—QY0250—for $8.95*; 500 Style Y—QY0500—for $13.95.*

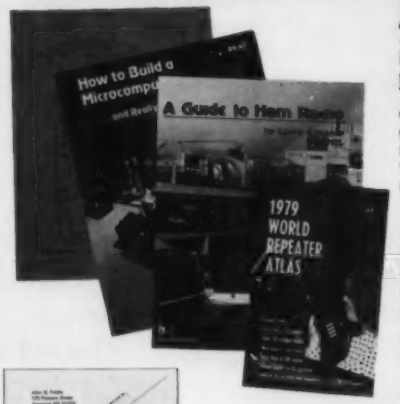

● **HOW TO BUILD A MICROCOMPUTER—AND REALLY UNDERSTAND IT**—BK7325—by Sam Creason. The electronics hobbyist who wants to build his own microcomputer system now has a practical "How-To" guidebook. Sam Creason's book is a combination technical manual and programming guide that takes the hobbyist step-by-step through the design, construction, testing and debugging of a complete microcomputer system. $9.95.*

● **1979 WORLD REPEATER ATLAS**—BK7346—With a new easy-to-use format, the **1979 World Repeater Atlas** is the largest ever published by 73. More than 230 pages of repeaters, listed by both location and frequency, together with over 50 location maps—make this the best repeater atlas ever! Nearly 2000 separate repeater locations are shown on the maps, with greater accuracy than ever before. **$4.95.***

● **BACK ISSUES**—Complete your collection; many are prime collectables now, classics in the field! A full collection is an invaluable compendium of radio and electronics knowledge!

Single back issue—ST0000—$3.00*;
25 our choice—ST2500—$12.00*;
25 your choice—ST2501—$25.00*;
5 your choice—ST0500—$8.50*;
10 your choice—ST1000—$14.00.*

Style X

Style Y

Style W

● **OWNER REPAIR OF AMATEUR RADIO EQUIPMENT**—BK7310—Frank Glass shares over 40 years of operating, servicing, and design experience in this book. There are several books and numerous articles available on the subject of repairs to electronic equipment. The information within these books ranges from the elementary to the highly technical written for the top engineers in the field. But this book stands out from the rest in that it is written in narrative style aimed at conveying the concept of electronic servicing. A written discussion of how components work and how they are combined to provide communication equipment is used to help the reader understand the concepts required to service station equipment. $7.95.*

● **A GUIDE TO HAM RADIO**—BK7321—by Larry Kahaner WB2NEL. What's Amateur Radio all about? You can learn the basics of this fascinating hobby with this excellent beginner's guide. It answers the most frequently asked questions in an easy-going manner, and it shows the best way to go about getting an FCC license. A Guide to Ham Radio is an ideal introduction to a hobby enjoyed by people around the world. $4.95.*

● **LIBRARY SHELF BOXES**—These sturdy white, corrugated, dirt-resistant boxes each hold a full year of *73* or *Kilobaud Microcomputing*. With your order, request self-sticking labels for any of the following: *73, Kilobaud Microcomputing, CQ, QST, Ham Radio, Personal Computing, Radio Electronics, Interface Age,* and *Byte*. Order 1—BX1000—for $2.00*; order 2-7—BX2002—for $1.50 each*; order 8 or more—BX1002—for $1.25 each*.

Use the order card in the back of this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop ● Peterborough NH 03458. Be sure to include check or detailed credit card information.
*Add $1.00 handling charge. Note: Prices subject to change on books not published by 73 Magazine.

FOR CUSTOMER SERVICE CALL (603) 924-7298

22,650 pages.

That's the size of the world's most comprehensive guide to the subject of ham radio: 18 years of 73 Magazine.

The back issues of 73 are a gold mine of interesting articles. Unlike the other magazines, which fill their pages with activity reports, there's little to go stale in 73. You'll find pioneering articles on SSTV, FM, repeaters, ICs, and computers. Even the editorials are fun as Wayne Green's dire predictions, like the debacle of incentive licensing, have come to pass.

Clip the coupon below and send for 73's new back issue catalogue. Treat yourself (or a friendly ham) to some fun, and a fantastic bargain to boot.

☐ YES! Rush me 73's FREE Back Issue Catalogue!

Name _____

Address _____

City _____ State _____ Zip _____

73 magazine
PETERBOROUGH NH 03458

ALL NEW 1979 REPEATER ATLAS OF THE WORLD

The all new **1979 Repeater Atlas** is now available as a result of the cooperation of hundreds of individuals, repeater groups, and coordinators. This is the largest atlas available anywhere. It includes 234 pages, 50 location maps, over 4,500 stations, and 9,000 entries, in a new, easy-to-use format indexed by location and frequency. Call Toll Free (800) 258-5473; have your credit card handy and order your **1979 Repeater Atlas** (BK 7346) today. $4.95

73 magazine
Peterborough NH 03458

MOVING?

Let us know 8 weeks in advance so that you won't miss a single issue of 73 Magazine.
Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly. Write to:

73 magazine
Subscription Department
P.O. Box 931
Farmingdale NY 11737

☐ Address change only
☐ Extend subscription
☐ Enter new subscription
☐ 1 year $18.00

☐ Payment enclosed
(1 extra BONUS issue)
☐ Bill me later

If you have no label handy, print OLD address here.

AFFIX LABEL

Name _____ Call _____
Address _____
City _____ State _____ Zip _____

print NEW address here:

SY-79

Name _____ Call _____
Address _____
City _____ State _____ Zip _____

propagation

by
J. H. Nelson

EASTERN UNITED STATES TO:

GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	14	14	7	7	7	14	14	14	14	14
ARGENTINA	21	14	14	14	7	7	14	21	21	21	21	21
AUSTRALIA	21	14	14	7A	7	7	7	7	7	7	14	21
CANAL ZONE	21	14	7A	7	7	7	7A	14	14	21	21	21A
ENGLAND	14	14	7A	7	7	7	14	14	21	21	21	14
HAWAII	21	21	14	7A	7	7	7	14	14	14	21	21
INDIA	14	14	14B	7B	7B	7B	14	14	14	14A	14	14
JAPAN	14A	14	7A	7	7B	7B	7B	14	14	14	14	14A
MEXICO	21	14A	14	7	7	7	7	14	14	14	21	21
PHILIPPINES	14A	14A	14	7B	7B	7B	7B	14	14	14	14	14
PUERTO RICO	14	14	7	7	7	7	7A	14	14	14	14	14
SOUTH AFRICA	7B	7	7	7	7B	14	21	21	21A	21	14	14B
U. S. S. R.	14	14	7A	7	7	7	14	14	14A	14A	14	14
WEST COAST	21	21	14	7	7	7	7	14	14	14	14A	14A

CENTRAL UNITED STATES TO:

ALASKA	14	14	14	14	7	7	7	14	14	14	14	14
ARGENTINA	21	21	14	14	7	7	14	14	21	21	21	21
AUSTRALIA	21	21	14	14	7A	7	7	7	7	7	14	21
CANAL ZONE	21	14A	14	7	7	7	14	14	21	21	21	21A
ENGLAND	14	14	7A	7	7	7	7	14	14	21	21	14
HAWAII	21	21	14	14	7	7	7	7A	14	21	21	21
INDIA	14	14	14B	7B	7B	7B	7B	14	14	14	14	14
JAPAN	14A	14	14	7A	7B	7B	7B	14	14	14	14	14A
MEXICO	14	14	7A	7	7	7	7	7A	14	14	14	14
PHILIPPINES	14	14A	14A	7B	7B	7B	7B	14	14	14	14	14
PUERTO RICO	21	14	14	7	7	7	14	14	14	21	21	21
SOUTH AFRICA	7B	7	7	7	7B	7B	14	14	21	21	14	14B
U. S. S. R.	14	14	7A	7	7	7	7	14	14	14	14	14

WESTERN UNITED STATES TO:

ALASKA	14	14	14	14	7	7	7	14	14	14	14	14
ARGENTINA	21	21	14	14	7	7	7	14	21	21	21	21
AUSTRALIA	21	21A	21A	21	14	7A	7	7	7	7	14	21
CANAL ZONE	21A	21	14	7	7	7	7	14	14	21	21	21
ENGLAND	14	14	7	7	7	7	7	14	14	14A	14A	14
HAWAII	21	21A	21A	21	14	14	7	7	14	21	21	21
INDIA	14	14	14	14B	7B	7B	7B	7A	14	14	14	14
JAPAN	21	21	21	14	7A	7	7	7A	14	14	14	14
MEXICO	21	14	14	7	7	7	7	14	14	14	21	21
PHILIPPINES	14	14A	14A	14	7A	7B	7B	14	14	14	14	14
PUERTO RICO	21	14A	14	7	7	7	7	14	14	21	21	21
SOUTH AFRICA	7B	7B	7	7	7B	7B	7B	14	14A	14A	14	14B
U. S. S. R.	14	14	7A	7	7	7	7	14	14	14	14	14
EAST COAST	21	21	14	7	7	7	7	14	14	14	14A	14A

A = Next higher frequency may also be useful
B = Difficult circuit this period
F = Fair
G = Good
P = Poor
SF = Chance of solar flares

july

sun	mon	tue	wed	thu	fri	sat
1 G	2 G	3 F	4 F	5 G	6 G	7 G
8 G	9 G	10 G	11 F/SF	12 F/SF	13 F/SF	14 P/SF
15 P/SF	16 F	17 F	18 F	19 G	20 G	21 G
22 G	23 G	24 F	25 F	26 F	27 G	28 G
29 G	30 G	31 G				

READER SERVICE

A46	ABC Communications	178
A1	Adirondack Radio Supply	177
A24	Adva Electronics	202
*	Advance Electronics	143
A60	AED Electronics	18
A92	AHF Antennas	128
A2	Aldelco	200
A97	Amateur Radio Center	112
A40	Amateur Radio Supply of Nashville, Inc.	165
A21	Amateur Wholesale Electronics	184, 185
A58	American Crystal	11
*	Amsat	38
A80	Anteck, Inc.	24, 179
A62	Antenna Specialists	93
A6	Aptron Laboratories	18
*	'79 ARRL Na't. Convention	169
*	Associated Radio	196
B52	Rex Bassett Electronics	160
B23	Barker-Williamson	152
B49	J.S. Betts Company	18
B10	Bird	23
B53	Bob's Amateur Radio Center/Lunar	39
B42	Brodie Electronics/Lunar	43
B8	Bullet Electronics	192, 193
C88	C & A Electronics Enterprises	167
C3	Clegg	153
C21	Coakit	11
C106	Command Productions	146
C58	Communications Center, NE	127, 151
C5	Communications Electronics	146
C115	Communications Electronics Specialties	114
C6	Communications Specialists	16, 17
C105	Communications & TV Unltd.	152
C9	Continental Specialties	174
C143	Cornell-Dubilier	24
D6	Peter W. Dahl Company	42
D35	Daytapro Electronics, Inc.	18
D29	Dielectric Communications	101
D20	Digital Research Corporation	190, 191
D23	Dovetron	114
D11	Drake Company	115
D25	DSI Instruments	21, 107, 161
*	Eagle Electronics	179
*	Ehrhorn Technological Operations, Inc.	173
F1	Fair Radio Sales	180
F5	Fiesher Corporation	177, 180
G12	Germantown Amateur Sup.	142
G22	G.I.S.M.O.	162
G4	Godbout Electronics	194
*	HAL Communications Corporation	15, 175
H24	Hal-Tronix	76
H2	Ham Radio Center	11, 18, 73, 88, 93, 138, 146
H16	Hamtronics, NY	189
H8	Hamtronics, PA	18
H26	Hartwell's Office World	146
H3	Henry Radio	Cii
H44	HFT, Inc.	179
H36	Hustler	38
I1	ICOM	25
I39	Inline Instruments, Inc.	180
I32	Instant Software	85, 89, 91
I9	Integrated Circuits, Unltd.	201
I27	IRL	50, 174
J1	Jameco Electronics	195
J8	JRS Electronics/Lunar	47
J2	Jan Crystals	138
K13	Kantronics	22
*	Kenwood	CIV, 5, 139
K14	Key Electronics	179
*	Kilobaud	83
K4	KLM Electronics	42
L23	Larsen Antennas	185
*	Little Rock Ham O Rama	179
L9	Long's Electronics	120-125
M48	Macrotronics, Inc.	146
M35	Madison Electronics Supply	71, 117
M35	Madison Electronics Supply/Lunar	51
M36	Maggiore Electronic Lab.	128
M101	Maury's VHF-UHF/Lunar	57
*	Melbourne Florida Hamfest.	114
M52	MFJ Enterprises	75, 171
M8	MHZ Electronics	186, 187
M89	Micro Control Specialties	11
M95	Micro Management Sys.	146
M100	Metz	23
M76	M & M RF Distributors/Lunar	33
N23	National Radio	22
N22	Non-Linear Systems	23
O5	OK Machine & Tool	97, 174
O3	Optoelectronics, Inc.	7, 174
O12	Outdoor Outfitters	152
*	Palomar Engineers	93
P41	P.C. Electronics	86
*	Peoria Hamfest	50
P44	Pickering Codemaster Company	69
*	Plainsman Micro Systems	77
P2	Poly Paks	197
Q3	Quest Electronics	181
R1	Radio Amateur Callbook, Inc.	115
*	Radio Shack	24
*	Radio World	93
R36	Radios Unlimited/Lunar	53
R8	Ramsey Electronics	188
R27	RF Power Labs, Inc.	64
R9	Robot/Tufts	32
R35	Ross Distributing Corp.	103
S100	Scott Manufacturing	117
S63	Semiconductors Surplus	199
S33	S-F Amateur Radio Services	11
S81	Spectronics, Inc.	148, 149
S8	Spectrum Commun.	28, 29
S10	SST Electronics	116
S18	Standard Communications	88
S43	Surplus Electronics	198
S44	Swan Electronics	8, 9, 22
T64	Technical Clinic	114
T52	Tele-Tow'r Mfg. Co., Inc.	116
*	Ten-Tec	13
T55	TET U.S.A.	129
T34	Thomas Communications	113
T48	Tower Electronics Corp.	117
T18	Trac Electronics, Inc.	116
T3	Tufts Radio Electronics	163
U10	UDM Enterprises	180
U9	Unadilla/Reyco Division	128
U2	Unarco-Rohn	175
U8	United Products	203
V5	VHF Engineering	163
V24	Vibroplex	155
V75	Vineyard Amateur Radio	114
W18	Western Electronics	138
W2	Wilson Electronics	3
X3	Xitex Corp.	119
Y1	Yaesu Electronics Corporation	Ciii, 65, 111

From 73 ..... page 11, 76, 131, 204-210

***Reader Service inquiries not honored. Please contact advertiser directly.**

BOOKS, ETC.

BK1016	73 DIPOLE & LONG WIRE ANTENNAS	$ 5.50
ST0000	73 BACK ISSUE	$ 3.00
ST2500	73 BACK ISSUES—25 OUR CHOICE	$10.00
ST0500	73 BACK ISSUES—5 YOUR CHOICE	$ 7.00
ST1000	73 BACK ISSUES—10 YOUR CHOICE	$12.00
ST2501	73 BACK ISSUES—25 YOUR CHOICE	$20.00
BK7307	BEHIND THE DIAL	$ 4.95
BN1001	BINDER—73—1	$ 6.50
BN1002	BINDER—73—2&UP	$ 6.00
BK7309	CHALLENGE OF 160	$ 4.95
CT7305	CODE TAPE—5 WPM	$ 4.95
CT7306	CODE TAPE—6 + WPM	$ 4.95
CT7310	CODE TAPE—10 + WPM	$ 4.95
CT7313	CODE TAPE—13 + WPM	$ 4.95
CT7320	CODE TAPE—20 + WPM	$ 4.95
CT7325	CODE TAPE—25 + WPM	$ 4.95
CT7394	CODE TAPES (ANY FOUR ABOVE)	$15.95
BK7321	GUIDE TO HAM RADIO	$ 4.95
BK7325	HOW TO BUILD A MICROCOMPUTER & REALLY UNDERSTAND IT	$ 9.95
BK7304	GIANT BOOK OF AMATEUR RADIO ANTENNAS	$12.95
BK1028	IC OP AMP COOKBOOK	$12.95
BK7380	INTRO TO RTTY	$ 2.00
CT7300	NOVICE THEORY TAPES	$15.95
BK7310	OWNER REPAIR OF AMATEUR RADIO EQUIPMENT	$ 7.95
BK7305	POWER SUPPLY HANDBOOK	$ 7.95
BK7302	PROPAGATION WIZARD'S HANDBOOK	$ 6.95
QW0250	QSL CARDS—STYLE W—250	$ 8.95
QW0500	QSL CARDS—STYLE W—500	$13.95
QX0250	QSL CARDS—STYLE X—250	$ 8.95
QX0500	QSL CARDS—STYLE X—500	$13.95
QY0250	QSL CARDS—STYLE Y—250	$ 8.95
QY0500	QSL CARDS—STYLE Y—500	$13.95
BK7346	1979 WORLD REPEATER ATLAS	$ 4.95
BK1044	RF DIGITAL TEST EQUIPMENT	$ 5.95
BK7347	RTTY HANDBOOK	$ 5.95
BX1000	SHELF BOX—1	$ 2.00
BX1001	SHELF BOX—2	$1.50 each
BX1002	SHELF BOX—8 UP	$1.25 each
BK7351	SSB THE MISUNDERSTOOD MODE	$ 5.50
BK7354	SSTV HANDBOOK (HARDCOVER)	$ 7.00
BK7355	SSTV HANDBOOK (SOFTCOVER)	$ 5.00
CT7350	SSTV TAPE	$ 5.95
SG1081	STUDY GUIDE—ADVANCED CLASS	$ 5.95
SG1080	STUDY GUIDE—EXTRA CLASS	$ 5.95
SG7358	STUDY GUIDE—GENERAL CLASS	$ 5.95
SG7357	STUDY GUIDE—NOVICE CLASS	$ 4.95
LB7359	TEST EQUIP LIB V1—COMP TESTERS	$ 4.95
LB7360	TEST EQUIP LIB V2—AUDIO TESTERS	$ 4.95
LB7361	TEST EQUIP LIB V3—RADIO EQUIP	$ 4.95
LB7362	TEST EQUIP LIB V4—IC TEST EQUIP	$ 4.95
BK1069	VERTICAL BEAM & TRIANGLE ANTNS	$ 5.50
BK7368	VHF ANTENNA HANDBOOK	$ 4.95
BK7370	WEATHER SATELLITE HANDBOOK	$ 4.95

73 magazine

READER SERVICE To receive more information from any of the advertisers in this issue of **73**, postage-paid return cards are provided here for your convenience. If you wish to hear from one or several advertisers, refer to the ad itself. You will find numbers near the logo of each advertiser. Each represents the advertiser's individual **Reader Service Number.** Circle the corresponding numbers on one of the cards on this page, include your name, address & zip, and drop in a mailbox. In 4-6 weeks you'll hear from the advertiser directly.

73 magazine

READER SERVICE REPLY CARD

Return this card to receive full information on the many products advertised in this issue. Limit: 25 requests. ☐ Subscriber ☐ Newsstand. This card is valid until September 30, 1979.

A1	A80	C3	C143	G4	H44	K13	M76	P41	S10	T34	V24
A2	A92	C5	D6	G12	I1	K14	M95	P44	S18	T48	V75
A6	A97	C6	D11	G22	I9	L9	M100	Q3	S33	T52	W2
A21	B8	C9	D20	H2	I27	L23	M101	R1	S43	T55	W18
A24	B10	C21	D23	H3	I32	M8	N22	R8	S44	T64	X3
A40	B23	C58	D25	H8	I39	M35	N23	R9	S63	U2	Y1
A46	B42	C88	D29	H16	J1	M36	O3	R27	S81	U8	
A58	B49	C105	D35	H24	J2	M48	O5	R35	S100	U9	
A60	B52	C106	F1	H26	J8	M52	O12	R36	T3	U10	
A62	B53	C115	F5	H36	K4	M69	P2	S8	T18	V5	

73 MICROCOMPUTING

This month's ARTICLE WINNER (title page number): _____

Name _____
(PLEASE TYPE OR PRINT CLEARLY)

Address _____

City _____ State _____ Zip _____

S7

BUSINESS REPLY CARD

FIRST CLASS PERMIT NO. 17 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

73 magazine
Peterborough NH 03458

NO POSTAGE NECESSARY IF MAILED IN THE UNITED STATES

Att: Mail Order

READER SERVICE REPLY CARD

Return this card to receive full information on the many products advertised in this issue. Limit: 25 requests. ☐ Subscriber ☐ Newsstand. This card is valid until September 30, 1979.

A1	A80	C3	C143	G4	H44	K13	M76	P41	S10	T34	V24
A2	A92	C5	D6	G12	I1	K14	M95	P44	S18	T48	V75
A6	A97	C6	D11	G22	I9	L9	M100	Q3	S33	T52	W2
A21	B8	C9	D20	H2	I27	L23	M101	R1	S43	T55	W18
A24	B10	C21	D23	H3	I32	M8	N22	R8	S44	T64	X3
A40	B23	C58	D25	H8	I39	M35	N23	R9	S63	U2	Y1
A46	B42	C88	D29	H16	J1	M36	O3	R27	S81	U8	
A58	B49	C105	D35	H24	J2	M48	O5	R35	S100	U9	
A60	B52	C106	F1	H26	J8	M52	O12	R36	T3	U10	
A62	B53	C115	F5	H36	K4	M69	P2	S8	T18	V5	

73 MICROCOMPUTING

This month's ARTICLE WINNER (title page number): _____

Name _____
(PLEASE TYPE OR PRINT CLEARLY)

Address _____

City _____ State _____ Zip _____

S7

BUSINESS REPLY CARD

FIRST CLASS PERMIT NO. 17 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

73 magazine
Peterborough NH 03458

Att: Reader Service

NO POSTAGE NECESSARY IF MAILED IN THE UNITED STATES

ORDER OF MFORM FORM DER ORDE FORM FOR ORDER OF MFORM FORM DER ORDE FORM FOR

73 magazine

radio bookshop order form

Please send me the following 73 products: (please print or type!)

Qty.	Catalog #	Description	Unit Price	Total
			Add $1.00 shipping & handling:	
			Total:	

Enclosed $_____ ☐ Check ☐ Money order

Bill: ☐ American Express ☐ BankAmericard/Visa ☐ MasterCharge

Credit Card # _____

Expiration date_____ Signature _____

Name _____

Address _____

City_____ State_____ Zip _____

S7A

ORDER OF MFORM FORM DER ORDE FORM FOR ORDER OF MFORM FORM DER ORDE FORM FOR

73 magazine

BUSINESS REPLY CARD

FIRST CLASS PERMIT NO. 17 PETERBOROUGH NH 03458

POSTAGE WILL BE PAID BY ADDRESSEE

73 magazine
Peterborough NH 03458

Att: Reader Service

NO POSTAGE NECESSARY IF MAILED IN THE UNITED STATES

ORDER OF MFORM FORM DER ORDE FORM FOR ORDER OF MFORM FORM DER ORDE FORM FOR

A Breakthrough In Technology!

THE YAESU FT-207R

MICROPROCESSOR CONTROLLED SYNTHESIZED HANDIE

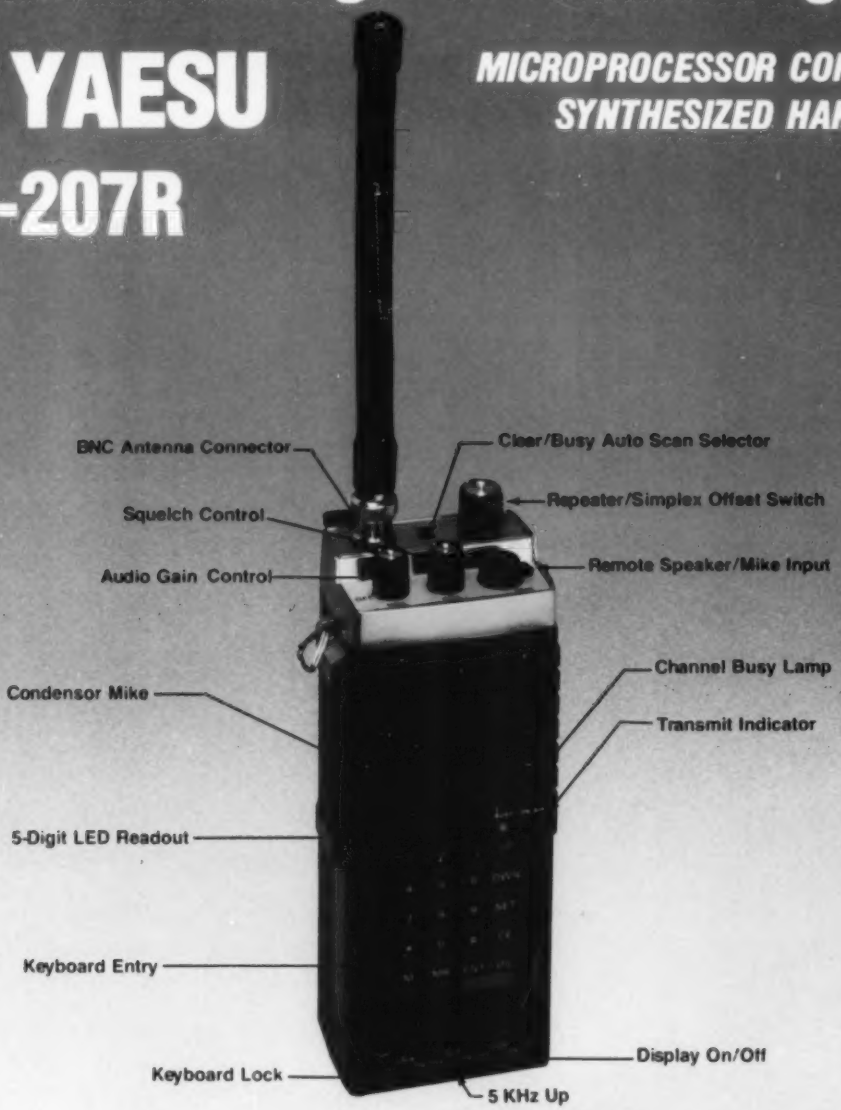

The Yaesu FT-207R Synthesized Handie has all the features you could want in a very compact package

- 144-148 MHz Range
- 10 KHz Steps
- 3 Watts Output
- 4 Memories plus Programmable Offset
- Priority Channel
- Memory and Band Auto Scan
- Optional Equipment:
- Keyboard Encoded Frequency Entry
- 2 Tone (Touchtone®) Input from Keyboard
- Keyboard Lock guards against accidental frequency change
- Odd Splits Can Be Programmed from Keyboard
- Automatic Battery Saver Feature for LED Display
- Rubber Flex Antenna

Tone Squelch, Speaker/Mike, Nicads, Battery Charger

arma

Price And Specifications Subject To Change Without Notice Or Obligation

YAESU **The radio.**

679X

YAESU ELECTRONICS CORP., 15954 Downey Ave., Paramount, CA 90723 ● (213) 633-4007
YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati OH 45246

TS-700SP

TR-7600 TR-7625

Looks the same as the TR-7625, but offers 10 watts RF output (switchable to 1 watt low power). Also uses RM-76 Microprocessor Control Unit. Offers one built-in memory.

Featuring 25 watts RF output (switchable to 5 watts low power), the TR-7625 is a high-performance 2-meter FM transceiver with built-in memory, and is designed to permit multi-channel (800-channel) operation. Compact and perfect for mobile or ham shack use. When used with optional RM-76 Microprocessor Control Unit, the TR-7625 offers a whole new dimension in channel memory and scanning capability.

RM-76

Optional Microprocessor Control Unit. Combines with either the TR-7600 or TR-7625. Stores frequencies in six memories (simplex/repeater), and it scans.

Here's an outstanding 2-meter ALL-MODE TRANSCEIVER that provides an extra dimension of versatility over the entire 2-meter band. Feature-packed and equipped for SSB, FM, CW and AM. Complete with built-in digital frequency readout, receiver preamplifier, VOX, sidetone, and microphone.

See your Authorized Kenwood Dealer for more details.

KENWOOD

... pacesetter in amateur radio

TRIO-KENWOOD COMMUNICATIONS INC.
1111 WEST WALNUT/COMPTON, CA 90220

See Kenwood's "TECH TALK" in this issue for information on the TS-120S.